 


Sequential Circuit Design



Dr. Bassam Jamil


**Adopted from slides of the
textbook**

Outline

- ❑ Latch
 - Operation
 - Dynamic and Static Latches
- ❑ Flip-Flop
 - Operation
 - Dynamic and Static Flip Flops
- ❑ Adding (Enable/ Reset / Set) to Latch/Flip-Flop
- ❑ Timing



D Latch

 - ❑ When $\text{CLK} = 1$, latch is *transparent*
 - D flows through to Q like a buffer
- ❑ When $\text{CLK} = 0$, the latch is *opaque*
 - Q holds its old value independent of D
- ❑ a.k.a. *transparent latch* or *level-sensitive latch*




D Latch Design


- ❑ Multiplexer chooses D or old Q

  


D Latch Operation

 

Write Data

 


Store Data

 

Dynamic Latch: Pass Transistor

 
- ❑ Pass Transistor Latch
- ❑ Pros
 - + Tiny
 - + Low clock load
- ❑ Cons
 - V_t drop
 - nonrestoring
 - backdriving
 - output noise sensitivity
 - diffusion input
 - **Dynamic → Leakage**



Used in 1970's


Dynamic Latch: Transmission Gate

 - ❑ Transmission gate
 - + No V_t drop
 - Requires inverted clock
 - **Dynamic \rightarrow Leakage**



Dynamic Latch: Transmission Gate

 
- ❑ Inverting buffer
 - + Restoring
 - + No backdriving
 - + Fixes either
 - Output noise sensitivity
 - Or diffusion input
 - Inverted output
 - **Dynamic → Leakage**



Static Latch Design


- ❑ Tristate feedback
 - + Static
 - Backdriving risk

 - ❑ **Static latches are now essential because of leakage**




Static Latch Design

 - ❑ Buffered input
 - + Fixes diffusion input
 - + Noninverting





Static Latch Design

- ❑ Buffered output
+ No backdriving

 


- ❑ Widely used in standard cells
 - + Very robust (most important)
 - Rather large (extra inverter)
 - Rather slow (1.5 – 2 FO4 delays)
 - High clock loading

  
- ❑ Datapath latch
 - + smaller
 - + faster
 - unbuffered input



D Flip-flop

 
- ❑ When CLK rises, D is copied to Q
- ❑ At all other times, Q holds its value
- ❑ a.k.a. *positive edge-triggered flip-flop, master-slave flip-flop*



 


Sequencing Elements

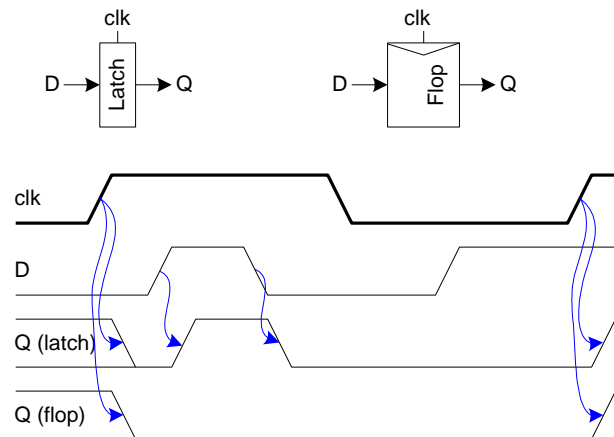- ❑ **Latch:** Level sensitive
 - a.k.a. transparent latch, D latch
- ❑ **Flip-flop:** edge triggered
 - A.k.a. master-slave flip-flop, D flip-flop, D register
- ❑ **Timing Diagrams**
 - Transparent
 - Opaque
 - Edge-trigger




D Flip-flop Design

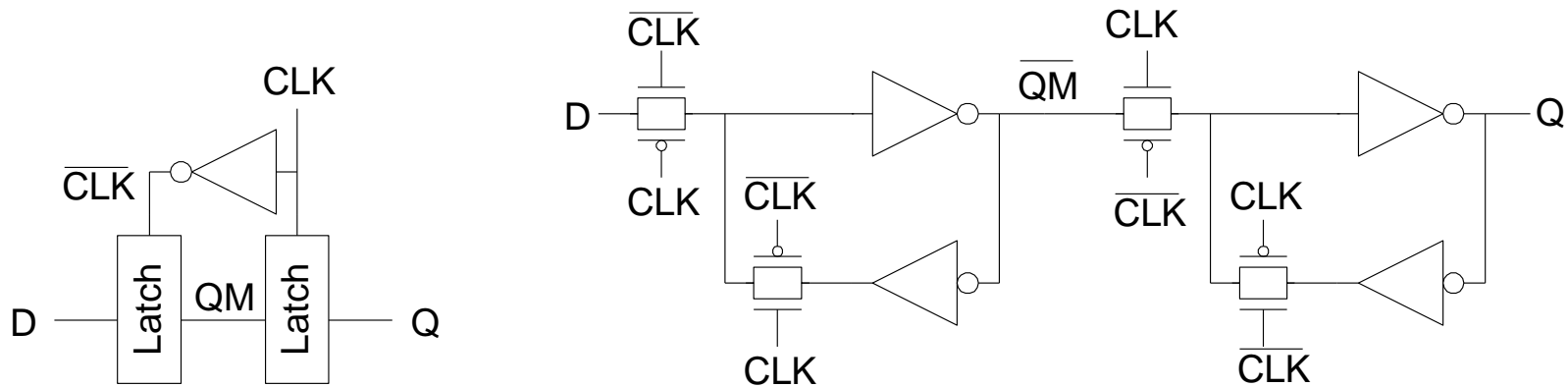- ❑ Built from master and slave D latches




Flip-Flop Design

 - ❑ Flip-flop is built as pair of back-to-back latches




Dynamic FF

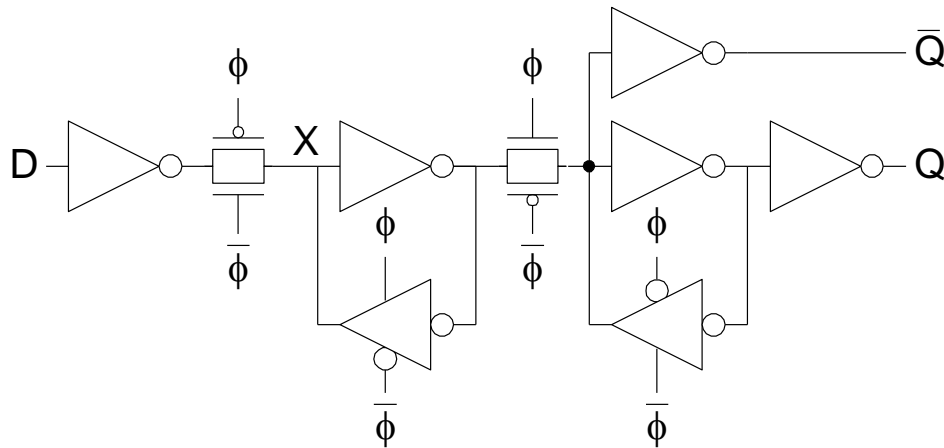

Static FF


Design of FF/Latch with Enable

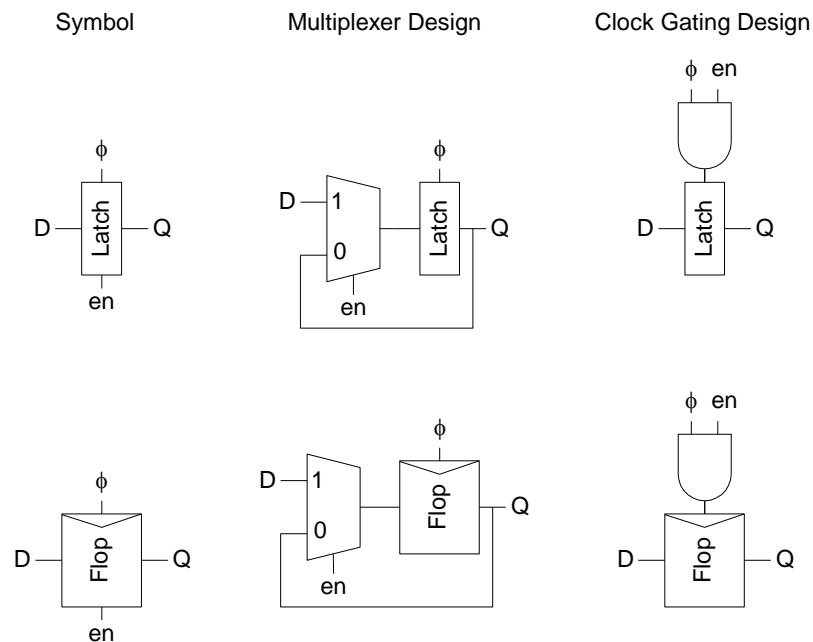- ❑ Enable: ignore clock when $en = 0$
 - Mux: increase latch D-Q delay
 - Clock Gating: increase en setup time, skew




Design of FF/Latch with Reset

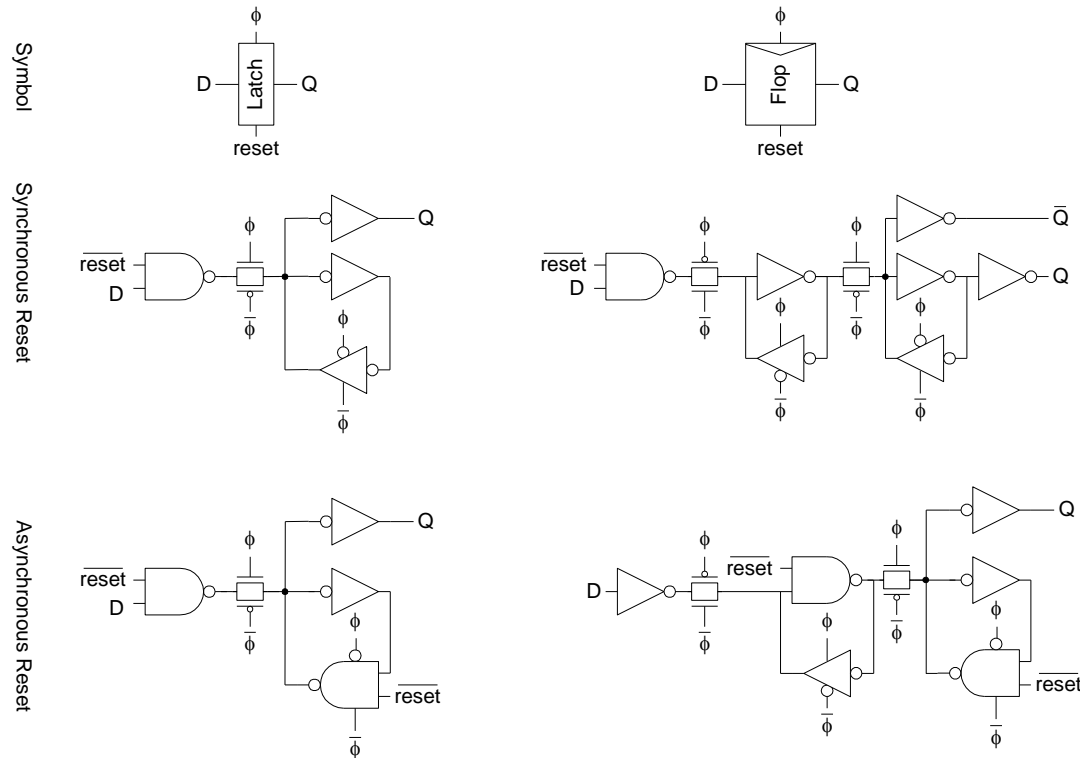- ❑ Force output low when reset asserted
- ❑ Synchronous vs. asynchronous




Design of FF with Set / Reset

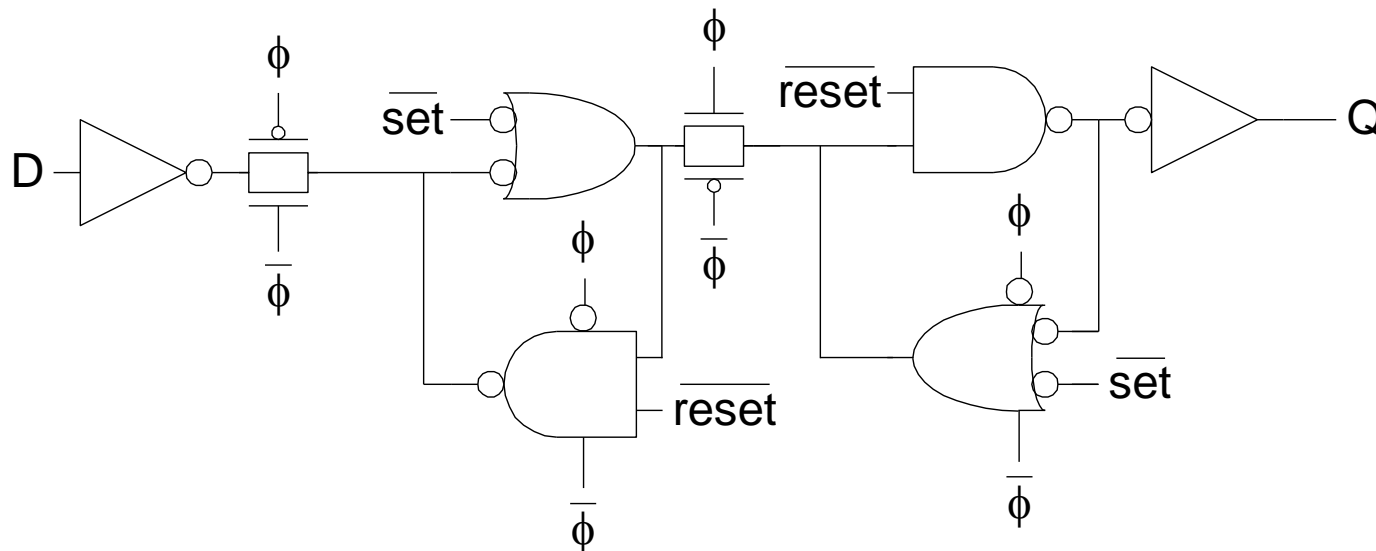- ❑ Set forces output high when enabled
- ❑ Flip-flop with asynchronous set and reset



Sequencing Methods






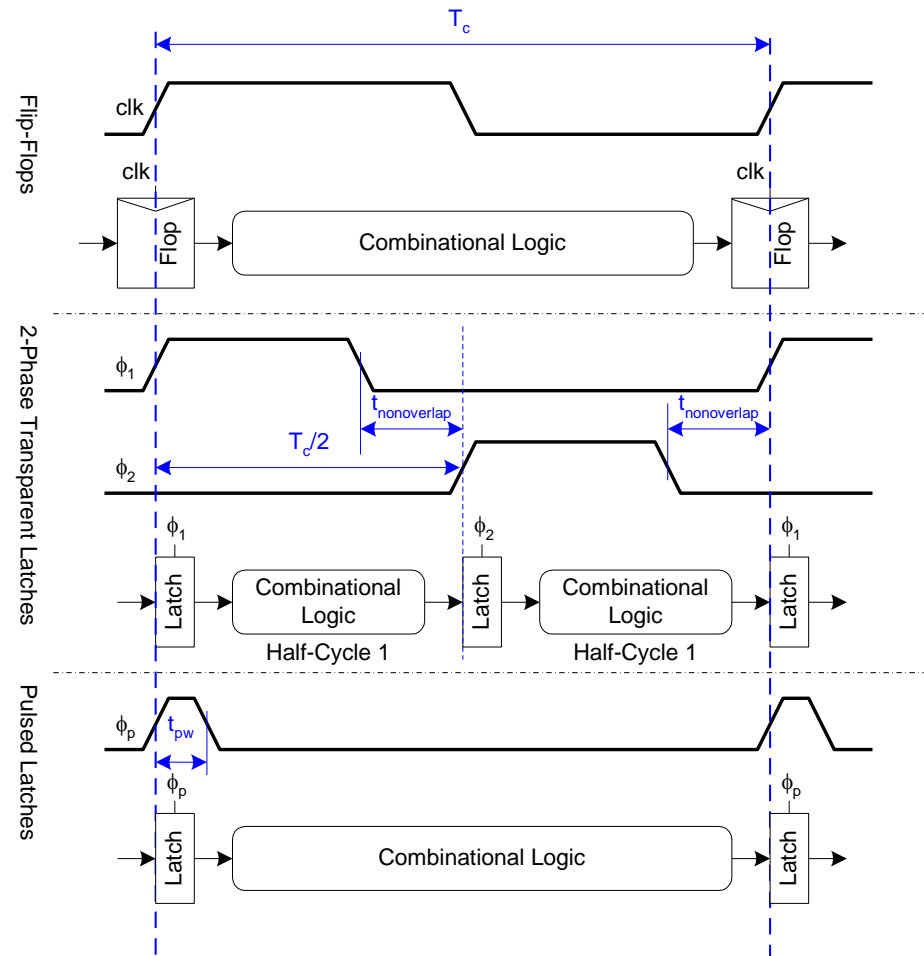
- ❑ Flip-flops
- ❑ 2-Phase Latches
- ❑ Pulsed Latches



Timing Diagrams


Contamination and Propagation Delays

t_{pd}	Logic Prop. Delay
t_{cd}	Logic Cont. Delay
t_{pcq}	Latch/Flop Clk->Q Prop. Delay
t_{ccq}	Latch/Flop Clk->Q Cont. Delay
t_{pdq}	Latch D->Q Prop. Delay
t_{cdq}	Latch D->Q Cont. Delay
t_{setup}	Latch/Flop Setup Time
t_{hold}	Latch/Flop Hold Time

      


Max-Delay: Flip-Flops
 
$$t_{pd} \leq T_c - \underbrace{(t_{\text{setup}} + t_{pcq})}_{\text{sequencing overhead}}$$




Max Delay: 2-Phase Latches (read)
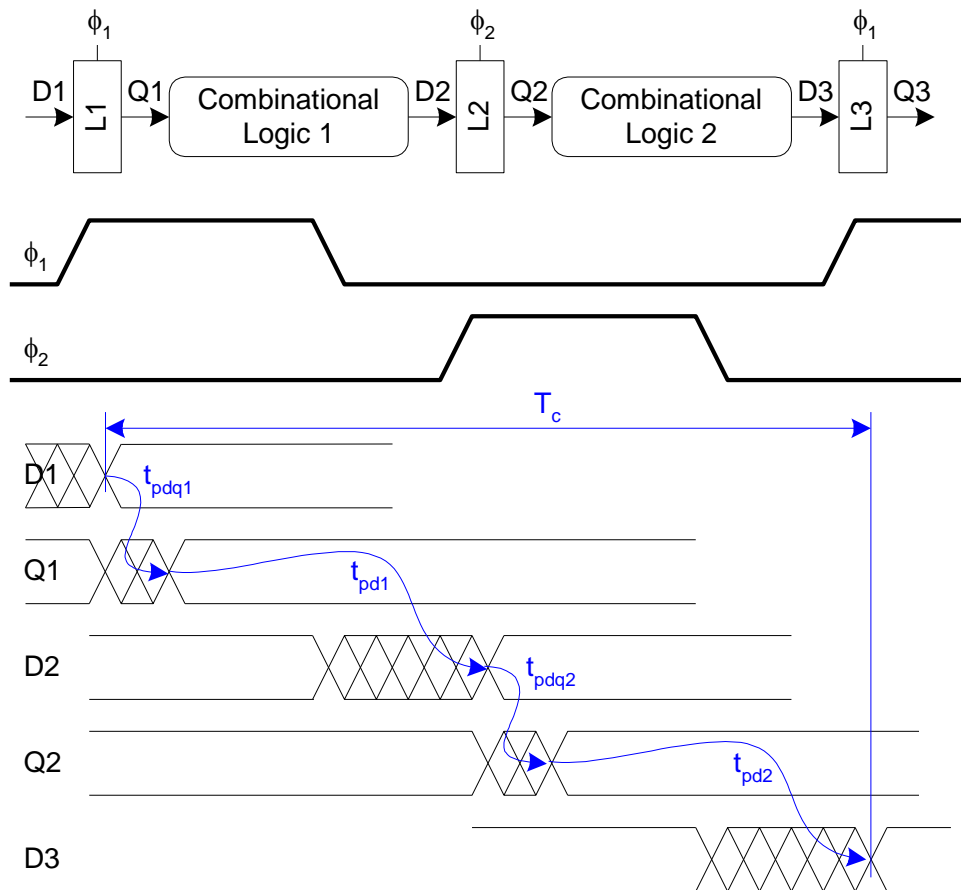
$$t_{pd} = t_{pd1} + t_{pd2} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$





Max Delay: Pulsed Latches (read)
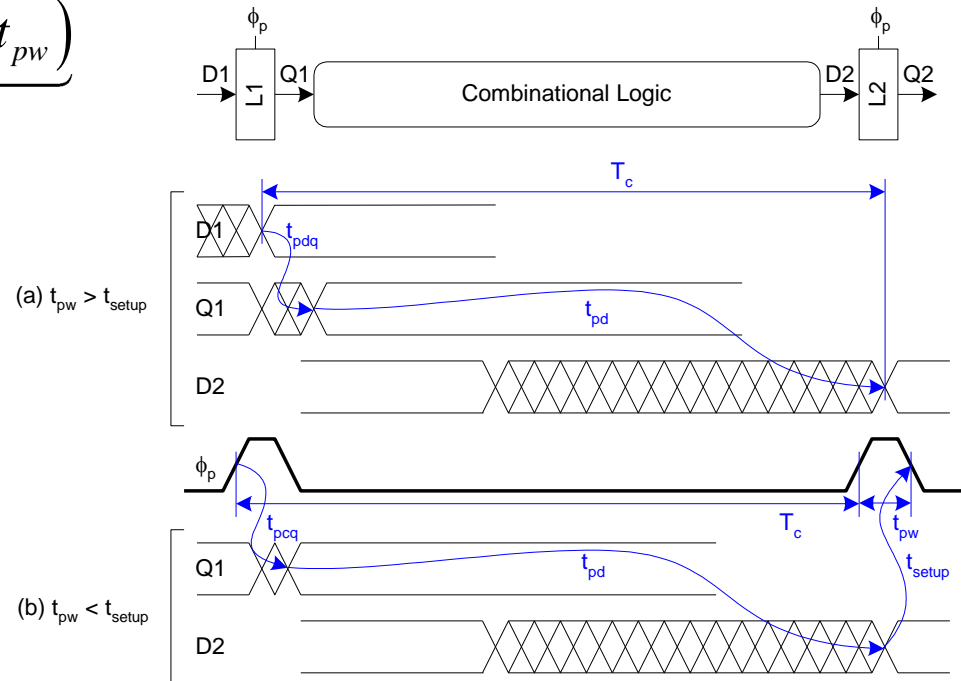
$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{\text{setup}} - t_{pw})}_{\text{sequencing overhead}}$$



Min-Delay: Flip-Flops
  
$$t_{cd} \geq t_{\text{hold}} - t_{ccq}$$




Min-Delay: 2-Phase Latches (read)

$$t_{cd1}, t_{cd2} \geq$$

Hold time reduced by nonoverlap

Paradox: hold applies twice each cycle, vs. only once for flops.


But a flop is made of two latches!

 

Min-Delay: Pulsed Latches (read)

$$t_{cd} \geq$$


Hold time increased
by pulse width

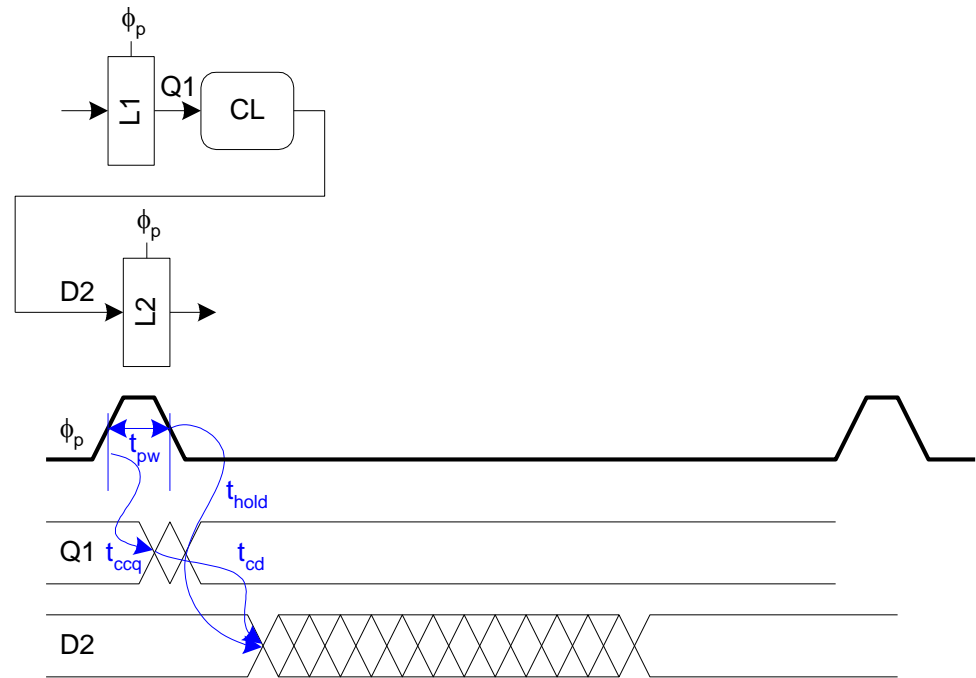

Time Borrowing (read)

- ❑ In a flop-based system:
 - Data launches on one rising edge
 - Must setup before next rising edge
 - If it arrives late, system fails
 - If it arrives early, time is wasted
 - Flops have hard edges
- ❑ In a latch-based system
 - Data can pass through latch while transparent
 - Long cycle of logic can borrow time into next
 - As long as each loop completes in one cycle

Time Borrowing Example (read)

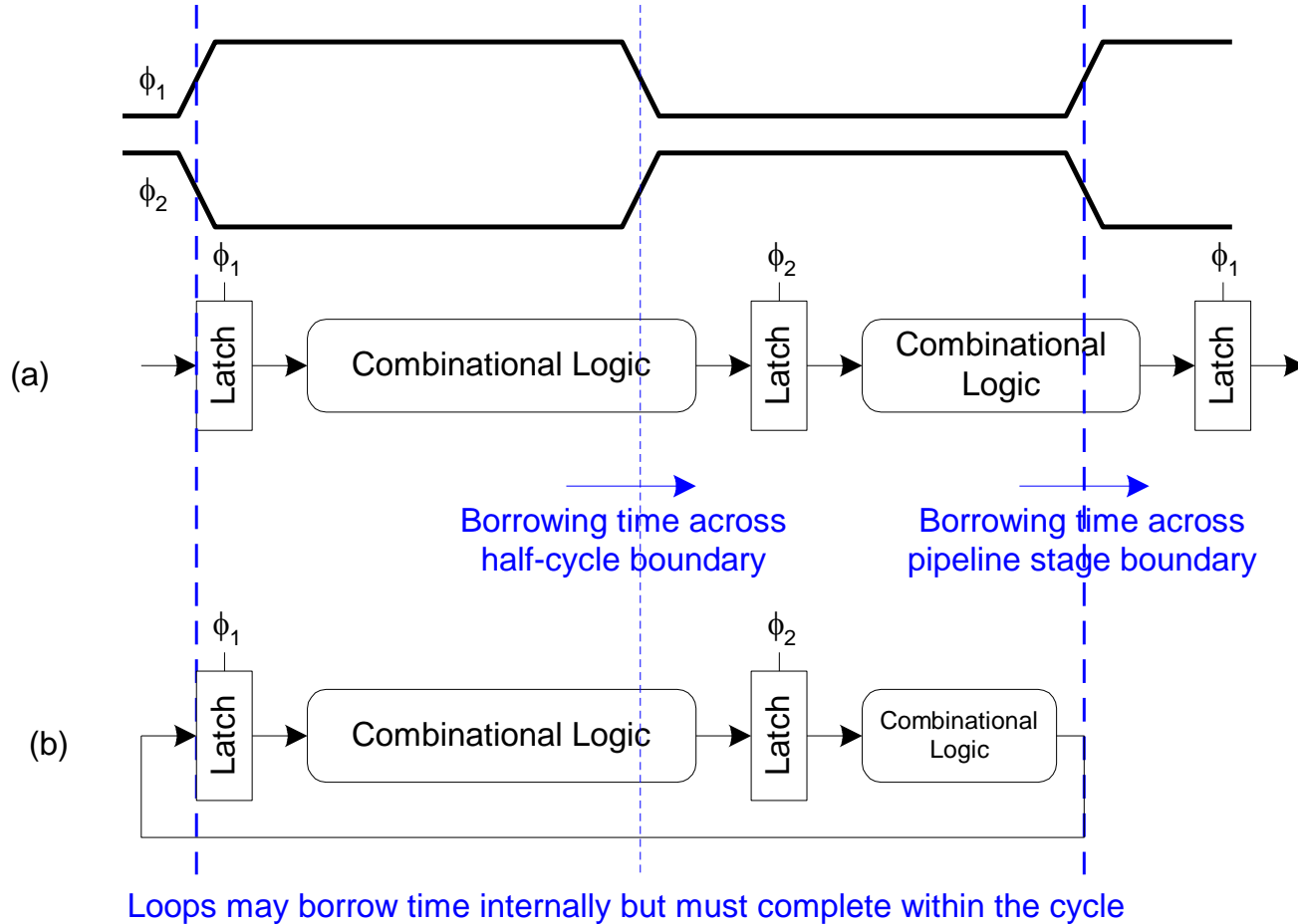


How Much Borrowing? (read)

2-Phase Latches

$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}})$$

Pulsed Latches
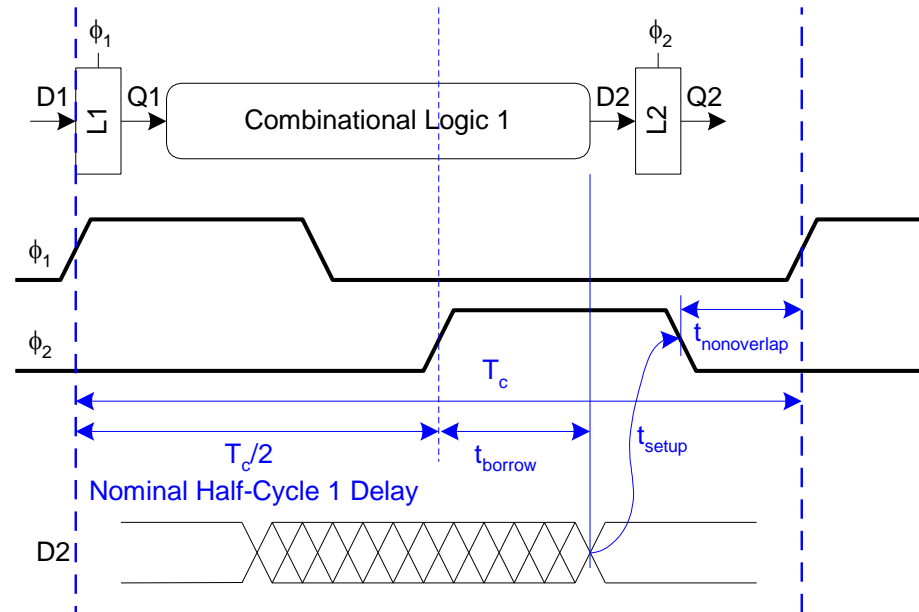
$$t_{\text{borrow}} \leq t_{pw} - t_{\text{setup}}$$




Clock Skew

- ❑ We have assumed zero clock skew
- ❑ Clocks really have uncertainty in arrival time
 - Decreases maximum propagation delay
 - Increases minimum contamination delay
 - Decreases time borrowing

Skew: Flip-Flops

$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$
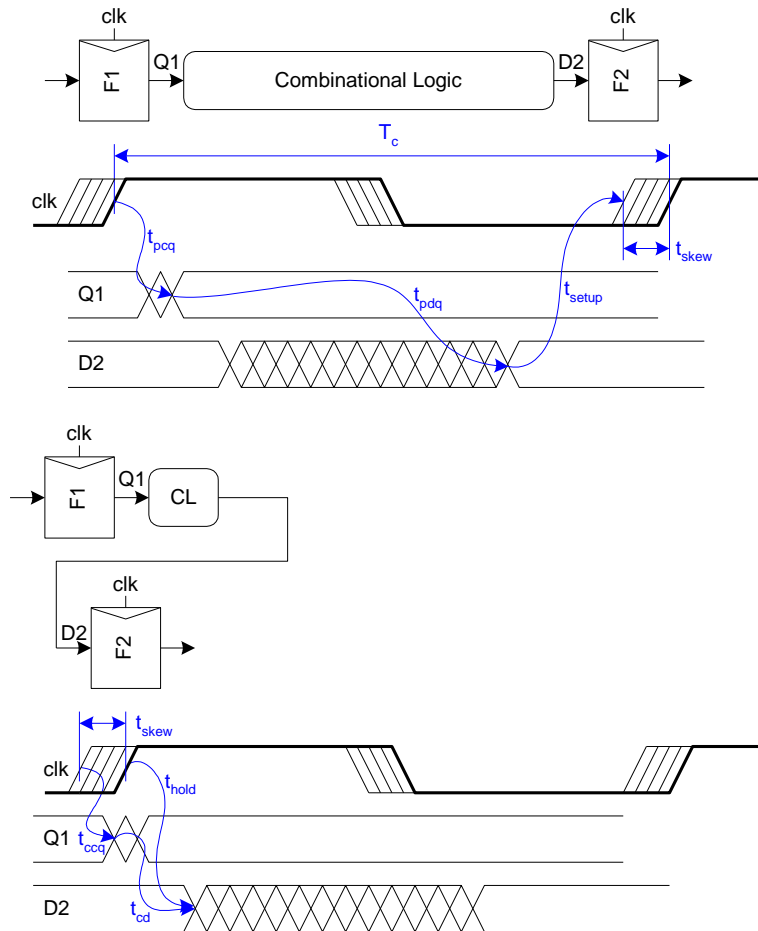
$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$




Skew: Latches (read)

2-Phase Latches

$$t_{pd} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$

$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}} + t_{\text{skew}}$$
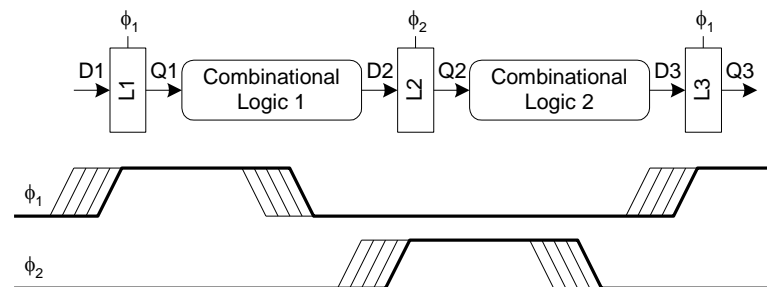
$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}} + t_{\text{skew}})$$



Pulsed Latches

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{\text{setup}} - t_{pw} + t_{\text{skew}})}_{\text{sequencing overhead}}$$

$$t_{cd} \geq t_{\text{hold}} + t_{pw} - t_{ccq} + t_{\text{skew}}$$


$$t_{\text{borrow}} \leq t_{pw} - (t_{\text{setup}} + t_{\text{skew}})$$

Two-Phase Clocking

- ❑ If setup times are violated, reduce clock speed
- ❑ If hold times are violated, chip fails at any speed
- ❑ In this class, working chips are most important
 - No tools to analyze clock skew
- ❑ An easy way to guarantee hold times is to use 2-phase latches with big nonoverlap times
- ❑ Call these clocks ϕ_1 , ϕ_2 (ph1, ph2)

Safe Flip-Flop


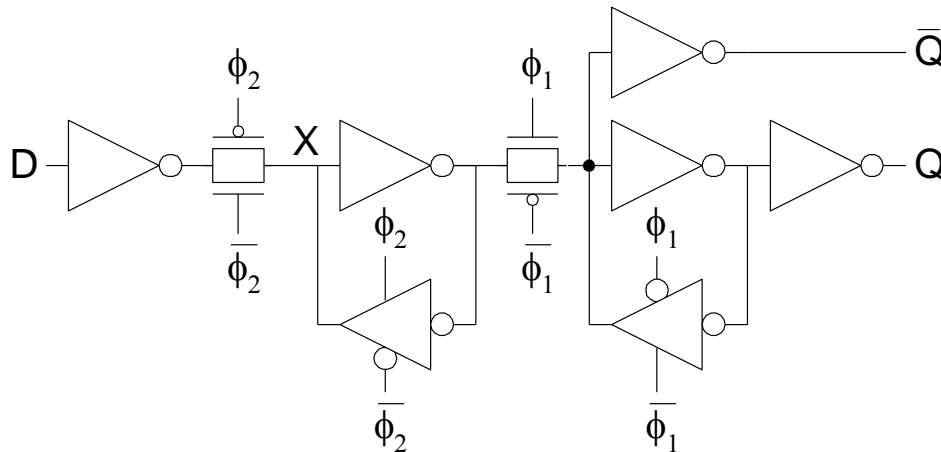
- ❑ Past years used flip-flop with nonoverlapping clocks
 - Slow – nonoverlap adds to setup time
 - But no hold times
- ❑ In industry, use a better timing analyzer
 - Add buffers to slow signals if hold time is at risk



Adaptive Sequencing (read)

❑ Designers include timing margin

  - Voltage
- Temperature
- Process variation
- Data dependency
- Tool inaccuracies



❑ Alternative: run faster and check for near failures

- Idea introduced as “Razor”
 - Increase frequency until at the verge of error
 - Can reduce cycle time by ~30%

Summary

- ❑ Flip-Flops:
 - Very easy to use, supported by all tools
- ❑ 2-Phase Transparent Latches:
 - Lots of skew tolerance and time borrowing
- ❑ Pulsed Latches:
 - Fast, some skew tol & borrow, hold time risk

	Sequencing overhead ($T_c - t_{pd}$)	Minimum logic delay t_{cd}	Time borrowing t_{borrow}
Flip-Flops	$t_{pcq} + t_{setup} + t_{skew}$	$t_{hold} - t_{ccq} + t_{skew}$	0
Two-Phase Transparent Latches	$2t_{pdq}$	$t_{hold} - t_{ccq} - t_{nonoverlap} + t_{skew}$ in each half-cycle	$\frac{T_c}{2} - (t_{setup} + t_{nonoverlap} + t_{skew})$
Pulsed Latches	$\max(t_{pdq}, t_{pcq} + t_{setup} - t_{p\omega} + t_{skew})$	$t_{hold} - t_{ccq} + t_{p\omega} + t_{skew}$	$t_{p\omega} - (t_{setup} + t_{skew})$