

1. Define percent error as $100 [e^x - (1 + x)] / e^x$

x	$1 + x$	e^x	% error
0.001	1.001	1.001	5×10^{-5}
0.005	1.005	1.005	1×10^{-3}
0.01	1.01	1.010	5×10^{-3}
0.05	1.05	1.051	0.1
0.10	1.10	1.105	0.5
0.50	1.50	1.649	9
1.00	2.00	2.718	26
5.00	6.00	148.4	96

Of course, “reasonable” is a very subjective term. However, if we choose $x < 0.1$, we ensure that the error is less than 1%.

2. (a) Short-circuit the 10 V source.

Note that $6 \parallel 4 = 2.4 \Omega$. By voltage division, the voltage across the 6Ω resistor is then

$$4 \frac{2.4}{3 + 2.4} = 1.778 \text{ V}$$

$$\text{So that } i_1' = \frac{1.778}{6} = \boxed{0.2963 \text{ A.}}$$

- (b) Short-circuit the 4 V source.

Note that $3 \parallel 6 = 2 \Omega$. By voltage division, the voltage across the 6Ω resistor is then

$$-10 \frac{2}{6} = -3.333 \text{ V}$$

$$\text{So that } i_1'' = \frac{-3.333}{6} = \boxed{-0.5556 \text{ A.}}$$

$$\text{(c) } i_1 = i_1' + i_1'' = \boxed{-259.3 \text{ mA}}$$

3. Open circuit the 4 A source. Then, since

$$(7 + 2) \parallel (5 + 5) = 4.737 \, \Omega, \text{ we can calculate } v_1' = (1)(4.737) = 4.737 \, \text{V.}$$

To find the total current flowing through the 7 Ω resistor, we first determine the total voltage v_1 by continuing our superposition procedure. The contribution to v_1 from the 4 A source is found by first open-circuiting the 1 A source, then noting that current division yields:

$$4 \frac{5}{5 + (5 + 7 + 2)} = \frac{20}{19} = 1.053 \, \text{A}$$

Then, $v_1'' = (1.053)(9) = 9.477 \, \text{V}$. Hence, $v_1 = v_1' + v_1'' = 14.21 \, \text{V}$.

We may now find the total current flowing downward through the 7 Ω resistor as

$$14.21/7 = 2.03 \, \text{A.}$$

4. One approach to this problem is to write a set of mesh equations, leaving the voltage source and current source as variables which can be set to zero.

We first rename the voltage source as V_x . We next define three clockwise mesh currents in the bottom three meshes: i_1 , i_y and i_4 . Finally, we define a clockwise mesh current i_3 in the top mesh, noting that it is equal to -4 A.

Our general mesh equations are then:

$$\begin{aligned} -V_x + 18i_1 - 10i_y &= 0 \\ -10i_1 + 15i_y - 3i_4 &= 0 \\ -3i_y + 16i_4 - 5i_3 &= 0 \end{aligned}$$

** Set $V_x = 10$ V, $i_3 = 0$. Our mesh equations then become:

$$\begin{aligned} 18i_1 - 10i'_y &= 10 \\ -10i_1 + 15i'_y - 3i_4 &= 0 \\ -3i'_y + 16i_4 &= 0 \end{aligned}$$

Solving, $i'_y = 0.6255$ A.

** Set $V_x = 0$ V, $i_3 = -4$ A. Our mesh equations then become:

$$\begin{aligned} 18i_1 - 10i''_y &= 0 \\ -10i_1 + 15i''_y - 3i_4 &= 0 \\ -3i''_y + 16i_4 &= -20 \end{aligned}$$

Solving, $i''_y = -0.4222$ A.

Thus, $i_y = i'_y + i''_y = \boxed{203.3 \text{ mA}}$.

5. We may solve this problem without writing circuit equations if we first realise that the current i_1 is composed of two terms: one that depends solely on the 4 V source, and one that depends solely on the 10 V source.

This may be written as $i_1 = 4K_1 + 10K_2$, where K_1 and K_2 are constants that depend on the circuit topology and resistor values.

We may not change K_1 or K_2 , as only the source voltages may be changed. If we increase both sources by a factor of 10, then i_1 increases by the same amount.

Thus, $4\text{ V} \rightarrow 40\text{ V}$ and $10\text{ V} \rightarrow 100\text{ V}$.

6. i_A, v_B "on", $v_C = 0$: $i_x = 20$ A
 i_A, v_C "on", $v_B = 0$: $i_x = -5$ A
 i_A, v_B, v_C "on" : $i_x = 12$ A

so, we can write $i_x' + i_x'' + i_x''' = 12$
 $i_x' + i_x'' = 20$
 $i_x' + i_x''' = -5$

In matrix form,
$$\begin{bmatrix} 1 & 1 & 1 \\ 1 & 1 & 0 \\ 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_x' \\ i_x'' \\ i_x''' \end{bmatrix} = \begin{bmatrix} 12 \\ 20 \\ -5 \end{bmatrix}$$

- (a) with i_A on only, the response $i_x = i_x' = 3$ A.
 (b) with v_B on only, the response $i_x = i_x'' = 17$ A.
 (c) with v_C on only, the response $i_x = i_x''' = -8$ A.
 (d) i_A and v_C doubled, v_B reversed: $2(3) + 2(-8) + (-1)(17) = -27$ A.

7. One source at a time:
The contribution from the 24-V source may be found by shorting the 45-V source and open-circuiting the 2-A source. Applying voltage division,

$$v_x' = 24 \frac{20}{10 + 20 + 45 \parallel 30} = 24 \frac{20}{10 + 20 + 18} = 10 \text{ V}$$

We find the contribution of the 2-A source by shorting both voltage sources and applying current division:

$$v_x'' = 20 \left[2 \frac{10}{10 + 20 + 18} \right] = 8.333 \text{ V}$$

Finally, the contribution from the 45-V source is found by open-circuiting the 2-A source and shorting the 24-V source. Defining v_{30} across the 30- Ω resistor with the “+” reference on top:

$$0 = v_{30}/20 + v_{30}/(10 + 20) + (v_{30} - 45)/45$$

solving, $v_{30} = 11.25 \text{ V}$ and hence $v_x''' = -11.25(20)/(10 + 20) = -7.5 \text{ V}$

Adding the individual contributions, we find that $v_x = v_x' + v_x'' + v_x''' = 10.83 \text{ V}$.

8. The contribution of the 8-A source is found by shorting out the two voltage sources and employing simple current division:

$$i_3' = -8 \frac{50}{50 + 30} = -5 \text{ A}$$

The contribution of the voltage sources may be found collectively or individually. The contribution of the 100-V source is found by open-circuiting the 8-A source and shorting the 60-V source. Then,

$$i_3'' = \frac{100}{(50 + 30) \parallel 60 \parallel 30} = 6.25 \text{ A}$$

The contribution of the 60-V source is found in a similar way as $i_3''' = -60/30 = -2 \text{ A}$.

The total response is $i_3 = i_3' + i_3'' + i_3''' = -750 \text{ mA}$.

9. (a) By current division, the contribution of the 1-A source i_2' is $i_2' = 1 (200) / 250 = 800 \text{ mA}$.

The contribution of the 100-V source is $i_2'' = 100 / 250 = 400 \text{ mA}$.

The contribution of the 0.5-A source is found by current division once the 1-A source is open-circuited and the voltage source is shorted. Thus,

$$i_2''' = 0.5 (50) / 250 = 100 \text{ mA}$$


Thus, $i_2 = i_2' + i_2'' + i_2''' = 1.3 \text{ A}$

(b)

$$\begin{aligned} P_{1A} &= (1) [(200)(1 - 1.3)] = 60 \text{ W} \\ P_{200} &= (1 - 1.3)^2 (200) = 18 \text{ W} \\ P_{100V} &= -(1.3)(100) = -130 \text{ W} \\ P_{50} &= (1.3 - 0.5)^2 (50) = 32 \text{ W} \\ P_{0.5A} &= (0.5) [(50)(1.3 - 0.5)] = 20 \text{ W} \end{aligned}$$

Check: $60 + 18 + 32 + 20 = +130$.

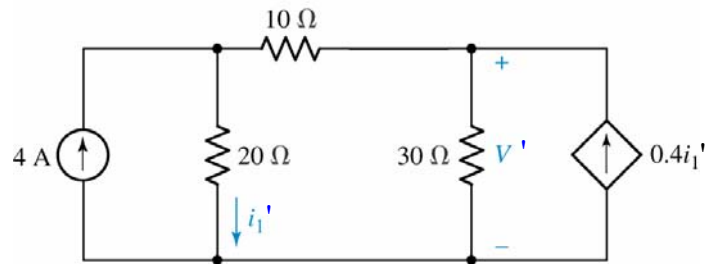10. We find the contribution of the 4-A source by shorting out the 100-V source and analysing the resulting circuit:



$$4 = V_1' / 20 + (V_1' - V') / 10 \quad [1]$$


$$0.4 i_1' = V_1' / 30 + (V' - V_1') / 10 \quad [2]$$

where $i_1' = V_1' / 20$

Simplifying & collecting terms, we obtain $30 V_1' - 20 V' = 800 \quad [1]$

$$-7.2 V_1' + 8 V' = 0 \quad [2]$$

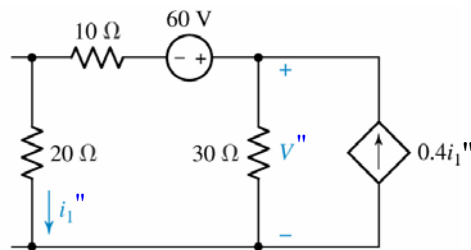Solving, we find that $V' = 60 \text{ V}$. Proceeding to the contribution of the 60-V source, we analyse the following circuit after defining a clockwise mesh current i_a flowing in the left mesh and a clockwise mesh current i_b flowing in the right mesh.



$$30 i_a - 60 + 30 i_a - 30 i_b = 0 \quad [1]$$

$$i_b = -0.4 i_1'' = +0.4 i_a \quad [2]$$

Solving, we find that $i_a = 1.25 \text{ A}$ and so $V'' = 30(i_a - i_b) = 22.5 \text{ V}$.

Thus, $V = V' + V'' = 82.5 \text{ V}$.

11. (a) Linearity allows us to consider this by viewing each source as being scaled by 25/10. This means that the response (v_3) will be scaled by the same factor:

$$25 i_A' / 10 + 25 i_B' / 10 = 25 v_3' / 10$$

$$\therefore v_3 = 25 v_3' / 10 = 25(80) / 10 = \boxed{200 \text{ V}}$$

(b)

$i_A' = 10 \text{ A}, i_B' = 25 \text{ A}$	$\rightarrow v_4' = 100 \text{ V}$
$i_A'' = 10 \text{ A}, i_B'' = 25 \text{ A}$	$\rightarrow v_4'' = -50 \text{ V}$
$i_A = 20 \text{ A}, i_B = -10 \text{ A}$	$\rightarrow v_4 = ?$

We can view this in a somewhat abstract form: the currents i_A and i_B multiply the same circuit parameters regardless of their value; the result is v_4 .

Writing in matrix form, $\begin{bmatrix} 10 & 25 \\ 25 & 10 \end{bmatrix} \begin{bmatrix} a \\ b \end{bmatrix} = \begin{bmatrix} 100 \\ -50 \end{bmatrix}$, we can solve to find

$a = -4.286$ and $b = 5.714$, so that $20a - 10b$ leads to $v_4 = \boxed{-142.9 \text{ V}}$

12. With the current source open-circuited and the 7-V source shorted, we are left with $100\text{k} \parallel (22\text{k} + 4.7\text{k}) = 21.07 \text{ k}\Omega$.

$$\text{Thus, } V_{3\text{V}} = 3 (21.07) / (21.07 + 47) = 0.9286 \text{ V.}$$

In a similar fashion, we find that the contribution of the 7-V source is:

$$V_{7\text{V}} = 7 (31.97) / (31.97 + 26.7) = 3.814 \text{ V}$$

Finally, the contribution of the current source to the voltage V across it is:

$$V_{5\text{mA}} = (5 \times 10^{-3}) (47\text{k} \parallel 100\text{k} \parallel 26.7\text{k}) = 72.75 \text{ V.}$$

$$\text{Adding, we find that } V = 0.9286 + 3.814 + 72.75 = \boxed{77.49 \text{ V.}}$$

13. We must find the current through the 500-k Ω resistor using superposition, and then calculate the dissipated power.

The contribution from the current source may be calculated by first noting that $1\text{M} \parallel 2.7\text{M} \parallel 5\text{M} = 636.8\text{ k}\Omega$. Then,


$$i_{60\mu\text{A}} = 60 \times 10^{-6} \left(\frac{3}{0.5 + 3 + 0.6368} \right) = 43.51\ \mu\text{A}$$

The contribution from the voltage source is found by first noting that $2.7\text{M} \parallel 5\text{M} = 1.753\text{ M}\Omega$. The total current flowing from the voltage source (with the current source open-circuited) is $-1.5 / (3.5 \parallel 1.753 + 1)\ \mu\text{A} = -0.6919\ \mu\text{A}$. The current flowing through the 500-k Ω resistor due to the voltage source acting alone is then

$$i_{1.5\text{V}} = 0.6919 (1.753) / (1.753 + 3.5)\ \text{mA} = 230.9\ \text{nA}.$$


The total current through the 500-k Ω resistor is then $i_{60\mu\text{A}} + i_{1.5\text{V}} = 43.74\ \mu\text{A}$ and the dissipated power is $(43.74 \times 10^{-9})^2 (500 \times 10^3) = 956.6\ \mu\text{W}$.

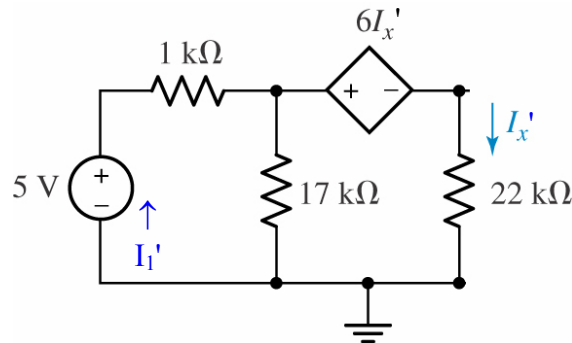14. We first determine the contribution of the voltage source:



Via mesh analysis, we write: $5 = 18000 I_1' - 17000 I_x'$
 $-6 I_x' = -17000 I_x' + 39000 I_x'$

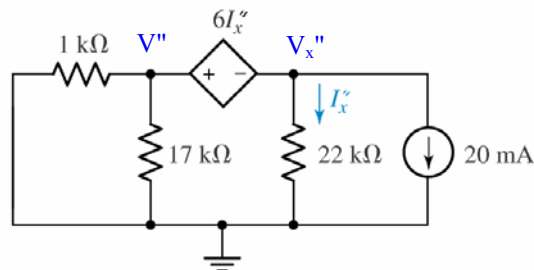Solving, we find $I_1' = 472.1$ mA and $I_x' = 205.8$ mA, so $V' = 17 \times 10^3 (I_1' - I_x') = 4.527$ V. We proceed to find the contribution of the current source:




Via supernode: $-20 \times 10^{-3} = V_x'' / 22 \times 10^3 + V'' / 0.9444 \times 10^3$ [1]
 and $V'' - V_x'' = 6 I_x''$ or $V'' - V_x'' = 6 V_x'' / 22 \times 10^3$ [2]

Solving, we find that $V'' = -18.11$ V. Thus, $V = V' + V'' = -13.58$ V.

The maximum power is $V^2 / 17 \times 10^3 = V^2 / 17$ mW = 250 mW, so
 $V = \sqrt{(17)(250)} = 65.19 = V' - (-18.11)$. Solving, we find $V'_{\max} = 83.3$ V.
 The 5-V source may then be increased by a factor of $83.3 / 4.527$, so that its
 maximum positive value is 92 V; past this value, and the resistor will overheat.

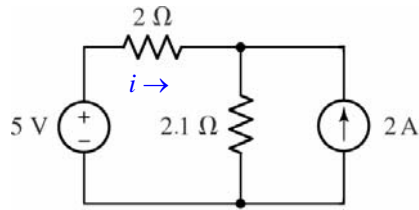15. It is **impossible** to identify the individual contribution of each source to the power dissipated in the resistor; superposition cannot be used for such a purpose.

Simplifying the circuit, we may at least determine the total power dissipated in the resistor:




Via superposition in one step, we may write

$$i = \frac{5}{2 + 2.1} - 2 \frac{2.1}{2 + 2.1} = 195.1 \text{ mA}$$

Thus,

$$P_{2\Omega} = i^2 \cdot 2 = \boxed{76.15 \text{ mW}}$$

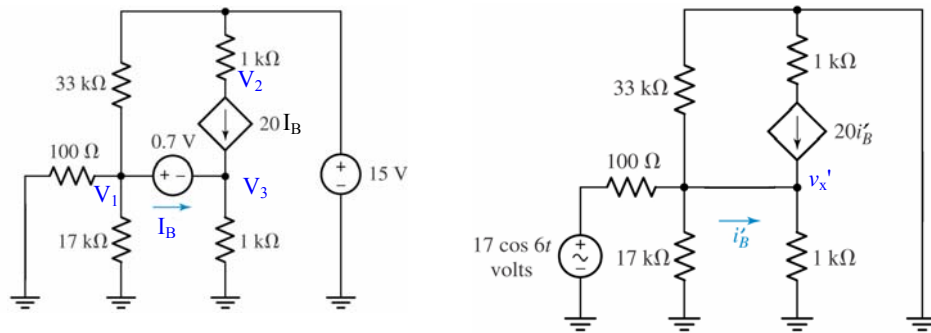16. We will analyse this circuit by first considering the combined effect of both dc sources (left), and then finding the effect of the single ac source acting alone (right).



$$1, 3 \text{ supernode: } V_1/100 + V_1/17 \times 10^3 + (V_1 - 15)/33 \times 10^3 + V_3/10^3 = 20 I_B \quad [1]$$

$$\text{and: } V_1 - V_3 = 0.7 \quad [2]$$

$$\text{Node 2: } -20 I_B = (V_2 - 15)/1000 \quad [3]$$

We require one additional equation if we wish to have I_B as an unknown:

$$20 I_B + I_B = V_3/1000 \quad [4]$$

Simplifying and collecting terms,

$$10.08912 V_1 + V_3 - 20 \times 10^3 I_B = 0.4545 \quad [1]$$

$$V_1 - V_3 = 0.7 \quad [2]$$

$$V_2 + 20 \times 10^3 I_B = 15 \quad [3]$$

$$-V_3 + 21 \times 10^3 I_B = 0 \quad [4]$$

Solving, we find that $I_B = -31.04 \mu\text{A}$.

To analyse the right-hand circuit, we first find the Thévenin equivalent to the left of the wire marked i'_B , noting that the 33-k Ω and 17-k Ω resistors are now in parallel. We find that $V_{\text{TH}} = 16.85 \cos 6t \text{ V}$ by voltage division, and $R_{\text{TH}} = 100 \parallel 17\text{k} \parallel 33\text{k} = 99.12 \Omega$. We may now proceed:


$$20 i'_B = v'_x / 1000 + (v'_x - 16.85 \cos 6t) / 99.12 \quad [1]$$

$$20 i'_B + i'_B = v'_x / 1000 \quad [2]$$

Solving, we find that $i'_B = 798.6 \cos 6t \text{ mA}$. Thus, adding our two results, we find the complete current is

$$i_B = i'_B + I_B = -31.04 + 798.6 \cos 6t \mu\text{A}.$$

17.

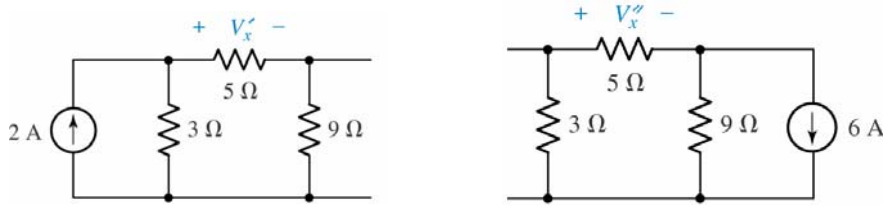

We first consider the effect of the 2-A source separately, using the left circuit:

$$V_x' = 5 \left[2 \frac{3}{3+14} \right] = 1.765 \text{ V}$$




Next we consider the effect of the 6-A source on its own using the right circuit:

$$V_x'' = 5 \left[6 \frac{9}{9+8} \right] = 15.88 \text{ V}$$


Thus, $V_x = V_x' + V_x'' = 17.65 \text{ V}$.

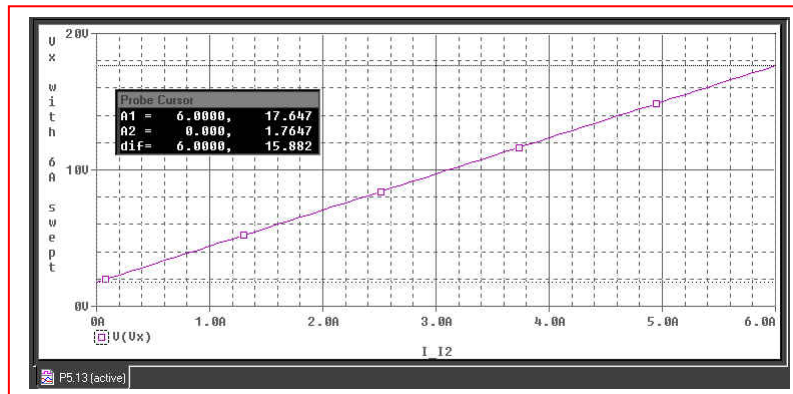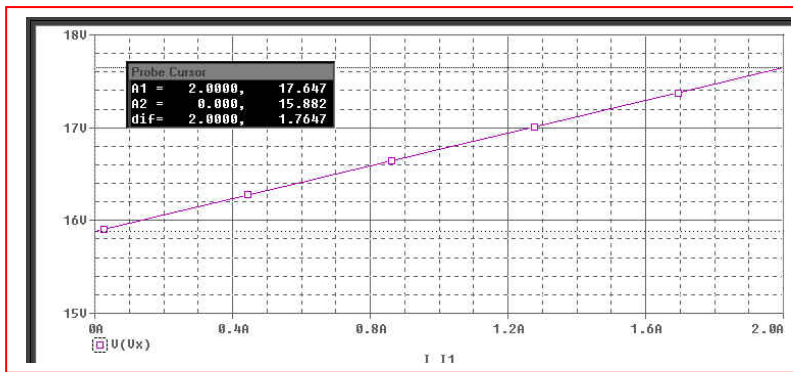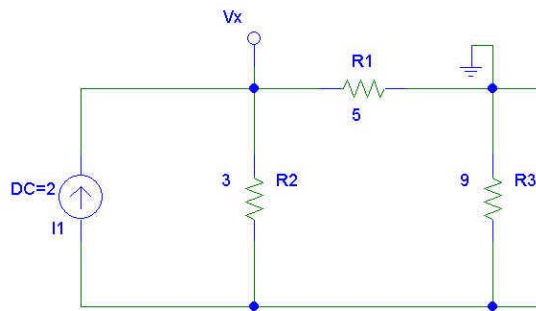(b) PSpice verification (DC Sweep)

The DC sweep results below confirm that $V_x' = 1.765 \text{ V}$



18.

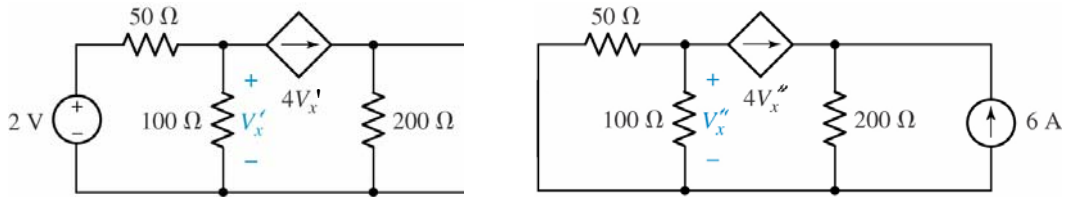

(a) Beginning with the circuit on the left, we find the contribution of the 2-V source to V_x :

$$-4V'_x = \frac{V'_x}{100} + \frac{V'_x - 2}{50}$$

which leads to $V'_x = 9.926 \text{ mV}$.


The circuit on the right yields the contribution of the 6-A source to V_x :

$$-4V''_x = \frac{V''_x}{100} + \frac{V''_x}{50}$$


which leads to $V''_x = 0$.

Thus, $V_x = V'_x + V''_x = 9.926 \text{ mV}$.


(b) PSpice verification.

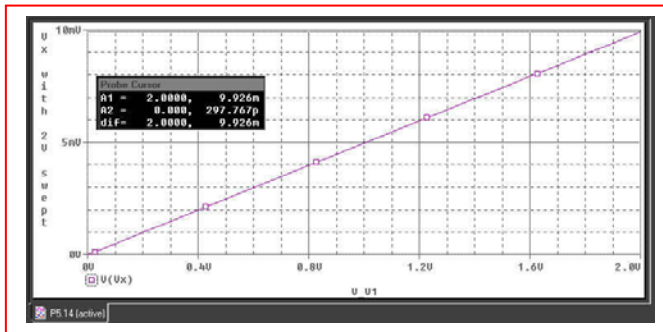

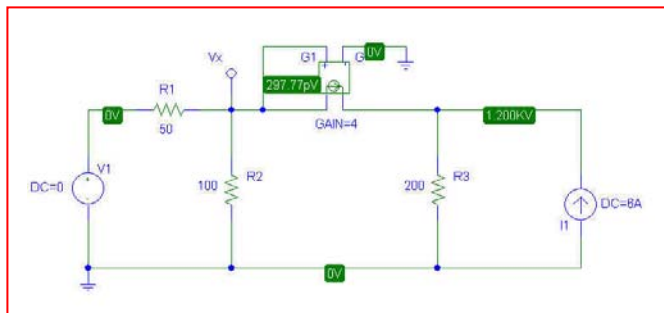As can be seen from the two separate PSpice simulations, our hand calculations are correct; the pV-scale voltage in the second simulation is a result of numerical inaccuracy.




19.

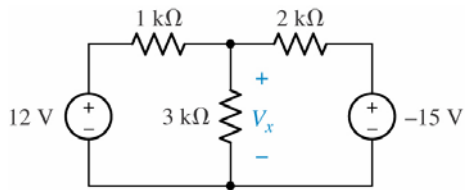


$$\frac{V_x - 12}{1} + \frac{V_x}{3} + \frac{V_x + 15}{2} = 0$$

so $V_x = 2.455 \text{ V}$

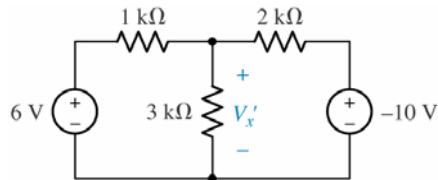

$$\frac{V'_x - 6}{1} + \frac{V'_x}{3} + \frac{V'_x + 10}{2} = 0$$

so $V'_x = 0.5455 \text{ V}$

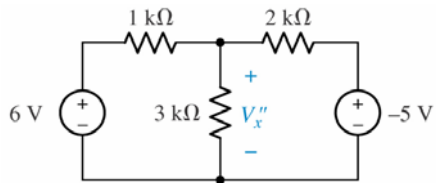


$$\frac{V''_x - 6}{1} + \frac{V''_x}{3} + \frac{V''_x + 5}{2} = 0$$


so $V''_x = 1.909 \text{ V}$

Adding, we find that $V_x' + V_x'' = 2.455 \text{ V} = V_x$ as promised.

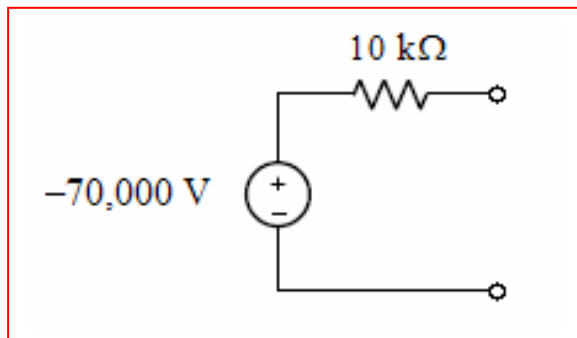
20. (a) We first recognise that the two current sources are in parallel, and hence may be replaced by a single -7 A source (arrow directed downward). This source is in parallel with a 10 k Ω resistor. A simple source transformation therefore yields a 10 k Ω resistor in series with a $(-7)(10,000) = -70,000$ V source (+ reference on top):



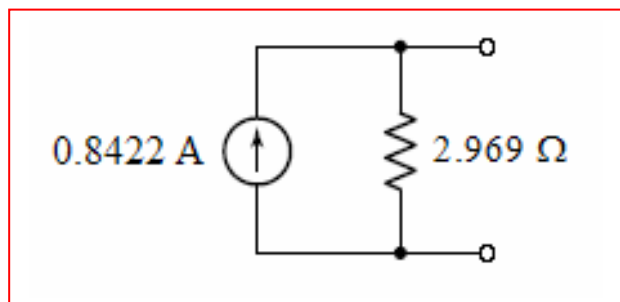- (b) This circuit requires several source transformations. First, we convert the 8 V source and 3 Ω resistor to an $8/3$ A current source in parallel with 3 Ω . This yields a circuit with a 3 Ω and 10 Ω parallel combination, which may be replaced with a 2.308 Ω resistor. We may now convert the $8/3$ A current source and 2.308 Ω resistor to a $(8/3)(2.308) = 6.155$ V voltage source in series with a 2.308 Ω resistor. This modified circuit contains a series combination of 2.308 Ω and 5 Ω ; performing a source transformation yet again, we obtain a current source with value $(6.155)/(2.308 + 5) = 0.8422$ A in parallel with 7.308 Ω and in parallel with the remaining 5 Ω resistor. Since 7.308 $\Omega \parallel 5$ $\Omega = 2.969$ Ω , our solution is:



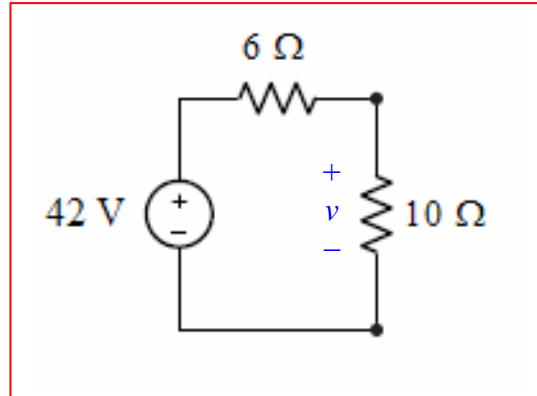
21. (a) First we note the three current sources are in parallel, and may be replaced by a single current source having value $5 - 1 + 3 = 7$ A, arrow pointing upwards. This source is in parallel with the $10\ \Omega$ resistor and the $6\ \Omega$ resistor. Performing a source transformation on the current source and $6\ \Omega$ resistor, we obtain a voltage source $(7)(6) = 42$ V in series with a $6\ \Omega$ resistor and in series with the $10\ \Omega$ resistor:




- (b) By voltage division, $v = 42(10)/16 = 26.25$ V.

- (c) Once the $10\ \Omega$ resistor is involved in a source transformation, it disappears, only to be replaced by a resistor having the same value – but whose current and voltage can be different. Since the quantity v appearing across this resistor is of interest, we cannot involve the resistor in a transformation.

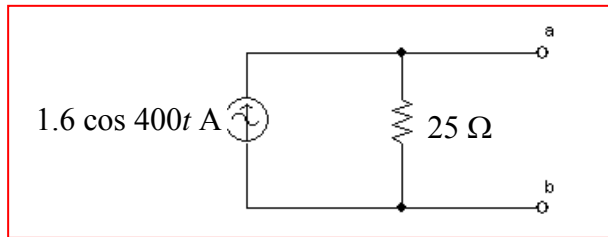
22. (a) $[120 \cos 400t] / 60 = 2 \cos 400t$ A. $60 \parallel 120 = 40 \Omega$.
 $[2 \cos 400t] (40) = 80 \cos 400t$ V. $40 + 10 = 50 \Omega$.
 $[80 \cos 400t] / 50 = 1.6 \cos 400t$ A. $50 \parallel 50 = 25 \Omega$.



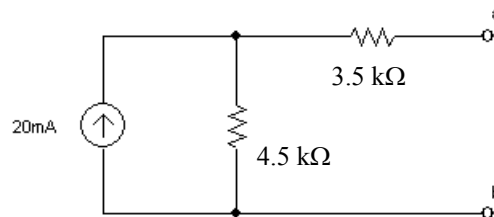- (b) $2k \parallel 3k + 6k = 7.2 \text{ k}\Omega$. $7.2k \parallel 12k = 4.5 \text{ k}\Omega$



$(20)(4.5) = 90$ V.

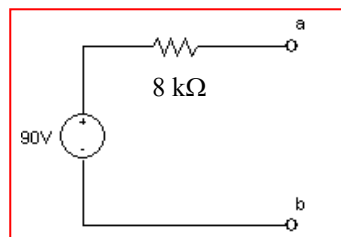


23. We can ignore the 1-k Ω resistor, at least when performing a source transformation on this circuit, as the 1-mA source will pump 1 mA through *whatever* value resistor we place there. So, we need only combine the 1 and 2 mA sources (which are in parallel once we replace the 1-k Ω resistor with a 0- Ω resistor). The current through the 5.8-k Ω resistor is then simply given by voltage division:

$$i = 3 \times 10^{-3} \frac{4.7}{4.7 + 5.8} = 1.343 \text{ mA}$$

The power dissipated by the 5.8-k Ω resistor is then $i^2 \cdot 5.8 \times 10^3 = 10.46 \text{ mW}$.


(Note that we did not “transform” either source, but rather drew on the relevant discussion to understand why the 1-k Ω resistor could be omitted.)

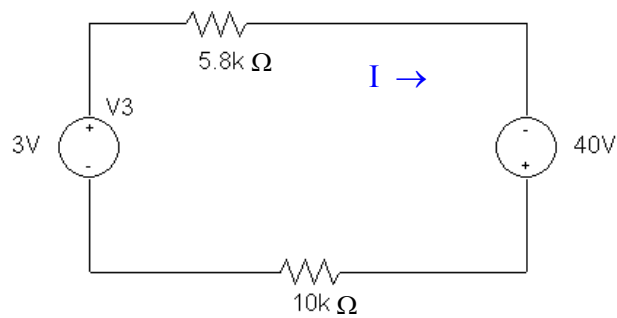24. We may ignore the 10-k Ω and 9.7-k Ω resistors, as 3-V will appear across them regardless of their value. Performing a quick source transformation on the 10-k Ω resistor/ 4-mA current source combination, we replace them with a 40-V source in series with a 10-k Ω resistor:



$$I = 43 / 15.8 \text{ mA} = 2.722 \text{ mA}. \text{ Therefore, } P_{5.8\Omega} = I^2 \cdot 5.8 \times 10^3 = \boxed{42.97 \text{ mW}}.$$

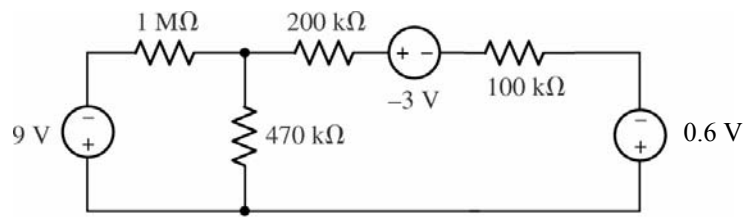
25. $(100 \text{ k}\Omega)(6 \text{ mA}) = 0.6 \text{ V}$



$$470 \text{ k} \parallel 300 \text{ k} = 183.1 \text{ k}\Omega$$

$$(-3 - 0.6) / 300 \times 10^3 = -12 \text{ }\mu\text{A}$$

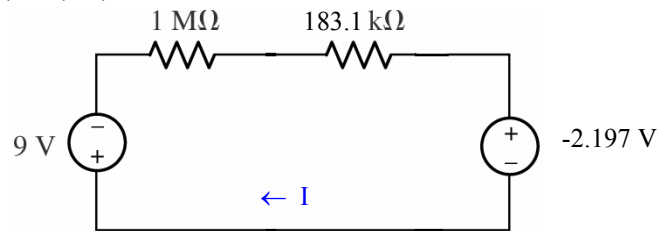
$$(183.1 \text{ k}\Omega)(-12 \text{ }\mu\text{A}) = -2.197 \text{ V}$$



Solving, $9 + 1183.1 \times 10^3 I - 2.197 = 0$, so $I = -5.750 \text{ }\mu\text{A}$. Thus,

$$P_{1\text{M}\Omega} = I^2 \cdot 10^6 = \boxed{33.06 \text{ }\mu\text{W}}$$

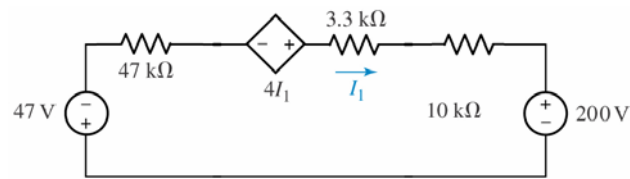26. (1)(47) = 47 V. (20)(10) = 200 V. Each voltage source “+” corresponds to its corresponding current source’s arrow head.




Using KVL on the simplified circuit above,

$$47 + 47 \times 10^3 I_1 - 4 I_1 + 13.3 \times 10^3 I_1 + 200 = 0$$

Solving, we find that $I_1 = -247 / (60.3 \times 10^3 - 4) = -4.096 \text{ mA}$.

27. (a) $(2 V_1)(17) = 34 V_1$

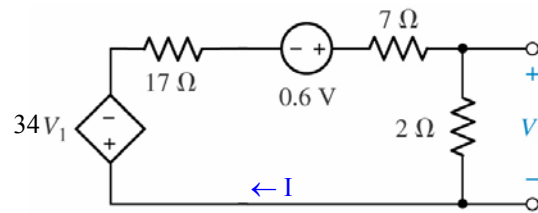


Analysing the simplified circuit above,

$$34 V_1 - 0.6 + 7 I + 2 I + 17 I = 0 \quad [1] \quad \text{and} \quad V_1 = 2 I \quad [2]$$


Substituting, we find that $I = 0.6 / (68 + 7 + 2 + 17) = 6.383 \text{ mA}$. Thus,

$$V_1 = 2 I = \boxed{12.77 \text{ mV}}$$


(b)

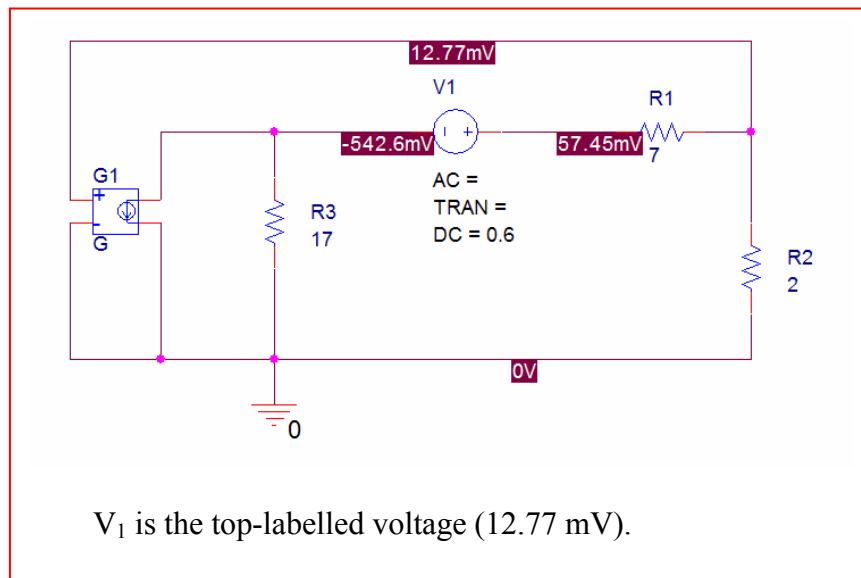

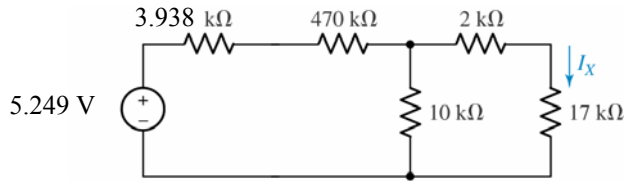
28. (a) $12 / 9000 = 1.333 \text{ mA}$. $9 \text{ k} \parallel 7 \text{ k} = 3.938 \text{ k}\Omega$. $\rightarrow (1.333 \text{ mA})(3.938 \text{ k}\Omega) = 5.249 \text{ V}$.


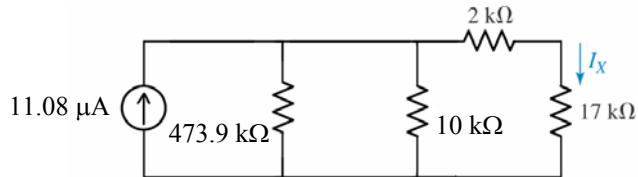
$$5.249 / 473.938 \times 10^3 = 11.08 \text{ }\mu\text{A}$$



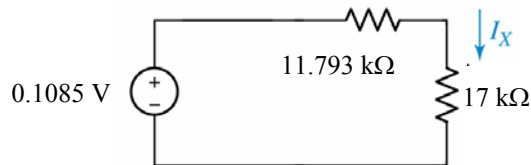
$$473.9 \text{ k} \parallel 10 \text{ k} = 9.793 \text{ k}\Omega. (11.08 \text{ mA})(9.793 \text{ k}\Omega) = 0.1085 \text{ V}$$




$$I_x = 0.1085 / 28.793 \times 10^3 = 3.768 \text{ }\mu\text{A}.$$

(b)

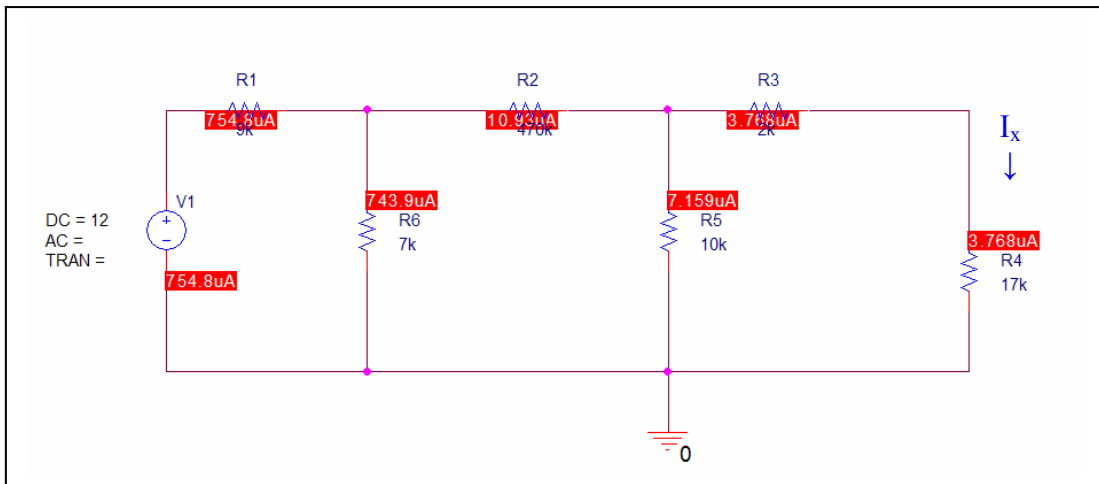

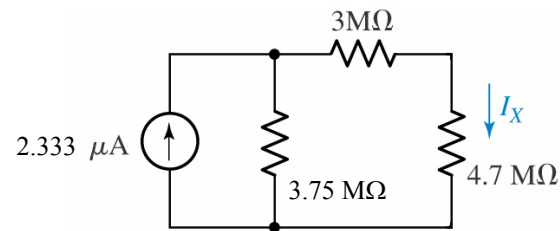
29. First, $(-7 \mu\text{A})(2 \text{ M}\Omega) = -14 \text{ V}$, “+” reference down. $2 \text{ M}\Omega + 4 \text{ M}\Omega = 6 \text{ M}\Omega$.
 $+14 \text{ V} / 6 \text{ M}\Omega = 2.333 \mu\text{A}$, arrow pointing up; $6 \text{ M}\Omega \parallel 10 \text{ M}\Omega = 3.75 \text{ M}\Omega$.



$$(2.333)(3.75) = 8.749 \text{ V. } R_{\text{eq}} = 6.75 \text{ M}\Omega$$


$$\therefore I_x = 8.749 / (6.75 + 4.7) \mu\text{A} = \boxed{764.1 \text{ nA}}$$

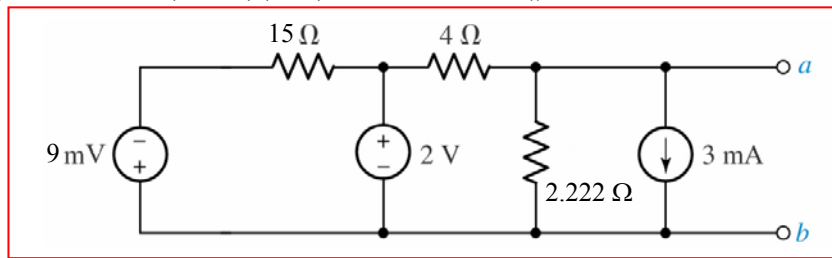30. To begin, note that $(1 \text{ mA})(9 \Omega) = 9 \text{ mV}$, and $5 \parallel 4 = 2.222 \Omega$.



The above circuit may not be further simplified using only source transformation techniques.

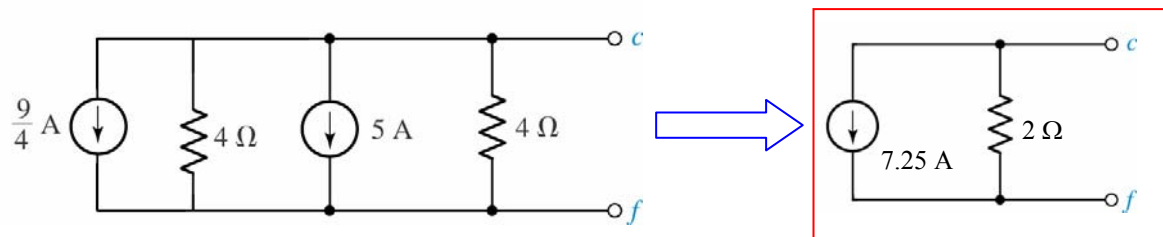31. Label the “-” terminal of the 9-V source node **x** and the other terminal node **x'**. The 9-V source will force the voltage across these two terminals to be -9 V regardless of the value of the current source and resistor to its left. These two components may therefore be neglected from the perspective of terminals **a** & **b**. Thus, we may draw:



32. Beware of the temptation to employ superposition to compute the dissipated power- *it won't work!*


Instead, define a current I flowing into the bottom terminal of the $1\text{-M}\Omega$ resistor. Using superposition to compute this current,

$$I = 1.8 / 1.840 + 0 + 0 \text{ }\mu\text{A} = 978.3 \text{ nA.}$$

Thus,

$$P_{1\text{M}\Omega} = (978.3 \times 10^{-9})^2 (10^6) = \boxed{957.1 \text{ nW.}}$$

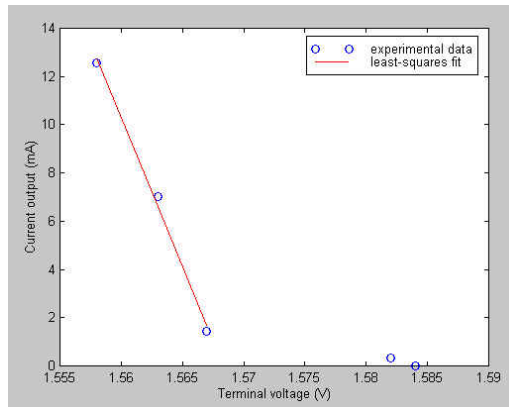33. Let's begin by plotting the experimental results, along with a least-squares fit to part of the data:



Least-squares fit results:

Voltage (V)	Current (mA)
1.567	1.6681
1.563	6.599
1.558	12.763

We see from the figure that we cannot draw a very good line through all data points representing currents from 1 mA to 20 mA. We have therefore chosen to perform a linear fit for the three lower voltages only, as shown. Our model will not be as accurate at 1 mA; there is no way to know if our model will be accurate at 20 mA, since that is beyond the range of the experimental data.


Modeling this system as an ideal voltage source in series with a resistance (representing the internal resistance of the battery) and a varying load resistance, we may write the following two equations based on the linear fit to the data:

$$1.567 = V_{\text{src}} - R_s (1.6681 \times 10^{-3})$$

$$1.558 = V_{\text{src}} - R_s (12.763 \times 10^{-3})$$

Solving, $V_{\text{src}} = 1.568 \text{ V}$ and $R_s = 811.2 \text{ m}\Omega$. It should be noted that depending on the line fit to the experimental data, these values can change somewhat, particularly the series resistance value.

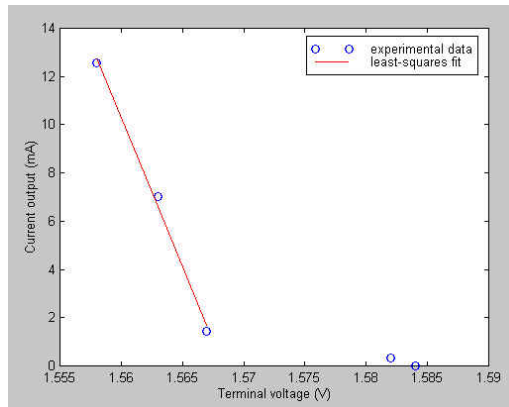34. Let's begin by plotting the experimental results, along with a least-squares fit to part of the data:



Least-squares fit results:

Voltage (V)	Current (mA)
1.567	1.6681
1.563	6.599
1.558	12.763

We see from the figure that we cannot draw a very good line through all data points representing currents from 1 mA to 20 mA. We have therefore chosen to perform a linear fit for the three lower voltages only, as shown. Our model will not be as accurate at 1 mA; there is no way to know if our model will be accurate at 20 mA, since that is beyond the range of the experimental data.

Modeling this system as an ideal current source in parallel with a resistance R_p (representing the internal resistance of the battery) and a varying load resistance, we may write the following two equations based on the linear fit to the data:

$$1.6681 \times 10^{-3} = I_{\text{src}} - 1.567 / R_p$$

$$12.763 \times 10^{-3} = I_{\text{src}} - 1.558 / R_p$$


Solving, $I_{\text{src}} = 1.933 \text{ A}$ and $R_s = 811.2 \text{ m}\Omega$. It should be noted that depending on the line fit to the experimental data, these values can change somewhat, particularly the series resistance value.

35. Working from left to right,

$$2 \mu\text{A} - 1.8 \mu\text{A} = 200 \text{ nA, arrow up.}$$

$$1.4 \text{ M}\Omega + 2.7 \text{ M}\Omega = 4.1 \text{ M}\Omega$$

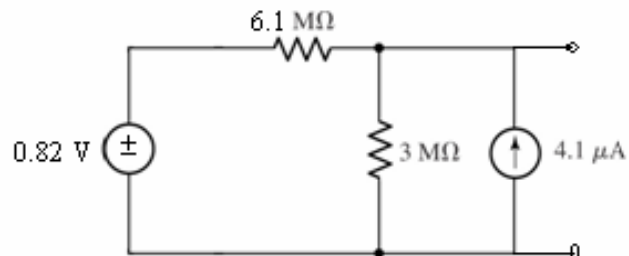A transformation to a voltage source yields $(200 \text{ nA})(4.1 \text{ M}\Omega) = 0.82 \text{ V}$ in series with $4.1 \text{ M}\Omega + 2 \text{ M}\Omega = 6.1 \text{ M}\Omega$, as shown below:




Then, $0.82 \text{ V} / 6.1 \text{ M}\Omega = 134.4 \text{ nA}$, arrow up.

$$6.1 \text{ M}\Omega \parallel 3 \text{ M}\Omega = 2.011 \text{ M}\Omega$$


$4.1 \mu\text{A} + 134.4 \text{ nA} = 4.234 \text{ mA}$, arrow up.

$$(4.234 \mu\text{A})(2.011 \text{ M}\Omega) = 8.515 \text{ V.}$$

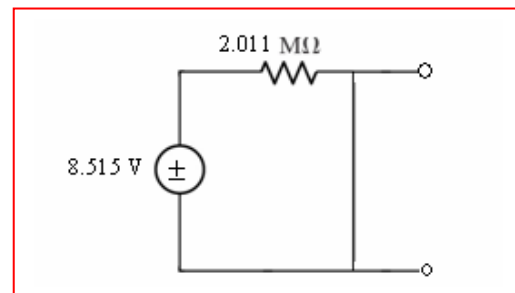
The final circuit is an 8.515 V voltage source in series with a 2.011 MΩ resistor, as shown:



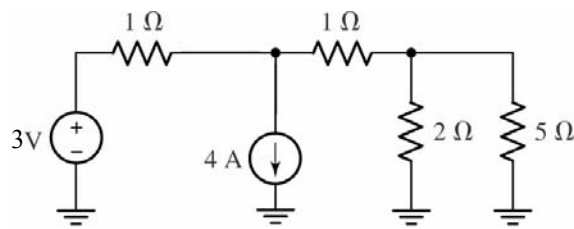36. To begin, we note that the 5-V and 2-V sources are in series:



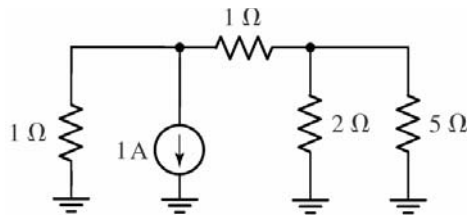
Next, noting that $3\text{ V} / 1\ \Omega = 3\text{ A}$, and $4\text{ A} - 3\text{ A} = +1\text{ A}$ (arrow down), we obtain:



The left-hand resistor and the current source are easily transformed into a 1-V source in series with a 1-Ω resistor:


By voltage division, the voltage across the 5-Ω resistor in the circuit to the right is:
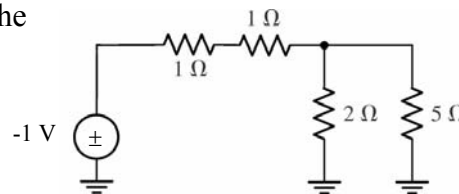
$$(-1) \frac{2 \parallel 5}{2 \parallel 5 + 2} = -0.4167\text{ V.}$$




Thus, the power dissipated by the 5-Ω resistor is $(-0.4167)^2 / 5 = 34.73\text{ mW}$.

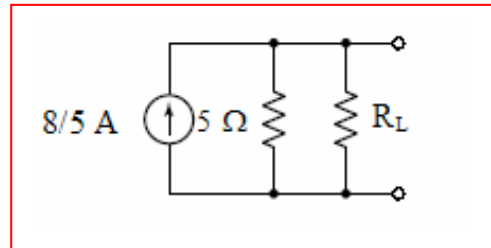37. (a) We may omit the $10\ \Omega$ resistor from the circuit, as it does not affect the voltage or current associated with R_L since it is in parallel with the voltage source. We are thus left with an $8\ \text{V}$ source in series with a $5\ \Omega$ resistor. These may be transformed to an $8/5\ \text{A}$ current source in parallel with $5\ \Omega$, in parallel with R_L .



(b)

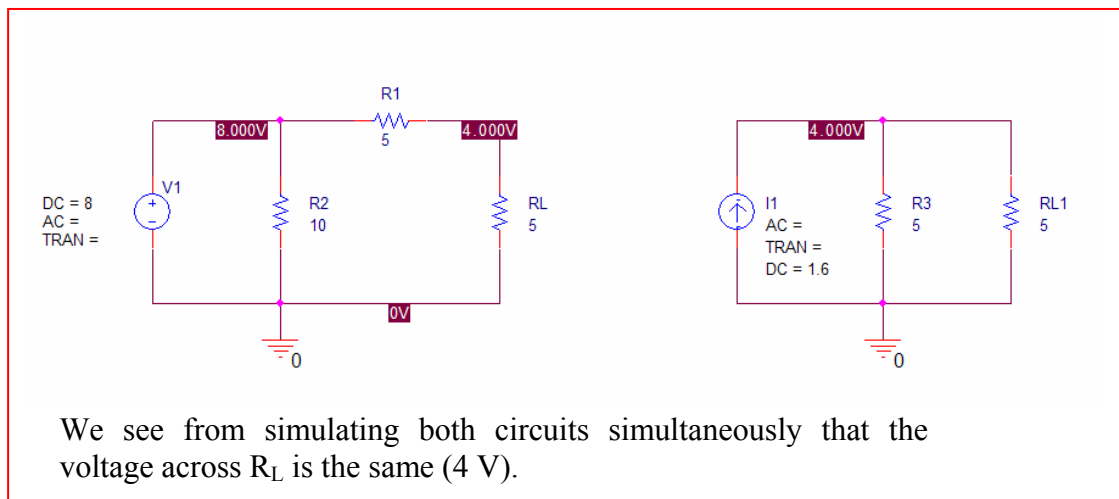


38. (a) We may begin by omitting the $7\ \Omega$ and $1\ \Omega$ resistors. Performing the indicated source transformations, we find a $6/4\ \text{A}$ source in parallel with $4\ \Omega$, and a $5/10\ \text{A}$ source in parallel with $10\ \Omega$. These are both in parallel with the series combination of the two $5\ \Omega$ resistors. Since $4\ \Omega \parallel 10\ \Omega = 2.857\ \Omega$, and $6/4 + 5/10 = 2\ \text{A}$, we may further simplify the circuit to a single current source ($2\ \text{A}$) in parallel with $2.857\ \Omega$ and the series combination of two $5\ \Omega$ resistors. Simple current division yields the current flowing through the $5\ \Omega$ resistors:

$$I = \frac{2(2.857)}{2.857 + 10} = 0.4444\ \text{A}$$

The power dissipated in either of the $5\ \Omega$ resistors is then $I^2R = 987.6\ \text{mW}$.

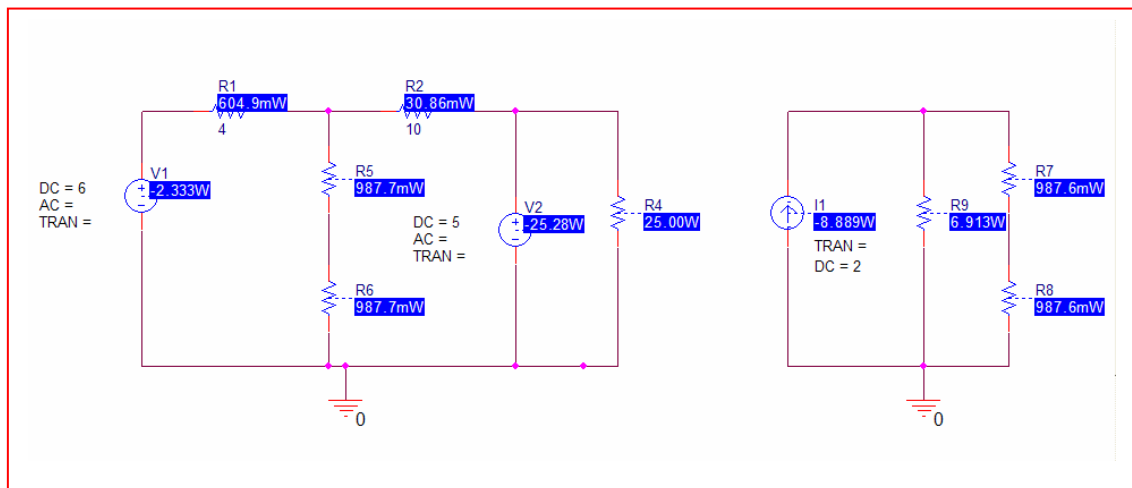- (b) We note that PSpice will NOT allow the $7\ \Omega$ resistor to be left floating! For both circuits simulated, we observe $987.6\ \text{mW}$ of power dissipated for the $5\ \Omega$ resistor, confirming our analytic solution.



- (c) Neither does. No current flows through the $7\ \Omega$ resistor; the $1\ \Omega$ resistor is in parallel with a voltage source and hence cannot affect any other part of the circuit.

39. We obtain a $5v_3/4$ A current source in parallel with 4Ω , and a 3 A current source in parallel with 2Ω . We now have two dependent current sources in parallel, which may be combined to yield a single $-0.75v_3$ current source (arrow pointing upwards) in parallel with 4Ω . Selecting the bottom node as a reference terminal, and naming the top left node V_x and the top right node V_y , we write the following equations:

$$-0.75v_3 = V_x/4 + (V_x - V_y)/3$$

$$3 = V_y/2 + (V_y - V_x)/3$$

$$v_3 = V_y - V_x$$

Solving, we find that $v_3 = -2$ V.

40. (a) $R_{TH} = 25 \parallel (10 + 15) = 25 \parallel 25 = 12.5 \Omega.$

$$V_{TH} = V_{ab} = 50 \left(\frac{25}{10 + 15 + 25} \right) + 100 \left(\frac{15 + 10}{15 + 10 + 25} \right) = 75 \text{ V.}$$

(b) If $R_{ab} = 50 \Omega,$

$$P_{50\Omega} = \left[75 \left(\frac{50}{50 + 12.5} \right) \right]^2 \left(\frac{1}{50} \right) = 72 \text{ W}$$

(c) If $R_{ab} = 12.5 \Omega,$

$$P_{12.5\Omega} = \left[75 \left(\frac{12.5}{12.5 + 12.5} \right) \right]^2 \left(\frac{1}{12.5} \right) = 112.5 \text{ W}$$

41. (a) Shorting the 14 V source, we find that $R_{TH} = 10 \parallel 20 + 10 = 16.67 \Omega$.

Next, we find V_{TH} by determining V_{OC} (recognising that the right-most 10 Ω resistor carries no current, hence we have a simple voltage divider):


$$V_{TH} = V_{OC} = 14 \frac{10+10}{10+10+10} = 9.333 \text{ V}$$

Thus, our Thevenin equivalent is a 9.333 V source in series with a 16.67 Ω resistor, which is in series with the 5 Ω resistor of interest.

- (b) $I_{5\Omega} = 9.333 / (5 + 16.67) = 0.4307 \text{ A}$. Thus,

$$P_{5\Omega} = (0.4307)^2 \cdot 5 = \boxed{927.5 \text{ mW}}$$

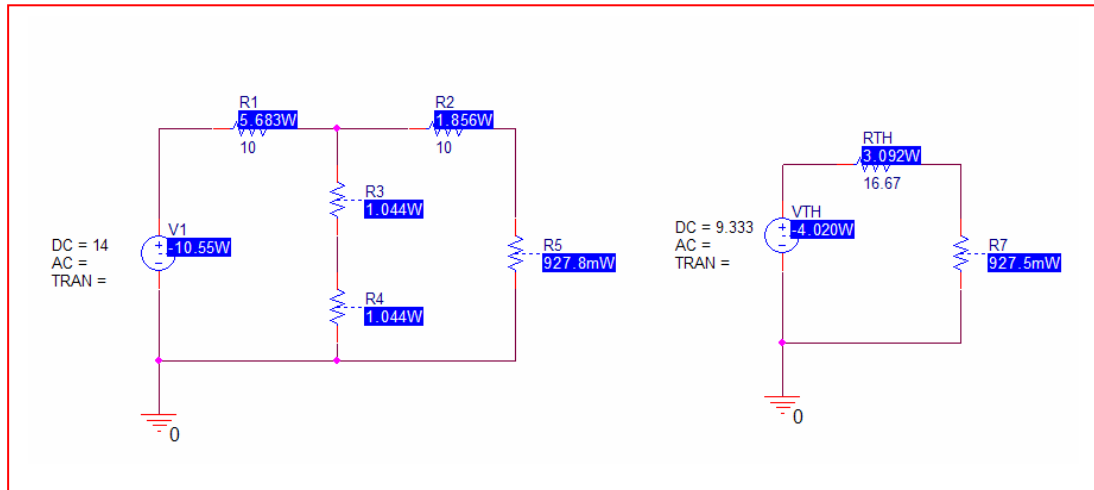- (c) We see from the PSpice simulation that keeping four significant digits in calculating the Thévenin equivalent yields at least 3 digits' agreement in the results.



42. (a) Replacing the $7\ \Omega$ resistor with a short circuit, we find

$$I_{SC} = 15(8)/10 = 12\text{ A.}$$

Removing the short circuit, and open-circuiting the 15 A source, we see that

$$R_{TH} = 2 + 8 = 10\ \Omega.$$

$$\text{Thus, } V_{TH} = I_{SC}R_{TH} = (12)(10) = 120\text{ V.}$$

Our Thévenin equivalent is therefore a 120 V source in series with $10\ \Omega$.

- (b) As found above, $I_N = I_{SC} = 12\text{ A}$, and $R_{TH} = 10\ \Omega$.

- (c) Using the Thévenin equivalent circuit, we may find v_1 using voltage division:

$$v_1 = 120(7)/17 = 49.41\text{ V.}$$

Using the Norton equivalent circuit and a combination of current division and Ohm's law, we find

$$v_1 = 7\left(12\frac{10}{17}\right) = 49.41\text{ V}$$

As expected, the results are equal.

- (d) Employing the more convenient Thévenin equivalent model,

$$v_1 = 120(1)/17 = 7.059\text{ V.}$$

43. (a) $R_{TH} = 10 \text{ mV} / 400 \text{ } \mu\text{A} = 25 \text{ } \Omega$

(b) $R_{TH} = 110 \text{ V} / 363.6 \times 10^{-3} \text{ A} = 302.5 \text{ } \Omega$

(c) Increased current leads to increased filament temperature, which results in a higher resistance (as measured). This means the Thévenin equivalent must apply to the specific current of a particular circuit – one model is not suitable for all operating conditions (the light bulb is nonlinear).

44. (a) We begin by shorting both voltage sources, and removing the $1\ \Omega$ resistor of interest. Looking into the terminals where the $1\ \Omega$ resistor had been connected, we see that the $9\ \Omega$ resistor is shorted out, so that

$$R_{TH} = (5 + 10) \parallel 10 + 10 = 16\ \Omega.$$

To continue, we return to the original circuit and replace the $1\ \Omega$ resistor with a short circuit. We define three clockwise mesh currents: i_1 in the left-most mesh, i_2 in the top-right mesh, and i_{sc} in the bottom right mesh. Writing our three mesh equations,

$$\begin{aligned} -4 + 9i_1 - 9i_2 + 3 &= 0 \\ -9i_1 + 34i_2 - 10i_{sc} &= 0 \\ -3 - 10i_2 + 20i_{sc} &= 0 \end{aligned}$$

Solving using MATLAB:

```
>> e1 = '-4 + 9*i1 - 9*i2 + 3 = 0';
>> e2 = '-9*i1 + 34*i2 - 10*isc = 0';
>> e3 = '-3 + 20*isc - 10*i2 = 0';
>> a = solve(e1,e2,e3,'i1','i2','isc');
```


we find $i_{sc} = 0.2125\ \text{A}$, so $I_N = 212.5\ \text{mA}$ and $V_{TH} = I_N R_{TH} = (0.2125)(16) = 3.4\ \text{V}$.

(b) Working with the Thévenin equivalent circuit, $I_{1\Omega} = V_{TH}/(R_{TH} + 1) = 200\ \text{mA}$. Thus, $P_{1\Omega} = (0.2)2.1 = 40\ \text{mW}$.


Switching to the Norton equivalent, we find $I_{1\Omega}$ by current division:

$I_{1\Omega} = (0.2125)(16)/(16+1) = 200\ \text{mA}$. Once again, $P_{1\Omega} = 40\ \text{mW}$ (as expected).

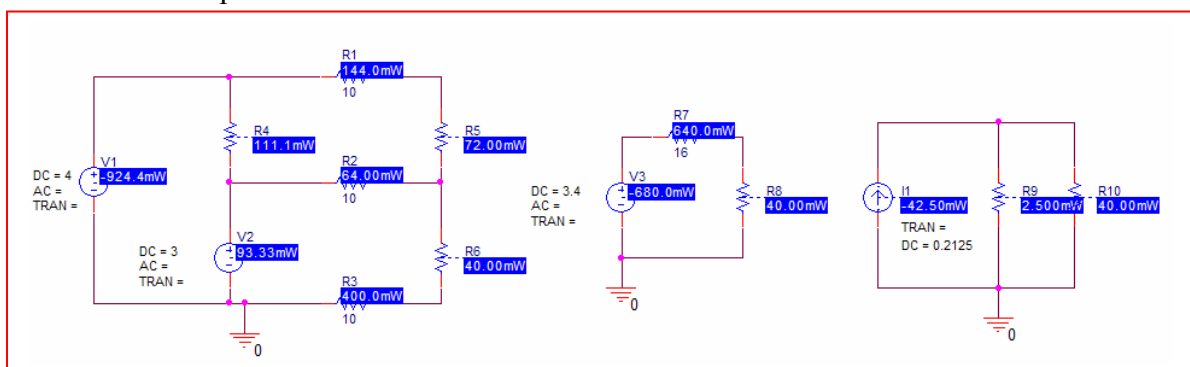(c) As we can see from simulating the original circuit simultaneously with its Thévenin and Norton equivalents, the $1\ \Omega$ resistor does in fact dissipate $40\ \text{mW}$, and either equivalent is equally applicable. Note all three SOURCES provide a different amount of power in total.



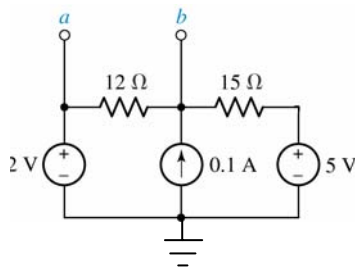45. (a) Removing terminal **c**, we need write only one nodal equation:



$$0.1 = \frac{V_b - 2}{12} + \frac{V_b - 5}{15}, \text{ which may be solved to}$$

yield $V_b = 4 \text{ V}$. Therefore, $V_{ab} = V_{TH} = 2 - 4 = -2 \text{ V}$.

$R_{TH} = 12 \parallel 15 = 6.667 \Omega$. We may then calculate I_N as $I_N = V_{TH} / R_{TH}$

$$= -300 \text{ mA (arrow pointing upwards).}$$

- (b) Removing terminal **a**, we again find $R_{TH} = 6.667 \Omega$, and only need write a single nodal equation; in fact, it is identical to that written for the circuit above, and we once again find that $V_b = 4 \text{ V}$. In this case, $V_{TH} = V_{bc} = 4 - 5 = -1 \text{ V}$, so $I_N = -1 / 6.667 = -150 \text{ mA (arrow pointing upwards)}$.

46. (a) Shorting out the 88-V source and open-circuiting the 1-A source, we see looking into the terminals x and x' a 50-Ω resistor in parallel with 10 Ω in parallel with (20 Ω + 40 Ω), so

$$R_{TH} = 50 \parallel 10 \parallel (20 + 40) = 7.317 \Omega$$

Using superposition to determine the voltage $V_{xx'}$ across the 50-Ω resistor, we find

$$\begin{aligned} V_{xx'} = V_{TH} &= \left[88 \frac{50 \parallel (20 + 40)}{10 + [50 \parallel (20 + 40)]} \right] + (1)(50 \parallel 10) \left[\frac{40}{40 + 20 + (50 \parallel 10)} \right] \\ &= \left[88 \frac{27.27}{37.27} \right] + (1)(8.333) \left[\frac{40}{40 + 20 + 8.333} \right] = 69.27 \text{ V} \end{aligned}$$

- (b) Shorting out the 88-V source and open-circuiting the 1-A source, we see looking into the terminals y and y' a 40-Ω resistor in parallel with [20 Ω + (10 Ω || 50 Ω)]:

$$R_{TH} = 40 \parallel [20 + (10 \parallel 50)] = 16.59 \Omega$$

Using superposition to determine the voltage $V_{yy'}$ across the 1-A source, we find

$$\begin{aligned} V_{yy'} = V_{TH} &= (1)(R_{TH}) + \left[88 \frac{27.27}{10 + 27.27} \right] \left(\frac{40}{20 + 40} \right) \\ &= 59.52 \text{ V} \end{aligned}$$

47. (a) Select terminal **b** as the reference terminal, and define a nodal voltage V_1 at the top of the 200- Ω resistor. Then,

$$0 = \frac{V_1 - 20}{40} + \frac{V_1 - V_{TH}}{100} + \frac{V_1}{200} \quad [1]$$

$$1.5 i_1 = (V_{TH} - V_1)/100 \quad [2]$$


where $i_1 = V_1/200$, so Eq. [2] becomes $150 V_1/200 + V_1 - V_{TH} = 0$ [2]

Simplifying and collecting terms, these equations may be re-written as:

$$(0.25 + 0.1 + 0.05) V_1 - 0.1 V_{TH} = 5 \quad [1]$$

$$(1 + 15/20) V_1 - V_{TH} = 0 \quad [2]$$

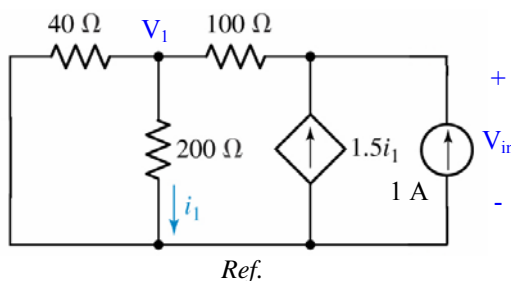Solving, we find that $V_{TH} = 38.89 \text{ V}$. To find R_{TH} , we short the voltage source and inject 1 A into the port:



$$0 = \frac{V_1 - V_{in}}{100} + \frac{V_1}{40} + \frac{V_1}{200} \quad [1]$$

$$1.5 i_1 + 1 = \frac{V_{in} - V_1}{100} \quad [2]$$

$$i_1 = V_1/200 \quad [3]$$

Combining Eqs. [2] and [3] yields $1.75 V_1 - V_{in} = -100$ [4]

Solving Eqs. [1] & [4] then results in $V_{in} = 177.8 \text{ V}$, so that $R_{TH} = V_{in}/1 \text{ A} = 177.8 \Omega$.

- (b) Adding a 100- Ω load to the original circuit or our Thévenin equivalent, the voltage across the load is

$$V_{100\Omega} = V_{TH} \left(\frac{100}{100 + 177.8} \right) = 14.00 \text{ V}, \text{ and so } P_{100\Omega} = (V_{100\Omega})^2 / 100 = 1.96 \text{ W}.$$

48. We inject a current of 1 A into the port (arrow pointing up), select the bottom terminal as our reference terminal, and define the nodal voltage V_x across the 200- Ω resistor.

$$\text{Then,} \quad 1 = V_1/100 + (V_1 - V_x)/50 \quad [1]$$

$$-0.1 V_1 = V_x/200 + (V_x - V_1)/50 \quad [2]$$

which may be simplified to

$$3 V_1 - 2 V_x = 100 \quad [1]$$


$$16 V_1 + 5 V_x = 0 \quad [2]$$

Solving, we find that $V_1 = 10.64$ V, so $R_{TH} = V_1/(1 \text{ A}) = 10.64 \Omega$.

Since there are no independent sources present in the original network, $I_N = 0$.

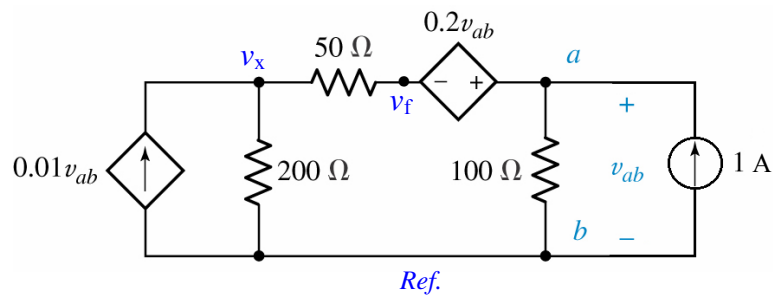49. With no independent sources present, $V_{TH} = 0$.

We decide to inject a 1-A current into the port:



$$\text{Node 'x':} \quad 0.01 v_{ab} = v_x / 200 + (v_x - v_f) / 50 \quad [1]$$

$$\text{Supernode:} \quad 1 = v_{ab} / 100 + (v_f - v_x) \quad [2]$$

$$\text{and:} \quad v_{ab} - v_f = 0.2 v_{ab} \quad [3]$$

Rearranging and collecting terms,


$$-2 v_{ab} + 5 v_x - 4 v_f = 0 \quad [1]$$

$$v_{ab} - 2 v_x + 2 v_f = 100 \quad [2]$$

$$0.8 v_{ab} - v_f = 0 \quad [3]$$

Solving, we find that $v_{ab} = 192.3 \text{ V}$, so $R_{TH} = v_{ab} / (1 \text{ A}) = 192.3 \Omega$.

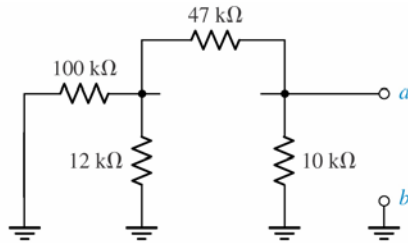50. We first find R_{TH} by shorting out the voltage source and open-circuiting the current source.



Looking into the terminals **a** & **b**, we see
 $R_{TH} = 10 \parallel [47 + (100 \parallel 12)]$
 $= 8.523 \Omega.$

Returning to the original circuit, we decide to perform nodal analysis to obtain V_{TH} :

$$-12 \times 10^3 = (V_1 - 12) / 100 \times 10^3 + V_1 / 12 \times 10^3 + (V_1 - V_{TH}) / 47 \times 10^3 \quad [1]$$

$$12 \times 10^3 = V_{TH} / 10 \times 10^3 + (V_{TH} - V_1) / 47 \times 10^3 \quad [2]$$

Rearranging and collecting terms,

$$0.1146 V_1 - 0.02128 V_{TH} = -11.88 \quad [1]$$

$$-0.02128 V_1 + 0.02128 V_{TH} = 12 \quad [2]$$

Solving, we find that $V_{TH} = 83.48 \text{ V}.$


51. (a) $R_{TH} = 4 + 2 \parallel 2 + 10 = 15 \Omega.$
(b) same as above: $15 \Omega.$

52. For Fig. 5.78a, $I_N = 12 / \sim 0 \rightarrow \infty \text{ A in parallel with } \sim 0 \Omega.$

For Fig. 5.78b, $V_{TH} = (2)(\sim \infty) \rightarrow \infty \text{ V in series with } \sim \infty \Omega.$

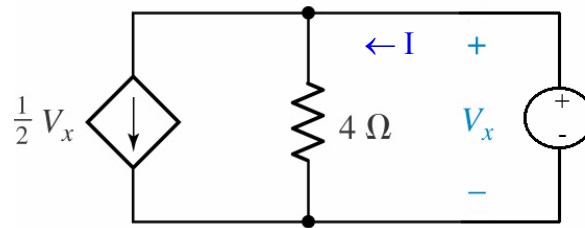53. With no independent sources present, $V_{TH} = 0$.

Connecting a 1-V source to the port and measuring the current that flows as a result,



$$I = 0.5 V_x + 0.25 V_x = 0.5 + 0.25 = 0.75 \text{ A.}$$

$$R_{TH} = 1/I = 1.333 \Omega.$$

The Norton equivalent is 0 A in parallel with 1.333 Ω .

54. Performing nodal analysis to determine V_{TH} ,

$$100 \times 10^{-3} = V_x / 250 + V_{oc} / 7.5 \times 10^3 \quad [1]$$


$$\text{and } V_x - V_{oc} = 5 i_x$$

where $i_x = V_x / 250$. Thus, we may write the second equation as

$$0.98 V_x - V_{oc} = 0 \quad [2]$$

Solving, we find that $V_{oc} = V_{TH} = 23.72 \text{ V}$.

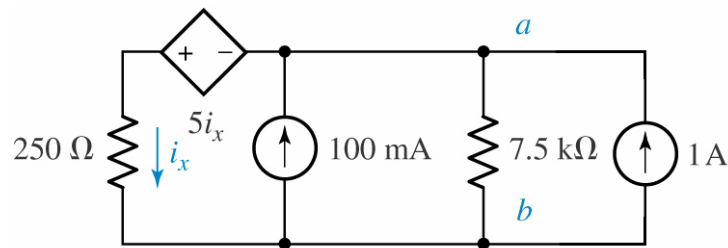In order to determine R_{TH} , we inject 1 A into the port:



$$V_{ab} / 7.5 \times 10^3 + V_x / 250 = 1 \quad [1]$$

$$\text{and } V_x - V_{ab} = 5 i_x = 5 V_x / 250 \quad \text{or}$$

$$-V_{ab} + (1 - 5 / 250) V_x = 0 \quad [2]$$

Solving, we find that $V_{ab} = 237.2 \text{ V}$. Since $R_{TH} = V_{ab} / (1 \text{ A})$, $R_{TH} = 237.2 \Omega$.

Finally, $I_N = V_{TH} / R_{TH} = 100 \text{ mA}$.

55. We first note that $V_{TH} = V_x$, so performing nodal analysis,

$$-5 V_x = V_x / 19 \quad \text{which has the solution } V_x = 0 \text{ V.}$$


Thus, V_{TH} (and hence I_N) = 0. (Assuming $R_{TH} \neq 0$)

To find R_{TH} , we inject 1 A into the port, noting that $R_{TH} = V_x / 1 \text{ A}$:

$$-5 V_x + 1 = V_x / 19$$

Solving, we find that $V_x = 197.9 \text{ mV}$, so that $R_{TH} = R_N = 197.9 \text{ m}\Omega$.

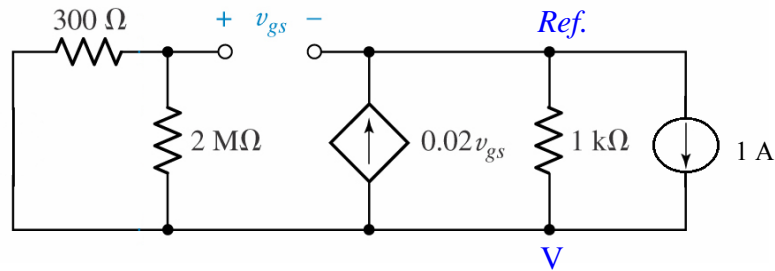56. Shorting out the voltage source, we redraw the circuit with a 1-A source in place of the 2-k Ω resistor:



Noting that $300\ \Omega \parallel 2\ \text{M}\Omega \approx 300\ \Omega$,

$$0 = (v_{gs} - V) / 300 \quad [1]$$

$$1 - 0.02 v_{gs} = V / 1000 + (V - v_{gs}) / 300 \quad [2]$$


Simplifying & collecting terms,

$$v_{gs} - V = 0 \quad [1]$$

$$0.01667 v_{gs} + 0.00433 V = 1 \quad [2]$$

Solving, we find that $v_{gs} = V = 47.62\ \text{V}$. Hence, $R_{TH} = V / 1\ \text{A} = 47.62\ \Omega$.

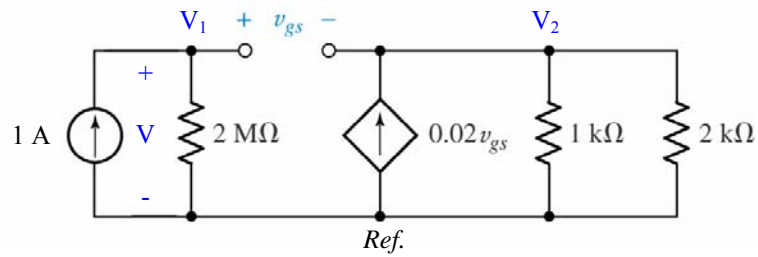
57. We replace the source v_s and the $300\text{-}\Omega$ resistor with a 1-A source and seek its voltage:



By nodal analysis, $1 = V_1 / 2 \times 10^6$ so $V_1 = 2 \times 10^6$ V.

Since $V = V_1$, we have $R_{in} = V / 1\text{ A} = 2\text{ M}\Omega$.

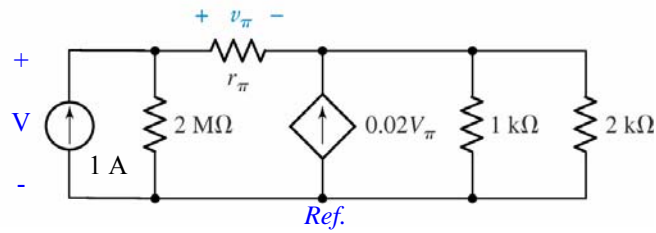58. Removing the voltage source and the 300- Ω resistor, we replace them with a 1-A source and seek the voltage that develops across its terminals:



We select the bottom node as our reference terminal, and define nodal voltages V_1 and V_2 . Then,

$$1 = V_1 / 2 \times 10^6 + (V_1 - V_2) / r_\pi \quad [1]$$

$$0.02 v_\pi = (V_2 - V_1) / r_\pi + V_2 / 1000 + V_2 / 2000 \quad [2]$$

where $v_\pi = V_1 - V_2$

Simplifying & collecting terms,

$$(2 \times 10^6 + r_\pi) V_1 - 2 \times 10^6 V_2 = 2 \times 10^6 r_\pi \quad [1]$$

$$-(2000 + 40 r_\pi) V_1 + (2000 + 43 r_\pi) V_2 = 0 \quad [2]$$

Solving, we find that $V_1 = V = 2 \times 10^6 \left(\frac{666.7 + 14.33 r_\pi}{2 \times 10^6 + 666.7 + 14.33 r_\pi} \right)$.

Thus, $R_{TH} = 2 \times 10^6 \parallel (666.7 + 14.33 r_\pi) \Omega$.

59. (a) We first determine v_{out} in terms of v_{in} and the resistor values only; in this case, $V_{\text{TH}} = v_{\text{out}}$. Performing nodal analysis, we write two equations:

$$0 = \frac{-v_d}{R_i} + \frac{(-v_d - v_{\text{in}})}{R_1} + \frac{(-v_d - v_o)}{R_f} \quad [1] \quad \text{and} \quad 0 = \frac{(v_o + v_d)}{R_f} + \frac{(v_o - Av_d)}{R_o} \quad [2]$$

Solving using MATLAB, we obtain:

```
>> e1 = 'vd/Ri + (vd + vin)/R1 + (vd + vo)/Rf = 0';
>> e2 = '(vo + vd)/Rf + (vo - A*vd)/Ro = 0';
>> a = solve(e1,e2,'vo','vd');
>> pretty(a.vo)
```

$$\frac{R_i v_{\text{in}} (-R_o + R_f A)}{R_1 R_o + R_i R_o + R_1 R_f + R_i R_f + R_1 R_i + A R_1 R_i}$$

Thus, $V_{\text{TH}} = \frac{v_{\text{in}} R_i (R_o - A R_f)}{R_1 R_o + R_i R_o + R_1 R_f + R_i R_f + R_1 R_i + A R_1 R_i}$, which in the limit of $A \rightarrow \infty$, approaches $-R_f/R_1$.

To find R_{TH} , we short out the independent source v_{in} , and squirt 1 A into the terminal marked v_{out} , renamed V_T . Analyzing the resulting circuit, we write two nodal equations:

$$0 = \frac{-v_d}{R_i} - \frac{v_d}{R_1} + \frac{(-v_d - v_T)}{R_f} \quad [1] \quad \text{and} \quad 1 = \frac{(v_T + v_d)}{R_f} + \frac{(v_T - Av_d)}{R_o} \quad [2]$$


Solving using MATLAB:

```
>> e1 = 'vd/R1 + vd/Ri + (vd + VT)/Rf = 0';
>> e2 = '1 = (VT + vd)/Rf + (VT - A*vd)/Ro';
>> a = solve(e1,e2,'vd','VT');
>> pretty(a.VT)
```

$$\frac{R_o (R_i R_f + R_1 R_f + R_1 R_i)}{R_i R_o + R_1 R_o + R_i R_f + R_1 R_f + R_1 R_i + A R_1 R_i}$$

$$\frac{R_o (R_i R_f + R_1 R_f + R_1 R_i)}{R_i R_o + R_1 R_o + R_i R_f + R_1 R_f + R_1 R_i + A R_1 R_i}$$

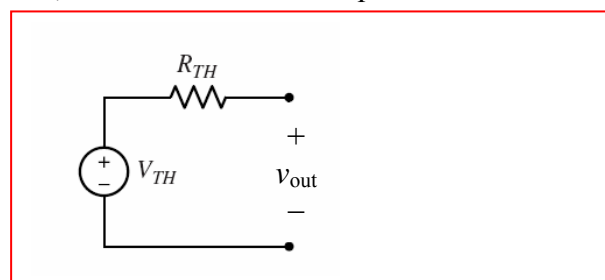Since $V_T/1 = V_T$, this is our Thévenin equivalent resistance (R_{TH}).




60. Such a scheme probably would lead to maximum or at least near-maximum power transfer to our home. Since we pay the utility company based on the power we use, however, this might not be such a hot idea...

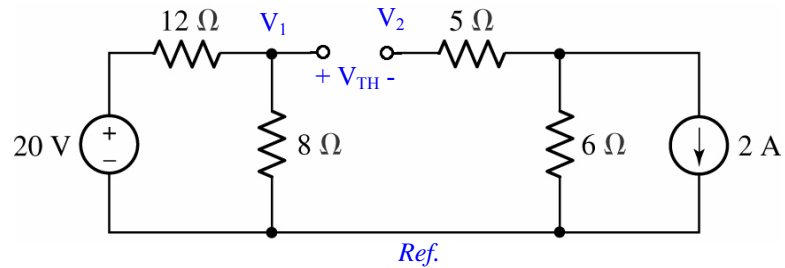61. We need to find the Thévenin equivalent resistance of the circuit connected to R_L , so we short the 20-V source and open-circuit the 2-A source; by inspection, then

$$R_{TH} = 12 \parallel 8 + 5 + 6 = 15.8 \Omega$$

Analyzing the original circuit to obtain V_1 and V_2 with R_L removed:



$$V_1 = 20 \cdot 8 / 20 = 8 \text{ V}; \quad V_2 = -2(6) = -12 \text{ V}.$$

We define $V_{TH} = V_1 - V_2 = 8 + 12 = 20 \text{ V}$. Then,

$$P_{R_L}|_{\max} = \frac{V_{TH}^2}{4 R_L} = \frac{400}{4(15.8)} = 6.329 \text{ W}$$

62. (a) $R_{TH} = 25 \parallel (10 + 15) = 12.5 \Omega$

Using superposition, $V_{ab} = V_{TH} = 50 \frac{25}{15 + 10 + 25} + 100 \frac{15 + 10}{50} = 75 \text{ V.}$

(b) Connecting a 50- Ω resistor,


$$P_{\text{load}} = \frac{V_{TH}^2}{R_{TH} + R_{\text{load}}} = \frac{75^2}{12.5 + 50} = 90 \text{ W}$$

(c) Connecting a 12.5- Ω resistor,

$$P_{\text{load}} = \frac{V_{TH}^2}{4 R_{TH}} = \frac{75^2}{4(12.5)} = 112.5 \text{ W}$$

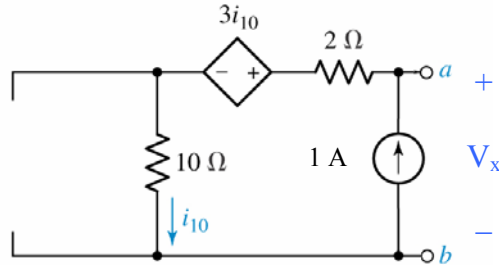63. (a) By inspection, we see that $i_{10} = 5$ A, so
 $V_{TH} = V_{ab} = 2(0) + 3 i_{10} + 10 i_{10} = 13 i_{10} = 13(5) = 65$ V.

To find R_{TH} , we open-circuit the 5-A source, and connect a 1-A source between terminals **a** & **b**:




A simple KVL equation yields $V_x = 2(1) + 3i_{10} + 10 i_{10}$.
 Since $i_{10} = 1$ A in this circuit, $V_x = 15$ V.

We thus find the Thevenin equivalent resistance is $15/1 = 15\ \Omega$.

$$(b) P_{\max} = \frac{V_{TH}^2}{4 R_{TH}} = \frac{65^2}{4(15)} = 70.42\text{ W}$$

64.

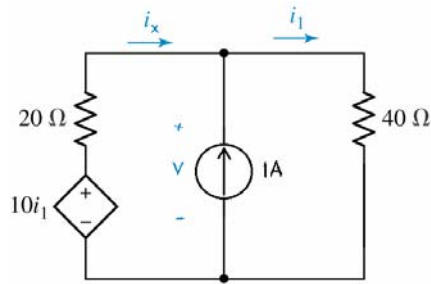- (a) Replacing the resistor R_L with a 1-A source, we seek the voltage that develops across its terminals with the independent voltage source shorted:




$$-10i_1 + 20i_x + 40i_1 = 0 \quad [1] \Rightarrow 30i_1 + 20i_x = 0 \quad [1]$$

$$\text{and } i_1 - i_x = 1 \quad [2] \Rightarrow i_1 - i_x = 1 \quad [2]$$

Solving, $i_1 = 400 \text{ mA}$

$$\text{So } V = 40i_1 = 16 \text{ V and } R_{TH} = \frac{V}{1 \text{ A}} = 16 \Omega$$

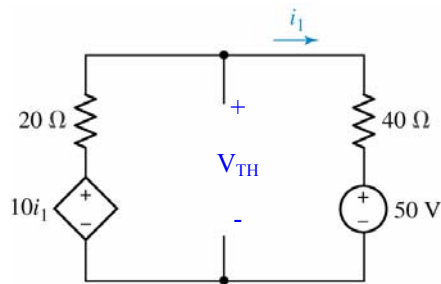- (b) Removing the resistor R_L from the original circuit, we seek the resulting open-circuit voltage:



$$0 = \frac{V_{TH} - 10i_1}{20} + \frac{V_{TH} - 50}{40} \quad [1]$$

$$\text{where } i_1 = \frac{V_{TH} - 50}{40}$$

$$\text{so [1] becomes } 0 = \frac{V_{TH}}{20} - \frac{1}{2} \left(\frac{V_{TH} - 50}{40} \right) + \left(\frac{V_{TH} - 50}{40} \right)$$

$$0 = \frac{V_{TH}}{20} + \frac{V_{TH} - 50}{80}$$

$$0 = 4V_{TH} + V_{TH} - 50$$

$$5V_{TH} = 50$$


$$\text{or } V_{TH} = 10 \text{ V}$$

Thus, if $R_L = R_{TH} = 16 \Omega$,

$$V_{R_L} = V_{TH} \frac{R_L}{R_L + R_{TH}} = \frac{V_{TH}}{2} = 5 \text{ V}$$

65.

(a) $I_N = 2.5 \text{ A}$

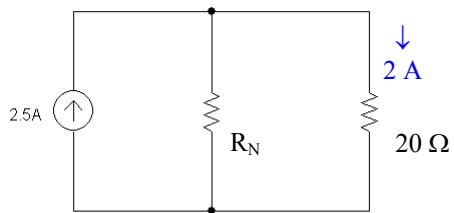

$$20i^2 = 80$$

$$i = 2 \text{ A}$$

By current division,

$$2 = 2.5 \frac{R_N}{R_N + 20}$$


Solving, $R_N = R_{TH} = 80 \Omega$

Thus, $V_{TH} = V_{OC} = 2.5 \times 80 = 200 \text{ V}$

(b) $P_{\max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{200^2}{4 \times 80} = 125 \text{ W}$

(c) $R_L = R_{TH} = 80 \Omega$

66.

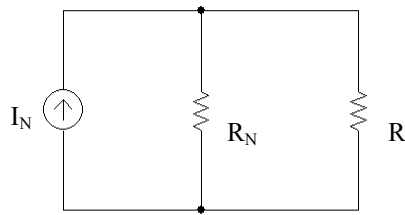10 W to 250Ω correspond to 200 mA.20 W to 80Ω correspond to 500 mA.

By Voltage \div , $I_R = I_N \frac{R_N}{R + R_N}$

So $0.2 = I_N \frac{R_N}{250 + R_N}$ [1]

$0.5 = I_N \frac{R_N}{80 + R_N}$ [2]

Solving, $I_N = 1.7\text{ A}$ and $R_N = 33.33\Omega$

(a) If $v_L i_L$ is a maximum,

$$R_L = R_N = 33.33\Omega$$

$$i_L = 1.7 \times \frac{33.33}{33.33 + 33.33} = 850\text{ mA}$$

$$v_L = 33.33 i_L = 28.33\text{ V}$$

(b) If v_L is a maximum

$$V_L = I_N (R_N \parallel R_L)$$

So v_L is a maximum when $R_N \parallel R_L$ is a maximum, which occurs at $R_L = \infty$.

Then $i_L = 0$ and $v_L = 1.7 \times R_N = 56.66\text{ V}$

(c) If i_L is a maximum

$$i_L = i_N \frac{R_N}{R_N + R_L}; \text{ max when } R_L = 0\Omega$$

So $i_L = 1.7\text{ A}$


$$v_L = 0\text{ V}$$

67. There is no conflict with our derivation concerning maximum power. While a dead short across the battery terminals will indeed result in maximum current draw from the battery, and power is indeed proportional to i^2 , the power delivered to the load is $i^2 R_{LOAD} = i^2(0) = 0$ watts. This is the *minimum*, not the maximum, power that the battery can deliver to a load.

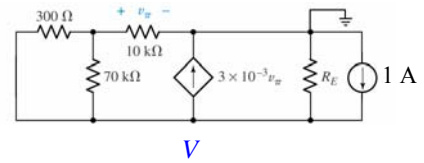68. Remove R_E : $R_{TH} = R_E \parallel R_{in}$

$$\text{bottom node: } 1 - 3 \times 10^{-3} v_{\pi} = \frac{V - v_{\pi}}{300} + \frac{V - v_{\pi}}{70 \times 10^3} \quad [1]$$

$$\text{at other node: } 0 = \frac{v_{\pi}}{10 \times 10^3} + \frac{v_{\pi} - V}{300} + \frac{v_{\pi} - V}{70 \times 10^3} \quad [2]$$



Simplifying and collecting terms,

$$210 \times 10^5 = 70 \times 10^3 V + 300V + 63000 v_{\pi} - 70 \times 10^3 v_{\pi} - 300 v_{\pi}$$

$$\text{or } 70.3 \times 10^3 V - 7300 v_{\pi} = 210 \times 10^5 \quad [1]$$

$$0 = 2100 v_{\pi} + 70 \times 10^3 v_{\pi} - 70 \times 10^3 V + 300 v_{\pi} - 300V$$

$$\text{or } -69.7 \times 10^3 V + 72.4 \times 10^3 v_{\pi} = 0 \quad [2]$$

$$\text{solving, } V = 331.9V \quad \text{So } R_{TH} = R_E \parallel 331.9\Omega$$

Next, we determine v_{TH} using mesh analysis:

$$-v_s + 70.3 \times 10^3 i_1 - 70 \times 10^3 i_2 = 0 \quad [1]$$

$$80 \times 10^3 i_2 - 70 \times 10^3 i_1 + R_E i_3 = 0 \quad [2]$$

$$\text{and: } i_3 - i_2 = 3 \times 10^{-3} v_{\pi} \quad [3]$$


$$\text{or } i_3 - i_2 = 3 \times 10^{-3} (10 \times 10^3) i_2$$

$$\text{or } i_3 - i_2 = 30 i_2$$

or

$$-31 i_2 + i_3 = 0 \quad [3]$$
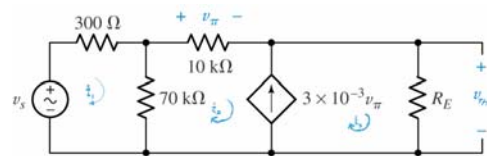
$$\text{Solving: } \begin{bmatrix} 70.3 \times 10^3 & -70 \times 10^3 & 0 \\ -70 \times 10^3 & 80 \times 10^3 & R_E \\ 0 & -31 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} v_s \\ 0 \\ 0 \end{bmatrix}$$



We seek i_3 :

$$i_3 = \frac{-21.7 \times 10^3 v_s}{7.24 \times 10^6 + 21.79 \times 10^3 R_E}$$

$$\text{So } V_{OC} = V_{TH} = R_E i_3 = \frac{-21.7 \times 10^3 R_E}{7.24 \times 10^6 + 21.79 \times 10^3 R_E} v_s$$

$$P_{8\Omega} = 8 \left[\frac{V_{TH}}{R_{TH} + 8} \right]^2 = \left[\frac{-21.7 \times 10^3 R_E}{7.24 \times 10^6 + 21.79 \times 10^3 R_E} \right]^2 \frac{8 v_s^2}{\left[\frac{331.9 R_E}{331.9 + R_E} \right]^2}$$

$$= \frac{11.35 \times 10^6 (331.9 + R_E)^2}{(7.24 \times 10^6 + 21.79 \times 10^3 R_E)^2} v_s^2$$

This is maximized by setting $R_E = \infty$.

69. Thévenize the left-hand network, assigning the nodal voltage V_x at the free end of right-most 1-k Ω resistor.



$$\text{A single nodal equation: } 40 \times 10^{-3} = \frac{V_x|_{oc}}{7 \times 10^3}$$

$$\text{So } V_{TH} = V_x|_{oc} = 280 \text{ V}$$

$$R_{TH} = 1 \text{ k} + 7 \text{ k} = 8 \text{ k}\Omega$$

$$\text{Select } R_1 = R_{TH} = 8 \text{ k}\Omega.$$

70.

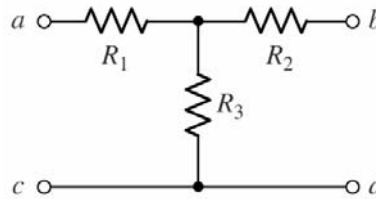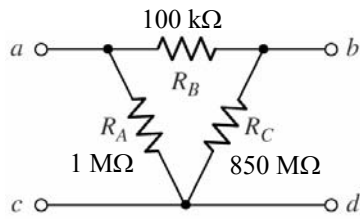



$$D = R_A + R_B + R_C = 1 + 850 + 0.1 = 851.1 \times 10^6$$

$$R_1 = \frac{R_A R_B}{D} = \frac{10^6 \times 10^5}{851.1 \times 10^6} = 117.5 \Omega$$

$$R_2 = \frac{R_B R_C}{D} = \frac{10^5 \times 850 \times 10^6}{851.1 \times 10^6} = 99.87 k\Omega$$

$$R_3 = \frac{R_C R_A}{D} = \frac{850 \times 10^6 \times 10^6}{851.1 \times 10^6} = 998.7 k\Omega$$

71.

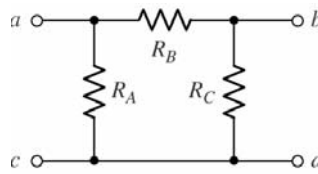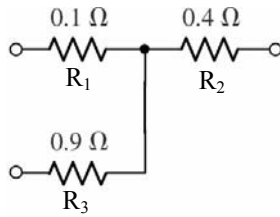

$$\begin{aligned} N &= R_1 R_2 + R_2 R_3 + R_3 R_1 \\ &= 0.1 \times 0.4 + 0.4 \times 0.9 + 0.9 \times 0.1 \\ &= 0.49 \Omega \end{aligned}$$

$$R_A = \frac{N}{R_2} = 1.225 \Omega$$

$$R_B = \frac{N}{R_3} = 544.4 \text{ m}\Omega$$

$$R_C = \frac{N}{R_1} = 4.9 \Omega$$

72.

$$\Delta_1 : 1 + 6 + 3 = 10 \Omega$$

$$\frac{6 \times 1}{10} = 0.6, \frac{6 \times 3}{10} = 1.8, \frac{3 \times 1}{10} = 0.3$$

$$\Delta_2 : 5 + 1 + 4 = 10 \Omega$$

$$\frac{5 \times 1}{10} = 0.5, \frac{1 \times 4}{10} = 0.4, \frac{5 \times 4}{10} = 2$$


$$1.8 + 2 + 0.5 = 4.3 \Omega$$

$$0.3 + 0.6 + 0.4 = 1.3 \Omega$$

$$1.3 \parallel 4.3 = 0.9982 \Omega$$

$$0.9982 + 0.6 + 2 = 3.598 \Omega$$
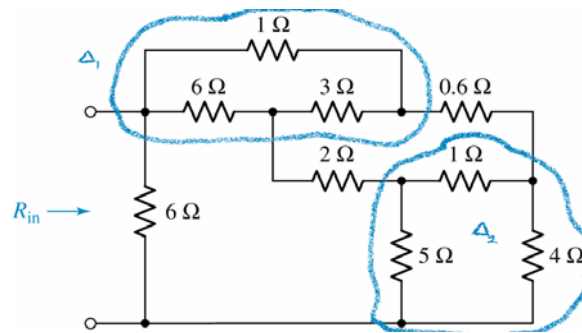
$$3.598 \parallel 6 = \boxed{2.249 \Omega}$$



73.

$$6 \times 2 + 2 \times 3 + 3 \times 6 = 36 \Omega^2$$

$$\frac{36}{6} = 6 \Omega, \quad \frac{36}{2} = 18 \Omega, \quad \frac{36}{3} = 12 \Omega$$

$$12 \parallel 4 = 3 \Omega, \quad 6 \parallel 12 \Omega = 4 \Omega$$

$$4 + 3 + 18 = 25 \Omega$$

$$3 \times \frac{18}{25} = 2.16 \Omega$$

$$4 \times \frac{18}{25} = 2.88 \Omega$$

$$4 \times \frac{3}{25} = 0.48 \Omega$$

$$9.48 \times 2.16 + 9.48 \times 2.88 + 2.88 \times 2.16 = 54 \Omega^2$$

$$\frac{54}{2.88} = 18.75 \Omega$$

$$\frac{54}{9.48} = 5.696 \Omega$$




$$\frac{54}{2.16} = 25 \Omega$$

$$75 \parallel 18.75 = 15 \Omega$$


$$100 \parallel 25 = 20 \Omega$$

$$(15 + 20) \parallel 5.696 = 4.899 \Omega$$
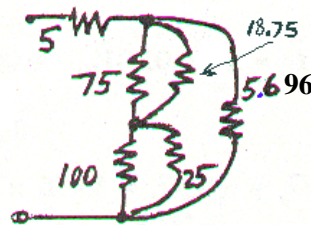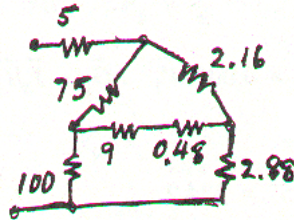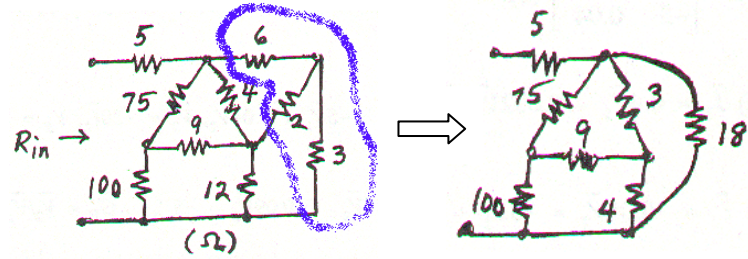
$$\therefore R_{in} = 5 + 4.899 = 9.899 \Omega$$



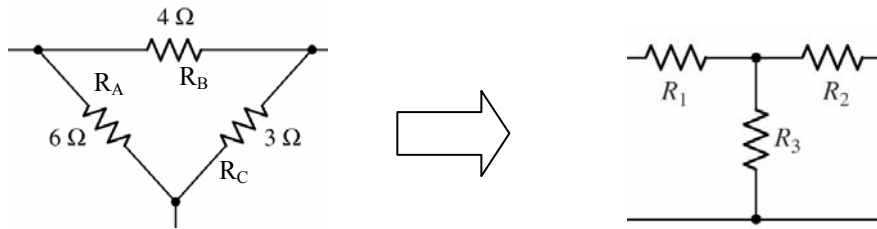74. We begin by converting the Δ -connected network consisting of the 4-, 6-, and 3- Ω resistors to an equivalent Y-connected network:




$$D = 6 + 4 + 3 = 13 \Omega$$

$$R_1 = \frac{R_A R_B}{D} = \frac{6 \times 4}{13} = 1.846 \Omega$$

$$R_2 = \frac{R_B R_C}{D} = \frac{4 \times 3}{13} = 0.9231 \text{ m}\Omega$$

$$R_3 = \frac{R_C R_A}{D} = \frac{3 \times 6}{13} = 1.385 \Omega$$

Then network becomes:

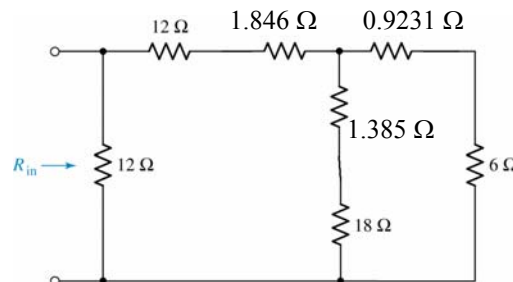


Then we may write

$$R_{in} = 12 \parallel [1.846 + (0.9231 \parallel 6.9231)]$$

$$= 7.347 \Omega$$

75.

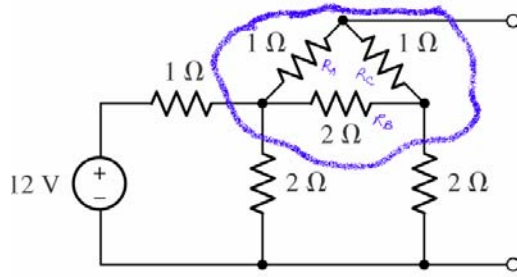


$$1 + 1 + 2 = 4\Omega$$

$$R_1 = \frac{1 \times 2}{4} = \frac{1}{2}\Omega$$

$$R_2 = \frac{2 \times 1}{4} = \frac{1}{2}\Omega$$
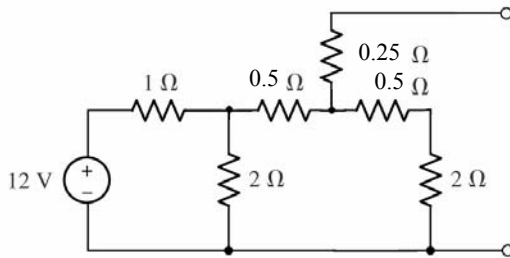
$$R_3 = \frac{1 \times 1}{4} = 0.25\Omega$$



Next, we convert the Y-connected network on the left to a Δ -connected network:


$$1 \times 0.5 + 0.5 \times 2 + 2 \times 1 = 3.5\Omega^2$$

$$R_A = \frac{3.5}{0.5} = 7\Omega$$

$$R_B = \frac{3.5}{2} = 1.75\Omega$$

$$R_C = \frac{3.5}{1} = 3.5\Omega$$

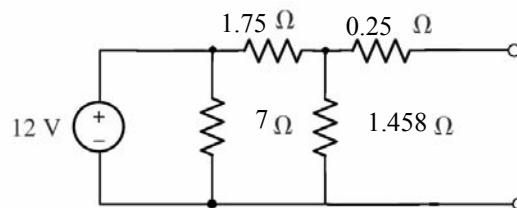After this procedure, we have a 3.5- Ω resistor in parallel with the 2.5- Ω resistor. Replacing them with a 1.458- Ω resistor, we may redraw the circuit:



This circuit may be easily analysed to find:

$$V_{oc} = \frac{12 \times 1.458}{1.75 + 1.458} = 5.454\text{ V}$$

$$R_{TH} = 0.25 + 1.458 \parallel 1.75 = 1.045\Omega$$


76. We begin by converting the Y-network to a Δ -connected network:

$$N = 1.1 + 1.1 + 1.1 = 3\Omega^2$$

$$R_A = \frac{3}{1} = 3\Omega$$

$$R_B = \frac{3}{1} = 3\Omega$$

$$R_C = \frac{3}{1} = 3\Omega$$

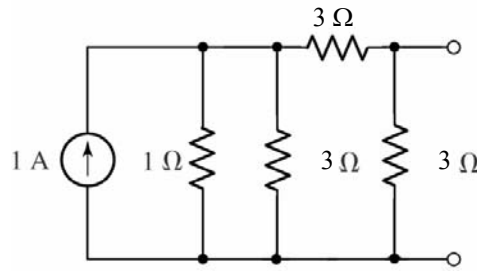


Next, we note that $1\parallel 3 = 0.75\Omega$, and hence have a simple Δ -network. This is easily converted to a Y-connected network:

$$0.75 + 3 + 3 = 6.75\Omega$$

$$R_1 = \frac{0.75 \times 3}{6.75} = 0.3333\Omega$$

$$R_2 = \frac{3 \times 3}{6.75} = 1.333\Omega$$
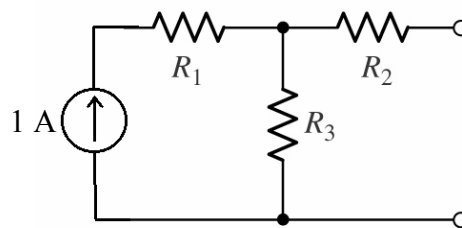
$$R_3 = \frac{3 \times 0.75}{6.75} = 0.3333\Omega$$



Analysing this final circuit,

$$R_N = 1.333 + 0.3333$$

$$= 1.667\Omega$$


$$I_N = I_{SC} = 1 \times \frac{1/3}{1/3 + 1 + 1/3}$$

$$= \frac{1}{1 + 3 + 1} = \frac{1}{5}$$

$$= 0.2\text{ A}$$

$$= 200\text{ mA}$$

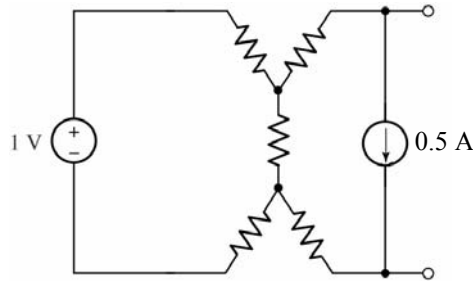77. Since 1 V appears across the resistor associated with I_1 , we know that $I_1 = 1 \text{ V} / 10 \Omega = 100 \text{ mA}$. From the perspective of the open terminals, the 10- Ω resistor in parallel with the voltage source has no influence if we replace the “dependent” source with a fixed 0.5-A source:



Then, we may write:

$$-1 + (10 + 10 + 10) i_a - 10 (0.5) = 0$$

so that $i_a = 200 \text{ mA}$.

We next find that $V_{\text{TH}} = V_{\text{ab}} = 10(-0.5) + 10(i_a - 0.5) + 10(-0.5) = -13 \text{ V}$.

To determine R_{TH} , we first recognise that with the 1-V source shorted, $I_1 = 0$ and hence the dependent current source is dead. Thus, we may write R_{TH} from inspection:


$$R_{\text{TH}} = 10 + 10 + 10 \parallel 20 = 26.67 \Omega.$$

78. (a) We begin by splitting the 1-kΩ resistor into two 500-Ω resistors in series. We then have two related Y-connected networks, each with a 500-Ω resistor as a leg. Converting those networks into Δ-connected networks,

$$\Sigma = (17)(10) + (1)(4) + (4)(17) = 89 \times 106 \Omega^2$$

$$89/0.5 = 178 \text{ k}\Omega; \quad 89/17 = 5.236 \text{ k}\Omega; \quad 89/4 = 22.25 \text{ k}\Omega$$

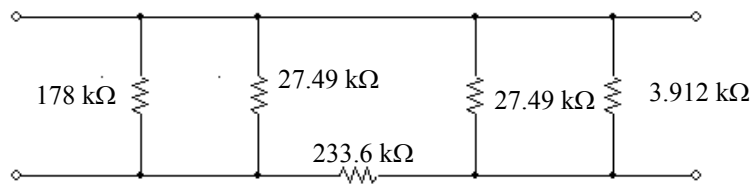Following this conversion, we find that we have two 5.235 kΩ resistors in parallel, and a 178-kΩ resistor in parallel with the 4-kΩ resistor. Noting that $5.235 \text{ k} \parallel 5.235 \text{ k} = 2.618 \text{ k}\Omega$ and $178 \text{ k} \parallel 4 \text{ k} = 3.912 \text{ k}\Omega$, we may draw the circuit as:



We next attack the Y-connected network in the center:

$$\Sigma = (22.25)(22.25) + (22.25)(2.618) + (2.618)(22.25) = 611.6 \times 106 \Omega^2$$

$$611.6/22.25 = 27.49 \text{ k}\Omega; \quad 611.6/2.618 = 233.6 \text{ k}\Omega$$



Noting that $178 \text{ k} \parallel 27.49 \text{ k} = 23.81 \text{ k}\Omega$ and $27.49 \parallel 3.912 = 3.425 \text{ k}\Omega$, we are left with a simple Δ-connected network. To convert this to the requested Y-network,

$$\Sigma = 23.81 + 233.6 + 3.425 = 260.8 \text{ k}\Omega$$

$$(23.81)(233.6)/260.8 = 21.33 \text{ k}\Omega$$

$$(233.6)(3.425)/260.8 = 3.068 \text{ k}\Omega$$

$$(3.425)(23.81)/260.8 = 312.6 \Omega$$

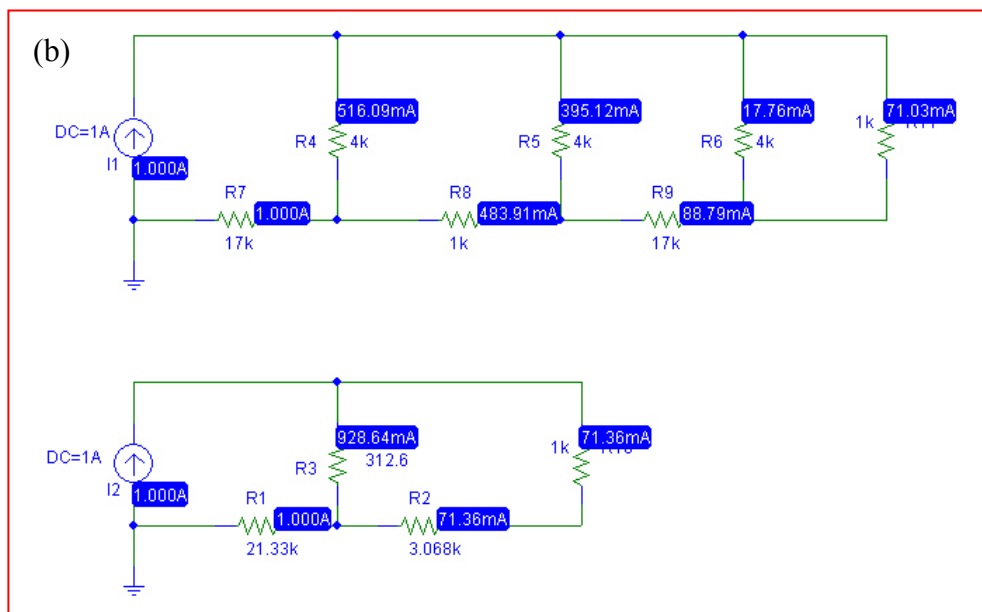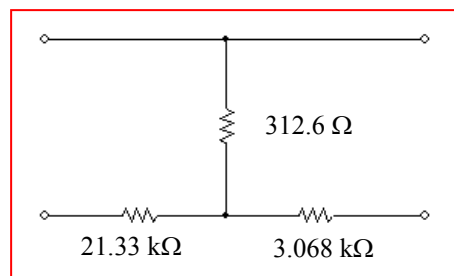


79. (a) Although this network may be simplified, it is not possible to replace it with a three-resistor equivalent.
- (b) See (a).

80. First, replace network to left of the 0.7-V source with its Thévenin equivalent:

$$V_{TH} = 20 \times \frac{15}{100+15} = 2.609 \text{ V}$$

$$R_{TH} = 100k \parallel 15k = 13.04 \text{ k}\Omega$$

Redraw:

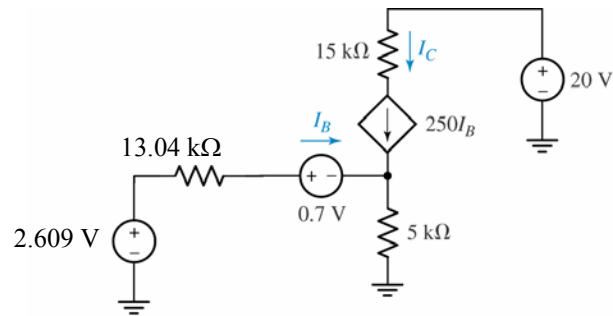

Analysing the new circuit to find I_B , we note that $I_C = 250 I_B$:

$$-2.609 + 13.04 \times 10^3 I_B + 0.7 + 5000(I_B + 250I_B) = 0$$

$$I_B = \frac{2.609 - 0.7}{13.04 \times 10^3 + 251 \times 5000} = 1.505 \mu\text{A}$$

$$I_C = 250 I_B = 3.764 \times 10^{-4} \text{ A}$$

$$= \boxed{376.4 \mu\text{A}}$$

81. (a) Define a nodal voltage V_1 at the top of the current source I_S , and a nodal voltage V_2 at the top of the load resistor R_L . Since the load resistor can safely dissipate 1 W, and we know that

$$P_{R_L} = \frac{V_2^2}{1000}$$

then $V_2|_{\max} = 31.62 \text{ V}$. This corresponds to a load resistor (and hence lamp) current of 32.62 mA, so we may treat the lamp as a 10.6- Ω resistor.

Proceeding with nodal analysis, we may write:

$$I_S = V_1/200 + (V_1 - 5 V_x)/200 \quad [1]$$

$$0 = V_2/1000 + (V_2 - 5 V_x)/10.6 \quad [2]$$

$$V_x = V_1 - 5 V_x \quad \text{or} \quad V_x = V_1/6 \quad [3]$$

Substituting Eq. [3] into Eqs. [1] and [2], we find that


$$7 V_1 = 1200 I_S \quad [1]$$

$$-5000 V_1 + 6063.6 V_2 = 0 \quad [2]$$

Substituting $V_2|_{\max} = 31.62 \text{ V}$ into Eq. [2] then yields $V_1 = 38.35 \text{ V}$, so that

$$I_S|_{\max} = (7)(38.35)/1200 = 223.7 \text{ mA.}$$

- (b) PSpice verification.

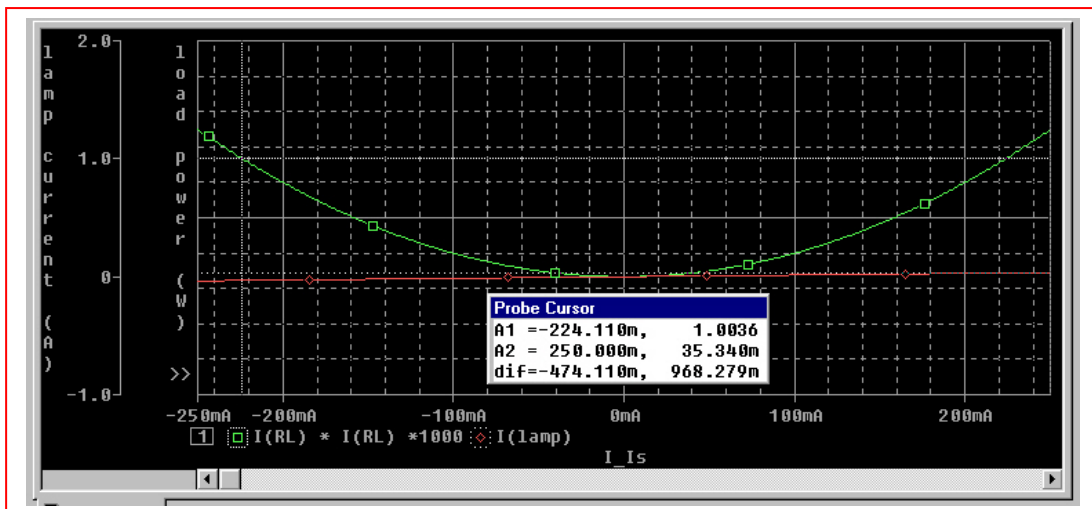

The lamp current does not exceed 36 mA in the range of operation allowed (*i.e.* a load power of < 1 W.) The simulation result shows that the load will dissipate slightly more than 1 W for a source current magnitude of 224 mA, as predicted by hand analysis.

82. Short out all but the source operating at 10^4 rad/s, and define three clockwise mesh currents i_1 , i_2 , and i_3 starting with the left-most mesh. Then

$$608 i_1 - 300 i_2 = 3.5 \cos 10^4 t \quad [1]$$

$$-300 i_1 + 316 i_2 - 8 i_3 = 0 \quad [2]$$

$$-8 i_2 + 322 i_3 = 0 \quad [3]$$

Solving, we find that $i_1(t) = 10.84 \cos 10^4 t$ mA

$$i_2(t) = 10.29 \cos 10^4 t \text{ mA}$$

$$i_3(t) = 255.7 \cos 10^4 t \text{ } \mu\text{A}$$

Next, short out all but the $7 \sin 200t$ V source, and define three clockwise mesh currents i_a , i_b , and i_c starting with the left-most mesh. Then

$$608 i_a - 300 i_b = -7 \sin 200t \quad [1]$$

$$-300 i_a + 316 i_b - 8 i_c = 7 \sin 200t \quad [2]$$

$$-8 i_b + 322 i_c = 0 \quad [3]$$

Solving, we find that $i_a(t) = -1.084 \sin 200t$ mA

$$i_b(t) = 21.14 \sin 200t \text{ mA}$$

$$i_c(t) = 525.1 \sin 200t \text{ } \mu\text{A}$$

Next, short out all but the source operating at 10^3 rad/s, and define three clockwise mesh currents i_A , i_B , and i_C starting with the left-most mesh. Then

$$608 i_A - 300 i_B = 0 \quad [1]$$

$$-300 i_A + 316 i_B - 8 i_C = 0 \quad [2]$$

$$-8 i_B + 322 i_C = -8 \cos 10^4 t \quad [3]$$

Solving, we find that $i_A(t) = -584.5 \cos 10^3 t$ μA

$$i_B(t) = -1.185 \cos 10^3 t \text{ mA}$$

$$i_C(t) = -24.87 \cos 10^3 t \text{ mA}$$


We may now compute the power delivered to each of the three $8\text{-}\Omega$ speakers:

$$p_1 = 8[i_1 + i_a + i_A]^2 = 8[10.84 \times 10^{-3} \cos 10^4 t - 1.084 \times 10^{-3} \sin 200t - 584.5 \times 10^{-6} \cos 10^3 t]^2$$

$$p_2 = 8[i_2 + i_b + i_B]^2 = 8[10.29 \times 10^{-3} \cos 10^4 t + 21.14 \times 10^{-3} \sin 200t - 1.185 \times 10^{-3} \cos 10^3 t]^2$$

$$p_3 = 8[i_3 + i_c + i_C]^2 = 8[255.7 \times 10^{-6} \cos 10^4 t + 525.1 \times 10^{-6} \sin 200t - 24.87 \times 10^{-3} \cos 10^3 t]^2$$

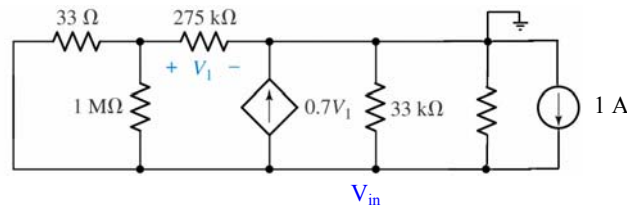83. Replacing the DMM with a possible Norton equivalent (a 1-M Ω resistor in parallel with a 1-A source):



We begin by noting that $33 \Omega \parallel 1 \text{ M}\Omega \approx 33 \Omega$. Then,

$$0 = (V_1 - V_{in})/33 + V_1/275 \times 10^3 \quad [1]$$

and

$$1 - 0.7 V_1 = V_{in}/10^6 + V_{in}/33 \times 10^3 + (V_{in} - V_1)/33 \quad [2]$$

Simplifying and collecting terms,

$$(275 \times 10^3 + 33) V_1 - 275 \times 10^3 V_{in} = 0 \quad [1]$$

$$22.1 V_1 + 1.001 V_{in} = 33 \quad [2]$$

Solving, we find that $V_{in} = 1.429 \text{ V}$; in other words, the DMM sees 1.429 V across its terminals in response to the known current of 1 A it's supplying. It therefore thinks that it is connected to a resistance of 1.429 Ω .


84. We know that the resistor R is absorbing maximum power. We might be tempted to say that the resistance of the cylinder is therefore $10\ \Omega$, but this is wrong: The larger we make the cylinder resistance, the smaller the power delivery to R:

$$P_R = 10 i^2 = 10 \left[\frac{120}{R_{cylinder} + 10} \right]^2$$

Thus, if we are in fact delivering the maximum possible power to the resistor from the 120-V source, the resistance of the cylinder must be zero.


This corresponds to a temperature of absolute zero using the equation given.

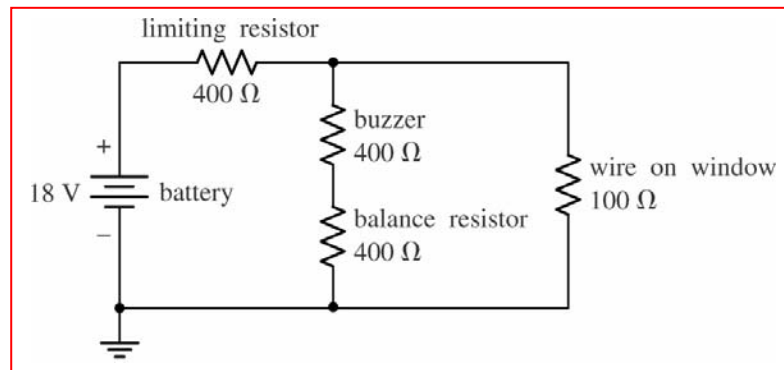85. We note that the buzzer draws 15 mA at 6 V, so that it may be modeled as a 400- Ω resistor. One possible solution of many, then, is:




Note: construct the 18-V source from 12 1.5-V batteries in series, and the two 400- Ω resistors can be fabricated by soldering 400 1- Ω resistors in series, although there's probably a much better alternative...

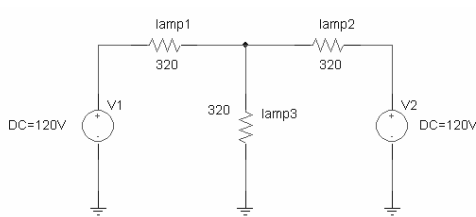86. To solve this problem, we need to assume that “45 W” is a designation that applies when 120 Vac is applied directly to a particular lamp. This corresponds to a current draw of 375 mA, or a light bulb resistance of $120/0.375 = 320 \Omega$.




Original wiring scheme

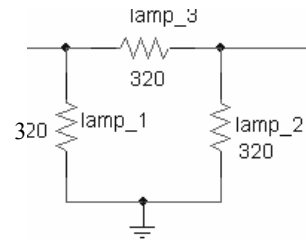

New wiring scheme

In the original wiring scheme, Lamps 1 & 2 draw $(40)^2 / 320 = 5 \text{ W}$ of power each, and Lamp 3 draws $(80)^2 / 320 = 20 \text{ W}$ of power. Therefore, none of the lamps is running at its maximum rating of 45 W. We require a circuit which will deliver the same intensity after the lamps are reconnected in a Δ configuration. Thus, we need a total of 30 W from the new network of lamps.

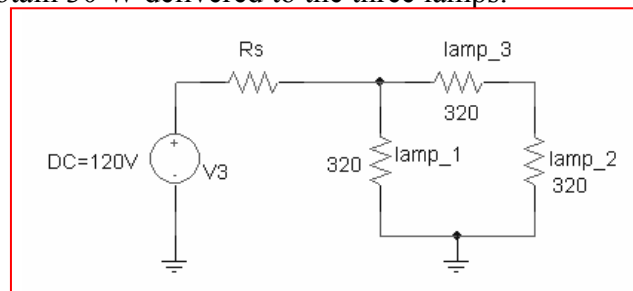
There are several ways to accomplish this, but the simplest may be to just use one 120-Vac source connected to the left port in series with a resistor whose value is chosen to obtain 30 W delivered to the three lamps.



In other words,

$$\left[\frac{120 \cdot 213.3}{R_s + 213.3} \right]^2 \frac{1}{320} + 2 \left[\frac{60 \cdot 213.3}{R_s + 213.3} \right]^2 \frac{1}{320} = 30$$

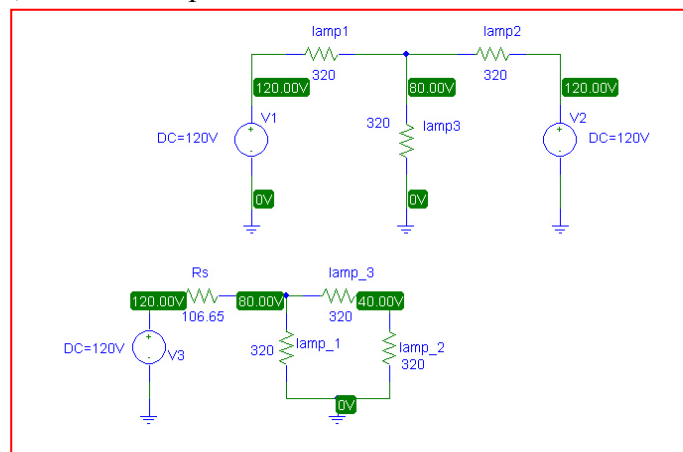Solving, we find that we require $R_s = 106.65 \Omega$, as confirmed by the PSpice simulation below, which shows that both wiring configurations lead to one lamp with 80-V across it, and two lamps with 40 V across each.



87.

- Maximum current rating for the LED is 35 mA.
- Its resistance can vary between 47 and 117 Ω .
- A 9-V battery must be used as a power source.
- Only standard resistance values may be used.

One possible current-limiting scheme is to connect a 9-V battery in series with a resistor R_{limiting} and in series with the LED.

From KVL,

$$I_{\text{LED}} = \frac{9}{R_{\text{limiting}} + R_{\text{LED}}}$$

The maximum value of this current will occur at the minimum LED resistance, 47 Ω .

Thus, we solve

$$35 \times 10^{-3} = \frac{9}{R_{\text{limiting}} + 47}$$

to obtain $R_{\text{limiting}} \geq 210.1 \Omega$ to ensure an LED current of less than 35 mA. This is not a standard resistor value, however, so we select

$$R_{\text{limiting}} = 220 \Omega.$$