


Name:

ID:

Razan Monther Jaradat.

1931783

Construct the circuit shown below:-

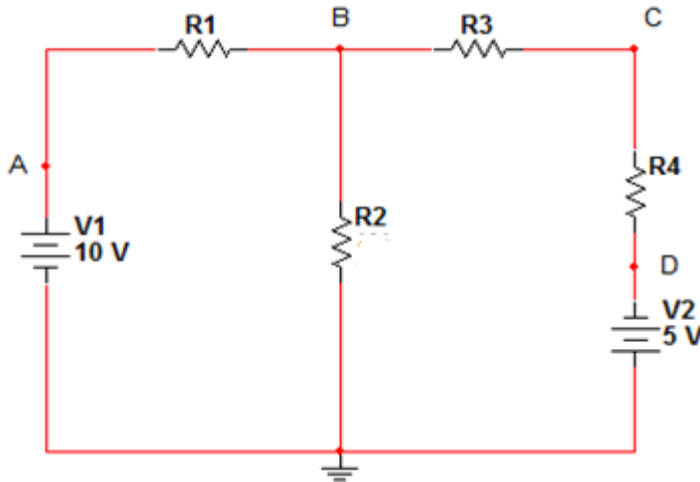

R	Theoretical Value (Kohm)	Measured Value
R1	1.8	1.79
R2	9.1	9.04
R3	3.9	3.83
R4	2.7	2.66

• Nodal Analysis:

Value	VA	VB	VC	VD
Measured	10	5.84	-0.55	-4.99
Theoretical	10	5.87	-0.552	-5

$$V_A = V_{S1} = 10 \text{ Volt}$$

$$V_D = -V_{S2} = -5 \text{ Volt}$$

To find  $V_B$  and  $V_C$ , use Nodal Analysis:

$$\frac{V_B - 10}{R1} + \frac{V_B}{R2} + \frac{V_B - V_C}{R3} = 0$$

$$\frac{V_C + 5}{R4} + \frac{V_C - V_B}{R3} = 0$$

$$V_C = -0.552 \text{ Volt}, V_B = 5.87 \text{ Volt}$$

1- Use the Nodal Analysis to find the theoretical values.

• Mesh Analysis:

Value	I1	I2
Measured	2.5	1.66
Theoretical	2.23	1.65

$$-10 + R1 * I1 + R2 * (I1 - I2) = 0$$

Name:

ID:

$$R2 * (I2 - I1) + R3 * I2 + R4 * I2 - 5 = 0$$

$$-10 + 10.9 * I1 - 9.1 * I2 = 0$$

$$-5 - 9.1 * I1 + 15.7 * I2 = 0$$

$$I1 = 2.23 \text{ mA}$$

$$I2 = 1.65 \text{ mA}$$

2- Use the Mesh Analysis to find the theoretical values.

• **Superposition Analysis:**

Value	$V_B'$	$V_B''$	$V_C'$	$V_C''$	$I_1'$	$I_1''$	$I_2'$	$I_2''$
Measured	6.78	-0.93	2.78	-3.32				
Theoretical	6.8	-0.98	2.782	-3.35				

$V_1 = 10 \text{ volt}$  and  $V_2 = 0 \text{ volt}$  :

$$\frac{V_B' - 10}{1.8} + \frac{V_B'}{9.1} + \frac{V_B' - V_C'}{3.9} = 0$$

$$\frac{V_C' - V_B'}{3.9} + \frac{V_C'}{2.7} = 0$$

$V_C' = 2.782 \text{ volt}$ ,  $V_B' = 6.8 \text{ volt}$

$V_1 = 0 \text{ volt}$  and  $V_2 = 5 \text{ volt}$  :

$$\frac{V_B''}{1.8} + \frac{V_B''}{9.1} + \frac{V_B'' - V_C''}{3.9} = 0$$

$$\frac{V_C'' - V_B''}{3.9} + \frac{V_B'' - (-5)}{2.7} = 0$$

$V_B'' = -0.98 \text{ volt}$ ,  $V_C'' = -3.35 \text{ volt}$



$V_B = V_B' + V_B'' = 6.8 - 0.98 = 5.82 \text{ volt}$

$V_C = V_C' + V_C'' = 2.782 - 3.35 = -0.568 \text{ volt}$

Name:

ID:

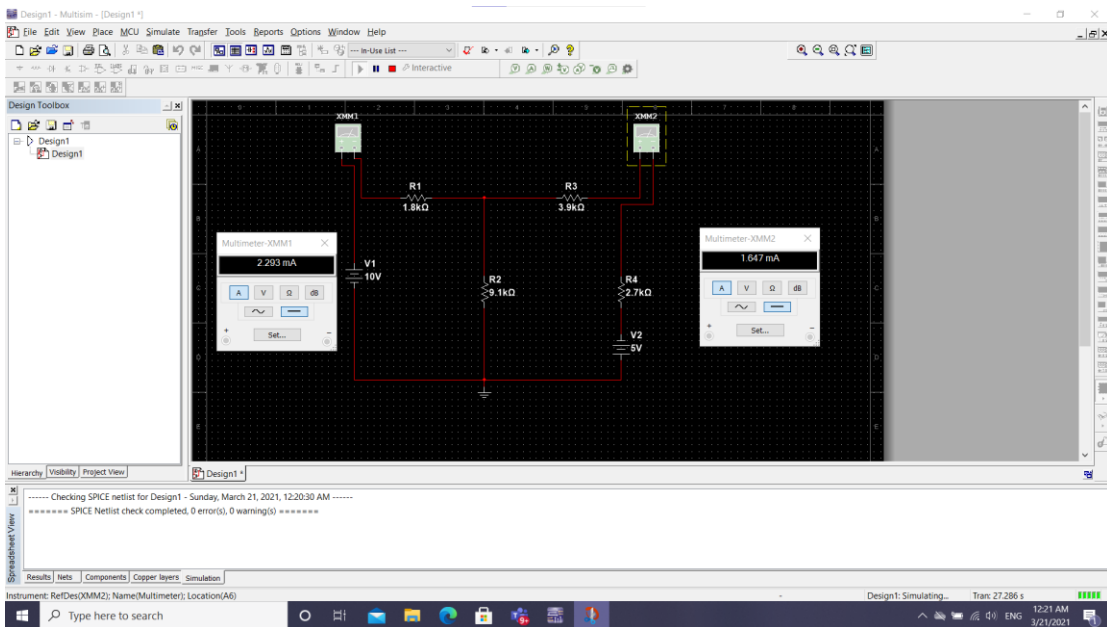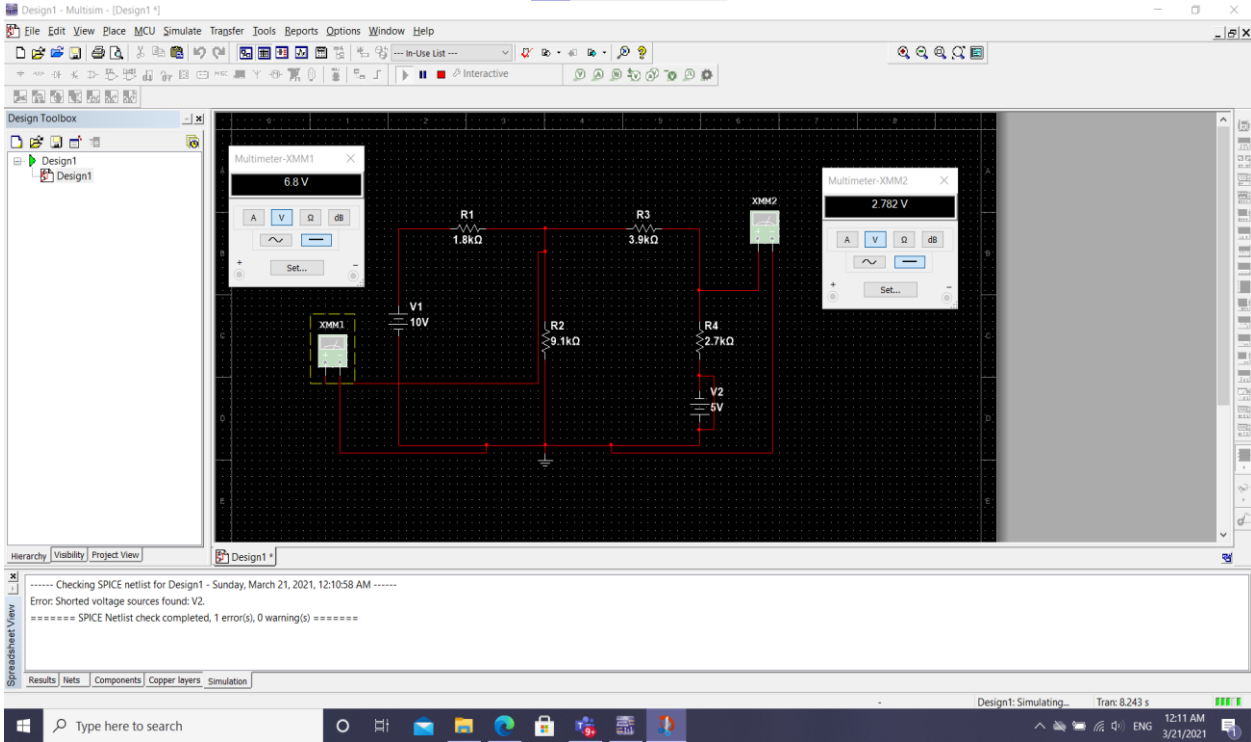3- Use the Superposition Analysis to find the theoretical values.



Name:

ID:

