

CHAPTER 2 (CONT)

2.17 FOR  $V_{IN_A}$  AND/OR  $V_{IN_B}$  HIGH: IF  $V_{IN} = 5V$

$$V_{out} = V_{OH} = V_{IN} - V_o(\text{on}) = 5 - 0.7 = 4.3V$$

FOR AN ADDITIONAL OR GATE:

$$V_{out} = V_{OH} = V_{IN} - 2 V_o(\text{on}) = 5 - 1.4 = 3.6V$$

2.18  $D_A$  OPEN:

$$I = \frac{V_{cc} - V_{OL} + V_{os}}{R_1 + R_2} = \frac{4 - 0.7 + 4}{2k} = 3.65 \text{ mA}$$

$$V_p = V_{cc} - IR_1 = 4 - 3.65 \text{ mA} (1k) = 0.35V$$

$$V_{IN} + V_{ON} = V_p \Rightarrow V_{IN} = V_p - V_{ON} = 0.35 - 0.7 = -0.35V, D_A \text{ ON FOR } V_{IN} \leq -0.35$$


$D_L$  OPEN:

$$\text{@ } V_{IN} = -4V$$

$$V_{out} = -V_{cc} = -4V$$

$$V_p = -4.3V \therefore D_L \text{ IS OFF } \therefore V_{out} = -4V$$

$$V_{IN} \geq -0.35V$$

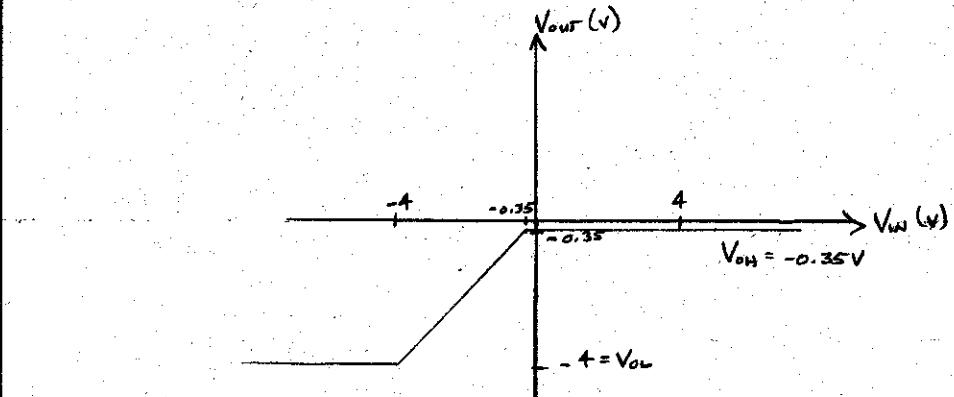

2.19 SEE PROBLEM 2.18:

$D_A$  OPEN:

$$I = 3.65 \text{ mA}$$

$$V_p = -0.35 \text{ mA}$$

$$V_{out} = 0.35 \text{ mA} = V_{cc} - IR_1$$

$$V_{IN} = V_p + V_o(\text{on}) = -0.35 + 0.7 = 0.35, D_A \text{ IS ON FOR } V_{IN} > 0.35V$$


2.19 (cont'd)

CHAPTER 2 (cont)

D<sub>B</sub> OPEN:

$$V_{out} = V_{cc} = 4V$$

$$V_{in} \leq 0.35V$$

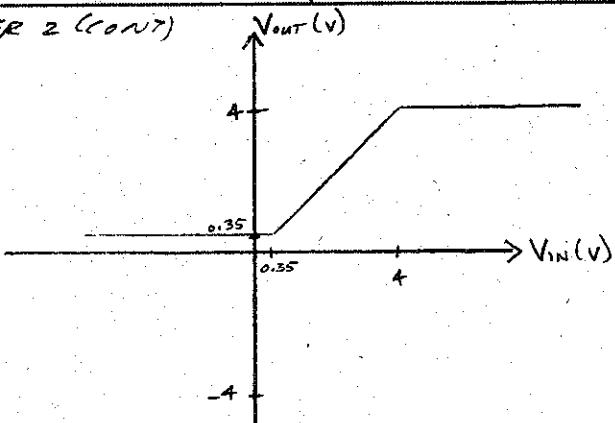

2.20 V<sub>INB</sub> = 0 FIRST CONSIDER BOTH DIODES OPEN

$$V_p = V_{cc} - R_1 \left( \frac{V_{cc} + V_{EE} - V_{D(on)}}{R_1 + R_2} \right)$$

$$V_p = 5 - 5 \left( \frac{10 - 0.7}{105} \right) = 4.56V$$

HOWEVER, FOR V<sub>p</sub> = 4.56V AND V<sub>INB</sub> = 0, D<sub>B</sub> IS NOT OPEN.  
HENCE, D<sub>B</sub> SHORTED AND V<sub>p</sub> ≠ 4.56V. INSTEAD

$$V_p = V_{D(on)} = 0.7V$$

AS V<sub>INA</sub> INCREASES FROM 0 TO 5V, D<sub>A</sub> IS OPEN AND


$$V_{out} = V_{INB} = 0V$$

V<sub>INB</sub> = 5V ⇒ D<sub>B</sub> OPEN, HOWEVER D<sub>A</sub> IS SHORTED AND  
CURRENT PASSES FROM V<sub>cc</sub> THROUGH R<sub>1</sub>, D<sub>A</sub> & D<sub>L</sub>.  
THEN

$$V_{out} = V_{INA}$$

UNTIL V<sub>INA</sub> INCREASES TO 4.3V, THEN D<sub>A</sub> OPENS AND
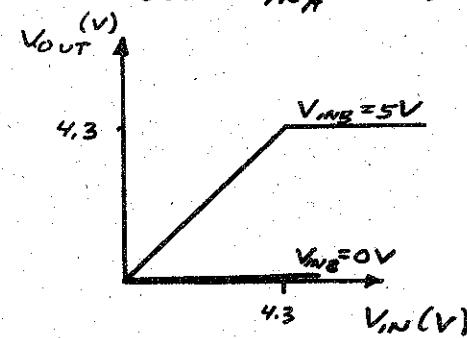
$$V_p = 5V \text{ WITH } V_{out} = V_{INA} = 4.3V$$



6.10 (CONT'D)

CHAPTER 6 (CONT)

$$(c) N = I_{OL}/I_{IL} = 61.5mA / 1.6mA = 38.5 \Rightarrow \text{MAX. FAN OUT} = 38$$

$$(d) I_{cc(0H)} = I_{IL} = 1.6mA$$

$$I_{cc(OL)} = 1.25mA + 0.95mA = 2.2mA$$

$$P_{cc(\text{avg})} = [(I_{cc(0H)} + I_{cc(OL)})/2]V_{cc} = [(1.6mA + 2.2mA)/2]4 = 7.65mW$$

6.11

SEE PROBLEM 6.10:

$$(a) I_{IL} = 0.62mA$$

$$(b) I_{OL} = I_{OL(\text{SAT})} - I_{cc} = 21.2mA$$

$$I_{cc} = 3.8mA$$

$$I_{cc,0(\text{SAT})} = 25.0mA$$

$$I_{cc,0} = 0.5mA$$

$$(c) N = I_{OL}/I_{IL} = 34.2 \Rightarrow \text{MAX. FAN OUT} = 34$$

$$(d) I_{cc(0H)} = 0.62mA \quad I_{cc(OL)} = 1.3mA$$

$$P_{cc(\text{avg})} = 9.84mW$$

6.12

$$V_{OH} = 5V$$


$$V_{OL} = 0.2V$$

$$V_{IL} = V_{BE,0}(\text{FET}) + V_{BE,L}(\text{FET}) = 0.7 + 0.7 = 1.4V$$

$$V_{IH} = V_{BE,L}(\text{FET}) + V_{BE,0}(\text{SAT}) = 0.7 + 0.8 = 1.5V$$

$$V_{NMH} = 3.5V$$

$$V_{NML} = 1.2V$$

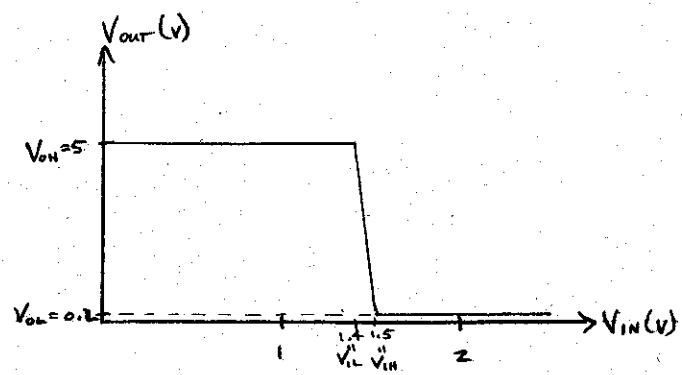

CHAPTER 7 (CONT)

7.13 (a) FOR  $V_{on}$ :

$Q_1$	SAT
$Q_2$	CUTOFF
$Q_3$	FA
$A_1$	ON
$Q_4$	CUTOFF

$Q_1$	RA
$Q_2$	SAT
$Q_3$	CUTOFF
$A_1$	CUTOFF
$Q_4$	SAT

(b) FOR  $V_{on}$ :

7.14 (a)  $Q_3, R_A$

(b)  $Q_3, R_C, R_B$

(c)  $Q_3, R_{CE}, R_C$

(d)  $Q_3$

7.15 SEE SECTION 7.4, TABLE 7-1.

7.16 FROM CIRCUIT

$$V_{B,P} = V_{BE,0}(\text{SAT}) + V_{CE,0}(\text{SAT})$$

WHILE

$$V_{E,P} = V_{CE,0}(\text{SAT}) + V_D$$

HENCE

$$V_{BE,P} = V_{B,P} - V_{E,P} = V_{BE,0}(\text{SAT}) + V_{CE,0}(\text{SAT}) - (V_{CE,0}(\text{SAT}) + V_D(\text{ON}))$$

$\therefore V_{BE,P} = V_{BE,0}(\text{SAT}) - V_D(\text{ON}) < V_{BE}(\text{FA})$  AND THEREFORE  $Q_3$  PFA.

7.17

PSPICE, JUST DO AS THE PROBLEM SAYS.

7.18

$$V_{on} = V_{cc} - V_{BE,P}(\text{FA}) - V_{BE,PZ}(\text{FA}) = 5 - 0.7 - 0.7 = 3.6V$$

$$V_{on} = V_{CE,0}(\text{SAT}) = 0.2V$$


$$V_{IL} = V_{BE,S}(\text{FA}) - V_{CE,I}(\text{SAT}) = 0.7 - 0.2 = 0.5V$$

$$V_{IH} = V_{BE,0}(\text{SAT}) + V_{BE,S}(\text{SAT}) - V_{CE,I}(\text{SAT}) = 0.8 + 0.8 - 0.2 = 1.4V$$

$$V_{IO} = V_{BE,0}(\text{FA}) + V_{BE,S}(\text{FA}) - V_{CE,I}(\text{SAT}) = 0.7 + 0.7 - 0.2 = 1.2V$$

$$V_{OB} = V_{cc} - I_{ce}R_C - V_{BE,P}(\text{FA}) - V_{BE,PZ}(\text{FA})$$
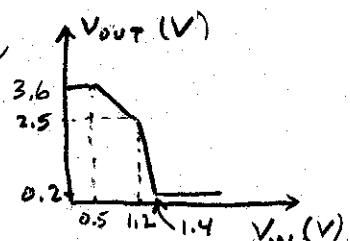
$$= V_{cc} - \left( \frac{R_C}{R_B + 1} \right) V_{BE,P}(\text{FA}) - V_{BE,PZ}(\text{FA}) = 5 - \left( \frac{760}{470 + 1} \right) 0.7 - 0.7 = 2.5V$$



CHAPTER 8 SOLUTIONS

8.1

$$(a) V_{ce} - I_c R_B - V_{ce} (sat) = 0 \quad V_{ce} = 0.5V$$

$$I_{ac} = (V_{ce} - V_{ce} (sat)) / R_C = (5.0 - 0.5) / 10k = 0.5mA = I_B$$

$$I_{ac} = (V_{ce} - V_{ce} (sat)) / R_C = (5 - 0.5) / 1k = 4.5mA$$

$$I_B = I_c / \beta = 4.5mA / 100 = 0.045mA$$

$$I_{SBO} = I_{ac} - I_B = 500mA - 45mA = 455mA$$

$$I_c = I_{ac} + I_{SBO} = 4.5mA + 0.455mA = 4.955mA \approx 5mA$$

(b) FORWARD ACTIVE

$$(c) I_B = (V_{ce} - V_{ce} (sat)) / R_B = (5.0 - 0.5) / 10k = 0.5mA = I_B$$

$$I_c = (V_{ce} - V_{ce} (sat)) / R_C = (5 - 0.2) / 1k = 4.8mA = I_c$$

$$V_{ce} = 0.2V$$

∴ THE BJT IS SATURATED.

8.2 SEE PROBLEM 8.1:

$$(a) I_{ac} = 0.99mA = I_B, \quad I_{ac} = 4.5mA, \quad I_B = 0.045mA, \quad I_{SBO} = 0.95mA$$

$$I_c = 5.45mA$$

(b) FORWARD ACTIVE

$$(c) I_B = 0.99mA = I_B$$

$$I_c = 4.8mA = I_c$$

$$V_{ce} = 0.2V$$

∴ THE BJT IS SATURATED.

8.3  $V_{out} = V_{ce} = 5V$


$$V_{ol} = V_{ce,0} (\text{HARD}) = 0.5V$$

$$V_{il} = V_{ce,0} (\text{sat}) = 0.7V$$

$$V_{in} = V_{ce,0} (\text{HARD}) + I_{BE0} R_B$$

$$V_{inmin} = V_{ce} - V_{il} = 5 - 0.7 = 3.8V$$
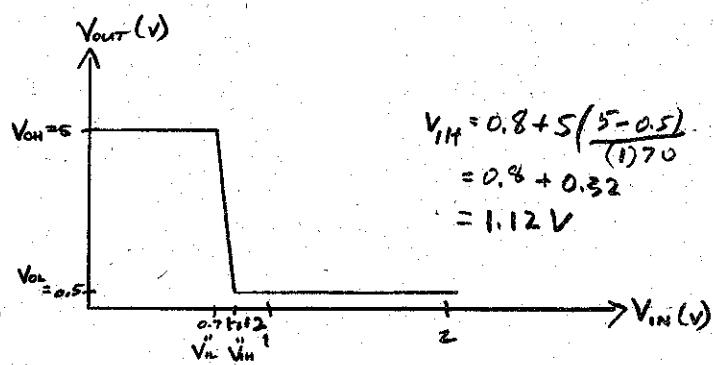
$$V_{num} = V_{il} - V_{ol} = 0.7 - 0.5 = 0.2V$$



CHAPTER 8 (CONT)

8.17 SEE SECTION 8.3, TABLE 8.2 :

	$V_{OH}$	$V_{OL}$
$Q_1$	ON-HARD	REVERSE
$Q_2$	CUTOFF	ON-HARD
$Q_P$	EDGE OF CONDUCTION	FORWARD ACTIVE
$Q_{Pz}$	EDGE OF CONDUCTION	CUTOFF
$Q_3$	CUTOFF	FORWARD ACTIVE
$Q_4$	CUTOFF	ON-HARD

8.18

$$V_{IN_1} = V_{IN_2} = 0 \quad V_{OUT} = 3.6V = V_{OH} \quad (\text{FROM } \#10)$$

$$V_{IN_1} = 0, V_{IN_2} = 5V \quad V_{OUT} = 3.6V = V_{OH} \quad (\text{FROM } \#10)$$

$$V_{IN_1} = 5V \quad V_{IN_2} = 0 \quad V_{OUT} = 3.6V = V_{OH} \quad (\text{FROM } \#10)$$

$$V_{IN_1} = V_{IN_2} = 5V \quad V_{OUT} = 0.5V = V_{OL} \quad (\text{FROM } \#10)$$

∴ THE NAND OPERATION IS SATISFIED.

8.19

$$V_{OH} = V_{CC} - V_{BE,F} (\text{FA}) = 5 - 0.7 = 4.3V$$


$$V_{OL} = V_{CE,0} (\text{HARD}) = 0.5V$$

$$V_{IL} = V_{BE,0} (\text{FN}) + V_{BE,S} (\text{FM}) - V_{SD0} (\text{ON}) = 0.7 + 0.7 - 0.3 = 1.1V$$

$$V_{IH} = V_{BE,0} (\text{HARD}) + V_{BE,S} (\text{HARD}) - V_{SD0} (\text{ON}) = 0.8 + 0.8 - 0.3 = 1.3V$$

$$V_{NMH} = V_{OH} - V_{IH} = 4.3 - 1.3 = 3.0V$$
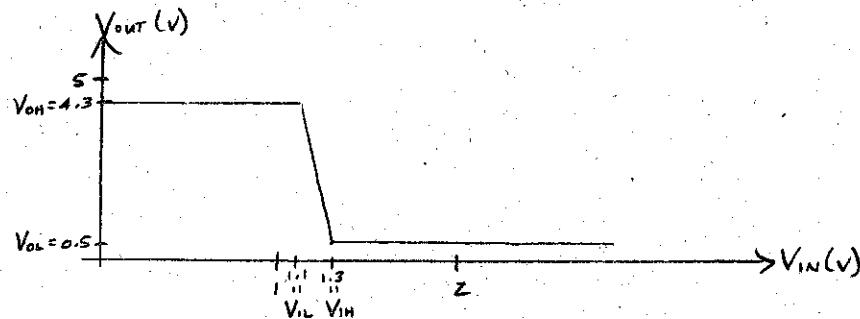
$$V_{NML} = V_{IL} - V_{OL} = 1.1 - 0.5 = 0.6V$$



8.20

$$(a) I_{IL} = (V_{CC} - V_{SD0, z} (\text{ON}) - V_{CE,0} (\text{HARD})) / R_E' = (5 - 0.3 - 0.5) / 20k = 0.21mA$$

$$(b) I_{OL} = I_{C,0} = \beta_F I_{B,0} = 50 (0.533mA) = 26.6mA$$

$$I_{E,0} = I_{E,S} - I_{C,0} = 0.633mA - 0.1mA = 0.533mA$$

8.20 (CONT'D)

CHAPTER 8 (CONT)

$$I_{C,0} = I_{RC0} = (V_{BE,0}(\text{HARD}) - V_{CE,0}(\text{HARD})) / R_{C0} = (0.8 - 0.5) / 3k = 0.1 \text{mA}$$

$$I_{E,S} = I_{O,S} + I_{C,S} = 0.17m + 0.463m = 0.633 \text{mA}$$

$$I_{C,S} = (V_{cc} - V_{CE,S}(\text{HARD}) - V_{BE,0}(\text{HARD})) / R_C = (5 - 0.5 - 0.8) / 8k = 0.463 \text{mA}$$

$$\begin{aligned} I_{B,S} &= I_{RB} = (V_{cc} - V_{BE,S}(\text{HARD}) - V_{BE,0}(\text{HARD})) / R_B \\ &= (5 - 0.8 - 0.8) / 20k = 0.17 \text{mA} \end{aligned}$$

$$(c) N = I_{OL} / I_{IL} = 26.6m / 0.21m = 126.67 \Rightarrow \text{MAX. FAN OUT} = 126$$

8.21  $I_{cc}(OH) = I_{IL} = 0.21 \text{mA}$  (FROM 8.20(a))

$$I_{RB}(OL) = 0.17 \text{mA}$$
 (FROM 8.20(b))

$$I_{RC}(OL) = 0.463 \text{mA}$$
 (FROM 8.20(b))

$$I_{cc}(OL) = I_{RB}(OL) + I_{RC}(OL) = 0.17m + 0.463m = 0.63 \text{mA}$$

$$P_{cc}(\text{AVG}) = [(I_{cc}(OL) + I_{cc}(OH)) / 2] V_{cc} = [(0.63m + 0.21m) / 2] 5 = 2.1 \text{mW}$$

8.22 SEE PROBLEMS 8.20 AND 8.21:

$$I_{IL} = 0.11 \text{mA}$$

$$I_{OL} = 8.5 \text{mA}$$

$$I_{B,0} = 0.17 \text{mA}, I_{C,0} = 0.1 \text{mA}, I_{E,S} = 0.27 \text{mA}, I_{C,S} = 0.19 \text{mA}, I_{B,S} = 0.09 \text{mA}$$

$$N = 80.95 \Rightarrow \therefore \text{MAX. FAN OUT} = 80$$

$$I_{cc}(OH) = 0.11 \text{mA}$$

$$I_{RB}(OL) = 0.09 \text{mA}$$

$$I_{RC}(OL) = 0.19 \text{mA}$$

$$I_{cc}(OL) = 0.28 \text{mA}$$

$$P_{cc}(\text{AVG}) = 0.98 \text{mW}$$

8.23

SEE PROBLEMS 8.20 AND 8.21:

$$I_{IL} = 1.05 \text{mA}$$

## CHAPTER 9 (CONT.)

$$9.9 \quad V_{OH} = V_{DD} - V_{BE,IP}(FA) = 5 - 0.7 = 4.3V$$

$$V_{OL} = V_{CE,0}(\text{HARD}) = 0.5V$$

$$V_{IL} = -V_{BE,IP}(FA) + 3V_{BE}(FA) = 1.4V$$

$$V_{IH} = -V_{BE,IP}(FA) + 3V_{BE}(\text{HARD}) = 1.7V$$

WITH NO KNEE

9.10 SAME ANSWER AS 9.2

9.11 SEE TABLE 9.4

ELEMENT STATE	$Q_{1P}$	$Q_{S2}$	$Q_S$	$Q_D$	$Q_K$	$Q_O$	$Q_P$	$Q_{DD}$	$Q_{P2}$	$Q_{P3}$
$V_{OH}$	FA	OFF	← SAME →	OFF	FA	OFF	OFF	OFF		
$V_{OL}$	OFF	HARD	← SAME →	HARD	FA	RS	OFF			

9.13 POWER DISS FOR 2 INPUT NAND  
(FIG 9.1a)

$$I_{CC}(0,0) = I_{RB}(1L) = \frac{5 - 0.8 - 0.5}{37k} = 0.1mA$$

$$I_{CC}(0,1) = I_{RB}(1L) = \frac{5 - 0.8 - 0.5}{37k} = 0.1mA = I_{CC}(1,0)$$

$$\begin{aligned} I_{CC}(1,1) &= I_{RB}(1H) + I_{RC}^{(OL)} + I_{RC}^{(0L)} + I_{RC}^{(0H)} \\ &= \frac{5 - 2.4}{37k} + \frac{5 - 0.5 - 1.6}{50k} + \frac{5 - 0.5 - 0.8}{14} \\ &= 0.07 + 0.058 + 0.264 = 0.39mA \end{aligned}$$

Zero drop across REP

$$P_{CC}(\text{AV}) = \frac{(0.1 + 2(0.1) + 0.39)}{4} \cdot 5 = 0.8625mW$$

CHAPTER 9 (CONT)

9.14 POWER DISS FOR 2 INPUT NAND (Fig 9.3a)

$$I_{CC}(0,0) = I_{RB}(1L) = \frac{5 - 0.3 - 0.5}{10} = 0.39 \text{ mA}$$

$$I_{CC}(0,1) = I_{CC}(1,0) = I_{CC}(0,0) = 0.39 \text{ mA}$$

$$\begin{aligned} I_{CC}(1,1) &= I_{RB}(0L) + I_{RC}(0L) + I_{RBOD}^{(0L)} + I_{RCB}^{(0L)} \\ &= \frac{5 - 3(0.8)}{10} + \frac{5 - 0.5 - 2(0.8)}{10} + \frac{5 - 0.5 - 0.8}{4,1} \\ &= 0.26 + 0.29 + 0.9 = 1.45 \text{ mA} \end{aligned}$$

$$P_{DISS} = I_{CC} V_{CC} = \frac{(0.39 \times 3 + 1.45)}{4} 5 = 3.275 \text{ mW}$$

9.15 Power Diss for 2 INPUT NAND (FIG 9.4)

$$I_{CC}(0,0) = I_{RBPI}^{(0H)} + I_{RR}^{(0H)} = \frac{5 - 0.3 + 0.7}{30k} + \frac{5 - 0.7 - 0.5}{10k} = 0.08 + 0.38 = 0.46 \text{ mA}$$

$$I_{CC}(0,1) = I_{CC}(1,0) = I_{CC}(0,0) = 0.46 \text{ mA}$$

$$I_{CC}(1,1) = I_{RB}(0L) + I_{RC}(0L) + I_{RBPI}^{(0L)} + I_{BOD}^{(0L)} + I_{RCB}^{(0L)}$$

$$I_{RB}(0L) = \frac{5 - 0.8(3)}{10k} = 0.26 \text{ mA}$$

NO DROP  
ACROSS  
REP

$$I_{RC}(0L) = \frac{5 - 0.5 - 0.8}{2k} = 1.85 \text{ mA}$$

$$I_{RBOD}^{(0L)} = \frac{5 - 0.3 - 0.5}{30k} = 0.14 \text{ mA}$$

$$I_{RBPI}^{(0L)} = \text{SAME} = 0.08 \text{ mA}$$

$$I_{CC}(1,1) = 0.26 + 1.85 + 0.14 + 0.08 = 2.33 \text{ mA}$$

$$P_{CC} = \frac{(2.33 + 0.46(3))}{4} 5 = 0.9275 \text{ mW}$$

CHAPTER 10 (CONT)

10.22 (CONT)

$$I_{CC}(11) = 2I_{R_B}(IH) + I_{R_C}(OH) \\ = 2(0.175) + 0.35 = 0.7 \text{ mA}$$

$$P_{CC}(\text{AVG}) = 5(0.73 + 2(0.73) + 0.7)/4 = 3.6 \text{ mW}$$

(b) COMPARE WITH LSTTL NAND OF EX 8.5  $\rightarrow P_{DISS} = 2.1 \text{ mW}$

NOTE  $3.6 > 2.1$

(c) PROBLEM 10.21  $P_{DISS} = 21.3 \text{ mW} \gg 3.6 \text{ mW}$

10.23 VTC OF LSTTL OR GATE

$$V_{OH} = V_{CC} - V_{BE,P}(\text{FA}) = 5 - 0.7 = 4.3 \text{ V}$$

$$V_{OL} = V_{CE,S_0}(\text{HARD}) = 0.5 \text{ V}$$

$$V_{IL} = -V_{SB_2,I}(\text{ON}) + V_{BE,S_2}(\text{FA}) + V_D(\text{ON}) = -0.3 + 0.7 + 0.7 = 1.1 \text{ V}$$

$$V_{IH} = -V_{SB_2,I}(\text{ON}) + V_{BE,S_2}(\text{HARD}) + V_D(\text{ON}) = -0.3 + 0.8 + 0.7 = 1.2 \text{ V}$$

10.24

(a) CRITICAL VOLTAGES

$$V_{OH} = V_{CC} - V_{BE,P}(\text{FA}) = 5 - 0.7 = 4.3 \text{ V}$$

Breakpoint at

$$V_{IB} = 1.2 \text{ V}$$

$$V_{OL} = V_{CE}(\text{SAT}) = 0.2 \text{ V}$$

$$V_{OB} = 5 - 20 \frac{(0.7)}{12} \\ - 0.7$$

$$V_{IL} = -V_{CE,I} - V_{BE,S}(\text{FA}) = -0.2 + 0.7 = 0.5 \text{ V}$$

$$V_{IH} = -0.2 + 1.6 = 1.4 \text{ V}$$

$\approx 3.13 \text{ V}$  and  
switch  
curve

b) AVG POWER DISSIPATION

$$P_{CC} = V_{CC} (I_{CC}(00) + I_{CC}(D1) + I_{CC}(10) + I_{CC}(11))$$

$$I_{CC}(00) = 2I_{R_B}(\text{IL}) = 2 \left( \frac{V_{CC} - V_{BE,I}(\text{SAT}) - V_{IL}}{R_B} \right)$$

$$= 2 \left( \frac{5 - 0.8 - 0.2}{40} \right) = 2(0.1) = 0.2 \text{ mA}$$

## CHAPTER 10 (CONT)

10.24 (CONT)

$$\begin{aligned}
 I_{CC}(0) &= I_{RB}(I_L) + I_{RB}(I_H) + I_{RC}(0_L) \\
 (&= I_{CC}(0)) \\
 &= 0.1 + \frac{V_{CC} - V_{BE,2}(RA) - V_{BE,S}^{(SAT)}}{R_B} + \frac{V_{CC} - V_{CE,I}^{(SAT)} - V_{BE,D}^{(SAT)}}{R_C} \\
 &= 0.1 + \frac{5 - 0.7 - 0.8}{40} + \frac{5 - 0.2 - 0.8}{20} \\
 &= 0.1 + 0.07 + 0.2 = 0.37 \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 I_{CC}(1) &= 2 I_{RB}(I_H) + I_{RC}(0_L) \\
 &= 2(0.07) + 0.2 = 0.34 \text{ mA}
 \end{aligned}$$

$$P_{CC}(\text{AVG}) = 5 \left( \frac{0.2 + 2(0.37) + 0.34}{4} \right) = 1.6 \text{ mW}$$

(c) COMPARE WITH EXAMPLE 10.2  $\rightarrow 17.88 \text{ mW}$   
     ; POWER DISS MUCH LESS FOR TTL GATE

10.25

a) VTC

$$V_{OH} = V_{CC} - 2V_{BE}(FA) = 5 - 2(0.7) = 3.6 \text{ V}$$

$$V_{OL} = V_{CE,D}^{(SAT)} = 0.2 \text{ V}$$

V<sub>IL</sub> FOR THE AND GATE, WHEN  $V_{IN} = V_{IL}$ ,  $V_{OUT} = V_{OL}$ . THUS

WHEN  $V_{AND}$  BEGINS TO INCREASE FROM  $V_{OL}$ , WE HAVE

$$V_{CS_2} = V_{BE,0}^{(SAT)} + V_{BE,S}^{(SAT)} + V_{DS}^{(ON)} = 2(0.8) + 0.7 = 2.3 \text{ V}$$

$$\therefore I_{RC_S} = \frac{V_{CC} - V_{CS_2}}{R_{CS}} = \frac{5 - 2.3}{1} = 2.7 \text{ mA} \Rightarrow \text{ALL THRU } D_5, \text{ SINCE } Q_{S2}, Q_{SD} \text{ CUTOFF}$$

WHEN  $V_{CS_2}$  BEGINS TO REDUCE FROM  $2.3 \text{ V}$ ,  $Q_0$  BEGINS TO CONDUCT. THIS OCCURS FOR

$$V_{IN} = V_{BE,S2} - V_{CE,I}^{(SAT)} = 0.7 - 0.2 = 0.5 \text{ V} = V_{IL}$$

FURTHERMORE, WHEN  $V_{CS_2} = 3(0.7) = 2.1 \text{ V}$ ,  $Q_0$  BECOMES CUTOFF AND

$$I_{RC_S} = \frac{V_{CC} - V_{CS_2}}{R_{CS}} = \frac{5 - 2.1}{1} = 2.9 \text{ mA} = I_{ES_2}$$

THIS CURRENT IS SUFFICIENT TO SATURATE  $Q_{SD}$  SINCE  $I_{RS_D} = 0.8/0.4 = 2 \text{ mA}$  PRODUCES  $V_{BE,S_D}^{(SAT)} = 0.8 \text{ V}$  HENCE,  $I_{BS_D} = 0.9 \text{ mA}$  AND

$$V_{IH} = V_{BE,S_D}^{(SAT)} + V_{BE,S_2}^{(SAT)} - V_{CE,I}^{(SAT)} = 0.8 + 0.8 - 0.2 = 1.4 \text{ V}$$

CHAPTER 11 (CONT)

11.13  $V_{NOR}$

$$V_{OH} = -V_{BE,N}(ECL) = -0.7V$$

$$V_{IL} = -1.175 - 0.05 = -1.225V$$

$$V_{IH} = -1.175 + 0.05 = -1.125V$$

$$V_{OL} = -I_C R_{C2} - V_{BE,N}(ECL)$$

$$= -\left(\frac{V_{IH} - V_{BE}(ECL) + V_{EE}}{R_E}\right) R_{C2} - V_{BE}(ECL)$$

$$= -\left(\frac{-1.125 - 0.75 + 5.2}{1.18}\right)(0.29) - 0.75$$

$$V_{OL} = -1.57V$$

$$= \frac{-0.75 + 5}{0.5 + 3(51)}$$

$$11.14 V_{OH} = V_{NOR} = -I_{C,BN} R_{C2} - V_{BE,BN}(ECL) = -(27.69mA)(500) - 0.75 = -0.76V.$$

$$I_{C,BN} = (V_{EE} - V_{BE,BN}(ECL)) / (R_{C2} + (1+\beta)R_{DN}) = (5 - 0.75) / (500 + 51(3k)) = 27.69mA$$

$$V_{IL} = V_{EE} - 0.05 = -1.175 - 0.05 = -1.225V$$

$$V_{IH} = V_{EE} + 0.05 = -1.175 + 0.05 = -1.125V$$


$$V_{OL} = -I_C R_C - V_{BE}(ECL) = -(1.845mA)(300) - 0.75 = -1.3V = V_{NOR}$$

$$I_{C,I} \approx I_{E,I} = (V_{IN} - V_{BE,I}(ECL) + V_{EE}) / R_E = (V_{OH} - V_{BE,I}(ECL) + V_{EE}) / R_E \\ = (-0.76 - 0.75 + 5) / 2k = 1.845mA$$

$$V_S = [V_{AC(SAT)} + \frac{R_{C2}}{R_E} (V_{AC(SAT)} - V_{EE})] / (1 + \frac{R_{C2}}{R_E}) = [0.6 + \frac{500}{2k} (0.8 - 5)] / (1 + \frac{500}{2k}) = -0.36V$$

From next page  $I_B = 27.69mA$

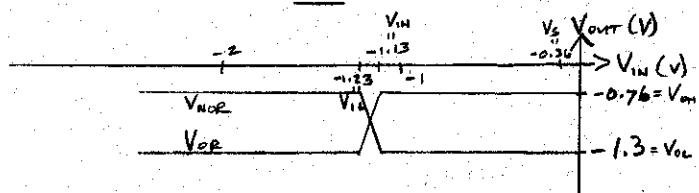THE OR CASE IS IDENTICAL TO THE NOR CASE, EXCEPT INVERTED.



CHAPTER 11 (CONT'D)

11.14 (CONT'D)

$$I_{B,00} = (V_{EE} - V_{BE,00}(\text{ECL})) / (R_{C,R} + (1+\beta) R_{D0}) = (5 - 0.75) / (500 + 51(2k)) = 27.69 \mu\text{A}$$

$$\therefore I_{B,00}(\text{OH}) = I_{B,BN}(\text{OH})$$

11.15

$$V_{OH} = V_{OB} = -I_{B,00} R_{CR} - V_{BE,00}(\text{ECL}) = -43.54(245) - 0.75 = -0.76 \text{V}$$

$$I_{B,00} = (V_{EE} - V_{BE,00}) / (R_{C,R} + (1+\beta_B) R_{D0}) = (5.2 - 0.75) / (245 + 51(2k)) = 43.54 \mu\text{A}$$


$$V_{OL} = -I_{RCR} R_{CR} - V_{BE,00}(\text{ECL}) = -4.04m(245) - 0.75 = -1.74 \text{V}$$

$$I_{RCR} \approx I_E = (V_{EE} - V_{BE,R}(\text{ECL}) + V_{EE}) / R_E = (-1.3 - 0.75 + 5.2) / 0.78k = 4.04 \text{mA}$$

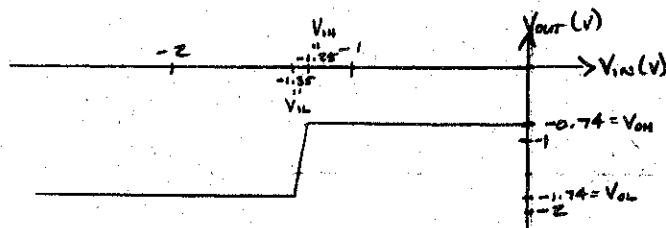11.16

$$V_{IL} = V_{OB} - 0.05 = -1.3 - 0.05 = -1.35 \text{V}$$

$$V_{IH} = V_{OB} + 0.05 = -1.3 + 0.05 = -1.25$$



11.17

$$V_{IH} = -1.1 \text{V}$$

$$V_{VOMH} = V_{OH} - V_{IH} = 0.2 \text{V}, \therefore V_{OH} = 0.2 - 1.1 = -0.9 \text{V} = V_{MIN} \text{ FOR MAX FAN-OUT}$$

$$I'_{IH} = \frac{I'_E}{\beta_F + 1} = \frac{V_{OH} - V_{BE}'(\text{FA}) + V_{EE}}{(B_F + 1) R_E} = \frac{-0.9 - 0.75 + 5.2}{51(0.78)} = 0.089 \text{mA}$$

$$I_{OH} = I_{EB0} - I_{RD0}$$

$$I_{EB0} = (1 + \beta_F) I_{B_{SO}} = (1 + \beta_F) \left| \frac{[-V_{BE}(\text{FA}) + V_{OH}]}{R_{CR}} \right| = 51 \left( \frac{-0.75 + 0.9}{0.245} \right) = 31.2 \text{mA}$$

$$I_{RD0} = \frac{V_{OH} + V_{BE}}{R_E} = \frac{-0.9 + 5.2}{2} = 2.15 \text{mA} \quad \therefore I_{OH} = 31.2 - 2.15 = 29.05 \text{mA}$$

$$N = \frac{29.05}{0.089} = 326.4 \text{ or } 326$$

11.18

$$V = V_{ZAH} = -0.7 \text{V}; Q_2(\text{FA}), Q_R(\text{OFF}), Q_O(\text{SAT})$$

$$I_{B,0} = \frac{5 - 0.8}{3} = 1.4 \text{mA}$$

$$I_C = 50(1.4) \text{mA} = \text{too large}$$

$$\therefore V_{out} = V_{C(\text{SAT})} = 0.2 \text{V} = V_{OL}$$

$$V_I = V_{IL} = -2 \text{V}; Q_2(\text{OFF}), Q_R(\text{ON})$$

AND Q\_O(OFF) SINCE

$$V_{B,0} = 5 - \left( \frac{5.2 - 1.3 - 0.75}{0.78} \right) 3$$

$$V_{B,0} = 5 - 12.09 = -7 \text{V}$$

$$\therefore V_{out} = V_{C} = 5 \text{V} = V_{OH}$$

## CHAPTER 12 (CONT)

12.10  $I_{EE}(\text{NoH})$ :

$$I_{RE}(\text{NoH}) = \frac{V_{BB} - V_{BE}(\text{ECL}) + V_{EE}}{R_E} = \frac{-1.175 - 0.75 + 5.2}{1.18} = 2.78 \text{ mA}$$

$$I_{RD_N}(\text{NoH}) = \frac{V_{OH} + V_{EE}}{R_{DN}} = \frac{-0.75 + 5.2}{1.5} = 2.97 \text{ mA}$$

$$I_{RD_O}(\text{NoH}) = \frac{V_{OL} + V_{EE}}{R_{DO}} = \frac{-1.58 + 5.2}{1.5} = 2.41 \text{ mA}$$

$$I_{RB_L} = \frac{V_{EE} - 2V_{B}(m)}{R_{BH} + R_{BL}} = \frac{5.2 - 1.5}{2.3 + 0.3} = 1.42 \text{ mA}$$

$$I_{RB_E} = \frac{V_{EE} - I_{RB_H} R_{BL} - V_{BB}(\text{ECL})}{R_{BE}} = \frac{5.2 - \frac{5.2 - 1.5(0.3)}{2.6} - 0.75}{2} = 2.015 \text{ mA}$$

$$I_{EE}(\text{NoH}) = 2.78 + 2.97 + 2.41 + 1.42 + 2.015 = 11.6 \text{ mA}$$

$I_{EE}(\text{NoL})$ :

$$I_{RE}(\text{NoL}) = \frac{V_{OH} - V_{BE}(\text{ECL}) + V_{EE}}{R_E} = \frac{-0.75 - 0.75 + 5.2}{1.18} = 3.7 \text{ mA}$$

$$I_{RD_N}(\text{NoL}) = \frac{V_{OL} + V_{EE}}{R_{DN}} = 2.41 \text{ mA}$$

$$I_{RD_O}(\text{NoL}) = \frac{V_{OH} + V_{EE}}{R_{DO}} = 2.97 \text{ mA}$$

$$I_{RB_L} = 1.42 \text{ mA}$$

$$I_{RB_E} \approx 2.015 \text{ mA}$$

$$\therefore I_{EE}(\text{NoL}) = 3.7 + 2.41 + 2.97 + 1.42 + 2.015 = 12.5 \text{ mA}$$

$$P_{EE}(\text{A4}) = \frac{(11.6 + 12.5)}{2} \cdot 5 = 60.3 \text{ mW}$$

(NEXT PAGE)

12.11 FROM 12.10 Substituting  $R_W = R_{DO} = 3k \rightarrow P_{EE} = 47.2 \text{ mW}$

12.12 FROM 12.10 Substituting  $R_E = 3k \rightarrow P_{EE} = 51.8 \text{ mW}$

CHAPTER 13 (CONT.)

13.6

$$\begin{aligned}
 V_{BB} &= -I_{RBH} R_{BH} - V_{BE}(ECL) \\
 &= -\left(\frac{V_{EE} - 2V_D(\text{ON})}{R_{BH} + R_{BL}}\right) R_{BH} - V_{BE}(ECL) = -\left(\frac{5.2 - 2(0.75)}{0.907 + 4.98}\right)(6.907) - 0.75 \\
 &= -1.32 \text{ V}
 \end{aligned}$$

13.7 FOR THE OR OUTPUT

$$V_{OH} = -V_{BE,BD}^{(ECL)} = -0.75 \text{ V}$$

$$\begin{aligned}
 V_{OL} &= +I_{RCR} R_{CR} - V_{BE,BD}^{(ECL)} = -\left(\frac{V_{BB} - V_{BE,R}^{(ECL)} + V_{EE}}{R_E}\right) R_{CR} - V_{BE}^{(ECL)} \\
 &= -\left(\frac{-1.32 - 0.75 + 5.2}{0.777}\right)(6.245) - 0.75 = -1.74 \text{ V}
 \end{aligned}$$

$$V_{IH} = V_{BB} + 0.05 = -1.315 \text{ V}$$

$$V_{IL} = V_{BB} - 0.05 = -1.325 \text{ V}$$

$$V_S = \frac{0.6 + \frac{217}{777}(0.75 - 5.2)}{1 + \frac{217}{777}} = \frac{-0.643}{1.279} = -0.5 \text{ V (FOR NOR)}$$

13.8 DOUBLING RE CHANGES VOL AND VS ONLY. THE NEW VALUES ARE

$$V_{OL} = -\frac{(-1.38 - 0.75 + 5.2)}{2(0.777)}(0.245) - 0.75 = -1.234 \text{ V}$$

$$V_S = \frac{0.6 + \frac{217}{2(777)}(0.75 - 5.2)}{1 + \frac{217}{2(777)}} = \frac{-0.02}{1.14} = -0.018 \text{ V}$$

13.9 DOUBLING RC CHANGES VOL AND VS ONLY. THE NEW VALUES ARE

$$V_{OL} = -\frac{(-1.38 - 0.75 + 5.2)}{0.777}(2)(0.245) - 0.75 = -2.69 \text{ V}$$

$$V_S = \frac{0.6 + \frac{2(217)}{777}(0.75 - 5.2)}{1 + 2(217)/777} = \frac{-1.886}{1.559} = -1.21 \text{ V}$$

13.10  $V_{OH}$  REDUCES BY 0.1 V. THEREFORE  $V_{OH} = -0.75 - 0.1$

$$V_{OH} = -0.85, V'_E = -0.85 - 0.75 = -1.6 \text{ V}$$

$$I'_{RE} = \frac{-1.6 + 5.2}{.365} = 9.86 \text{ mA}$$

$$I'_B = \frac{9.86}{49+1} = 0.197 \text{ mA}$$

$$I'_{RP} = \frac{-0.85 + 5.2}{50} = 0.087 \text{ mA}$$

CHAPTER 13 (CONT)

13.10 (CONT)

$$I_{IH}' = 0.087 + 0.197 = 0.284$$

$$I_{RC_2} = \frac{(-0.75) - (-0.85)}{0.1} = -1 \text{ mA}$$

$$I_{OH} = (49+1)(1) = 50 \text{ mA}$$

$$N = \frac{50 \text{ mA}}{0.284 \text{ mA}} = 176.05 \rightarrow N = 176$$

13.11 ALLOWABLE  $V_{OH} = -0.75 - 0.1 = -0.85$

$$I_{RE}' = \frac{V_E' + 5.2}{R_E} = -\frac{0.85 - 0.75 + 5.2}{0.777} = 4.63 \text{ mA}$$

$$I_B' = \frac{I_E'}{\beta_F + 1} = \frac{4.63}{50} = 0.093 \text{ mA}$$

$$I_{RP}' = -\frac{0.85 + 5.2}{50} = 0.087 \text{ mA}$$

$$I_{IH}' = 0.087 + 0.093 = 0.18 \text{ mA}$$

$$I_{RC_2} = -\frac{-0.75 - (-0.85)}{0.217} = 0.46 \text{ mA}$$

$$I_{OH} = (49+1)(0.46) = 23.04$$

$$N = \frac{23.04}{0.18} = 128.01 \rightarrow N = 128$$

13.12 BIAS NETWORK POWER DISS

$$I_{RB_L} = \frac{5.2 - 2(0.75)}{0.350 + 1.95B} = 1.6 \text{ mA}$$

$$I_{RB_E} = \frac{5.2 - 1.6(0.35) - 0.75}{2} = 1.95 \text{ mA}$$

THUS, FOR BIAS NETWORK

$$P_{DISS} = V_{EE}(I_{RB_L} + I_{RB_E}) = 5.2(1.6 + 1.95)$$

$$= 18.46 \text{ mW}$$

CHAPTER 14 SOLUTIONS

14.1

$$V_{BB} = -I_R R - V_{BE,B_1}(ECL) = -I_{C_{S_2}} R - V_{BE}(ECL)$$

$$= -\left(\frac{V_{D(0n)} - V_{BE}(ECL)}{R_{E_2}}\right)R - V_{BB}(ECL)$$

$$V_{BB} = -\left(\frac{0.8 - 0.75}{0.1}\right)(0.9) - 0.75 = -1.2 V$$

$$V'_{BB} = -V_{EE} + V_{BE}(ECL) + I_R R = -4.5 + 0.75 + 0.45 = -3.3 V$$

14.2  $R = 500 \Omega$

$$V_{BB} = -\left(\frac{0.8 - 0.75}{0.1}\right)(0.5) - 0.75 = -1 V$$

$$V'_{BB} = -4.5 + 0.75 + 0.25 = -3.5 V$$

14.3 AS EXPLAINED IN TEXT

14.4  $V_{EE} = 5.2 V$

$$V_{BB} \text{ UNCHANGED} = -1.2 V$$

$$V'_{BB} = -5.2 + 0.75 + 0.25 = -4.2 V$$

14.5  $R'_E = 0.5 k\Omega$

$$I_E = \frac{V'_{BB} - V_{BE,E}(ECL) + V_{EE}}{R'_E} = \frac{-3.2 - 0.75 + 4.5}{0.5}$$

$$I_E = 1.1 \text{ mA}$$

14.6 CRITICAL VOLTAGES

$$V_{OH}^{(NOH)} = -V_{BE}(ECL) - I_{R_C}^{(NOH)} R_{C_I}$$



$$= -V_{BE}(ECL) - I_{R_C} R_{C_I}$$

$$= -0.75 + \left(\frac{V_{B,0} + V_{D,L}(0N)}{2R}\right)R$$


$$= -0.75 + \frac{-0.85 + 0.75}{2} = -0.8 V$$

CHAPTER 15 SOLUTIONS

15.1

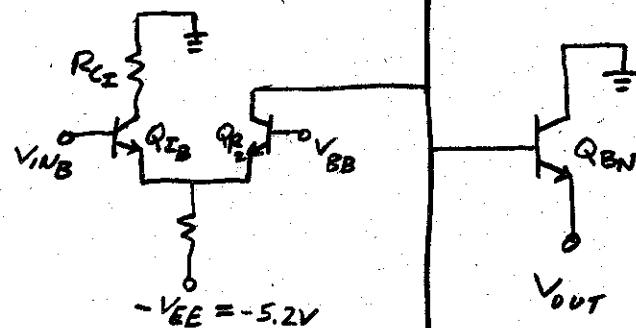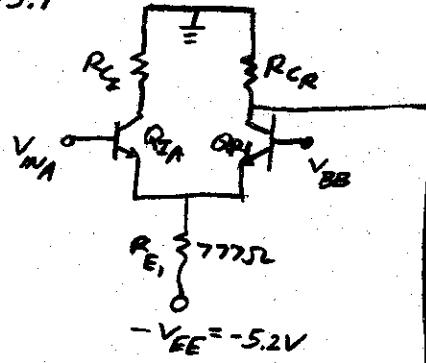

$F = A \text{ AND } B \text{ AND } C$

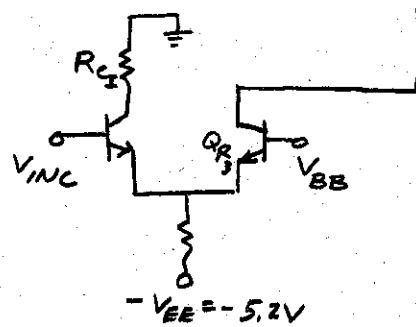

15.2

$$V_{OH} = -I_{R_{CR}} R_{CR} - V_{BE, BN} \text{ (ECL)}$$

$$V_{OH} = 0 - 0.75 = -0.75V$$

$$V_{OL} = -I_{RE} R_{CR} - V_{BE, BN} \text{ (ECL)}$$

$$V_{OL} = -\left(\frac{V_{BB} - V_{BE, R} \text{ (ECL)} + V_{EE}}{R_E}\right) R_{CR} - V_{BE, BN} \text{ (ECL)}$$

$$V_{OL} = -\left(\frac{-1.32 - 0.75 + 5.2}{772}\right)(245) - 0.75$$

$$\therefore V_{OL} = -0.99 - 0.75 = -1.74V$$

$$V_{IL} = V_{BB} - 0.05 = -1.32 - 0.05 = -1.37V$$

$$V_{IH} = V_{BB} + 0.05 = -1.32 + 0.05 = -1.27V$$

$V_S$  IS NONEXISTANT SINCE  $Q_R$  DOES NOT SATURATE

## CHAPTER 16 (CONT)

16.5 NPN LAYERS S/D - SUBSTRATE - SUBSTRATE  
 N P N

PNP LAYERS S/D - SUBSTRATE - SUBSTRATE  
 P N P

16.6 BEGIN BY REARRANGING  $I_D(SAT)$  AS

$$I_D(SAT) = \frac{5}{4} (2 + V_{GS})^2$$


THUS,  $V_T = -2V$

AND

$$\frac{R}{2} = \frac{5}{4} = 1.25 \text{ mA/V}^2$$

SAT CALCULATIONS

$V_{GS}$ (V)	$I_D(SAT)$ (mA)
-2	0
-1	$5/4 = 1.25 \text{ mA}$
0	$5 = 5 \text{ mA}$
1	$9(5/4) = 11.25 \text{ mA}$

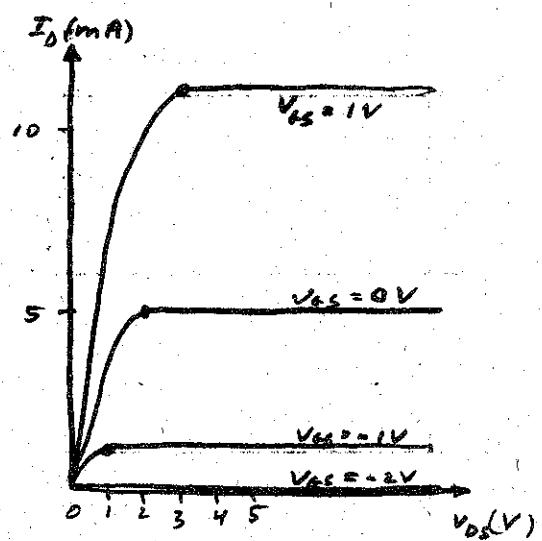

16.7 REARRANGE  $I_D(SAT)$

$$I_D(SAT) = \frac{5}{4} (V_{GS} - 2)^2$$

THUS,


$$V_T = 2V$$

AND

$$\frac{R}{2} = \frac{5}{4} = 1.25 \text{ mA/V}^2$$

SAT CALCULATIONS

$V_{GS}$ (V)	$I_D(SAT)$ (mA)
2	0
3	1.25
4	5
5	$9(5/4) = 11.25$

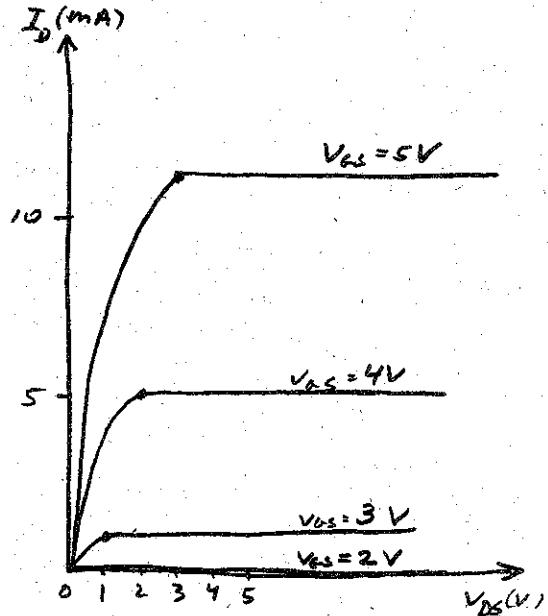

CHAPTER 17 SOLUTIONS

17.1 SEE SOLUTION FOR PROBLEM 16.6.

17.2 " " " " " 16.7

17.3 " " " " " 16.8

17.4 CONVERT  $I_D(\text{LIN})$  TO  $I_D(\text{SAT})$

WHERE (BY INSPECTION)  $V_T = 1V$ ,  $k = 5\text{mA/V}^2$

$$\therefore I_D(\text{SAT}) = \frac{5}{2} (V_{GS} - 1)^2$$

AND THIS IS TWICE THE CURRENT OF PROB 17.1


17.5 CONVERT  $I_D(\text{LIN})$  TO  $I_D(\text{SAT})$

WHERE (BY INSPECTION)  $V_T = -2V$ ,  $k = 4\text{mA/V}^2$

$$\therefore I_D(\text{SAT}) = 2 (V_{GS} - 2)^2$$

SAT CALCULATIONS  $I_D(\text{mA})$



$V_G(V)$	$I_D(\text{mA})$
2	0
3	2
4	8
5	18

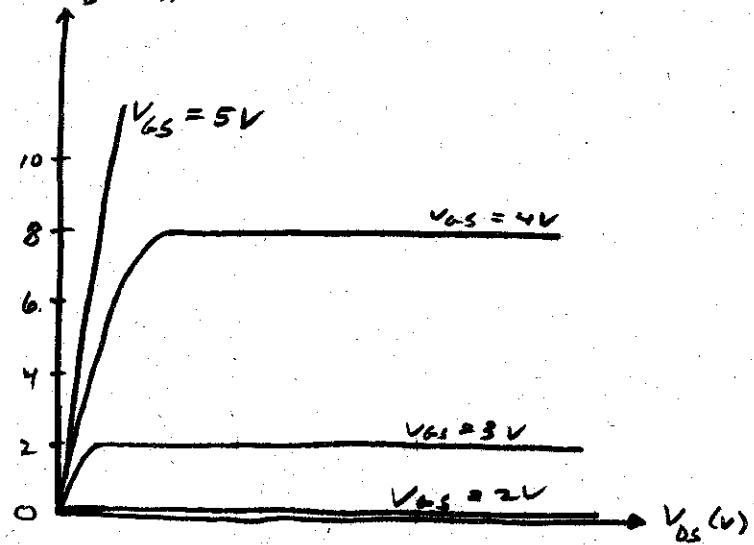

17.6 THIS  $I_D$  VS  $V_{DS}$  AND  $V_{GS}$  CORRESPONDS TO PROBLEM 17.3



CHAPTER 17 (CONT)

17.9

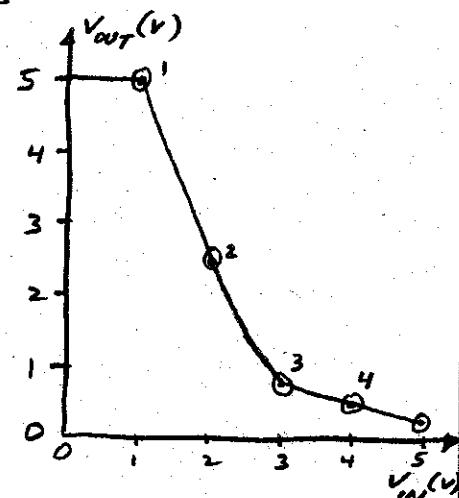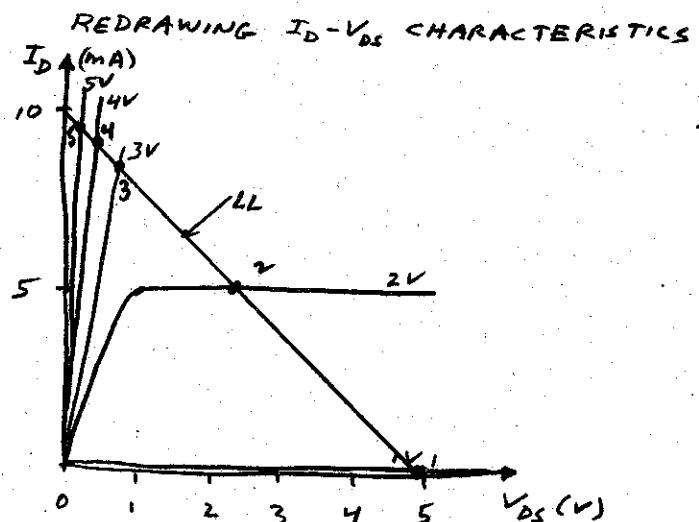

17.10 SAME SOLUTION AS PROBLEM 17.7

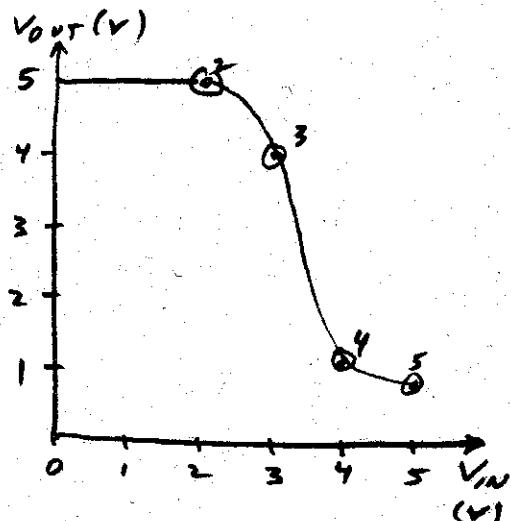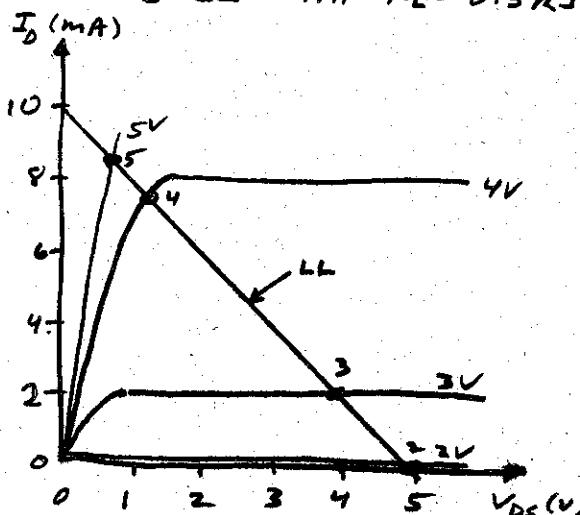17.11 REDRAWING  $I_D$  CHARACTERISTICS FROM 17.5 AND LL WITH  $R_L = 0.5k\Omega$ ,  $V_{DD} = 5V$



17.12 SAME SOLUTION AS PROBLEM 17.9.

17.13 AVG STATIC POWER DISSIPATION

$$V_{DD} = 5V, I_{DD(0V)} = 0, I_{DD(0.5V)} = 0.3mA$$

$$P_{DD(AV)} = 5 \left( \frac{0 + 0.3}{2} \right) = 0.75mW$$

CHAPTER 18. SOLUTIONS



18.1

CRITICAL VOLTAGE       $V_{OH}$      $V_{OL}$      $V_{IL}$      $V_{IH}$      $V_M$   
 BJT STATE               OFF    LIN    SAT    LIN    SAT

18.2     $V_T = 1V$ ,  $R = 0.1mA/V^2$

$$I_D(\text{SAT}) = \frac{k}{2} (V_{GS} - V_T)^2 = \frac{0.1}{2} (V_{GS} - 1)^2$$

$V_{GS}$	$I_D(\text{SAT})(\text{mA})$
1	0
2	0.05
3	0.20
4	0.45
5	0.8

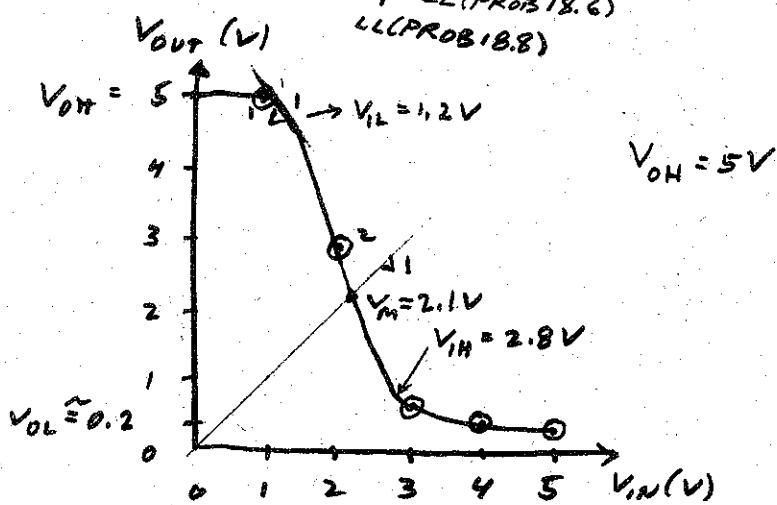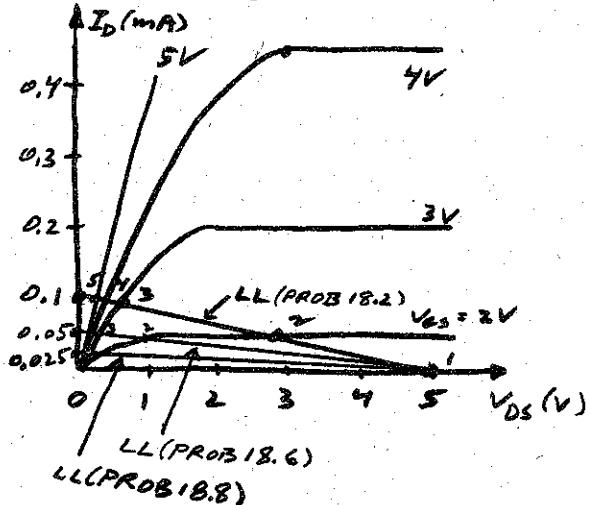

18.3     $V_{IN} < 1V$ , NO CUTOFF AND  $V_{OH} = 5V$

$$V_{IL} = V_T + \frac{1}{RR_L} = 1 + \frac{1}{0.1(50)} = 1.2V, V_{OL} = \frac{V_{DD}}{RR_L(V_{DD}-V_T)+1} = 0.238V$$

$$V_{IH}: \quad \frac{3R}{8}(V_{IH}-V_T)^2 + \frac{1}{2R_H}(V_{IH}-V_T) - \frac{V_{DD}}{R_L} = 0$$

$$V_{IH}-V_T = -\frac{1}{2R_L} \pm \sqrt{\frac{1}{4R_L^2} + \frac{3R}{2R_H}} = -0.01 \pm \sqrt{0.0001 + 0.015} \\ 3R/4 \qquad \qquad \qquad 0.075$$

$$V_{IH}-V_T = 1.505V \rightarrow V_{IH} = 2.505V$$

CHAPTER 19 SOLUTIONS

19.1

	$V_{OH}$	$V_{OL}$	$V_{IL}$	$V_{IH}$	$V_m$
$N_o$	CUTOFF	LIN	EOS	LIN	SAT
$N_L$	SAT	SAT	SAT	SAT	SAT

19.2

$$k_o = k' \left( \frac{w}{L} \right)_o = 20 \mu \frac{20 \mu}{2 \mu} = 200 \mu A/V^2$$

$$k_L = k' \left( \frac{w}{L} \right)_L = 20 \mu \frac{10 \mu}{5 \mu} = 40 \mu A/V^2$$


I-V EXPRESSION FOR  $N_L$ :

$$I_{D,L}(\text{SAT}) = \frac{k_L}{2} (V_{DS,L} - V_{T,L})^2 = \frac{k_L}{2} ([V_{DD} - V_{DS,o}] - V_{T,L})^2 = \frac{40 \mu}{2} (5 - 1) - V_{DS,o})^2$$

$$I_{D,L}(\text{SAT}) = 20 \mu (4 - V_{DS,o})^2$$

$I_{D,L}(\text{mA})$	$V_{DS}(\text{V})$
0	4
0.08	2
0.32	0


$I_D(\text{mA})$

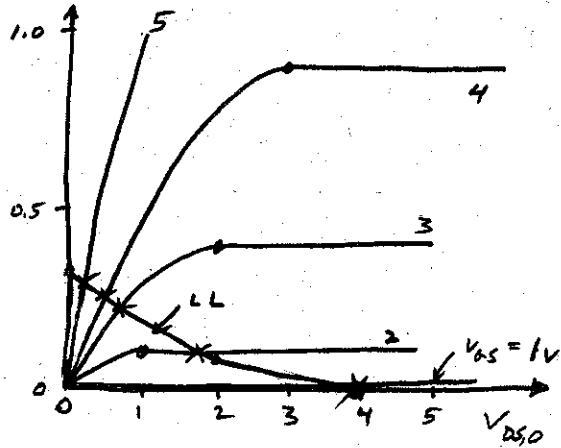

I-V SAT EXPRESSION FOR  $N_o$ :

$$I_{D,o}(\text{SAT}) = \frac{k_o}{2} (V_{DS} - V_T)^2 = 100 \mu (V_{DS} - 1)^2$$

$V_{DS}(\text{V})$	$I_{D,o}(\text{SAT}) \text{ mA}$
1	0
2	0.1
3	0.4
4	0.9

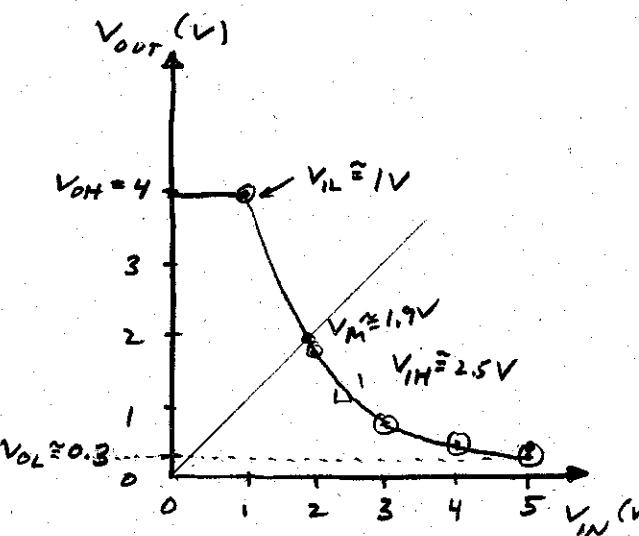

CHAPTER 20 SOLUTIONS

20.1

OPERATING STATES AT CRITICAL POINTS  
E-ONLY LOAD

CRITICAL POINT	OUTPUT NO.	LOAD
----------------	------------	------

$V_{OH}$	CUTOFF	LIN
$V_{IL}$	SAT	LIN
$V_M$	SAT	LIN
$V_{IH}$	LIN	LIN
$V_{OL}$	LIN	LIN

20.2


$$k_0 = k'(\omega_L)_0 = 20\mu\text{A} \left( \frac{20\text{m}}{2\text{m}} \right) = 200\mu\text{A/V}^2, V_T = 1\text{V}$$

$$k_L = k'(\omega_L)_L = 20\mu\text{A} \left( \frac{10\text{m}}{5\text{m}} \right) = 40\mu\text{A/V}^2$$

$$N_0: I_{D,0}(\text{SAT}) = \frac{k_0}{2}(V_{GS} - V_T)^2$$

$$I_{D,0}(\text{SAT}) = 100\mu\text{A} (V_{GS} - 1)^2$$

$V_{GS}$	$I_D(\text{mA})$
1	0
2	0.1
3	0.4
4	0.9
5	1.6

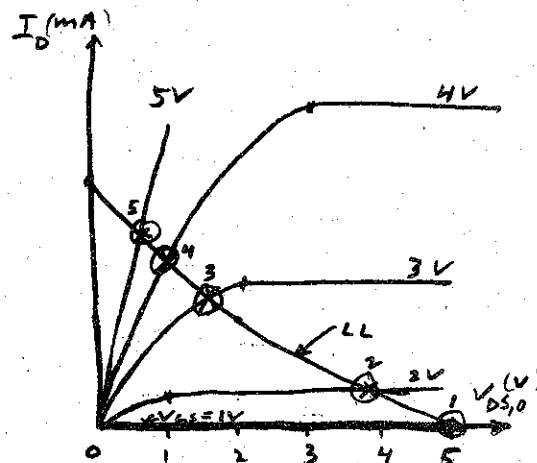

$$N_L: I_{D,L}(\text{LIN}) = k_L / ((V_{GS} - V_T) V_{DS,L} - V_{DS,L}^2/2)$$

$$I_{D,L}(\text{LIN}) = k_L / ((V_{GS} - V_{DS,0} - V_T)(V_{DD} - V_{DS,0}) - (V_{DD} - V_{DS,0})^2/2)$$


$$= 40\mu\text{A} \left[ (7-1-V_{DS,0})(5-V_{DS,0}) - \left( \frac{5-V_{DS,0}}{2} \right)^2 \right] V_{DS,0} = 5$$

$$= 40\mu\text{A} \left[ (6-V_{DS,0})(5-V_{DS,0}) - \left( \frac{5-V_{DS,0}}{2} \right)^2 \right]$$

$V_{DS,0}$	$I_{D,L}(\text{mA})$
5	0

$$0: 40\mu\text{A} \left[ 30 - \frac{25}{2} \right] = 0.7$$
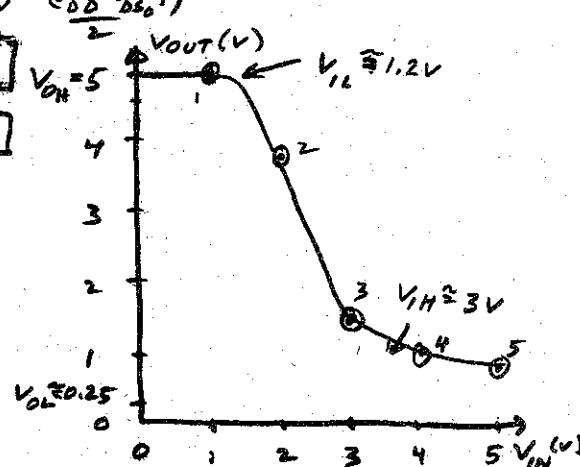
$$2: 0.04 \left( 4(3) - \frac{25}{2} \right) = 0.3$$



CHAPTER 21 SOLUTIONS

21.1

STATES OF THE MOSFETS  $N_D$  AND  $N_L$

CRITICAL OUTPUT LOAD  
POINT  $N_D$   $N_L$

$V_{OH}$	CUTOFF	LINEAR
$V_{IL}$	SAT	LIN
$V_M$	SAT	SAT
$V_{IH}$	LIN	SAT
$V_{OL}$	LIN	SAT

21.2 GRAPHICAL DETERMINATION OF CRITICAL POINTS

$$k_0 = k' \left( \frac{w}{L} \right)_0 = 20\mu \left( \frac{20m}{5m} \right) = 80 \mu A/V^2$$

$$k_L = k' \left( \frac{w}{L} \right)_L = 20\mu \left( \frac{10m}{5m} \right) = 40 \mu A/V^2$$

$N_D$ :

$$I_{D,0}(\text{SAT}) = \frac{80\mu}{2} (V_{GS}-1)^2$$

$V_{GS}(V)$  |  $I_{D,0}(\text{mA})$

1	0
2	.040
3	.160
4	.360
5	0.64


$N_L$ :

$$I_{D,L} = \frac{k_L}{2} (V_{GS,L} - V_{T,L})^2 = \frac{k_L}{2} V_{T,L}^2$$

$$= \frac{0.04}{2} (-3)^2 = 0.18 \text{ mA}$$


$$V_{NMH} = 5 - 3.5 = 1.5V$$

$$V_{NML} = 2.5 - 0.4 = 2.1V$$

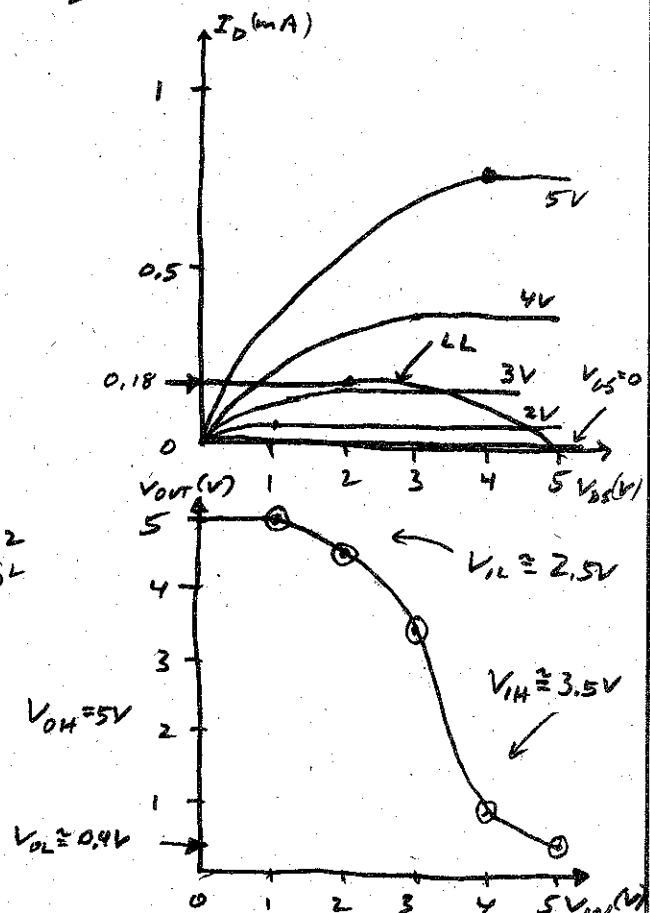


## CHAPTER 22 SOLUTIONS

22.1

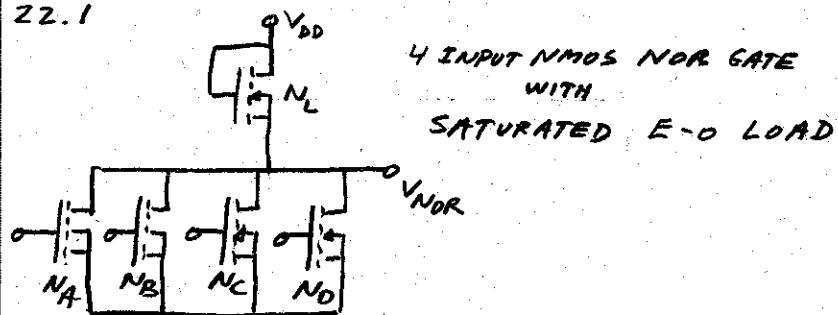

4 INPUT NMOS NOR GATE  
WITH  
SATURATED E-O LOAD

22.2

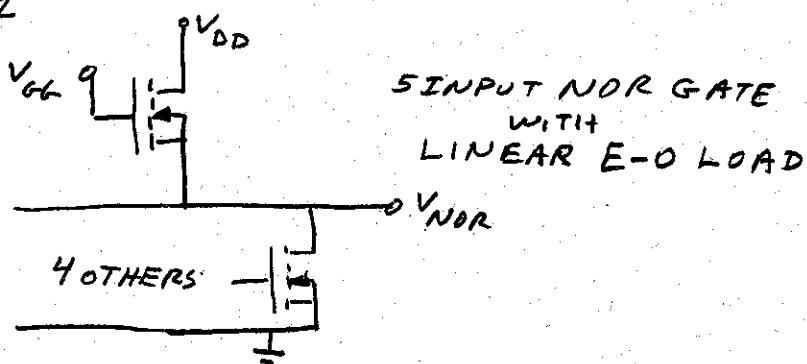

5 INPUT NMOS NOR GATE  
WITH  
LINEAR E-O LOAD

22.3 3 INPUT NOR GATE  
WITH E-D LOAD

FOR ONE INPUT HIGH

$$V_{OL}(\text{E-D LOADED}) = \frac{k_L V_T^2}{2k_o(V_{DD} - V_{TO})}$$


$$V_{OL} = \frac{k(w_L)_L V_T^2}{2k'(w_L)_o(V_{DD} - V_{TO})}$$

$$0.08 = \frac{(w_L)_L (-1)^2}{2(w_L)_o (5-1)}$$

$$\therefore \frac{(w_L)_L}{(w_L)_o} = (0.08)(8) = 0.64$$

$$\text{LET } L = 2\mu\text{m}, \text{ THEN } \frac{w_L}{w_o} = 0.64$$
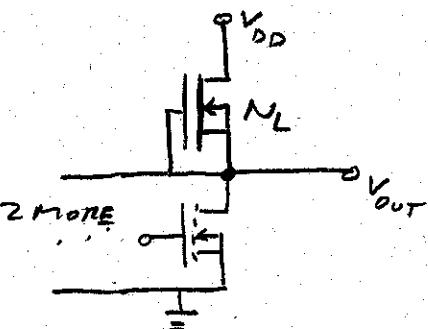
$$\text{THEN LET } w_o = 10\mu\text{m} \text{ AND } w_L = 6.4\mu\text{m}$$



CHAPTER 22 (CONT)

22.37

$$\overline{A \oplus B + C}$$

22.38

C IS AN ENABLE TERMINAL

$$\text{FOR } C = 0, V_{\text{OUT}} = \overline{A+B}$$

$$\text{FOR } C = 1, V_{\text{OUT}} = \overline{B}$$

22.39

$$F = \overline{A(B+C) + (D+E)F}$$


22.40

$$F = \overline{(A+B)(C+D+E)} + FG$$

22.41 SIMPLY REDRAW CIRCUIT

22.42 SIMPLY REDRAW CIRCUIT

22.43

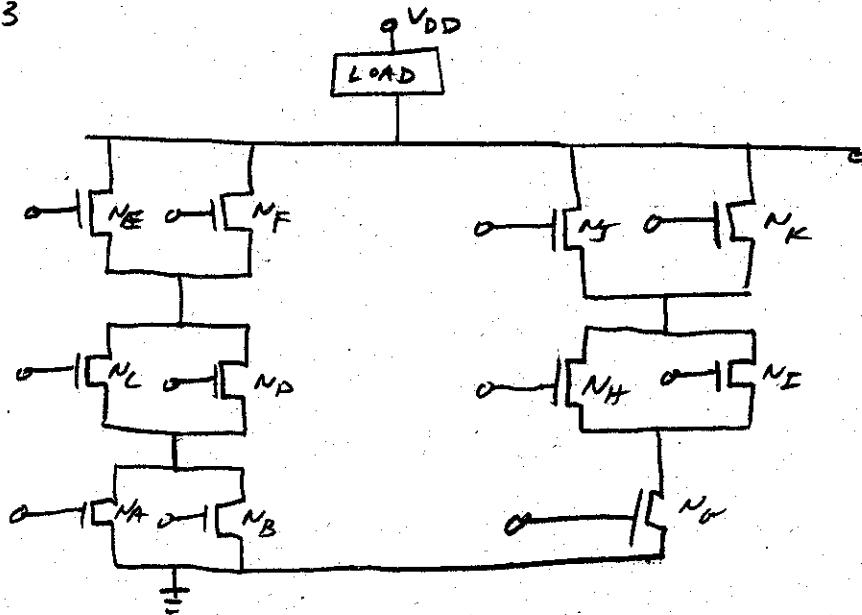

CHAPTER 23 (CONT)

23.3 (CONT)

$$3V_{IH}^2 - 6V_{IH} - 3V_{IH} + 6 - 2\left(\frac{9}{16}V_{IH}^2 - \frac{9}{4}V_{IH} + \frac{9}{4}\right) = 16 - 8V_{IH} + V_{IH}^2$$

$$V_{IH}^2(3 - \frac{9}{8} - 1) + V_{IH}(-6 - 3 + \frac{9}{2} + 8) + (6 - \frac{9}{2} - 16) = 0$$

$$V_{IH}^2(0.875) + V_{IH}(3.5) - 14.5 = 0$$

$$V_{IH}^2 + 0.4V_{IH} - 16.6 = 0$$

$$\therefore V_{IH} = \frac{-0.4}{2} + \frac{\sqrt{(0.4)^2 + 4(16.6)}}{2} = -2 + 4.54 = 2.54V$$

$V_M$ :

$$\begin{aligned} V_M &= [V_{DD} + V_{TP} + V_{TN} \sqrt{\frac{K_N}{K_P}}] / [1 + \sqrt{\frac{K_N}{K_P}}] \\ &= [5 + (-1) + 1 \sqrt{\frac{100}{50}}] / [1 + \sqrt{\frac{100}{50}}] = \frac{5.4142}{2.416} \\ &= 2.24V \end{aligned}$$

$$V_{NMN} = V_{OH} - V_{IH} = 5 - 2.54 = 2.46V$$

$$V_{NMZ} = V_{IL} - V_{OL} = 1.79 - 0 = 1.79V$$

23.4 GRAPHICAL DETERMINATION OF CRITICAL VOLTAGES

$$V_{DD} = 10V$$

$$I_{D,N}(\text{SAT}) = 50\mu(V_{IN} - 1)^2 \quad \text{UNCHANGED FROM PROBLEM } 23.2$$

$$I_{D,P}(\text{SAT}) = \frac{50}{2} (V_{AS,P} + V_T)^2 = 25\mu(10 - V_{IN} - 1)^2$$



$$I_{D,A}(\text{SAT}) = 25\mu(9 - V_{IN})^2$$

$V_{IN}$	$I_{D,N}^{(\text{SAT})}$	$V_{IN}$	$I_{D,P}(\text{SAT}) \text{ mA}$	$V_{SGP} = (10 - V_{IN})$
1	0	1	1.6	9
2	0.05	2	1.225	8
4	0.45	4	0.625	6
6	0.8	6	0.225	4
8	2.45	8	0.025	2
10	4.05	9	0	$1 - V_T$

IV CHARACTERISTICS  
ON NEXT PAGE

CHAPTER 23 (CONT)

23.4 (CONT)

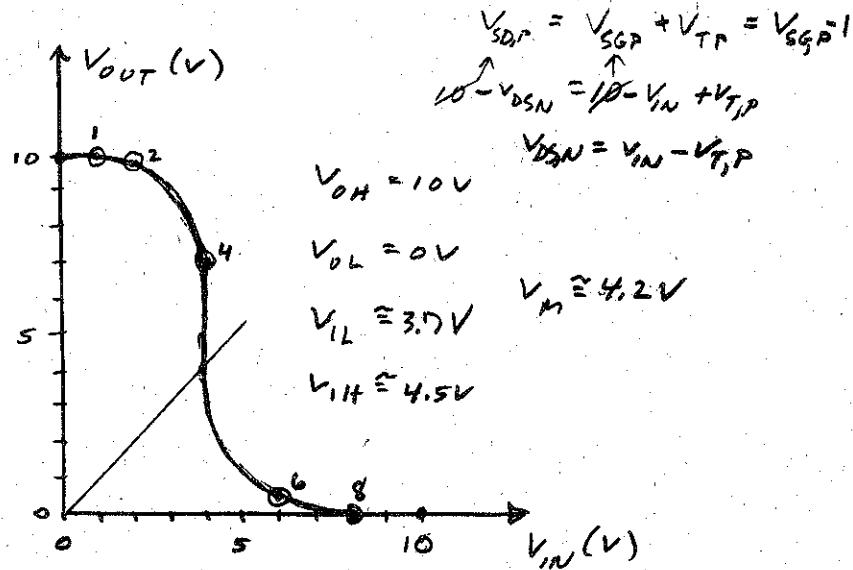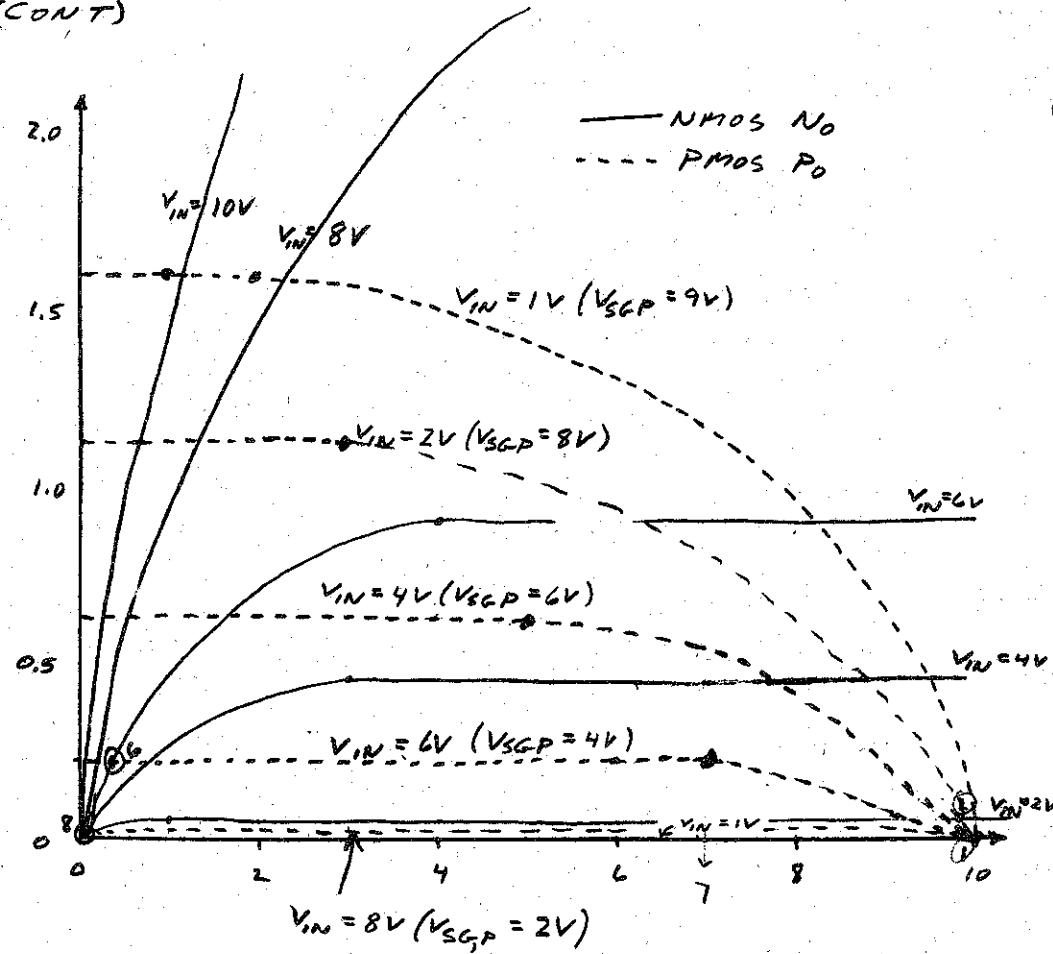

CHAPTER 24 (CONT)

24.11 BY INSPECTION OF THE CIRCUIT

$$F = \overline{AB} + \overline{A}\overline{B} = (\overline{A}+B)(A+\overline{B}) = \overline{A}\overline{B} + AB \quad XNOR$$

24.12 XOR

24.13 THE RELATION FOR W/L RATIOS FOR CMOS NAND GATES WITH  $m$  INPUTS, IS

$$\frac{2.5}{2} \left( \frac{W}{L} \right)_N = \left( \frac{W}{L} \right)_P$$

THUS, FOR A 2 INPUT NAND gate

$$\frac{2.5}{2} \left( \frac{W}{L} \right)_N = \left( \frac{W}{L} \right)_P$$

CASE A: CHOOSE MINIMUM SIZE NMOSFETs

$$\left( \frac{W}{L} \right)_N = \frac{4m}{2\mu m}$$

AND THUS

$$\left( \frac{W}{L} \right)_P = \frac{4m}{2\mu m} \left( \frac{2.5}{2} \right) = \frac{5m}{2\mu m}$$

FOR THIS CASE THE CHIP AREA FOR THE 4 TRANSISTORS IS

$$\text{AREA} = 2(A_N + A_P) = 2(4 \times 2 + 5 \times 2) = 36 \mu m^2$$

CASE B CHOOSE MINIMUM SIZE PMOSFETs

$$\left( \frac{W}{L} \right)_P = \frac{4m}{2\mu m}$$

THUS,

$$\left( \frac{W}{L} \right)_N = \left( \frac{4}{2} \right) \left( \frac{2}{2.5} \right) = \frac{4m}{2.5\mu m} = \frac{3.2m}{2\mu m}$$

AND

$$\text{AREA} = 2(4 \times 2 + 3.2 \times 2) = 28.8 \mu m^2$$

CHAPTER 25 SOLUTIONS  
(CONT'D)

25.6)

$V_{IN}$	N	P	PULL-UP PATH	PULL-DOWN PATH	$V_{OUT}$
1. LOW	OFF	ON	YES	NO	HIGH
2. HIGH	ON	OFF	NO	YES	LOW
3. Z	?	?	NO	NO	Z
4. X	?	?	YES	YES	X

25.7) EQUATE THE LINEAR DRAIN CURRENTS FOR THE N- AND P- CHANNEL MOSFETS:

$$I_{D,N} (lin) = I_{D,P} (lin)$$

$$k_N [(V_{GS,N} - V_{TN}) V_{GS,N} - \frac{V_{DS,N}^2}{2}] = k_P [(V_{GS,P} + V_{TN}) V_{GS,P} - \frac{V_{DS,P}^2}{2}]$$

SUBSTITUTE:

$$V_{GS,N} = V_{IN,N} = V_{in} = 5V$$

$$V_{GS,P} = V_{DD} - V_{IN,P} = V_{DD} - V_{in} = 5V$$

$$V_{DS,N} = V_{out}$$

$$V_{DS,P} = V_{DD} - V_{out}$$

$$80\mu \left[ (5-1) V_{out} - \frac{V_{out}^2}{2} \right] = 80\mu \left[ (5+(-1))(5-V_{out}) - \frac{(5-V_{out})^2}{2} \right]$$

$$\underline{4V_{out} - \frac{V_{out}^2}{2}} = 20 - 4V_{out} - \frac{25}{2} + 5V_{out} - \frac{V_{out}^2}{2} \rightarrow 3V_{out} = 20 - \frac{25}{2} = 7.5$$

COLLECT LIKE TERMS AND SOLVE FOR  $V_{out}$ :


$$V_{out} = 2.5V = V_x$$

25.8	$V_A$	$V_B = V_C$	$V_{out}$
LOW	LOW	$V_{DD}$	
LOW	HIGH	LOW	
HIGH	LOW	LOW	
HIGH	HIGH	LOW	

25.9	$V_{IN}$	$V_{PEN}$	$V_{NEN}$	$V_{TINV}$
LOW	LOW	LOW	HIGH	
LOW	LOW	HIGH	HIGH	
LOW	HIGH	LOW	X	
LOW	HIGH	HIGH	X	
HIGH	LOW	LOW	X	
HIGH	LOW	HIGH	LOW	
HIGH	HIGH	LOW	X	
HIGH	HIGH	HIGH	LOW	

CHAPTER 15 (CONT)

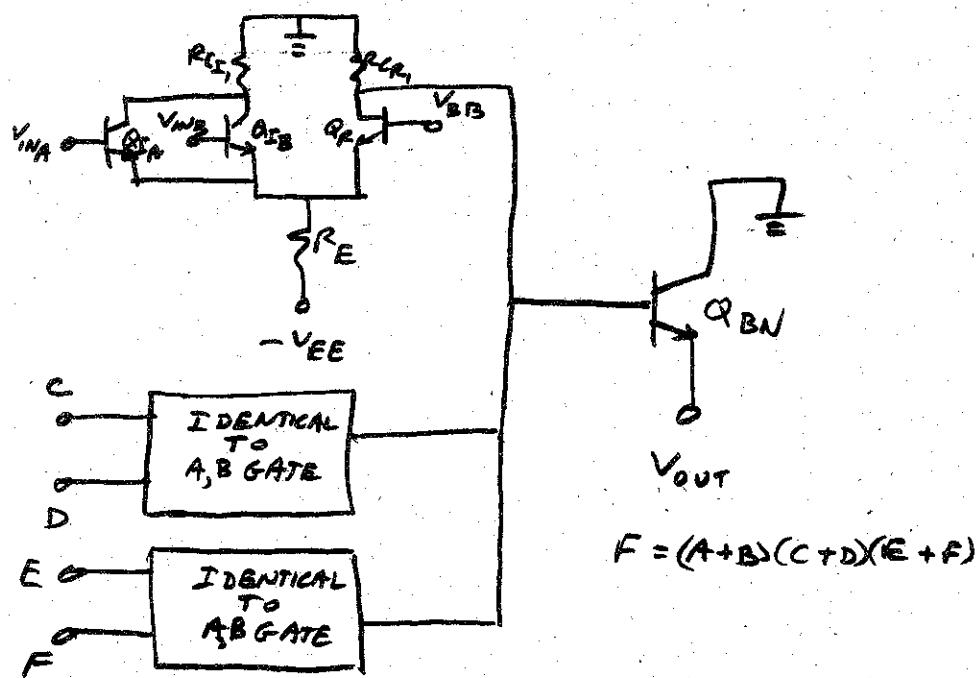15.11 REALIZE THE LOGIC FUNCTION  $F = (A+B)(C+D)(E+F)$



$$F = (A+B)(C+D)(E+F)$$

15.12 TO OBTAIN THE INVERSE OF F, FROM

PROBLEM 15.11,  $F = \overline{(A+B)(C+D)(E+F)}$

USE SAME CIRCUIT AS PROBLEM 15.11  
EXCEPT COLLECTOR DOTTING OF INPUT  
TRANSISTOR COLLECTORS WITH OUTPUT  
BUFFER BJT  $Q_{BINV}$ .

15.13

A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0

15.14

A	B	XNOR
0	0	1
0	1	0
1	0	0
1	1	1

CHAPTER 26 SOLUTIONS (CONT.)

26.10 TWICE THE DRIVE STRENGTH IMPLIES THAT THE W/L RATIOS OF THE DEVICES IN THE STACK SHOULD BE DOUBLED. THUS,

$$\frac{W_{N0}}{L_{N0}} = \frac{W_{N2}}{L_{N2}} = 2 \left( \frac{8 \mu m}{2 \mu m} \right) = 8$$

AND

$$\frac{W_{P0}}{L_{P0}} = \frac{W_{P2}}{L_{P2}} = 2 \left( \frac{20 \mu m}{2 \mu m} \right) = 20$$

HENCE

$$R_{NI} = k_{NO} = k'_{N2} \frac{W_{N2}}{L_{N2}} = 40 \mu A/V^2 = 320 \mu A/V^2$$

$$R_{PI} = k_{PO} = k'_{P2} \frac{W_{P2}}{L_{P2}} = 16 \mu A/V^2 = 320 \mu A/V^2$$

ALSO

$$\frac{W_{NF}}{L_{NF}} = \left[ \frac{V_{ID} - V_{TN}}{V_{DD} - V_{ID}} \right]^2 \frac{W_{NE}}{L_{NE}} = \left[ \frac{4-1}{5-4} \right]^2 8 = 72$$

$$\frac{W_{PF}}{L_{PF}} = \left[ \frac{V_{SD} + V_{TP} - V_{IU}}{V_{IU}} \right]^2 \frac{W_{PE}}{L_{PE}} = \left[ \frac{5-1-1}{1} \right]^2 20 = 180$$

26.11 USING THE Eqs. OF THE PREVIOUS PROBLEM. (26.10)

$$\frac{W_{N0}}{L_{N0}} = \frac{W_{N2}}{L_{N2}} = 2 \left( \frac{8 \mu m}{2 \mu m} \right) = 8 \text{ AND } \frac{W_{P0}}{L_{P0}} = \frac{W_{P2}}{L_{P2}} = 2 \left( \frac{20 \mu m}{2 \mu m} \right) = 20$$

$$\frac{W_{NF}}{L_{NF}} = \left[ \frac{4-1}{7-4} \right]^2 8 = 8$$

$$\frac{W_{PF}}{L_{PF}} = \left[ \frac{7-1-1}{1} \right]^2 20 = 25 (20) = 500$$

26.12 USING THE Eqs. OF THE PREVIOUS PROBLEMS

SAME RESULTS FOR  $N_0, P_0, N_2, P_2$ . THEN

$$\frac{W_{NF}}{L_{NF}} = \left[ \frac{4-1}{10-4} \right]^2 8 = \left[ \frac{1}{4} \right] 8 = 2$$

$$\frac{W_{PF}}{L_{PF}} = \left[ \frac{10-1-1}{1} \right]^2 20 = 64 (20) = 1280$$

## CHAPTER 27 (CONT)

### 27.4 (CONT)

For the third stage:

$$k_{N_3} = k_{P_3} = k'_N (W/L)_{N_3} = 40\mu (120/2) = 2.4 \text{ mA/V}^2$$

$$C_{L3} = [(W/L)_{N_4} + (W/L)_{P_4}] C_o = [1750 \times 2 + 700 \times 2] 690 \text{ a}$$

$$= (3500 + 1400) 690 = 3.38 \text{ pF}$$

$$\tau_{P_3} = A C_{L3} / k_{P_3} = \frac{0.322 \times 3.38 \text{ p}}{2.4 \text{ m}} = 0.45 \text{ ms}$$

For the Fourth Stage:

$$k_{N_4} = k_{P_4} = (40\mu)(700/2) = 14 \text{ mA/V}^2$$

$$C_{L4} = C_L = 5 \text{ pF}$$

$$\tau_{P_4} = \frac{0.322 (5 \text{ p})}{14 \text{ m}} = 0.115 \text{ ms}$$

$$\tau_{P_{\text{TOTAL}}} = 0.39 + 0.47 + 0.45 + 0.115 = 1.425 \text{ ms}$$

27.5 ALL  $k_N$  and  $k_P \times \frac{1000}{690}$  and ALL  $C_{in} \times \frac{1000}{690}$

$\therefore$  ALL  $\tau$  unchanged except  $\tau_y$

27.6 Transconductance Parameters doubled

From Problem 27.4:

$$A = B = 0.322 \text{ V}, k_P = 160 \mu \text{A/V}^2, C_L = 96.6 \text{ fF}$$

$$\tau_{P_1} = \frac{0.322 (96.6 \text{ fF})}{160 \mu} = \frac{0.39}{2} = 0.195 \text{ ms}$$

For the second stage

$$\tau_{P_2} = A C_{L2} / k_{P_2} = 0.47 / 2 = 0.235 \text{ ms}$$

For the 3rd stage

$$\tau_{P_3} = A C_{L3} / k_{P_3} = 0.45 / 2 = 0.225 \text{ ms}$$

For the 4th stage  $\tau_{P_4} = \frac{0.115}{2} = 0.0575 \text{ ms}$

$$\therefore \tau_{\text{TOTAL}} = 0.7125 \text{ ms}$$

CHAPTER 34 (CONT)

PRODUCED DUE TO THE LARGE GATE CURRENT,  
THE FANOUT AND RELIABILITY OF THE GATE  
ALSO BECOME UNACCEPTABLE.

34.6

$$\begin{aligned} a &= 0.1 \mu\text{m} \\ W &= 0.6 \mu\text{m} \\ L &= 3.0 \mu\text{m} \end{aligned}$$

$B'$  = PROCESS TRANSCONDUCTANCE  
 $B$  = DEVICE TRANSCONDUCTANCE

$$B' = \frac{UN\epsilon_{\text{GaAs}}}{2a} = 8600 \frac{\text{cm}^2}{\text{V}\cdot\text{s}} \times 1.16 \times 10^{-12} \text{ F/cm} \\ = 2 \times 10^{-5} \text{ cm}^{-5}$$

$$\therefore B' = 498.8 \mu\text{A/V}^2 \approx 500 \mu\text{A/V}^2$$

$$B = B' \cdot W/L = 498.8 \times \frac{0.6}{3.0} = 99.76 \mu\text{A/V}^2$$

$$\therefore B = 99.76 \mu\text{A/V}^2 \approx 100 \mu\text{A/V}^2$$

34.7

$$V_p = \frac{qN_D a^2}{2\epsilon_{\text{GaAs}}} \quad N_D = 10^{17}/\text{cm}^3$$

$$= \frac{1.6 \times 10^{-19} \times 10^{17} \times 10^{-5}}{2 \times 1.16 \times 10^{-12}}$$

$$V_p = 0.69 \text{ V}$$

$$\begin{aligned} V_T &= V_{bi} - V_p \\ &= 0.8 - 0.69 \\ &= 0.11 \text{ V} \end{aligned}$$

$$V_T = 0.11 \text{ V}$$

CHAPTER 35 (CONT)

35.7

a)  $V_{OH} = V_{SBOD, GaAs} (ON) = 0.8V$

$V_{OH} = 0.8V$

1/2

$$V_{IL} = V_{T,0} + |V_{T,L}| \left[ \frac{\beta_L [1 + \lambda_L (V_{DD} - V_{SBOD, GaAs})]}{\beta_0 (1 + \lambda_0 V_{SBOD, GaAs})} \tanh \lambda_L (V_{DD} - V_{SBOD, GaAs}) \right]$$

$$= 0.2 + |-1| \left[ \frac{1}{10} \frac{\tanh^2(0.2)}{\tanh^2(0.8)} \right]^{1/2} = 0.2 + 0.2$$

$V_{IL} = 0.4V$

$$V_{OL} = \frac{1}{\alpha_0} \cdot \frac{\beta_L}{\beta_0} \cdot \frac{V_{T,L}^2}{(V_{OH} - V_{T,0})^2} \cdot (1 + \lambda_L \cdot V_{DD}) = \frac{1}{2} \frac{1}{10} \frac{(-1)^2}{(0.8 - 0.2)^2}$$

$V_{OL} = 0.139V = 0.14V$

FOR DETERMINATION OF  $V_{IH}$ , NUMERICAL SOLUTION OF TWO EQUATIONS, AS IN PROBLEM 35.2, IS REQUIRED. STARTING WITH A GUESS VALUE FOR EACH OF  $V_{IN}$  i.e.  $V_{IH}$  AND  $V_{OUT}$ , SOLUTION CAN BE WORKED OUT ON MATHCAD.

$V_{OUT} = 0.22V$

$V_{IH} = 0.69V$  SEE NEXT PAGE FOR DETAILS

$V_{NMH} = V_{OH} - V_{IH} = 0.11V$

$V_{NML} = V_{IL} - V_{OL} = 0.26V$

b) DIRECT SUBSTITUTION INTO THE EXPRESSIONS AS IN 35.5 GIVES

$$I_{DD(OH)} = \frac{88.535}{100} \mu A \leftarrow \frac{\beta_L V_{T,L}^2 (1 + \lambda_L (V_{DD} - V_{OH})) \tanh \lambda_L (V_{DD} - V_{OH})}{(-1)^2 (1 + \lambda_0 (0.7)) \tanh^2(0.7)}$$

$$I_{DD(OL)} = 99.14 \mu A \leftarrow 100 (-1)^2 \tanh^2(1.5 - 0.14)$$

$$P_{DD} = \frac{(88.535 + 99.14) \cdot (1.5)}{2}$$

$P_{DD} = 140.8 \text{ mW}$


CHAPTER 35 (CONT)

35.7

Determination of  $V_{IH}$

$$(1) V_{IH} = 0.2 + \frac{1}{10 \tanh 2V_{out}}$$
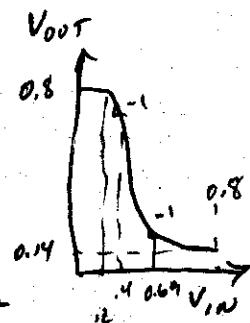
$$(2) V_{IH} = 0.2 + \cosh^2 2V_{out} \tanh 2V_{out}$$



Equate

$$0.316 = \frac{1}{\sqrt{10}} = \cosh^2 2V_{out} \tanh^{3/2} 2V_{out}$$

choose  
 $2V_{out}$

calculate

$$\cosh^2(2V_{out}) (\tanh^{3/2}(2V_{out})) =$$

0.22

$$(1.0492)(1.007) = 0.1$$

0.4

$$(1.169)(0.234) = 0.274$$

0.38

$$(1.151)(0.218) = 0.25$$

0.5

$$(1.271)(0.314) = 0.4$$

0.45

$$(1.217)(0.274) = 0.33$$

0.44

$$(1.21)(0.266) = 0.32$$

$$1.2V_{out} \approx 0.44V \rightarrow V_{out} = 0.22$$

$$V_{IH} = 0.2 + \cosh^2(0.44) \tanh(0.44)$$

$$= 0.2 + \underbrace{(1.206)(0.91)}_{0.49}$$

$$= \underline{\underline{0.69V}}$$

as a check

$$V_{IH} = 0.2 + \frac{1}{\sqrt{10} \tanh 0.44} = 0.2 + .49 = 0.69$$

c) MAXIMUM FANOUTMAXIMUM FANOUT IS OBTAINED FOR  $V_{OUT} = V_{IH}$ 

$$I_{D,L} = \beta_L V_{T,L}^2 \cdot \tanh(\alpha_L(V_{DD} - V_{IH})) (1 + \gamma_L(V_{DD} - V_{IH}))$$

$$= 92.34 \text{ mA}$$

$$I_{G'_o(IH)} = I_{SBD} \cdot \exp\left[\frac{V_{IH}}{0.026}\right] = (10^{-12} \text{ mA}) \left(\exp\left[\frac{0.69}{0.026}\right]\right)$$

$$= 0.335 \text{ mA}$$

$$N = \frac{I_{D,L}}{I_{G'_o(IH)}} = 275.64$$

$N_{MAX} = 275$

FANOUT FOR  $N_{MH} = 0.1 \text{ V}$ 

$$V_{OUT} = V_{IH} + N_{MH}$$

$$V_{OUT} = 0.79$$

$$I_{D,L}(V_{OUT}=0.79) = \beta_L \cdot V_{T,L}^2 \cdot \tanh[\alpha_L(V_{DD}-V_{OUT})(1+\gamma_L(V_{DD}-V_{OUT}))]$$

$$= 88.809 \text{ mA}$$

$$I_{G'_o(V_{OUT}=0.794)} = (I_{SBD}) \cdot \exp\left(\frac{V_{OUT}}{0.026}\right)$$

$$= 15.6 \text{ mA}$$

$$N = I_{D,L} / I_{G'_o}$$

$$= 5.69$$

$N = 5$

CHAPTER 36 (CONT)


$$V_{IH} = 1.4 + (0.32) \tanh^{-1/2} (0.426)$$

$$= 1.4 + 0.5$$

$$\boxed{V_{IH} = 1.9 V}$$

$$V_{NML} = V_{IL} - V_{OL} = 1.4 - 0.05 = 1.35 V$$
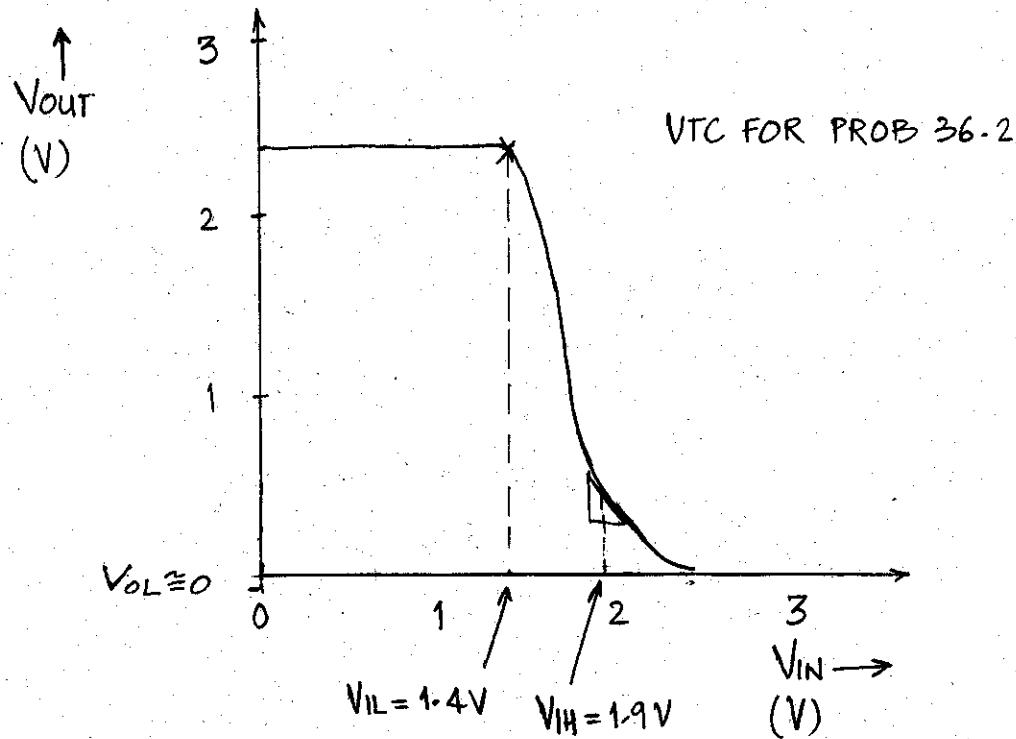
$$V_{NMH} = V_{OH} - V_{IH} = 2.4 - 1.9 = 0.5 V$$



36.3.

AVERAGE POWER DISSIPATION

$$P_{DISS} = I_{DD} \cdot V_{DD} + I_{SS} \cdot V_{SS}$$

$$\text{WHERE } I_{DD} = \frac{I_{DD(OH)} + I_{DD(OL)}}{2}$$

$$I_{SS} = \frac{I_{SS(OH)} + I_{SS(OL)}}{2}$$

## CHAPTER 36 (CONT)

36.3 (CONT)

$$I_{DD}(OL) = I_{DCE}(OL) = \beta_L V_{T,L}^2 (1 + \gamma_L (V_{DD} - V_{OL}))$$

$$= \left(\frac{100}{10}\right)(-1)^2 (1 + 0.2(3 - 0.05))$$

$$= 10 (1 + 0.59) = \underline{15.9 \mu A}$$

$$I_{DD}(OH) = \beta_L V_{T,L}^2 (1 + \gamma_L V_{DS,L}) \tanh \alpha_L V_{DS,L}$$

$$= \left(\frac{100}{10}\right)(-1)^2 (1 + 0.2(3 - 2.4)) \tanh \underbrace{2}_{0.83}^{\frac{1.2}{(3 - 2.4)}}$$

$$= 10 (1 + 0.12)(0.83)$$

$$= \underline{9.3 \mu A}$$

$$I_{SS}(OL) = \beta_D V_{T,D}^2 (1 + \gamma_D (V_{OL} - 3V_{SDL}^{(ON)} + V_{SS}))$$

$$= 100 (-1)^2 (1 + 0.2(2.4 - 2.4 - (-3)))$$

$$= 100 (1 + 0.6) = \underline{160 \mu A}$$

$$I_{SS}(OH) = \beta_D V_{T,L}^2 (1 + \gamma_D (V_{OL} - 3V_{SDL}^{(ON)} + V_{SS})) \tanh \alpha_D V_{DS,L}$$

$$= 100 (-1)^2 (1 + 0.2(0.05 - 2.4 + 3)) \tanh 2(0.65)$$

$$= 100 (1 + 0.2(0.65)) (0.86) = \underline{97.2 \mu A}$$

$$P_{DSS}(AV) = V_{DD} I_{DD} + V_{SS} I_{SS} = 3 \left( \frac{15.9 + 9.3}{2} \right) + 3 \left( \frac{160 + 97.2}{2} \right)$$

$$= 37.8 + 386 = 423.8 \mu W$$

$$= 0.42 mW$$

## CHAPTER 37 (CONT)

$$37.4 \quad V_{OH} = V_{DD} - 3V_{SBD, GaAs(ON)} = 0.6V$$

a)

$$V_{IL} = V_{T,O} = -1.5V$$

$$V_{OL} = -3V_{SBD, GaAs(ON)} = -2.4V$$

THE FOLLOWING EXPRESSIONS ARE NUMERICALLY SOLVED FOR  $V_{IH}$ 

$$B_L \cdot V_{T,L}^2 \cdot \tanh \alpha_L \cdot V_{DS,L} \cong B_0 (V_{IN} - V_{T,O})^2 \cdot \tanh \alpha_O \cdot V_{DS,O} + \beta_C \cdot V_{T,C}^2 - \beta_F (V_{GS,F} - V_{T,F})^2$$

AND

$$\frac{\alpha_L \cdot V_{T,L}^2}{\cosh^2 \alpha_L \cdot V_{DS,L}} + \frac{(\beta_0/B_L) \alpha_L \cdot (V_{IN} - V_{T,O})^2}{\cosh^2 \alpha_O \cdot V_{DS,O}} = 2 \frac{B_0 (V_{IN} - V_{T,O}) \tanh \alpha_O \cdot V_{DS,O}}{B_L}$$

$$\text{WHERE } V_{DS,L} = V_{DD} - [V_{OUT} + 3V_{SBD, GaAs(ON)}]$$

$$V_{DS,O} = V_{OUT} + 3V_{SBD, GaAs(ON)}$$

WE GET,

$$V_{OUT} = -1.95V \quad \text{AND} \quad V_{IH} = -0.05V \quad \text{SEE NEXT PAGE}$$

AND,

$$V_{NMH} = V_{OH} - V_{IH} \quad \text{AND} \quad V_{NML} = V_{IL} - V_{OL}$$

$$V_{NMH} = 0.65V \quad V_{NML} = -1.5 + 2.4 = 0.9V$$

$$b) \quad I_{SS(OL)} = \frac{\beta_C \cdot V_{T,C}^2}{2} \left[ 1 + \lambda_C (V_{OL} + V_{SS}) \right] \cdot \tanh \left[ \alpha_C (V_{OL} + V_{SS}) \right] \\ = 187.6 \mu A$$

$$I_{SS(OH)} = \frac{\beta_C \cdot V_{T,C}^2}{2} \left[ 1 + \lambda_C^0 (V_{OH} + V_{SS}) \right] \cdot \tanh \left[ \alpha_C^0 (V_{OH} + V_{SS}) \right] \\ = 225 \mu A$$

$$I_{SS} = (I_{SS(OL)} + I_{SS(OH)})/2 = 206.3 \mu A$$

$$I_{DD(OL)} = I_{D,L(OL)} + I_{D,F(OL)} \\ = B_L \cdot V_{T,L}^2 \left( 1 + \lambda_L \cdot V_{DD} \right) \cdot \tanh \alpha_L \cdot V_{DD} + \beta_F (V_{GS,F} - V_{T,F})^2 \\ \{ 1 + \lambda_F \cdot V_1 \} \cdot \tanh \alpha_F \cdot V_1 \quad \text{WHERE } V_1 = V_{DD} + V_{SBD, GaAs(ON)} \\ = 377 \mu A$$

$$I_{DD(OH)} = I_{SS(OH)} = 225 \mu A$$

$$I_{DD} = (I_{DD(OL)} + I_{DD(OH)})/2 = 301 \mu A$$

$$P_{DISS} = V_{DD} \cdot I_{DD} + V_{SS} \cdot I_{SS} = 1.522 \text{ mW}$$

CHAPTER 37 (CONT)

37.4 (CONT)

V<sub>IN</sub>: 2 EQUATIONS

$$(1) \frac{50(-1.5)^2 \tanh^2(0.6 - V_{out})}{\cosh^2(\frac{V_{out} + 2.4}{0.6 - V_{out}})} = \frac{100(V_{in} + 1.5)^2 \tanh^2(V_{out} + 2.4)}{\cosh^2(V_{out} + 2.4)} + 100(1.5)^2 - 50(0.8 + 1.5)^2$$

$$(-1.5)^2 = 2(V_{in} + 1.5)^2 \tanh^2 \underbrace{z(V_{out} + 2.4)}_x + 2(2.25) - (2.3)^2$$

$$2.25 - 4.5 + 5.25 = 2(V_{in} + 1.5)^2 \tanh^2(x)$$

$$3 = 2(V_{in} + 1.5)^2 \tanh^2(x)$$

$$(1) V_{in} + 1.5 = \sqrt{\frac{3}{2} \frac{1}{\tanh^2(x)}} = \frac{1.225}{\tanh^{1/2}(x)}$$

$$(2) \frac{z(-1.5)^2}{\cosh^2(\frac{V_{out} + 2.4}{0.6 - V_{out}})} + \frac{(100)(2(V_{in} + 1.5)^2)}{\cosh^2(V_{out} + 2.4)} = z \left( \frac{100}{50} \right) (V_{out} + 2.4) \tanh(x)$$

$$\stackrel{z=0}{=} 0$$

$$(2) V_{in} + 1.5 = \cosh^2 x \tanh x$$

$$\text{where } x = z(V_{out} + 2.4)$$

Equate (1) & (2)

$$\frac{1.225}{\tanh^{1/2} x} = \cosh^2 x \tanh x$$

$$\text{or } 1.225 = \cosh^2 x \tanh^{3/2} x$$

choose x	calculate $\cosh^2 x \tanh^{3/2} x$
1	$2.381 \times 0.665 = 1.58$
0.85	$1.714 \times 0.574 = 1.1$
0.9	$2.054 \times 0.6 = 1.25$ close enough


$$\therefore x = 0.9 \approx z(V_{out} + 2.4) \rightarrow V_{out} = -1.95V$$

Back substitution

$$V_{in} + 1.5 = \frac{1.225}{\tanh^{1/2}(0.9)} \rightarrow V_{in} = -1.5 + 1.45 = -0.05V$$

37.4

## CHAPTER 37 (CONT)

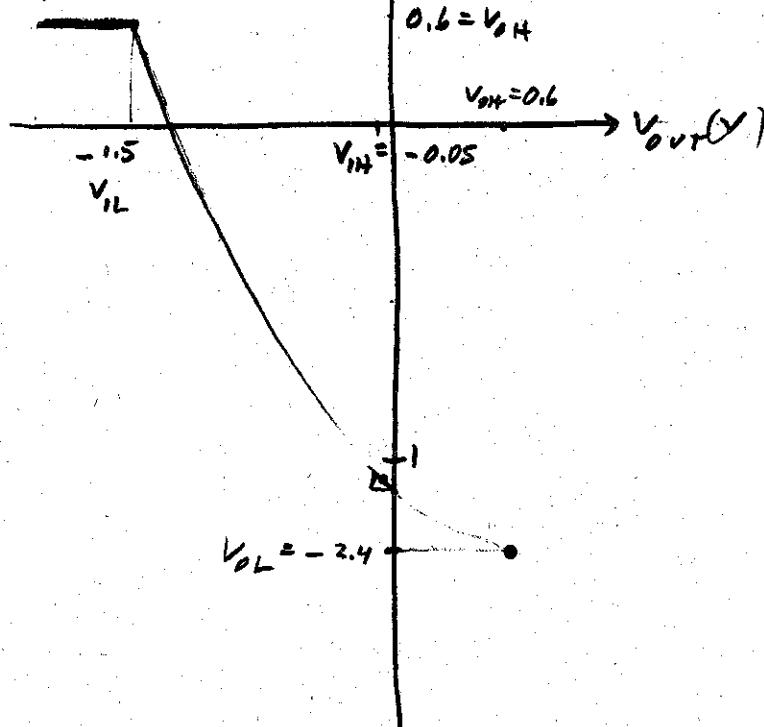

$$37.5 \quad V_{OH} = V_{DD} - 3V_{SBD, GaAs(ON)} = 0.6V$$

$$V_{IL} = V_{T_{D0}} = -1.5V$$

$$V_{OL} = -3V_{SBD, GaAs(ON)} = -2.4V$$

THE Eqs TO SOLVE ARE:

$$\beta_L V_{T,L}^2 \tanh \alpha_L V_{DS,L} \approx \beta_0 (V_{IN} - V_{T,0})^2 \tanh \alpha_0 V_{DS,0} + \beta_C V_{T,C}^2 - \beta_F (V_{GS,F} - V_{T,0})^2$$

and

$$\frac{\alpha_L V_{T,L}^2}{\cosh^2 \alpha_L V_{DS,L}} + \frac{\beta_0 \alpha_L (V_{IN} - V_{T,0})^2}{\cosh^2 \alpha_0 V_{DS,0}} = 2 \frac{\beta_0}{\beta_L} (V_{IN} - V_{T,0}) \tanh \alpha_0 V_{DS,0}$$

where

$$V_{DS,L} = V_{DD} - (V_{OUT} + 3V_{SBD, GaAs(ON)})$$

and

$$V_{DS,0} = V_{OUT} + 3V_{SBD, GaAs(ON)}$$

Substituting into the Eqs YIELDS

$$500(1.5)^2(1) = 1000(V_{IN} + 1.5)^2 \tanh \alpha_0 V_{DS,0} + 100(1.5)^2 - 100(0.8 + 1.5)^2 \quad (1)$$

and

$$\frac{1000}{500} \frac{2(V_{IN} + 1.5)^2}{\cosh^2 2(V_{OUT} + 2.4)} = 2 \left(\frac{1000}{500}\right) (V_{IN} + 1.5) \tanh 2(V_{OUT} + 2.4) \quad (2)$$

## CHAPTER 39 (SOLUTIONS)

39.1 ANALYZE THE CIRCUIT TO SEE THAT

$$V_{out} = \text{HIGH FOR } V_{IN_A} = \text{HIGH OR } V_{IN_B} = \text{HIGH}$$

ALSO, When  $V_{IN_A} = V_{IN_B} = \text{HIGH}$ ,  $V_{out} = \text{High}$   
and  $V_{out} = \text{LOW FOR } V_{IN_A} = V_{IN_B} = \text{LOW}$

THIS GATE PERFORMS XOR

39.2 BY INSPECTION OF THE FIGURE, THE LOGIC  
OUTPUT IS  $\overline{(A \oplus C)(B + D)}$

$$V_{OH} = V_{DD}, V_{OL} = 2V_{OL} (\text{ONE MESFET})$$

Yes, Fig 39.9

39.3 BY INSPECTION OF THE FIGURE, THE LOGIC  
OUTPUT IS  $\overline{AB + CD}$

$$V_{OH} \approx V_{DD} - 3V_{SD}(\text{ON})$$

$$V_{OL} = 2V_{OL} (\text{ONE MESFET})$$

39.4

OUTPUT IS  $\overline{A + B}$

39.5

OUTPUT IS  $\overline{A \cdot B}$

## CHAPTER 30 SOLUTIONS (CONT)

### 30.4 a) STATIC POWER DISSIPATION

$$P_{Diss} = I_{DD} V_{DD}$$

OUTPUT HIGH STATE :  $N_D(ON) \Rightarrow I_{DD(H)} = 0$

OUTPUT LOW STATE :  $P_D(OFF) \Rightarrow I_{DD(L)} = 0$

$$\therefore I_{DD} = \frac{I_{DD(H)} + I_{DD(L)}}{2} = 0$$

$$P_{Diss} = 0$$

### b) DYNAMIC POWER DISSIPATION

$$P_{DD} = C_L V_{DD}^2 = 0.08 \times 10^{-12} \times 50 \times 10^6 \times 5^2$$

$$P_{DD} = 100 \mu W, \text{ Total Power Diss} = 100 \mu W$$


### 30.5 $V_{IN}(LOW)$ ; $N_D(ON)$ , $P_D(ON)$ , $Q_D(OFF)$ , $Q_P(SAT)$

$$V_{OUT} = V_{DD} - V_{CE,P(SAT)} = V_{OH} = 10 - 0.2 = 9.8V$$
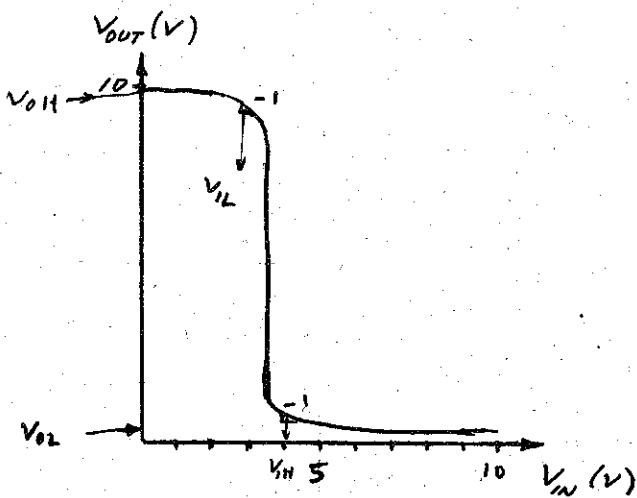
### $V_{IN}(HIGH)$ ; $N_D(ON)$ , $P_D(OFF)$ , $Q_P(OFF)$ , $Q_N(SAT)$

$$V_{OUT} = V_{CE,N(SAT)} = V_{OL} = 0.2V$$

TO FIND  $V_{IL}$  &  $V_{IH}$  USE TEXT PROCEDURE



CHAPTER 30 SOLUTIONS (CONT)

30.6 a) STATIC POWER DISSIPATION

$$P_{DISS} = I_{DD} V_{DD}$$

$$I_{DD} = \frac{I_{DD}(04) + I_{DD}(02)}{2} = \frac{0+0}{2} = 0$$

$P_{DISS} = 0$  REGARDLESS OF  $V_{DD}$  VALUE

b) DYNAMIC POWER DISSIPATION

$$P_{DD} = C_L \cdot 2 V_{DD}^2 = 0.05 \times 10^{-12} \times 25 \times 10^6 \times 10^2$$

$$P_{DD} = 125 \mu W$$

$$\text{Total Power DISS} = 125 \mu W$$

30.7  $V_{IN}(\text{LOW})$ ;  $N_I(\text{OFF})$ ,  $P_I(\text{ON})$ ,  $Q_N(\text{ON})$ ,  $Q_P(\text{OFF})$

$Q_N$  GIVES LARGE CURRENT INITIALLY

$$V_{OUT} = V_{DD} - V_{BE,N}(\text{FA}) = V_{OH} = 5 - 0.7 = 4.3V$$

$V_{IN}(\text{HIGH})$ ;  $P_I(\text{OFF})$ ,  $N_I(\text{ON})$ ,  $Q_N(\text{OFF})$ ,  $Q_P(\text{ON})$  - PROVIDES PULL-DOWN

$$V_{OUT} = V_{BE,P}(\text{FA}) = V_{OL} = 0.7V$$

$$\text{LOGIC SWING} = V_{DD} - 2V_{BE}(\text{FA}) = 5 - 2(0.7) = 3.6V$$

30.8 STATIC POWER DISSIPATION =  $I_{DD} V_{DD} = 0 / V_{DD} = 0$

30.9  $V_{OH}$  IS  $V_{DD} - V_{BE,N_2}(\text{FA}) = 5 - 0.7 = 4.3V$  ( $N_3$  AND  $P_I$  ON)

$V_{OL}$  IS  $V_{BE,N_1}(\text{FA}) = 0.7V$  ( $N_1$  IS ON &  $N_2$  OFF)

30.10 STATIC POWER DISSIPATION = 0

30.11  $V_{OH} = V_{DD}$ ,  $V_{OL} = 0$

30.12 STATIC POWER DISSIPATION = 0