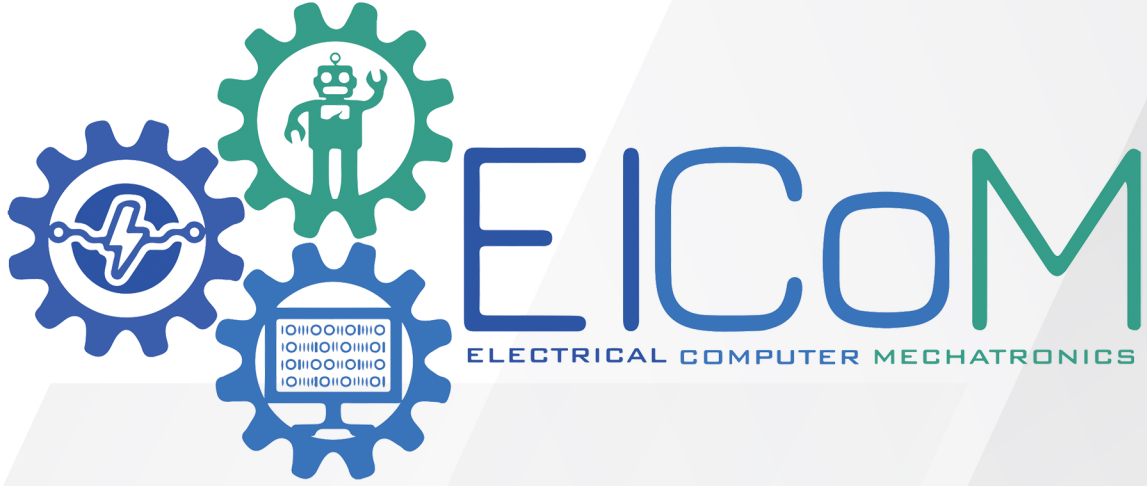


تقدم لجنة ElCoM الاكاديمية




تلخيص سكند لمادة:

# الالكترونيات القوى

جزيل الشكر للطالب:

بدر بلييله




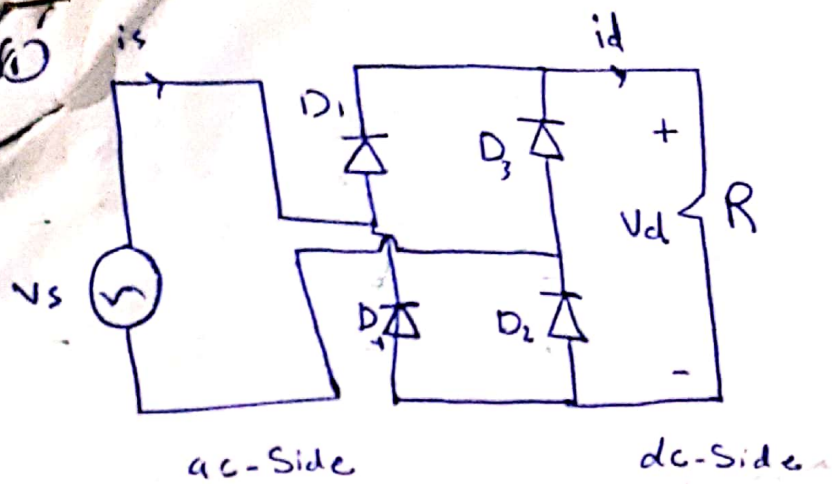

$$-V_s = -V_d$$

$$V_d = -V_s$$

uncontrolled

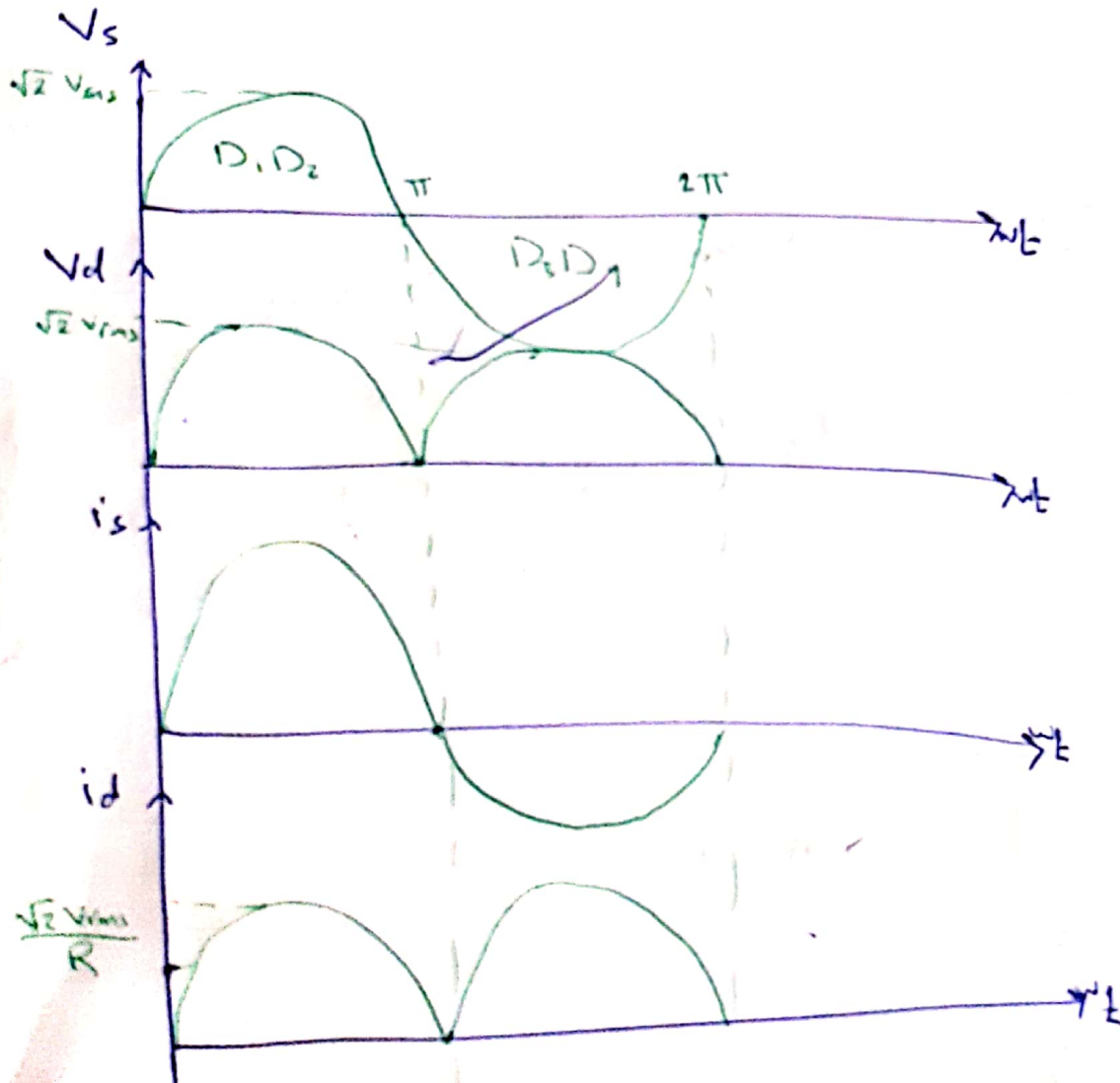


$\cdot V_{g1} \cos \omega t$


in Thyristor can't use different AC waveform  
just AC Sinusoidal


$$PIV = V_{sp} + V_{battery}$$

2

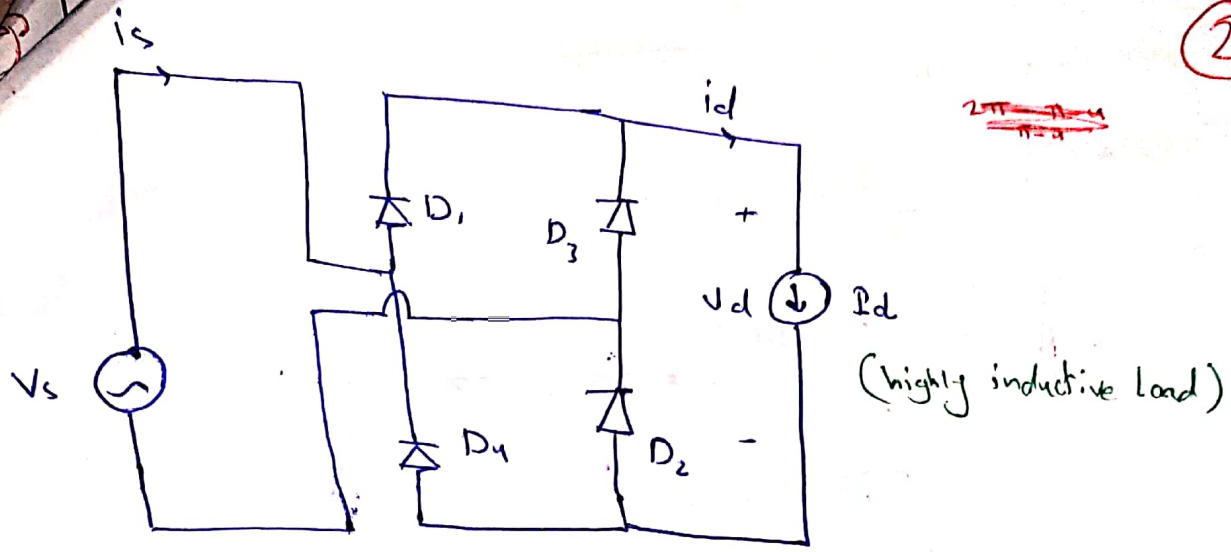


uncontrolled full bridge

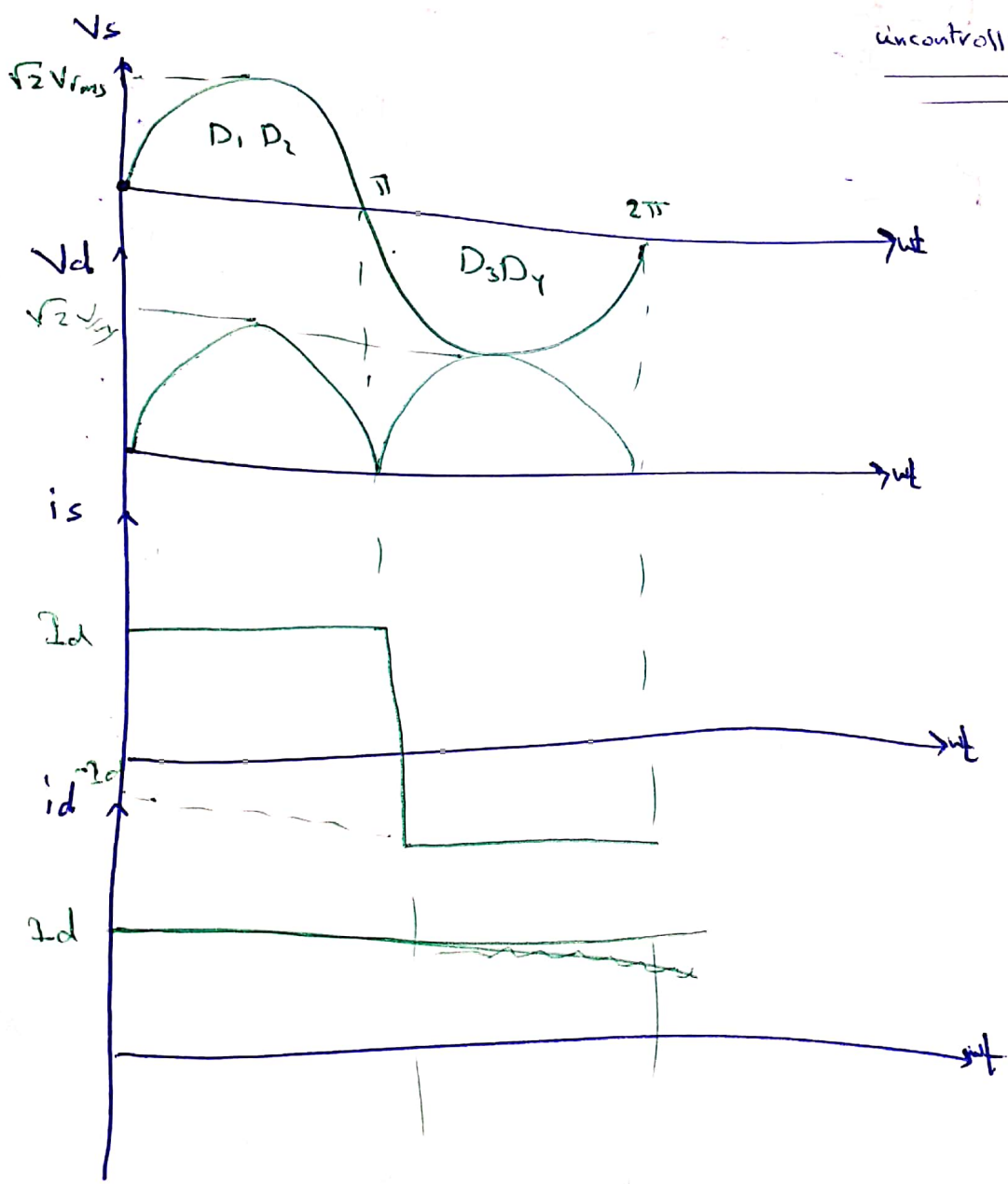

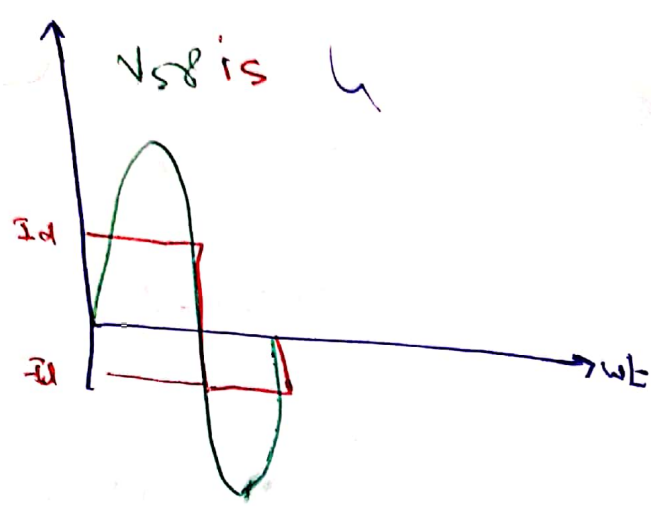

$I_{S1} = 0.4 I_d \rightarrow$  rms value of the fundamental component of  $i_s(t)$
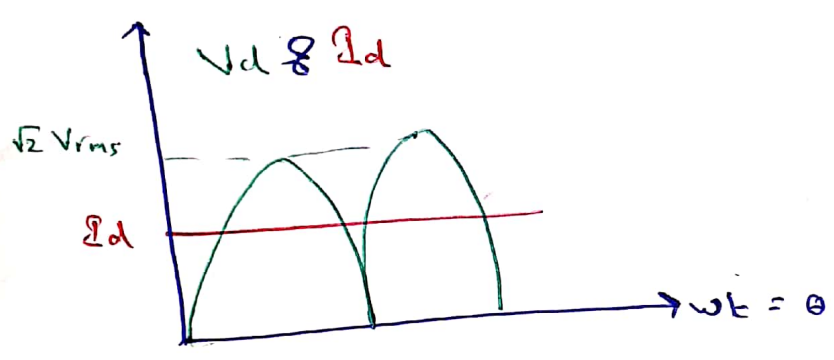
$$P = V I_{S1} \cos \theta = V (0.4 I_d) = 0.4 V I_d \quad (\text{avg Power from the ac-side})$$



$$\begin{aligned}
 P &= \frac{1}{2\pi} \int_0^{2\pi} v_d(\theta) i_d(\theta) d\theta \\
 &= \frac{I_d}{2\pi} \int_0^{2\pi} \sqrt{2} V \sin \theta d\theta \\
 &= \frac{I_d}{\pi} \int_0^{\pi} \sqrt{2} V \sin \theta d\theta \\
 &= \frac{2 \sqrt{2}}{\pi} \cdot I_d \cdot V \cdot \cos(\theta) \Big|_0^{\pi}
 \end{aligned}$$

$$\boxed{P = 0.9 \cdot V \cdot I_d} \quad (\text{avg Power from the dc-side})$$



\* Back to ac-Side

$$I_s = I_d$$

4

$$\text{THD}\% = \frac{\sqrt{I_s^2 - I_{s1}^2}}{I_{s1}} * 100\% =$$

$$= \frac{\sqrt{I_d^2 - (0.9 I_d)^2}}{0.9 I_d} * 100\% = 48.43\%$$

$$\text{DPF} = \cos(0) = 1$$

$$\text{PF} = \frac{I_{s1}}{I_s} \cdot \cos \theta = 0.9$$


$$I_{s1} = 0.9 I_d$$

$$I_s = I_d$$

$$P = 0.9 V_d I_d$$

ac or dc

of (Ls) on current commutation

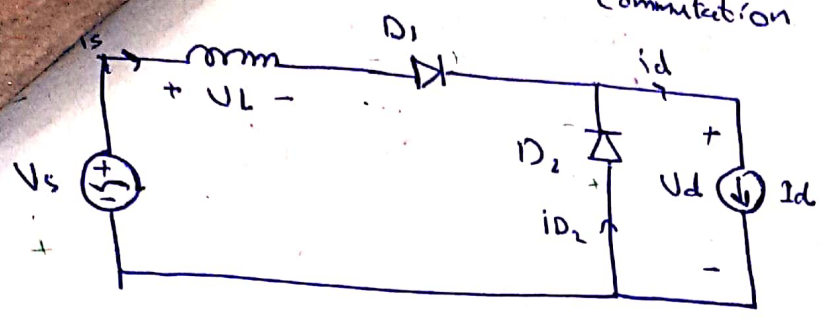


(Half wave-rectifier)

$$i_s + i_{D2} = i_{D1}$$


$$\frac{di_s}{dt} + \frac{di_{D2}}{dt} = \frac{di_{D1}}{dt}$$
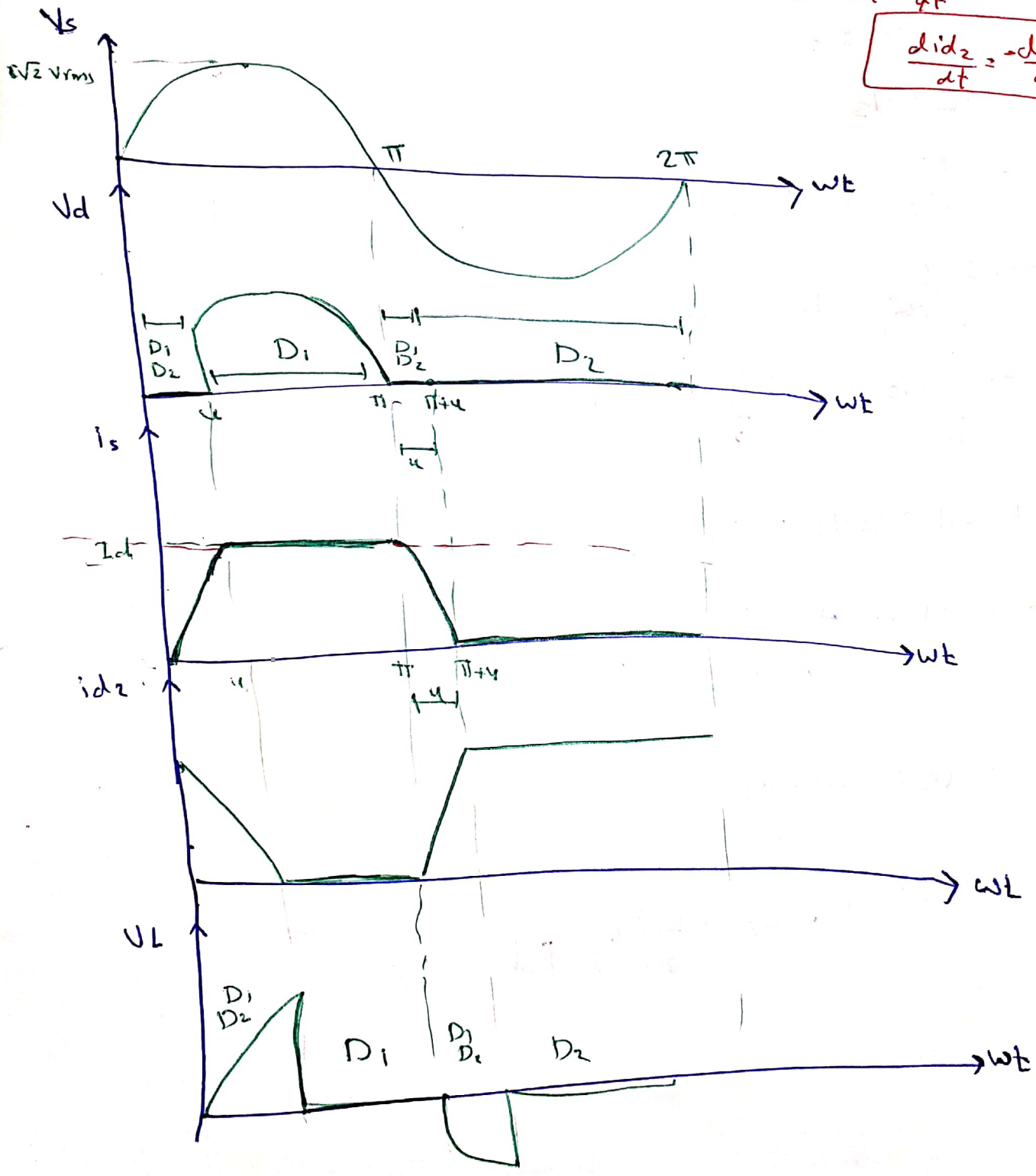
$$\frac{di_{D2}}{dt} = -\frac{di_s}{dt}$$



$$* V_d = \frac{1}{2\pi} \int_0^{2\pi} v_d(\theta) d\theta = \frac{1}{2\pi} \int_{\mu}^{\pi} \sqrt{2} V \sin(\theta) d\theta$$
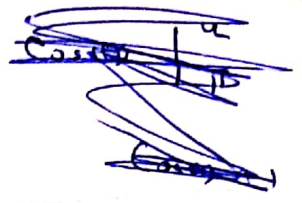
$$V_d = \frac{\sqrt{2} V}{2\pi} [\cos(\mu) + 1]$$



\* During Commutation

$$V_L = V_s$$

$$L_s \frac{di_s}{dt} = \sqrt{2} V \sin \omega t$$

$$\omega L_s \frac{di_s}{dt} = \sqrt{2} V \sin \omega t$$


$$\omega L_s \int_0^{\mu} di_s = \sqrt{2} V \int_0^{\mu} \sin(\theta) d\theta$$

$$\omega L_s I_d = \sqrt{2} V [1 - \cos(\mu)]$$

$$\cos(\mu) = 1 - \frac{\omega L_s I_d}{\sqrt{2} V}$$

$$V_d = 0.45V - \frac{\omega L_s I_d}{2\pi}$$

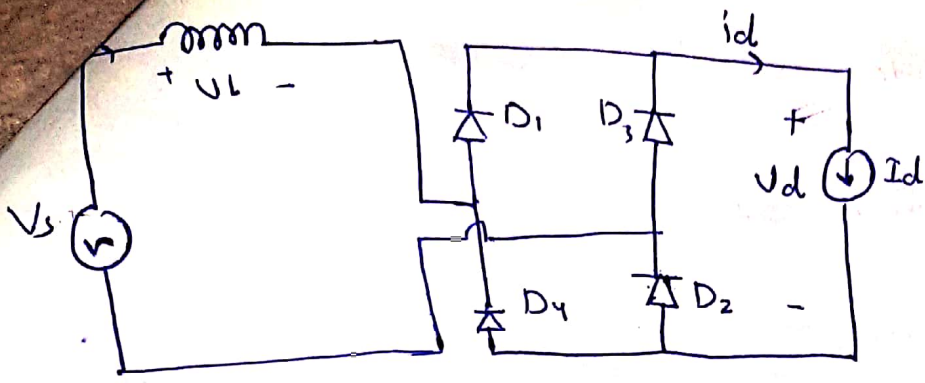
$$P = I_d \cdot V_d = \left( 0.45V - \frac{\omega L_s I_d}{2\pi} \right) \cdot I_d$$



Full-wave Bridge rectifier (Single-phase) with constant current and inductor

$$P_d = 1.35 V_{LL} \cdot I_d$$

↓  
Three phase

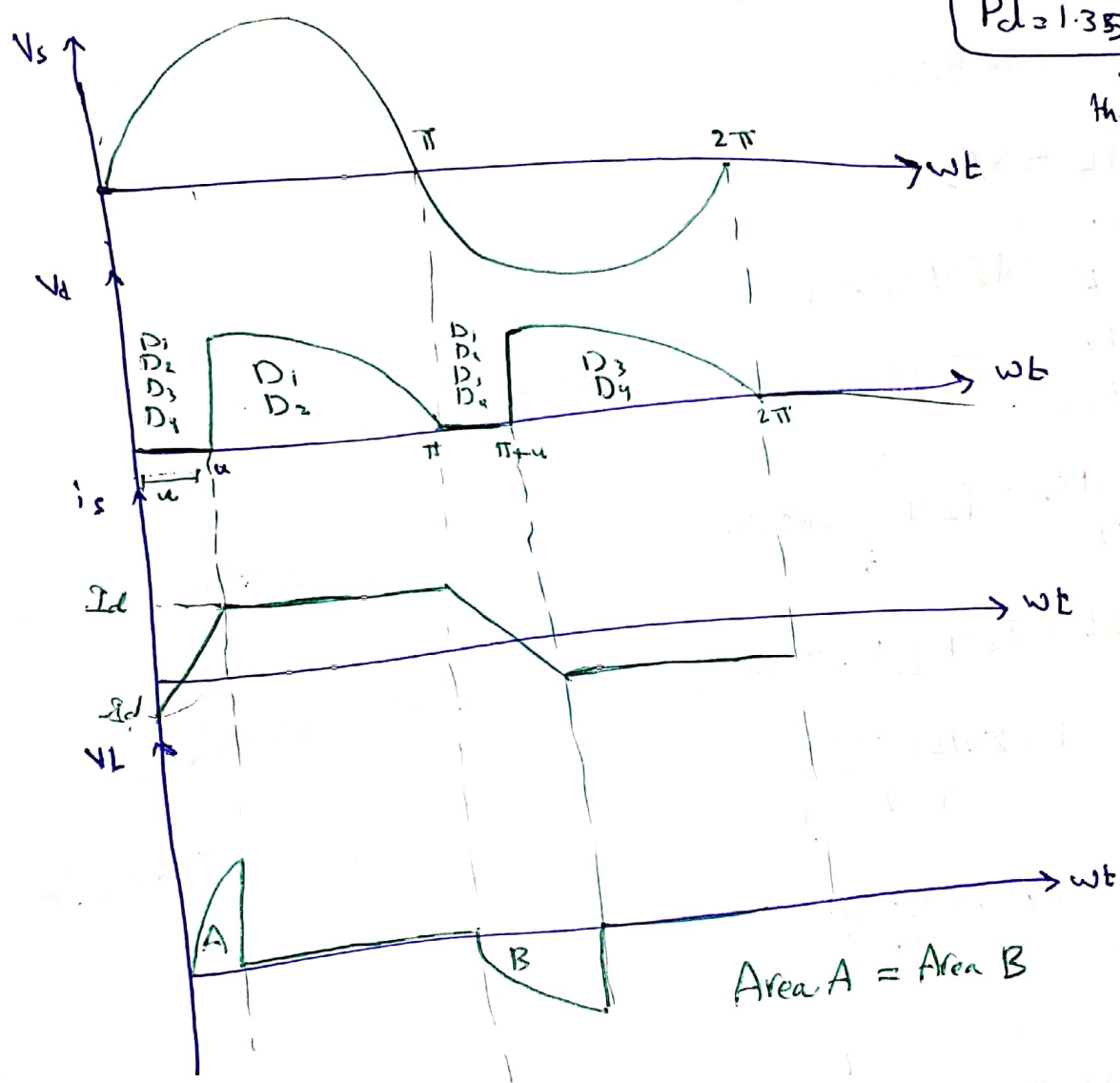

\* effect of "Ls" <sup>∝ Id</sup>  
 ↓ all source inductance

- ① reduces the Avg value of the out voltage
- ② reduces the Avg output Power
- ③ introduces the commutation interval, all diode on and  $V_d = 0$

\* The commutation interval increase with Ls and Id and decrease with Vs



$$* V_d = \frac{1}{2\pi} \int_0^{2\pi} v_d(\theta) d\theta$$

$$V_d = \frac{1}{2\pi} \times 2 \int_u^{\pi} \sqrt{2} V \sin \theta d\theta$$

$$V_d = \frac{\sqrt{2} V}{\pi} [\cos u + 1]$$

\* During commutation

$$V_L = V_s$$

$$L_s \frac{di_s}{dt} = \sqrt{2} V \sin(\omega t)$$

$$\omega L_s \frac{di_s}{d\omega t} = \sqrt{2} V \sin(\omega t) \Rightarrow \int \omega L_s di_s = \int \sqrt{2} V \sin \omega t \cdot d\omega t$$

$$\omega L_s \int_{-I_d}^{I_d} di_s = \sqrt{2} V \int_0^u \sin \theta d\theta$$

~~$$\omega L_s \int di_s = \int \sqrt{2} V \sin(\omega t) d\omega t$$~~

$$2\omega L_s I_d = \sqrt{2} V [1 - \cos(u)]$$

~~$$\omega L_s \frac{di_s}{d\theta} = \sqrt{2} V \sin(\theta)$$~~

$$\boxed{\cos(u) = 1 - \frac{2\omega L_s I_d}{\sqrt{2} V}}$$

~~$$\omega L_s \int di_s = \int \sqrt{2} V \sin(\theta) d\theta$$~~

$$V_d = 0.9 V - \frac{2\omega L_s I_d}{\pi}$$

$$P_d = V_d \cdot I_d$$

\*  $i_s(t)$  during  $u$


$$\omega L_s \frac{di_s}{d\theta} = \sqrt{2} V \sin \theta$$

$$\omega L_s \int di_s = \sqrt{2} V \int \sin \theta d\theta + K$$

$$\omega L_s i_s(\theta) = -\sqrt{2} V \cos(\theta) + K$$


$$i_s(\theta) = \frac{-\sqrt{2} V \cos(\theta)}{\omega L_s} + K_1$$
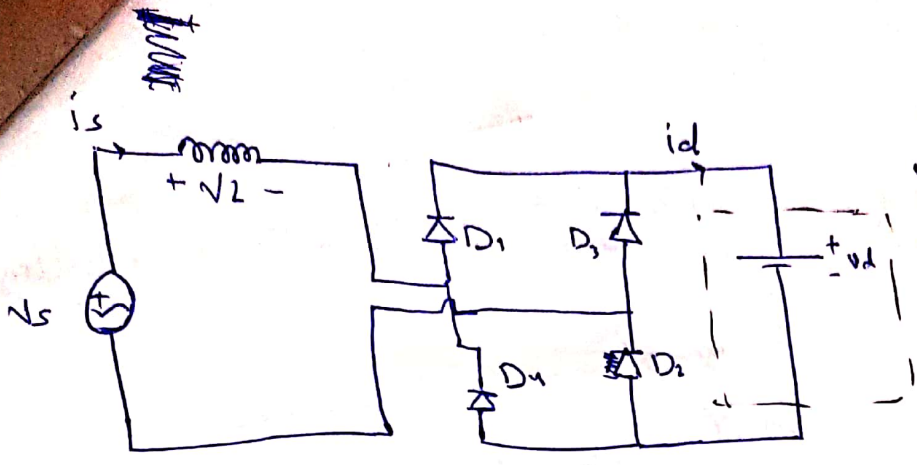
$$i_s(0) = -I_d = \frac{-\sqrt{2} V}{\omega L_s} + K_1$$



$V_d(t) = V_d$

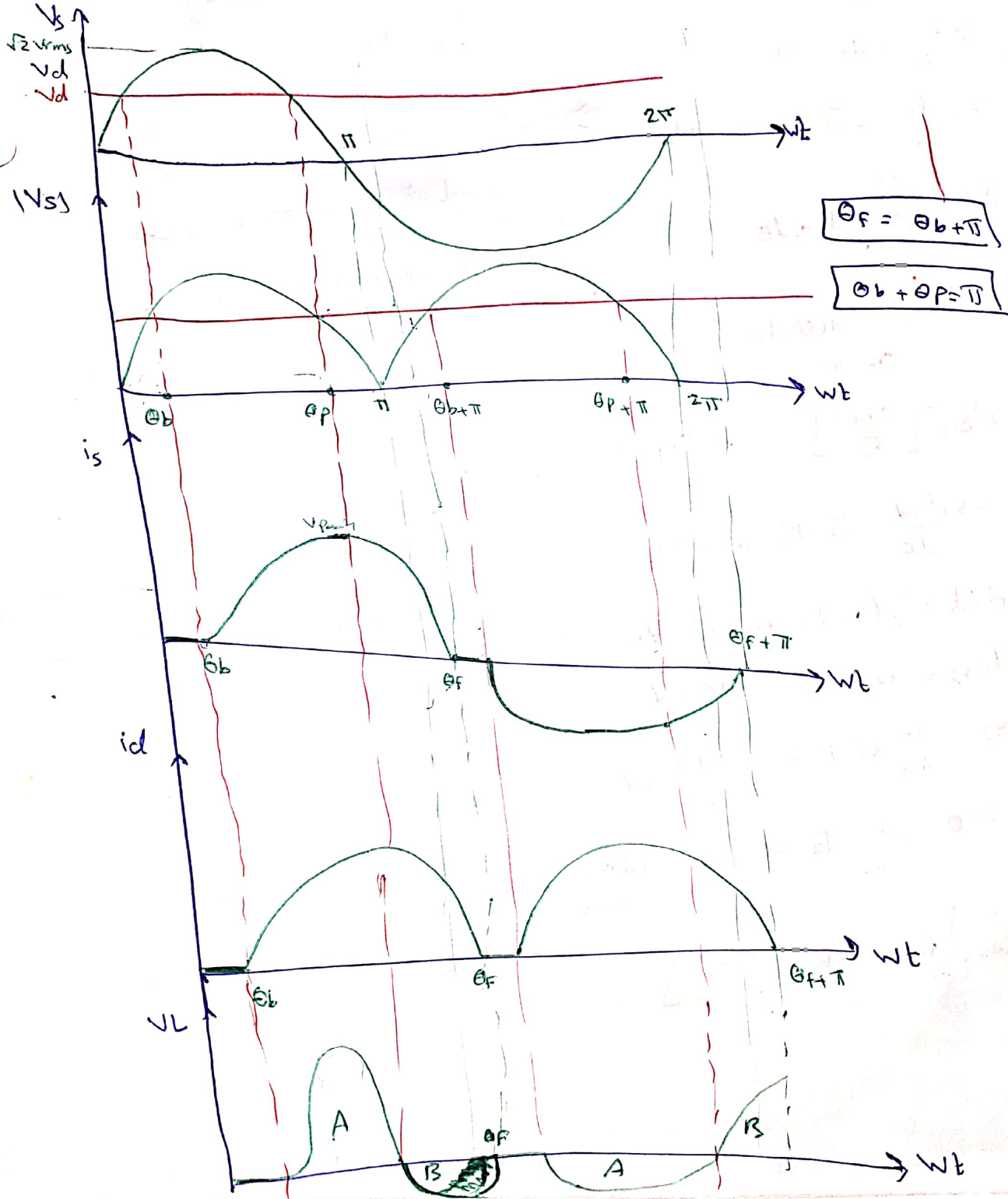$C = \infty$   
 $R = \infty = R_c$   
 $\Rightarrow$  DC-voltage



$\theta_f = \theta_b + \pi$

$\theta_b + \theta_f = \pi$

$$\theta_b = \pi - \theta_p = 0$$

at  $V_d = V_s$

$$V_d = \sqrt{2} V_{rms} \sin \theta_b$$

$$\theta_b = \sin^{-1} \left[ \frac{V_d}{\sqrt{2} V_{rms}} \right]$$

$$\theta_p = \pi - \theta_b$$

$$\theta_f \geq \theta_p$$

$$-V_s + L_s \frac{di_s}{dt} + V_d = 0$$

$$L_s \frac{di_s}{dt} = V_s - V_d$$

$$\omega L_s \frac{di_s}{d\omega t} = \sqrt{2} V \sin(\omega t) - V_d$$

$$I_d = \frac{1}{2\pi} \int_0^{2\pi} i_d(\theta) d\theta$$

$$I_d = \frac{1}{2\pi} \int_{\theta_b}^{\theta_f} i_d(\theta) d\theta$$

$$\theta_b = \sin^{-1} \left[ \frac{V_d}{\sqrt{2} V} \right], \quad \theta_p = \pi - \theta_b$$

$$\omega L_s \frac{di_d}{d\theta} = \sqrt{2} V \sin(\theta) - V_d$$

$$\omega L_s \int di_d = \int (\sqrt{2} V \sin(\theta) - V_d) d\theta$$

$$\omega L_s i_d(\theta) = -\sqrt{2} V \cos(\theta) - V_d \theta + K_1$$

$$i_d(\theta) = \frac{-1}{\omega L_s} \cdot \sqrt{2} V \cos \theta - \frac{V_d \theta}{\omega L_s} + K_1$$

$$i_d(\theta_b) = 0 = \frac{-1}{\omega L_s} \cdot \sqrt{2} V \cos(\theta_b) - \frac{V_d \theta_b}{\omega L_s} + K_1$$

$$K_1 = \frac{1}{\omega L_s} \left[ \sqrt{2} V \cos \theta_b + V_d \theta_b \right]$$

$$i_d(\theta) = \frac{-1}{\omega L_s} \cdot \sqrt{2} V \cos \theta - \frac{V_d \theta}{\omega L_s} + \frac{1}{\omega L_s} \cdot \sqrt{2} V \cos(\theta_b) + \frac{1}{\omega L_s} V_d \theta_b$$

Constant

general form:  $i_d(\theta) = C_1 \cos \theta - C_2 \theta + C_3$

$$0 = i_d(\theta_f) = \frac{-1}{\omega L_s} \cdot \sqrt{2} V \cos(\theta_f) - \frac{1}{\omega L_s} V_d \theta_f + \frac{1}{\omega L_s} \cdot \sqrt{2} V \cos(\theta_b) + \frac{1}{\omega L_s} V_d \theta_b$$



→ conducting interval

$$\omega t_{cond} = \theta_f - \theta_b \Rightarrow \omega = 2\pi f$$

$$i_d(\theta_f) = 0 = C_1 \cos(\theta_f) + C_2 \theta_f + C_3$$
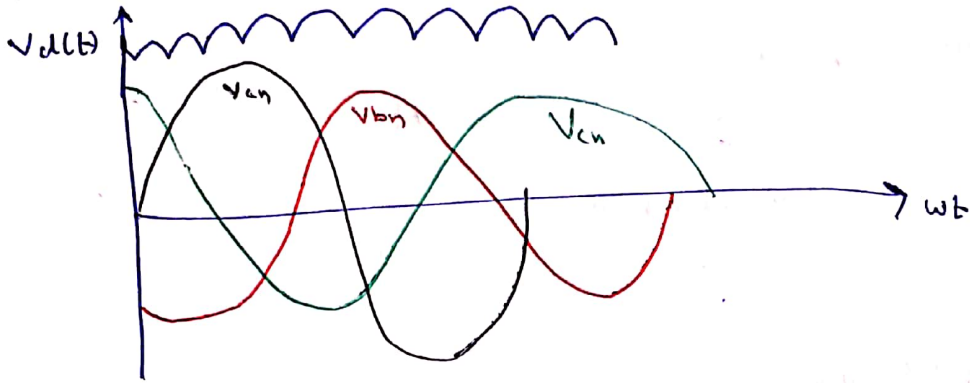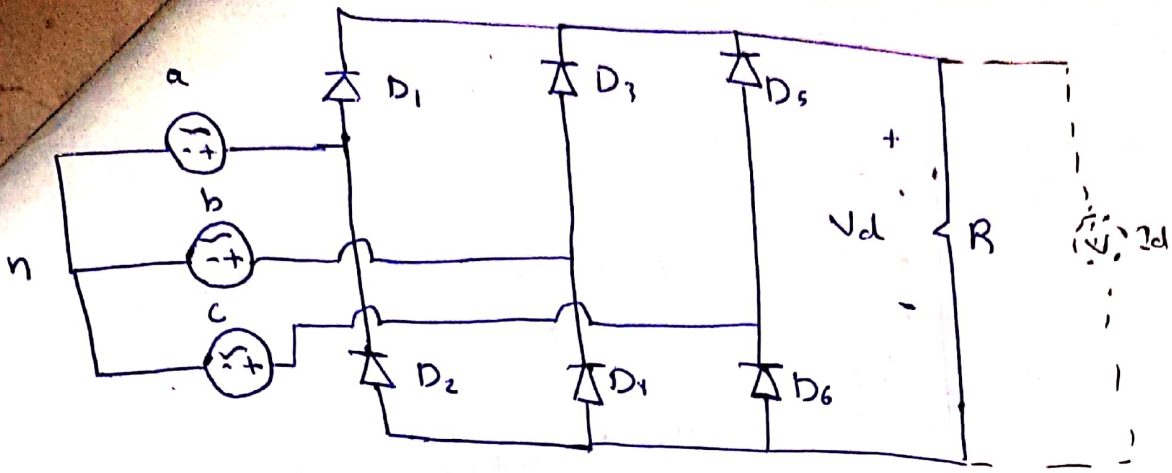
$$I_d = \frac{1}{\pi} \int_{\theta_b}^{\theta_f} \left( \frac{-\sqrt{2} V \cos \theta}{\omega L_s} - \frac{V_d \cdot \theta}{\omega L_s} + \frac{\sqrt{2} V \cos(\theta_b)}{\omega L_s} + \frac{1}{\omega L_s} V_d \theta_b \right) d\theta$$





\* Three phase rectifier circuit have, Compared to Single phase rectifier

- ① Lower ripple content in the wave form
- ② higher Power-handling capacity

\* average  $\leftarrow V_d = 1.35 V_{LL}$   $\leftarrow$  rms value of the three phase Line Voltage  
value of the o/p voltage

$$V_d = \frac{6}{2\pi} \int_0^{\frac{\pi}{3}} V_m \sin(\theta) d\theta$$

$$= \frac{3}{\pi} \int_0^{\frac{\pi}{3}} \sqrt{2} V \sin(\theta) d\theta = 1.35 V_{LL}$$


$$P_d = 1.35 V_{LL} \cdot I_d$$

↓  
Diodes (3 phase)

$$P_d = 1.35 V_{LL} I_d \cdot \cos \phi$$

↓  
Thyristores (3 phase)



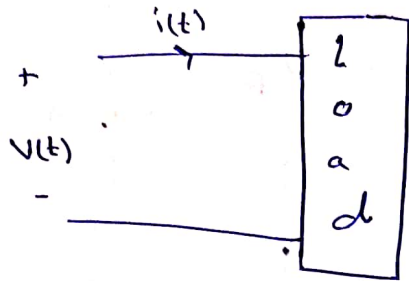

$$v(t) = V_d + \sqrt{2} V_1 \cos \omega t + \sqrt{2} V_1 \sin \omega t + \sqrt{2} V_3 \cos(\omega_3 t) \text{ Volt}$$

$$i(t) = I_d + \sqrt{2} I_1 \cos(\omega t) + \sqrt{2} I_3 \cos(\omega_3 t - \phi_3) \text{ A}$$

$$(a) \quad P = \frac{1}{T} \int_0^T v(t) \cdot i(t) dt = \frac{1}{T} \int_0^T ( \quad ) \cdot ( \quad ) dt$$

$$= V_d I_d + V_1 I_1 + V_3 I_3 \cos \phi_3$$

$$(b) \quad V = \sqrt{V_d^2 + V_1^2 + V_1^2 + V_3^2}$$



$$I = \sqrt{I_d^2 + I_1^2 + I_3^2}$$

$$(c) \quad S = V I$$

$$PF = P/S = \frac{V_d I_d + V_1 I_1 + V_3 I_3 \cos \phi_3}{V I}$$

- Symm about t-axis →  $a_0 = 0$
- $x(t)$  → even signal →  $b_n = 0$
- $x(t)$  → odd signal →  $a_n = 0$

Ex ⇒

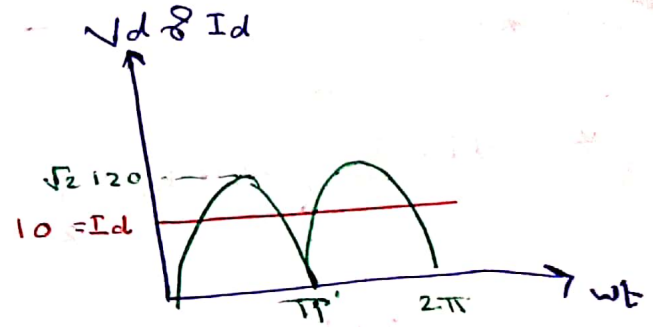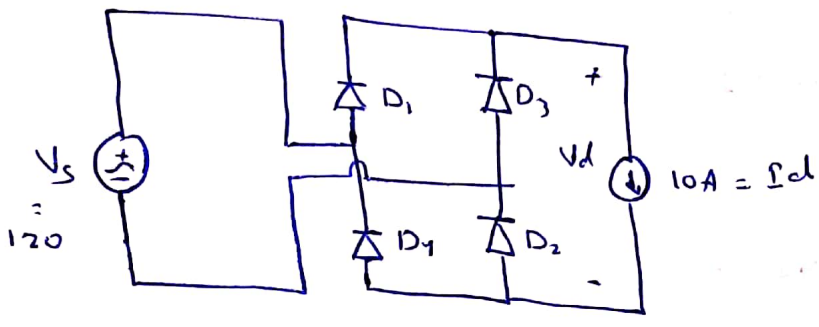


calculate P

$$P = \frac{1}{T} \int_0^T v(t) \cdot i(t) dt$$

$$= \frac{1}{2\pi} \left[ \int_0^{\pi} 10 \cdot \sqrt{2} \cdot 120 \cdot \sin(\omega t) d\omega t + \int_{\pi}^{2\pi} 10 \cdot \sqrt{2} \cdot 120 \cdot \sin(\omega t) d\omega t \right]$$

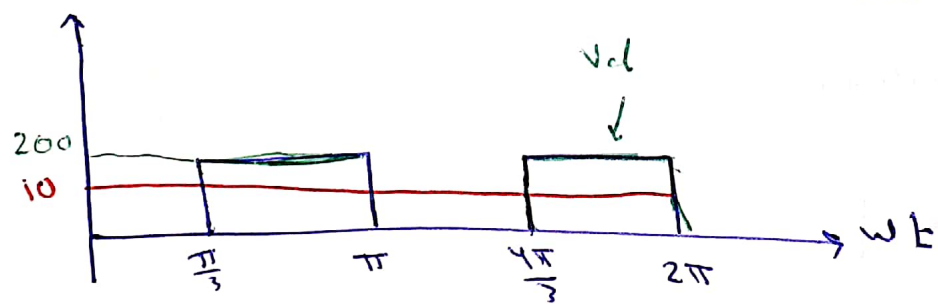
$$= 0.9 V \cdot I_d = (0.9)(120)(10) = 1080 \text{ W}$$



$$P = \frac{1}{2\pi} \left[ \int_{\frac{\pi}{3}}^{\pi} (200)(10) d\omega t + \int_{\frac{4\pi}{3}}^{2\pi} (200)(10) d\omega t \right]$$

$$= 1333.33 \text{ W}$$

E.x →

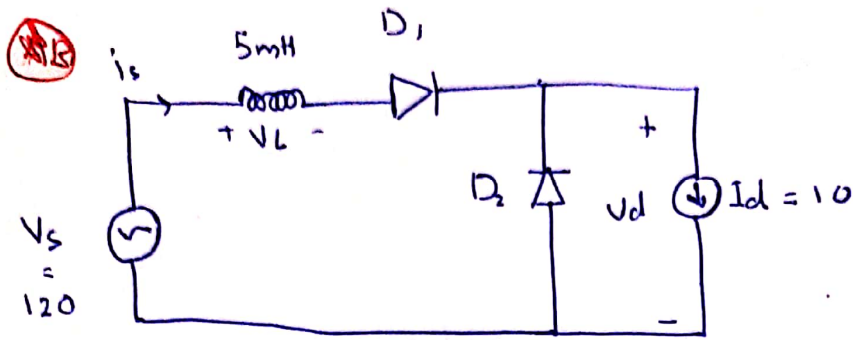

$L_s = 5 \text{ mH}$

$$* V_d = \frac{1}{2\pi} \int_0^{2\pi} V_d(\theta) d\theta = \frac{1}{2\pi} \int_u^{\pi} \sqrt{2} \cdot 120 \cdot \sin(\theta) d\theta$$

$$V_d = \frac{\sqrt{2} \cdot 120}{2\pi} [\cos(u) + 1]$$

\* During commutation

$V_L = V_s$

$L_s \frac{di_s}{dt} = \sqrt{2} \cdot 120 \cdot \sin(\omega t)$

$\omega L_s \frac{di_s}{d\omega t} = \sqrt{2} \cdot 120 \cdot \sin \omega t$

$\omega L_s \int_0^{I_d} di_s = \int_0^u \sqrt{2} \cdot 120 \cdot \sin(\theta) d\theta$

$\omega L_s I_d = \sqrt{2} \cdot 120 \cdot \cos \theta \Big|_u^0$

$\omega L_s \cdot I_d = \sqrt{2} \cdot 120 [1 - \cos(u)]$

$\cos(u) = 1 - \frac{\omega L_s I_d}{\sqrt{2} \cdot 120} = 0.8889$

$V_d = \frac{51.01}{51.01} \text{ volt}$

$u = 27.2^\circ$


$u = 0.47589 \text{ radian}$

$P_d = \frac{51.01}{51.01} \text{ W}$



(C)

(15)

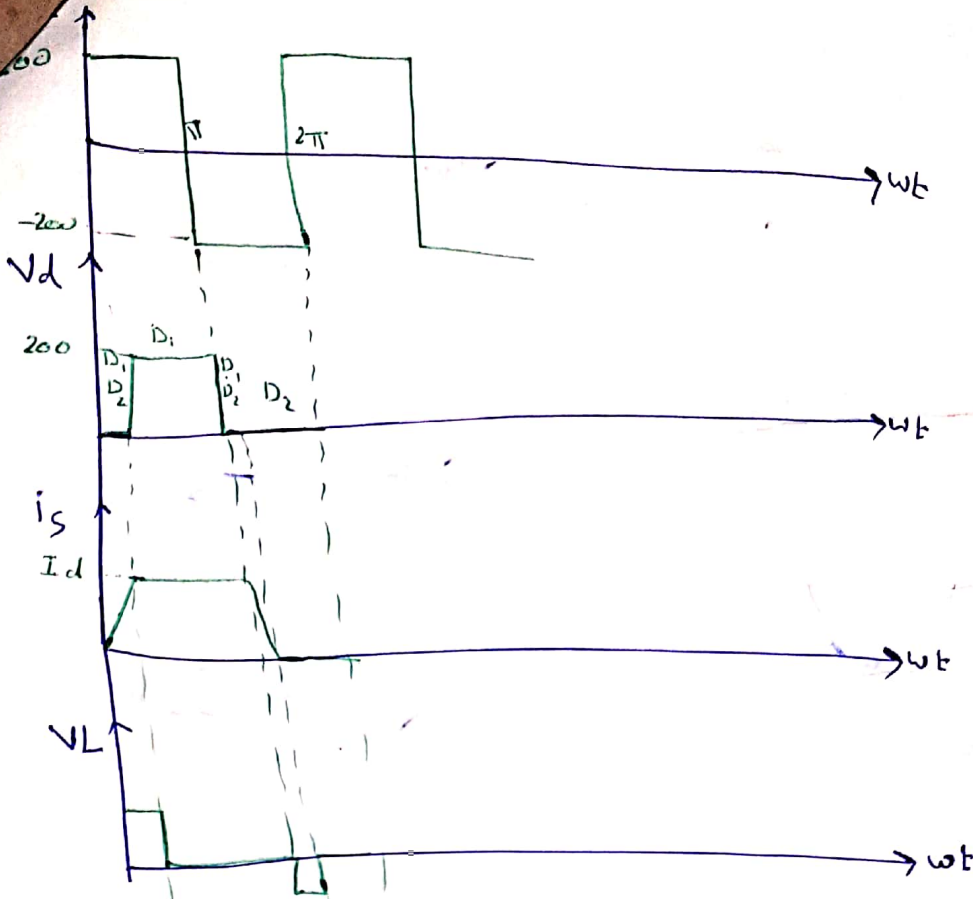

$$* V_d = \frac{1}{2\pi} \int_0^{2\pi} v_d(\theta) d\theta = \frac{1}{2\pi} \int_{\pi}^{2\pi} 200 d\theta = \frac{1}{2\pi} \cdot 200(\pi - 0) = 97 \text{ Volt}$$

\* During commutation

\*  $i_s(\theta)$  during commutation

$$V_L = V_s$$

$$W L_s \frac{di_s}{dt} = \int 200 dt$$

$$i_s(0) = 0$$

$$L_s \frac{di_s}{dt} = 200$$

$$W L_s i_s(\theta) = 200\theta + K$$

$$0 = K_1$$

$$W L_s \frac{di_s}{dt} = 200$$

$$i_s(\theta) = \frac{200\theta}{W L_s} + K_1$$

$$i_s(\theta) = \frac{200\theta}{W L_s}$$

$$W L_s \int di_s = \int_0^u 200 dt$$

$$i_s(0) = 0 = K_1$$

$$K_1 = \frac{200\theta}{W L_s}$$

$$W L_s I_d = 200 u$$


$$u = \frac{W L_s \cdot I_d}{200} = \frac{2\pi(60)(5m)(10)}{200} = 0.09424 \text{ radian}$$

$$i_s(\theta) = \frac{200\theta}{W L_s}$$

$$P_d = (97)(0) = 970 \text{ W}$$



(D)

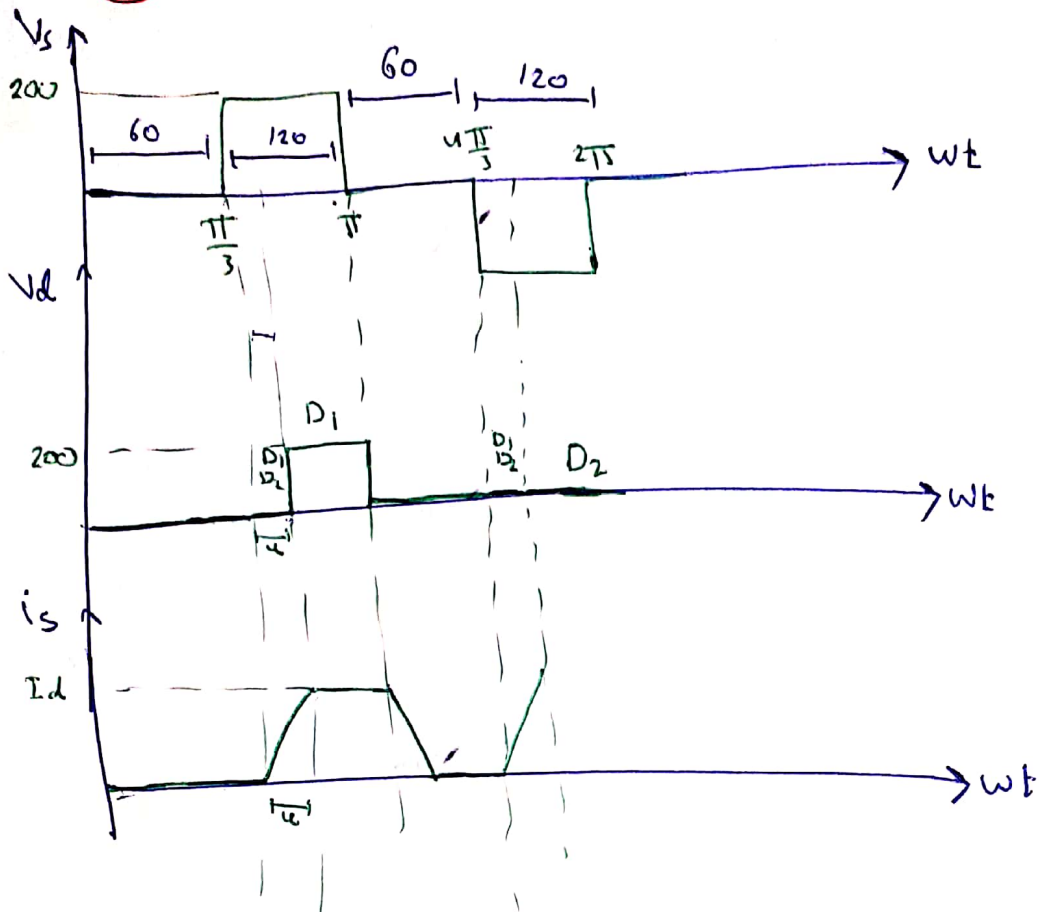

\* during commutation

$$V_L = V_s$$

$$\omega L \frac{di_s}{d\omega t} = 200$$

$$\omega L \int i_s = \int 200 d\omega t$$


$$\omega L i_d = 200 \left[ u - \frac{\pi}{3} \right]$$

$$\omega L i_d = 200u - \frac{200\pi}{3}$$

$$\frac{\omega L i_d + \frac{200\pi}{3}}{200} = u = 1.1414 \text{ radian}$$

$$* V_d = \frac{1}{2\pi} \int_0^{2\pi} V_d(\theta) d\theta = \frac{1}{2\pi} \int_u^{\pi} 200 d\theta = \frac{1}{2\pi} \cdot 200 [\pi - u] = 63.66 \text{ Volt}$$
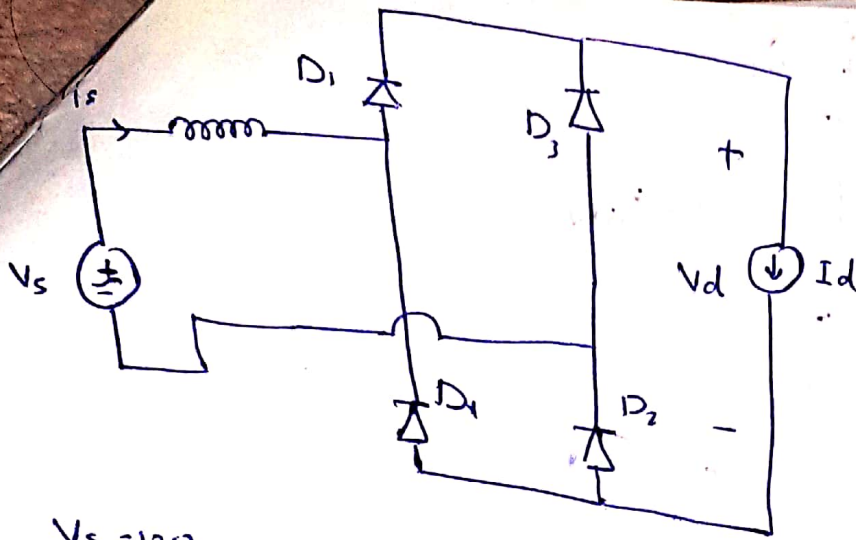
$$* P_d = V_d \cdot I_d = 636.7 \text{ W}$$



$V_s = 120$   
 $L_s = 1 \text{ mH}$   
 $I_d = 10 \text{ A}$

$$* V_d = \frac{1}{2\pi} \int_0^{2\pi} V_d(\theta) d\theta = \frac{1}{\pi} \int_{\pi}^{\pi} \sqrt{2} \cdot 120 \cdot \sin(\theta) d\theta$$

$$V_d = \frac{\sqrt{2} \cdot 120}{\pi} [\cos(\omega) + 1]$$

\* During commutation

$$V_L = V_s$$

$$L_s \frac{di_s}{dt} = \sqrt{2} \cdot 120 \cdot \sin(\omega t)$$


$$\int_{-I_d}^{I_d} \omega L_s di_s = \int_0^{\omega} \sqrt{2} \cdot 120 \cdot \sin(\omega t) \cdot d\omega t$$

$$2\omega L_s I_d = \sqrt{2} \cdot 120 [\cos(0) - \cos(\omega)]$$

$$\cos(\omega) = 1 - \frac{2\omega L_s I_d}{\sqrt{2} \cdot 120} = 0.9555$$

$$V_d = 105.634$$

$$\omega = 17.157^\circ$$

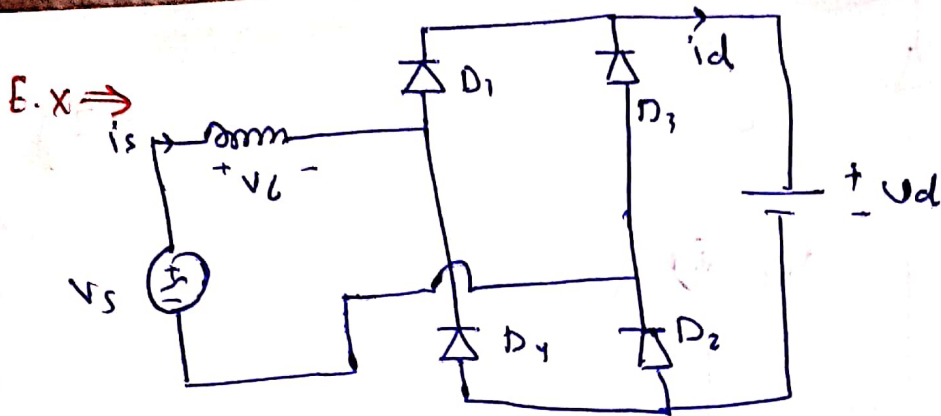


$$V_s = 120$$

$$f = 60 \text{ Hz}$$

$$L_s = 1 \text{ mH}$$

$$V_d = 150$$

Solu:-

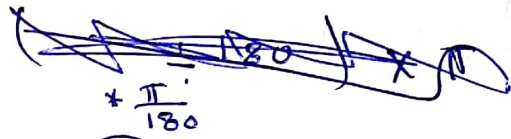

$$\theta_b = \sin^{-1} \left( \frac{V_d}{\sqrt{2} \cdot V} \right) = \sin^{-1} \left( \frac{150}{\sqrt{2} \cdot 120} \right) = 62.11^\circ = 1.0841 \text{ rad}$$



$$\theta_f = \pi - \theta_b = 117.886^\circ = 2.058 \text{ rad}$$

$$i_d(\theta) = \frac{\sqrt{2} \cdot V}{\omega L_s} \left[ \cos \theta_b - \cos \theta \right] - \frac{V_d \cdot \theta}{\omega L_s} + \frac{V_d \cdot \theta_b}{\omega L_s}$$

$$i_d(\theta_f) = 0 = \frac{\sqrt{2} \cdot V}{\omega L_s} \left[ \cos \theta_b - \cos \theta_f \right] - \frac{V_d \cdot \theta_f}{\omega L_s} + \frac{V_d \cdot \theta_b}{\omega L_s}$$

$$\theta_f = 0.4819 \text{ rad} = 27.61^\circ$$

$$I_d = 1.1 \text{ kA}$$

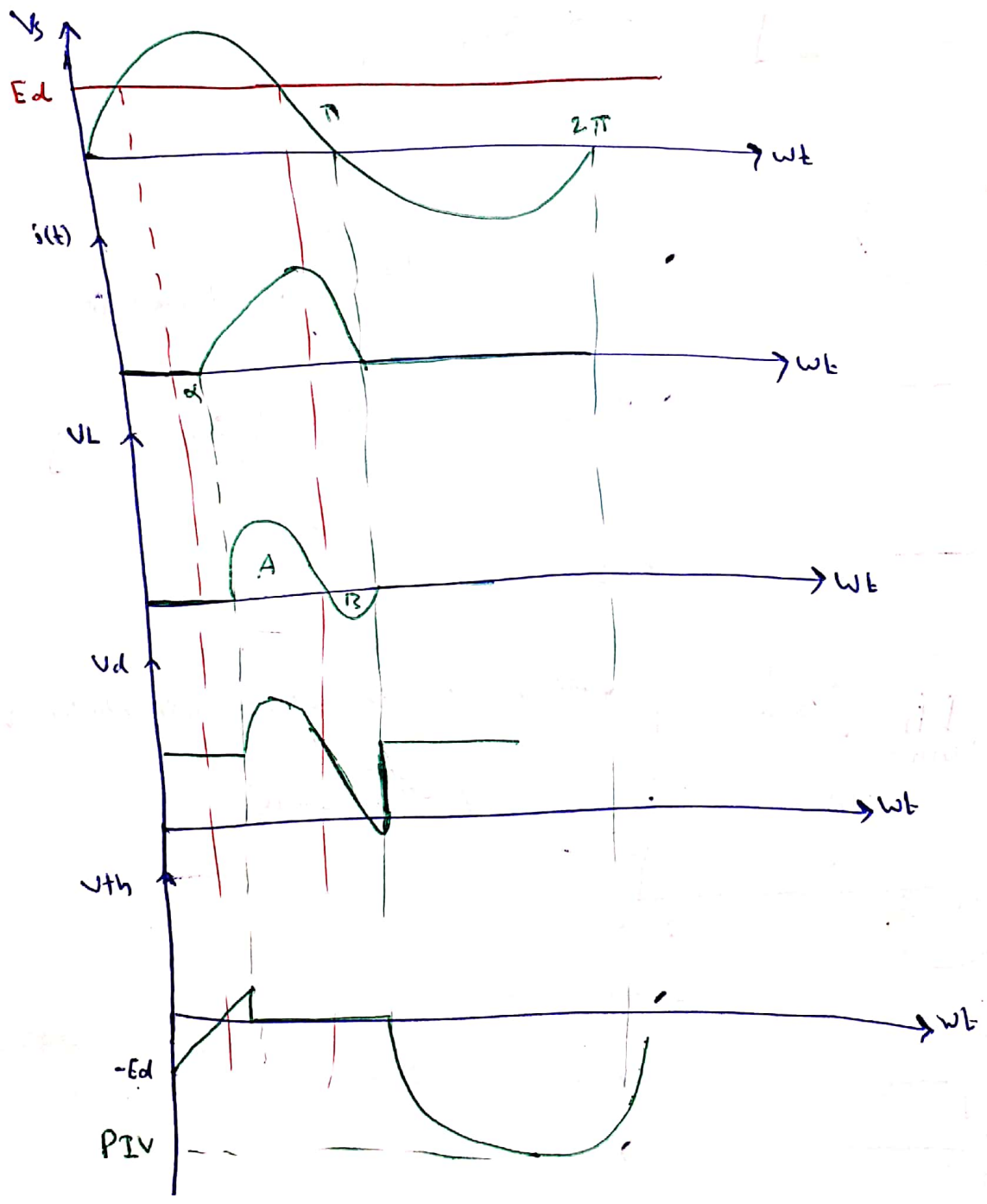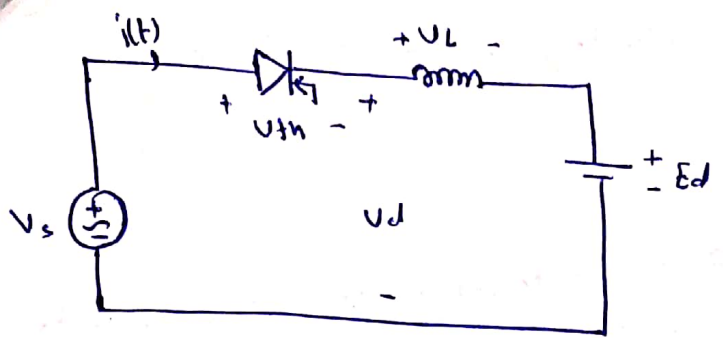


$$PIV = \sqrt{2} V_s = E_d$$




\* Controlled rectifiers and inverters  
 Line freq Ac → controlled DC

"Basic Thyristor circuit"

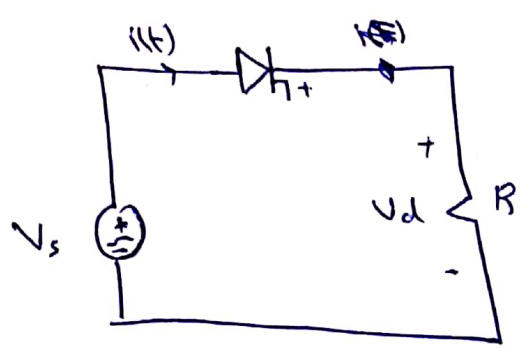


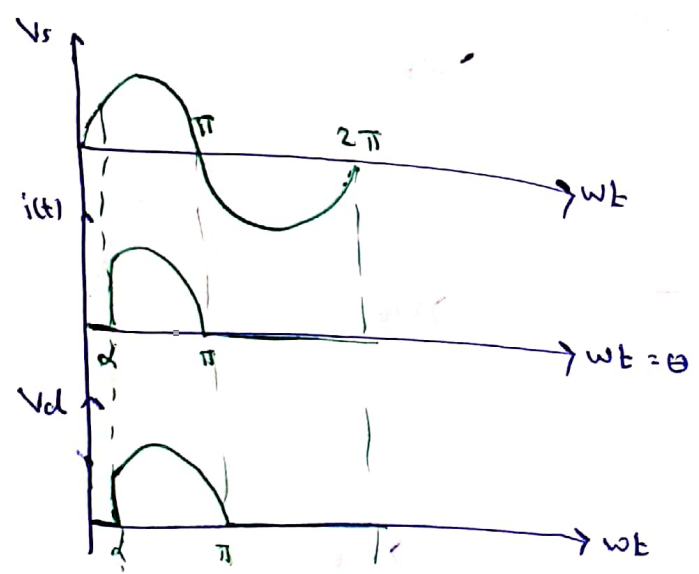\* Half wave controlled rectifier circuit with Pure resistive  
 \*  $\alpha$ : firing angle



$$V_d = \frac{1}{2\pi} \int_{\alpha}^{\pi} \sqrt{2} \cdot V \sin(\theta) d\theta$$

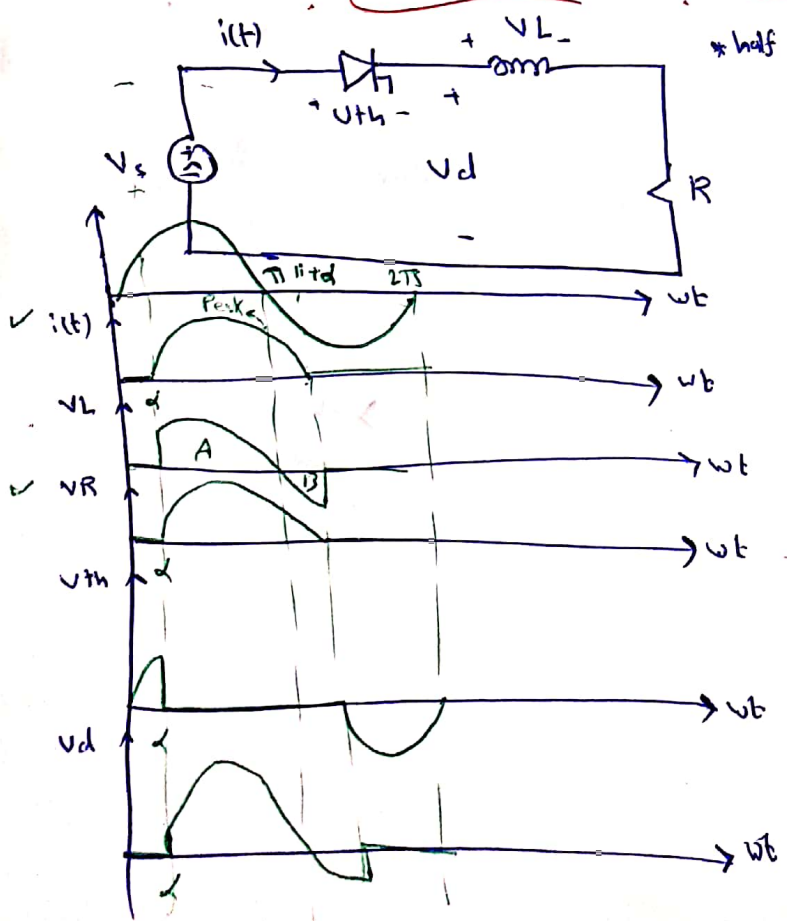
$$= \frac{\sqrt{2} \cdot V}{2\pi} [\cos(\alpha) + 1]$$



\* half wave controlled rectifier with inductive Load


$$V_d = V_L + V_R$$

# "Single Phase Converters"

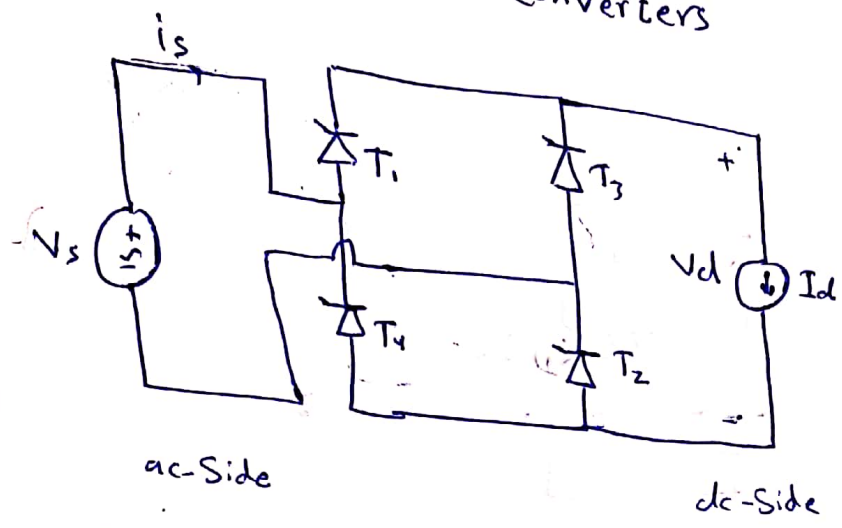

$L_s = \infty$   
(highly inductive Load)

$-V_s - V_d = 0$   
 $V_d = -V_s$

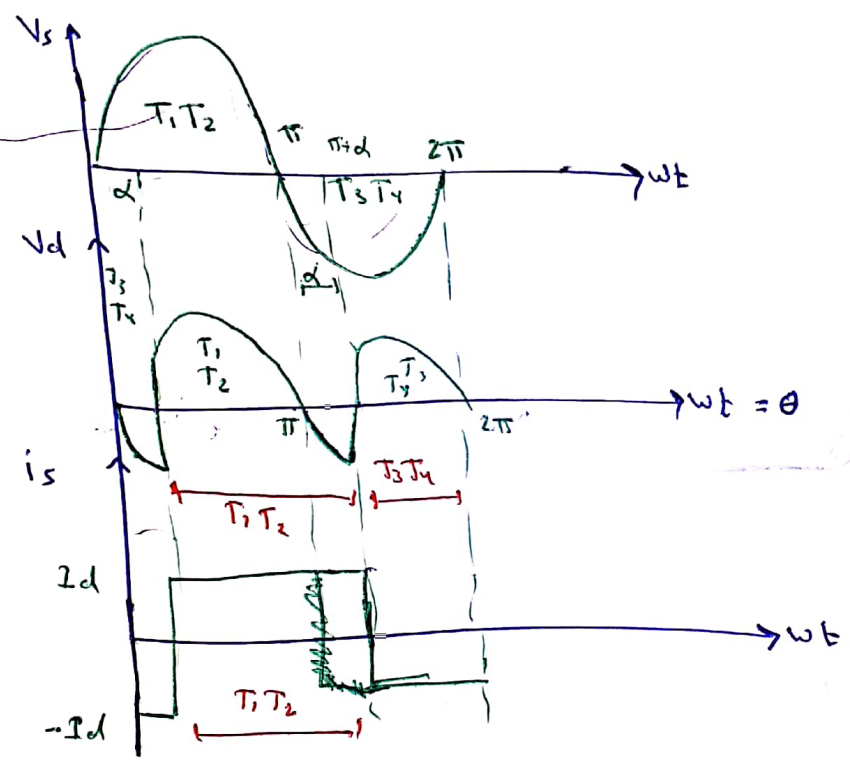

\*  $T_1$  and  $T_2$  on at  $\alpha$   
\*  $T_3$  and  $T_4$  on at  $\pi + \alpha$

$$V_d = \frac{1}{2\pi} \int_0^{2\pi} v_d(\theta) d\theta = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} \sqrt{2} \cdot V \sin(\theta) d\theta = \frac{\sqrt{2} \cdot V}{\pi} [\cos(\alpha) - \cos(\pi + \alpha)]$$

\*  $THD\% = \frac{\sqrt{(I_d)^2 - (0.9 I_d)^2}}{0.9 I_d} \times 100\% = 0.9 \cdot V \cos(\alpha)$



$= 48.43\%$

- \*  $DPF = \cos \alpha$
- \*  $Pf = 0.9 \cos \alpha$

\*  $P_d = V_d \cdot I_d$   
 $P = V [I_s] \cos \alpha$   
 $= V [0.9 I_d] \cdot \cos \alpha$   
 $P_d = 0.9 V I_d \cos \alpha$

$I_s = I_d$   
 $I_{s1} = 0.9 I_d$

\* effect of  $L_s$  :-

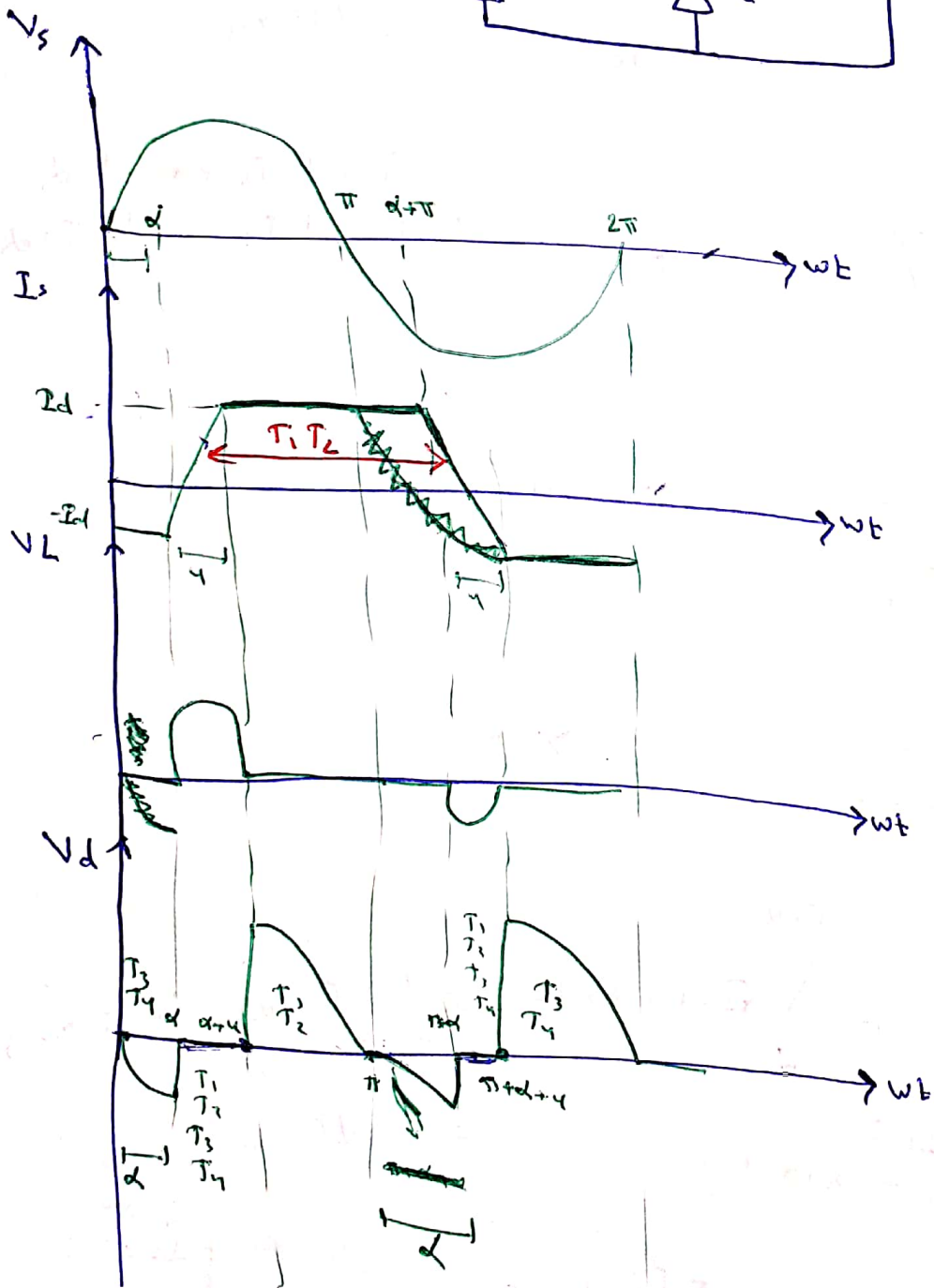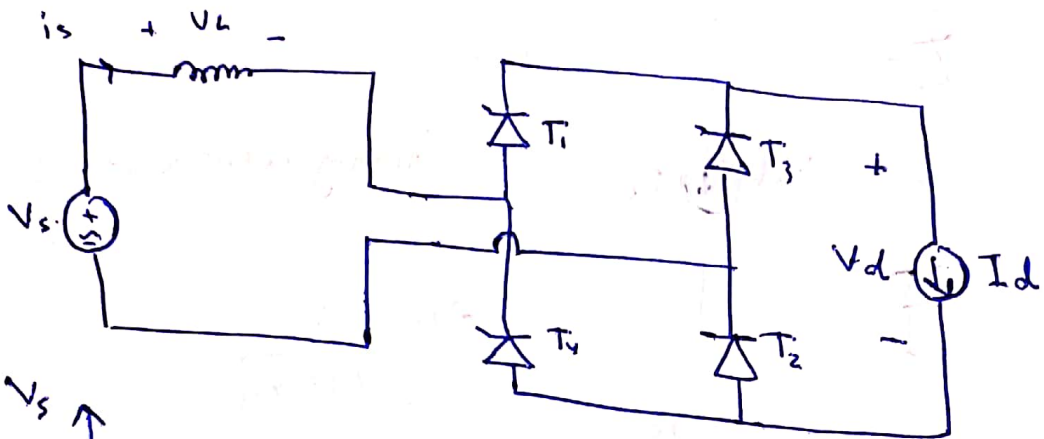



$$V_{dc} = \frac{2}{2\pi} \int_{\alpha+\pi}^{\alpha+\pi} \sqrt{2} \cdot V \sin \theta \, d\theta = \frac{\sqrt{2} \cdot V}{\pi} \cos \theta \Big|_{\alpha+\pi}^{\alpha+\pi}$$

$$V_{dc} = \frac{\sqrt{2} \cdot V}{\pi} [\cos(\alpha+\pi) - \cos(\alpha+\pi)] \Rightarrow V_{dc} = \frac{\sqrt{2} \cdot V}{\pi} [\cos(\alpha+\pi) + \cos \alpha]$$

\* During commutation

$$V_L = V_s$$

$$L_s \frac{di_s}{dt} = \sqrt{2} \cdot V \sin \omega t$$


$$\int \frac{\omega L_s di_s}{dt} = \sqrt{2} \cdot V \cdot \sin \omega t$$

$$\omega L_s \int_{-I_d}^{I_d} di_s = \int_{\alpha}^{\alpha+\pi} \sqrt{2} \cdot V \sin \theta \, d\theta$$


$$I_d \cdot 2\omega L_s = \sqrt{2} \cdot V [\cos(\alpha) - \cos(\alpha+\pi)]$$

$$V_{dc} = 0.9 V \cos \alpha - \frac{2\omega L_s I_d}{\pi}$$

\* inverter mode of operation

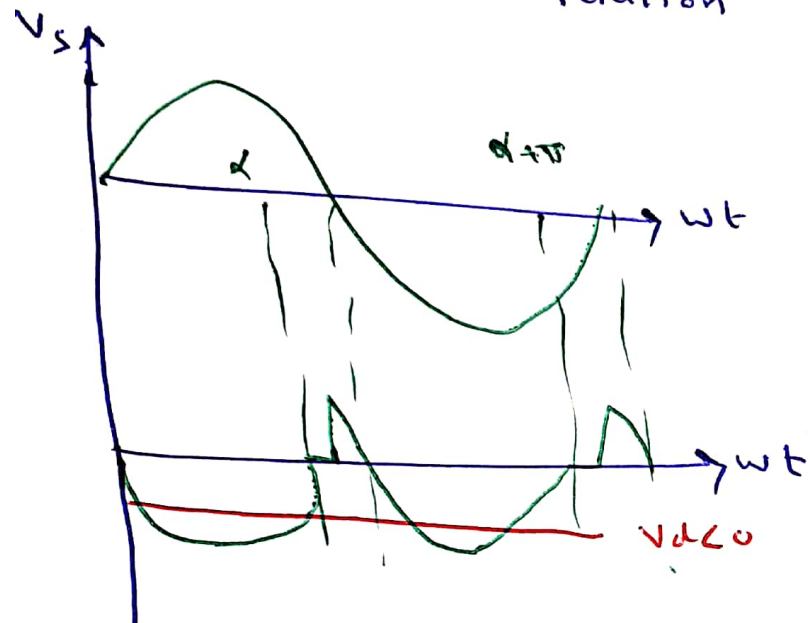

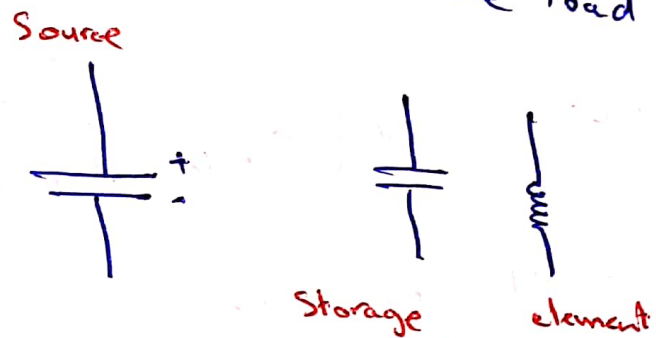controlled rectifier cts can run in the inverter mode if  $\alpha$  is greater than  $90^\circ$  and there is a source in the load



$$V_d = 0.9 V_c \cos \alpha - \frac{2 \omega L_s I_d}{\pi} < 0$$


- ①  $\alpha < 90$
- ② Storage element

\* 3 $\phi$  Phase Converter


$$V_d = 1.35 V_{LL} \cos \alpha \Rightarrow \frac{3\sqrt{2}}{\pi} V_{LL}$$

Line to line value of the input voltage

Ex  $\Rightarrow$  6-3

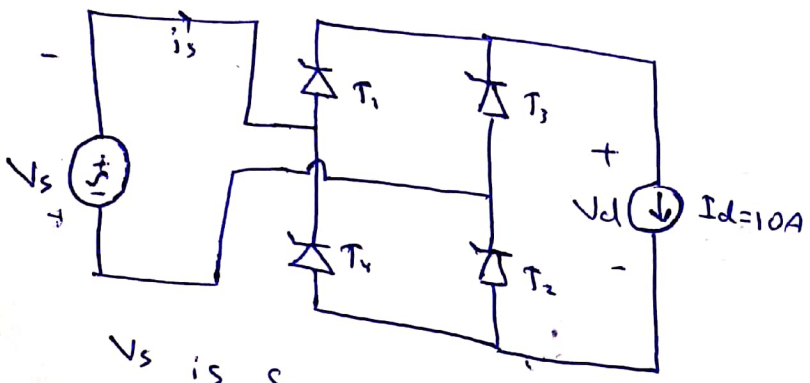

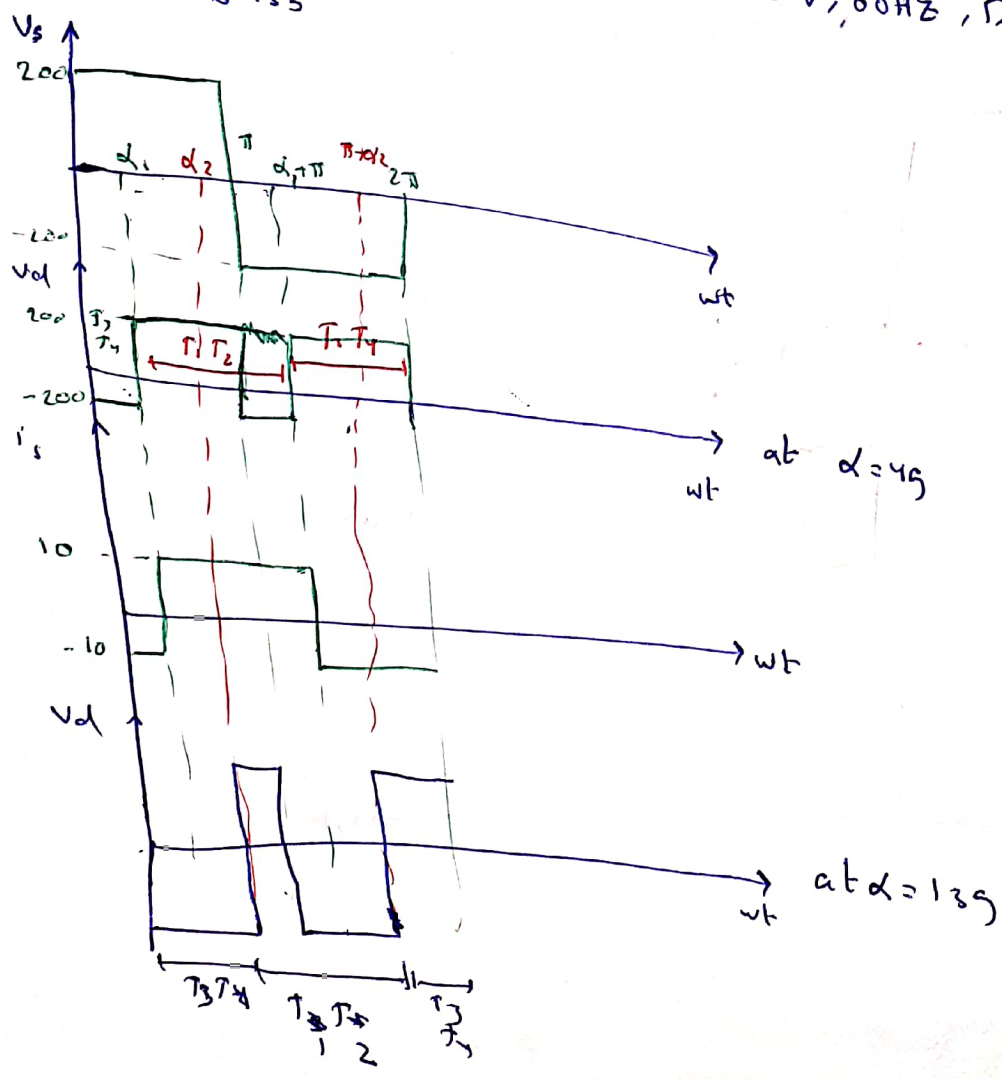$V_s$  is square wave with amplitude of 200V, 60Hz, Draw wave-forms at  $\alpha = 45^\circ$  &  $135^\circ$







$$V_d = \frac{1}{\pi} \left[ \int_{\alpha_1}^{\pi} 200 \sin \theta \, d\theta + \int_{\pi}^{\pi + \alpha_1} -200 \sin \theta \, d\theta \right]$$

$$P_d = V_d I_d = 10 \cdot V_d$$

26

Ex →

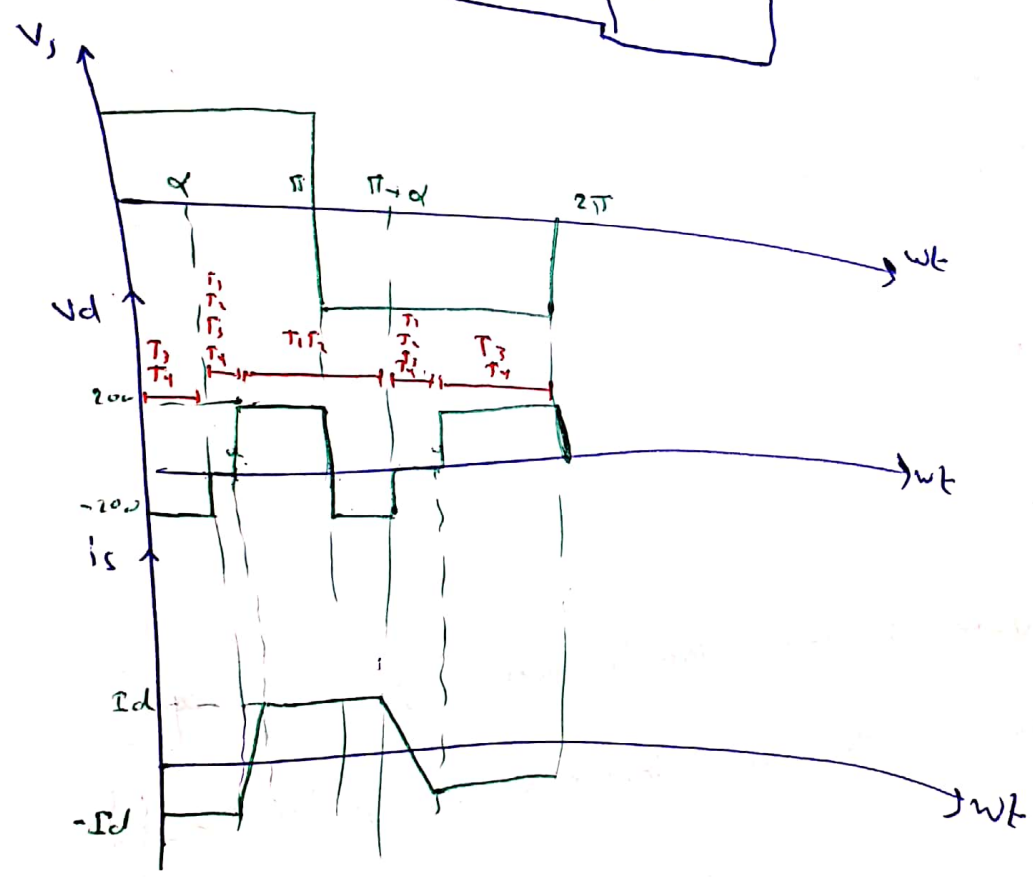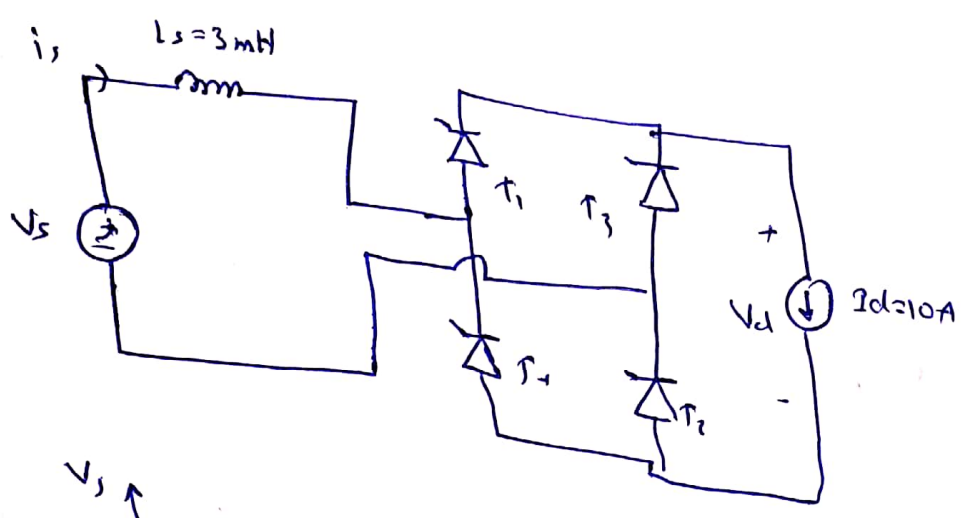

\* During commutation

$$V_L = V_s$$

$$\omega L_s \frac{di_s}{d\omega t} = 200$$

$$\omega L_s \int_{-I_d}^{I_d} di_s = \int_{\alpha}^{\alpha+\mu} 200 d\theta = 2\omega L_s I_d = 200(\alpha+\mu) - 200\alpha \Rightarrow \mu = -0.11 \text{ rad}$$

$$V_d = \frac{1}{\pi} \left[ \int_{\alpha+\mu}^{\pi} 200 d\theta + \int_{\pi}^{\pi+\mu} -200 d\theta \right] = \dots$$

$\mu = 6.3^\circ$

\*  $i_s(t)$  during commutation

$$V_L = V_s$$

$$\omega L_s \left\{ \frac{di_s}{d\omega t} \right\} = 200$$

$$di_s = \frac{1}{\omega L_s} 200 d\theta$$

$$i_s(\theta) = \frac{1}{(377)(3m)} 200 \theta + K_1$$

$$i_s(\theta) = 176.8 \theta + K_1$$

$$i_s\left(\frac{\pi}{2}\right) = -10 = (176.8)\left(\frac{\pi}{2}\right) + K_1$$

$$K_1 = -148$$

$$i_s(\theta) = 176.8 \theta - 148$$

\* Some information

- ① The average value of current through each Thyristor is zero
- ② The rms value of the current through each Thyristor is  $I_d$