

تقدم لجنة EiCoM الاكاديمية

دفتر لمادة:

# الالكترونيات القوي


من شرح:

د. محمد وديان

جزيل الشكر للطالب:

عمر الدغيم



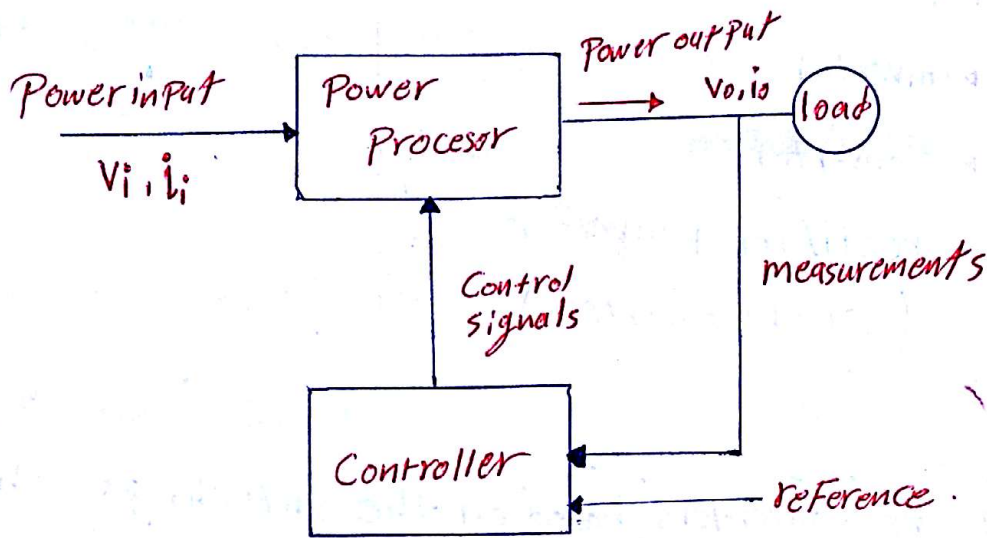

"Block diagram of PE system"


\* Power Processor :-

1. Dc

- a) regulated (constant) magnitude
- b) adjustable (constant) magnitude


2. Ac

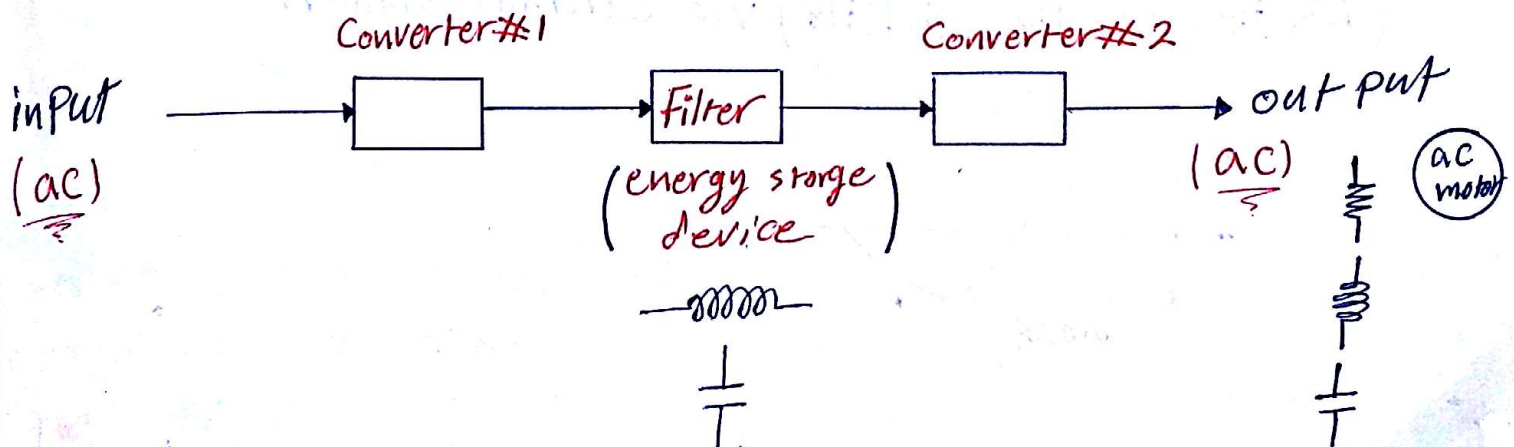- a) constant Frequency adjustable magnitude.
- b) adjustable Frequency adjustable magnitude



\* Power Converters :-

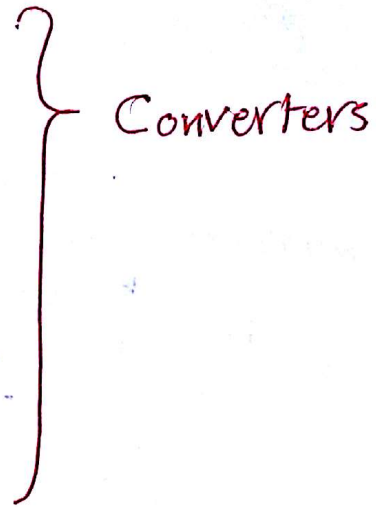
- 1) AC - DC → rectifier
- 2) DC - AC → inverter
- 3) DC - DC → Converter
- 4) AC - AC → rectifier + inverter  
(cycloconverters)



\* Classifications of converters based on the switching scheme of the switches :-

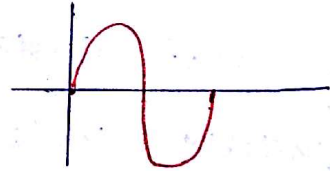
1) Line Frequency (naturally commutated) converters :-

⇒ the switches <sup>Diodes</sup> inside the converter are turned on & off at the line frequency (50 or 60 Hz)



2) Switched (Forced commutated) converters :-

⇒ the switches inside the converter are turned on & off at frequencies much higher than the line frequency (5K Hz, 20K Hz, 25K Hz) via external signals

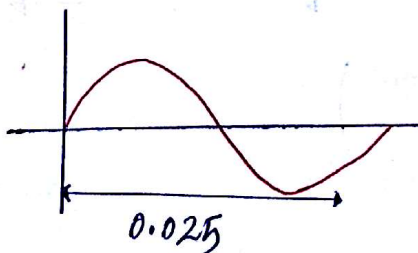


Ch2

\* Overview of Power semiconductor switches

\* According to the degree of controllability:

1. Diodes: on and off by nature of the power supply "uncontrolled"
2. Thyristors: on by the an external signal and off the nature of the power supply ("semi controlled")
3. Controllable switches: on and off by external signals through additional circuits (GTO, BJT, IGBT, MOSFET)

\* Diodes

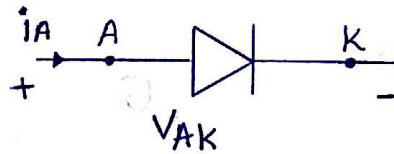

$r_{on}$   $\Rightarrow$  <sup>on</sup> stated device resistance

$$r_{on} = \frac{V_{AK0}}{i_{A0}}$$


$$r_{off} = \frac{-V_{AK0}}{0} \rightarrow \infty$$

$$V_{on} = i_{A0} r_{on}$$

$$P_{on} = (i_{A0})^2 r_{on}$$

PIV  $\equiv V_{rated}$

$1 \times 10^9$  A

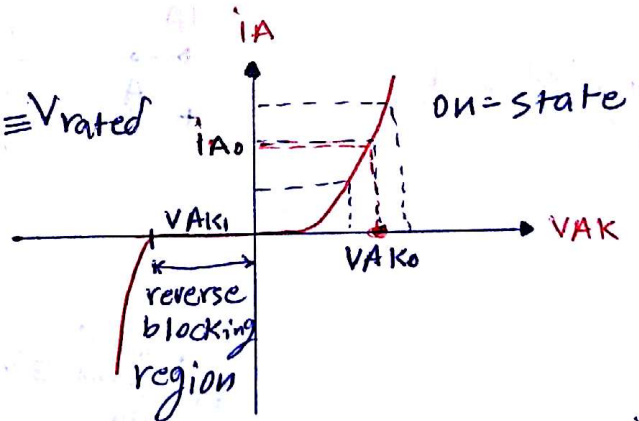

i-v cha of diode (Practical)

$$r_{on} = \frac{0}{i_{A0}} = 0$$


$$r_{off} = \infty$$

$$V_{on} = 0$$


$$V_{off} = r_{off} I_{off} = 0$$

$$P_{on} = 0$$

$$P_{off} = 0$$

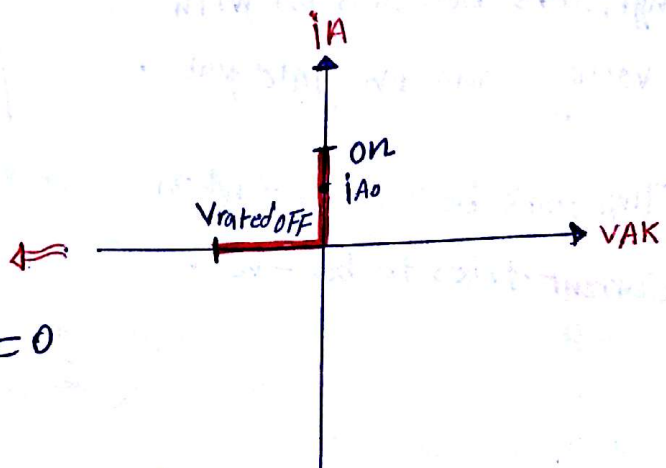

ideal i-v cha

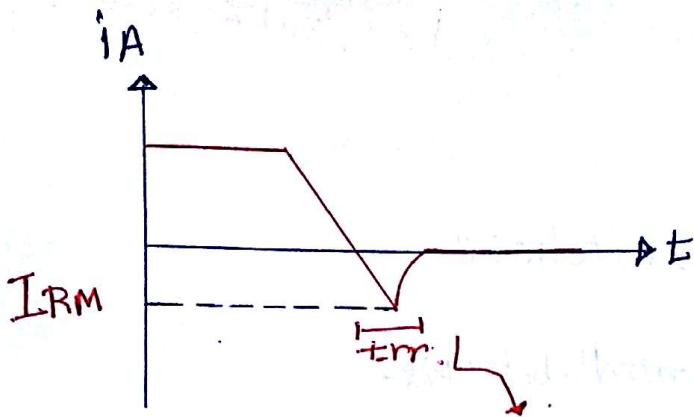



Power Semiconductor diodes

reverse recovering interval

Power Semiconductor Diodes

- 1 Schottky Diodes
- 2 Fast recovering Diodes
- 3 line-Frequency Diodes


Thyristors :-

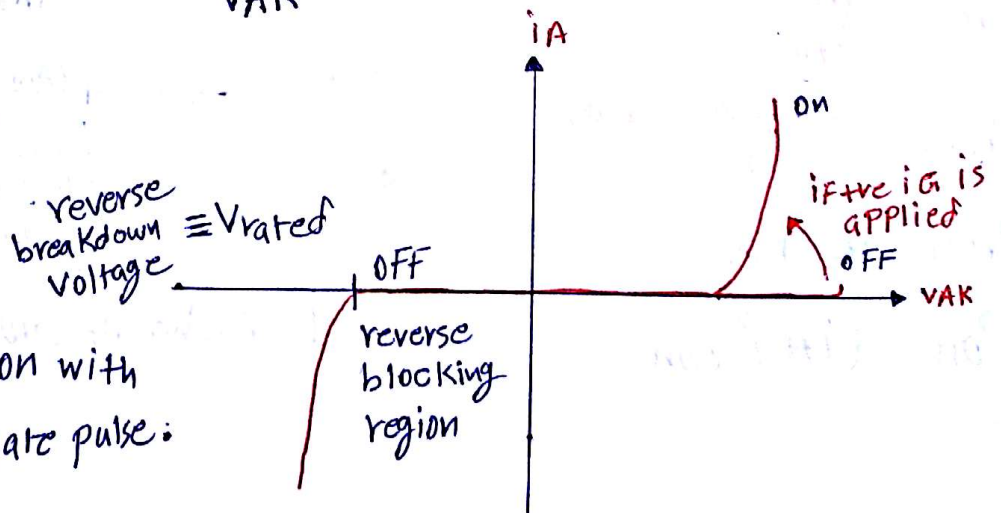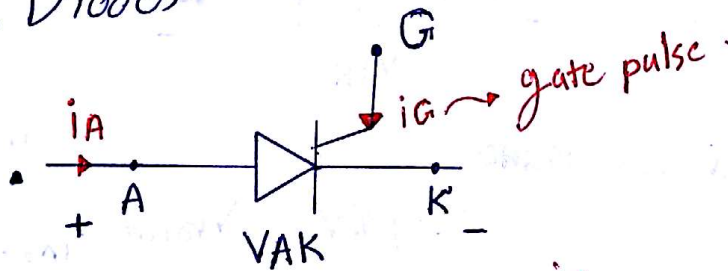

\* the Thyristors becomes ON with +ve voltage and +ve gate pulse.

\* the Thyristors becomes OFF when the current tries to be -ve.



Practical i-v cha

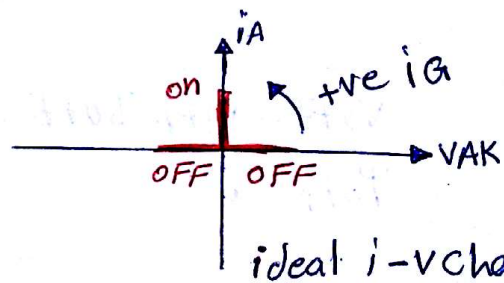

ideal i-v cha


Ex:- Consider the following ckt Draw the waveform of  $(V_s, i_A, V_{AK})$  for triggering pulse at  $t = \frac{T}{4}$  where  $T$  is the period of  $V_s(t)$ ?  
 $(V_s(t) = V_m \sin \omega t \text{ volt})$  --- ?

15

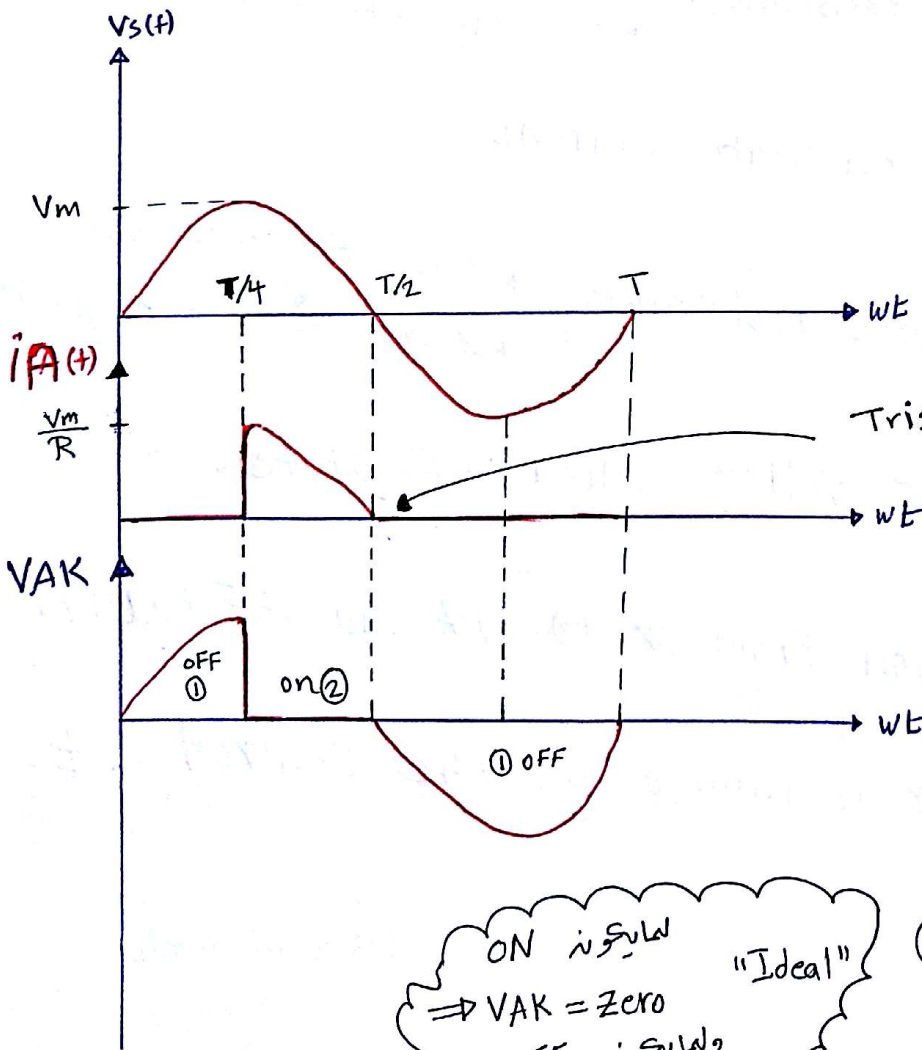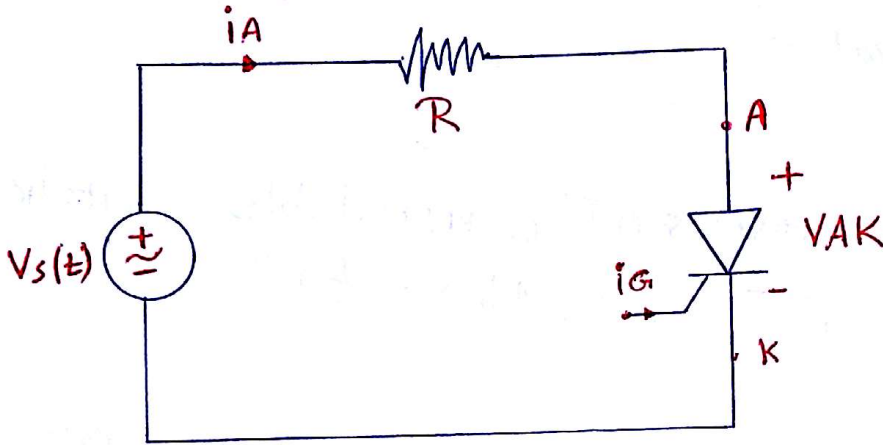

Trise to be -ve  $\Rightarrow$  OFF

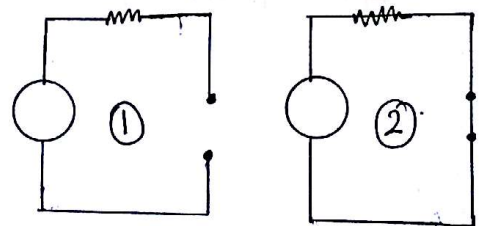ON  $\Rightarrow$   $V_{AK} = \text{Zero}$   
 OFF  $\Rightarrow$   $V_s$  نفس  $\omega t$   
 "Ideal"



12

## \* Types of thyristors :-


- 1] Phase controlled.
- 2] Inverter grade.
- 3] Light activated.

## \* Desired characteristics of Controllable Switches. "BJT, IGBT, GTO, MOSFET"

- \* Zero on state resistance  $\rightarrow$  Zero on-state voltage drop  
 $\rightarrow$  Zero on-state power loss
- \* Conduct a large on state current
- \* infinite OFF-state resistance  $\rightarrow$  Zero OFF-state voltage drop  
 $\rightarrow$  Zero OFF-state power loss
- \* Block a large voltage when OFF-state.
- \* Fast transition from on to OFF and OFF to ON.
- \* Small power consumed by the control ckt.

7

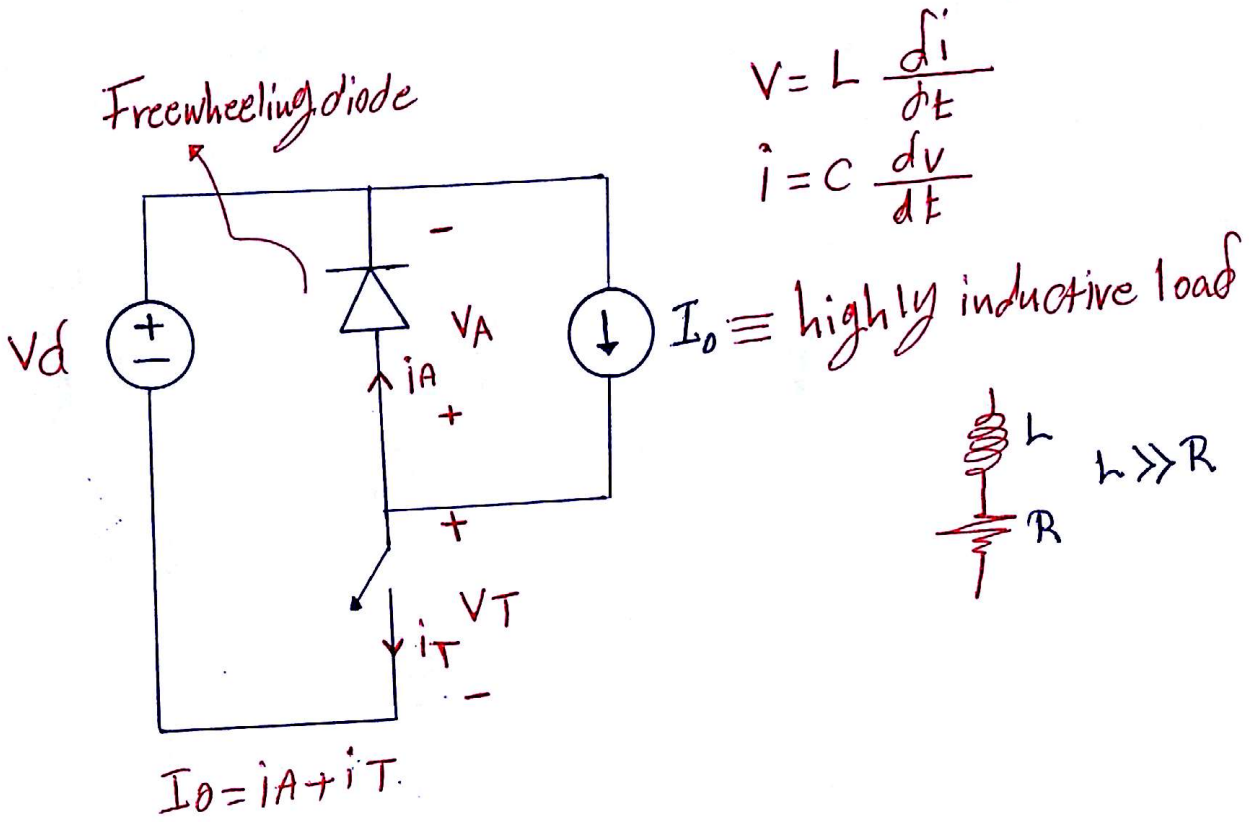\* Consider the following commonly encountered COT in PE systems



\* anti Parallel diode:

- switch on  $\rightarrow$  diode off.  
(-ve) voltage.

- switch off  $\rightarrow$  diode on.

بدأ في التفرغ (وتبقى الجهد  
وتمثل دمولية لـ (-ve) تشغيل (التيود)

$$I_o = i_A + i_T$$





9

$t_d(\text{on})$ : On-state delay time

$t_{ri}$ : rising time for the current

$t_{rf}$ : Falling time for the Voltage

$V_{on}$ : on-state voltage across the switch

$t_d(\text{off})$ : off-state delay time

$t_{rv}$ : rising time for the Voltage

$t_{fi}$ : Falling time for the current

$t_c(\text{on})$ : Crossover on state time

$t_c(\text{off})$ : Crossover off state time

Switch on  $\rightarrow -V\delta + V + V_T = 0$   
 $-V\delta + V + V_{on} = 0$   
 $V = V\delta - V_{on}$

Switch off  $\rightarrow V = 0$

$$-V\delta + V + V_T = 0$$

$$-\frac{\delta V\delta}{\delta t} + \frac{\delta V}{\delta t} + \frac{\delta V_T}{\delta t} = 0$$

$$\frac{\delta V}{\delta t} = -\frac{\delta V_T}{\delta t}$$

$w_c(\text{on})$ : energy dissipated in the switch during the turn-on crossover internal

$w_c(\text{off})$ : energy dissipated in the switch during the turn-off crossover internal.

$$w = \int P(t) \delta t$$

$$w_c(\text{on}) = \frac{1}{2} V\delta I_0 t_c(\text{on})$$

$$w_c(\text{off}) = \frac{1}{2} V\delta I_0 t_c(\text{off})$$

$w_{on}$ : energy dissipated in the switch during the on internal.

$$w_{on} = V_{on} I_0 t_{on}$$

\* Average Switching Power dissipated in the switch.

$$P_s = \frac{1}{2} V \delta I_o f_s [t_c(\text{on}) + t_c(\text{OFF})] \quad [10]$$




$$= \frac{1}{2} V \delta I_o \frac{[t_c(\text{on}) + t_c(\text{OFF})]}{T_s}$$

$$P_s = \frac{1}{T_s} \int_0^{T_s} v(t) i(t) dt$$

$$P_{\text{on}} = \frac{V_{\text{on}} I_o t_{\text{on}}}{T_s} \equiv \text{average on state power in the switch}$$

$$P_{\text{tot}} = P_s + P_{\text{on}}$$




\* BJT :-

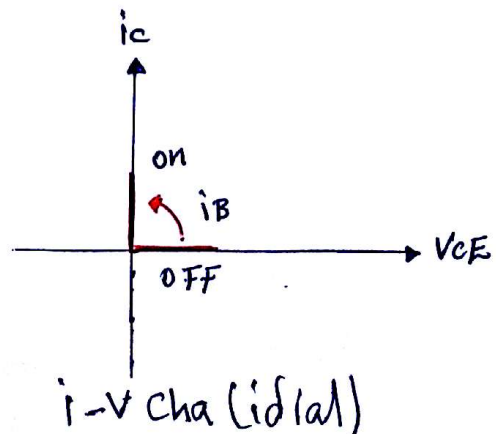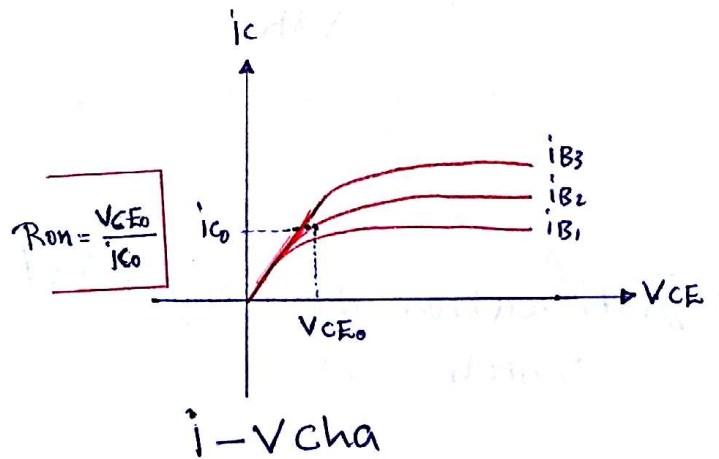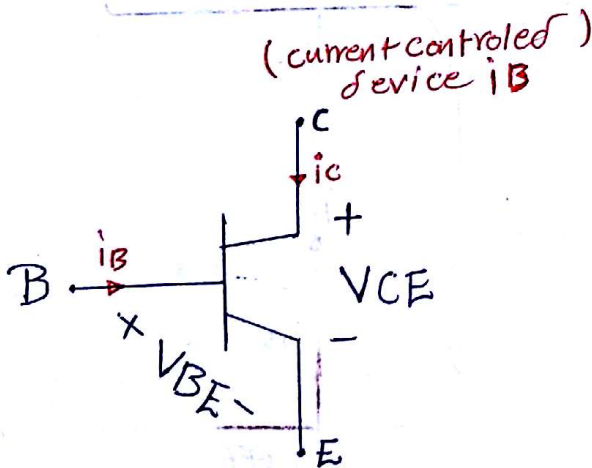



\* MOSFET :-

III


Voltage Controlled Device (VGS)

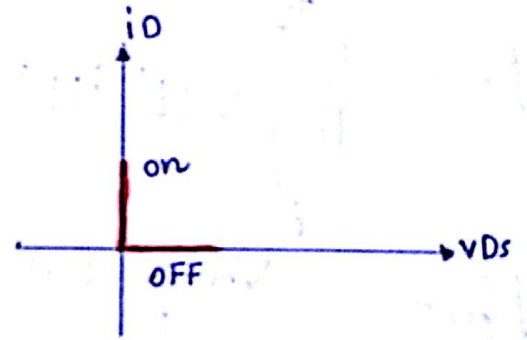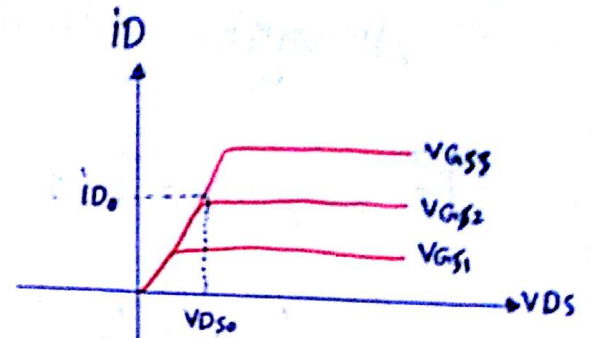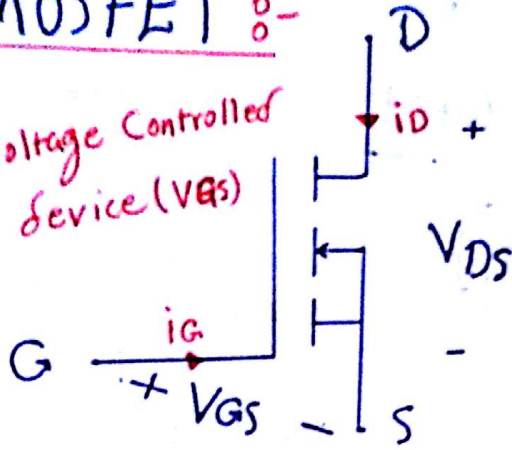

\* GTO :-

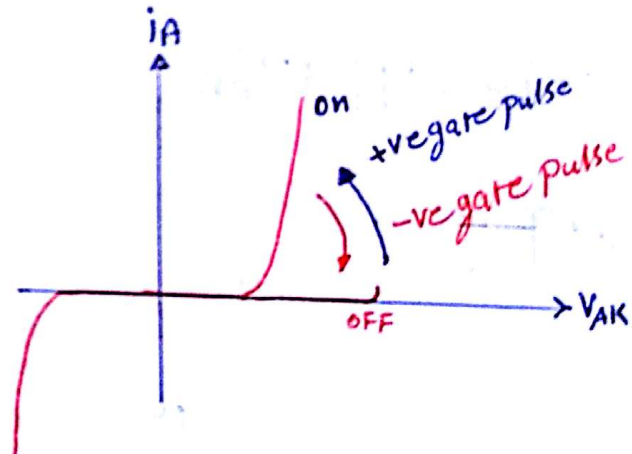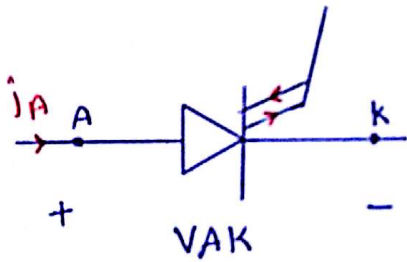

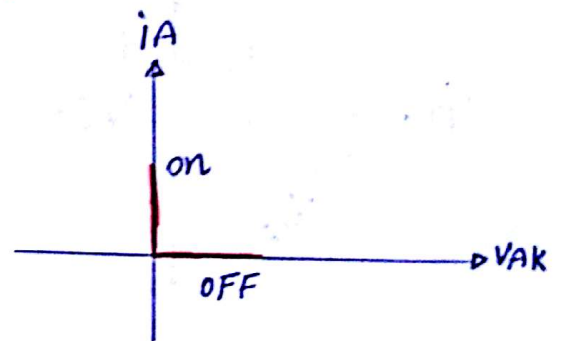\* Justifications OF using ideal switch cha



112

Exo- 2-1

$t_{ri} = 100\text{ns}$     $t_{FV} = 50\text{ns}$     $t_{rV} = 100\text{ns}$     $t_{Fi} = 200\text{ns}$     $V\delta = 300\text{V}$

Sol<sup>o</sup> -  $I_0 = 4\text{A}$   
 average switching Power losses

→ Calculate  $P_s$  as fn of  $F$  ( $f_s$ ) in the range of (25-100) KHz? ↓ switching Freq

$$P_s = \frac{1}{2} V\delta I_0 f_s [t_c(\text{on}) + t_c(\text{OFF})]$$

$$t_c(\text{on}) = t_{ri} + t_{FV} = 150\text{ns}$$


$$t_c(\text{OFF}) = t_{rV} + t_{Fi} = 300\text{ns}$$

$$P_s = 2.7 \times 10^{-4} f_s$$

$$f_s = 25 - 100 \text{ KHz}$$

$$P_s |_{f_s = 25 \text{ KHz}} = 6.75 \text{ W}$$

$$P |_{f_s = 100 \text{ KHz}} = 27 \text{ W}$$

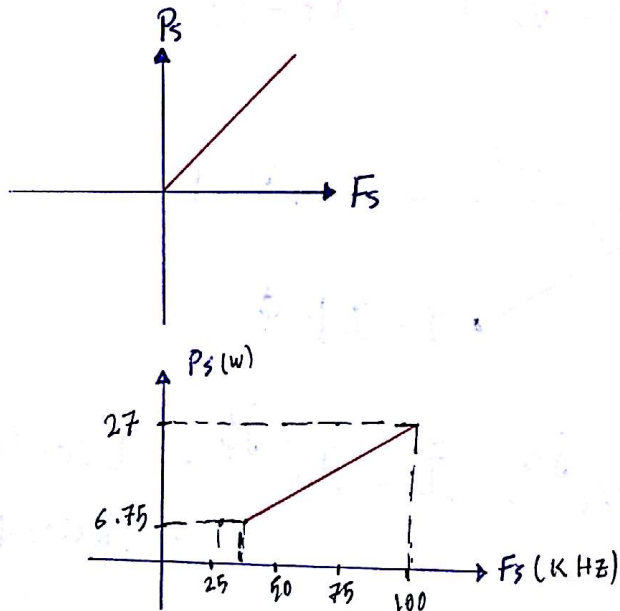

\* Review of Basic Electrical Circuits Concepts.

\* Average Power and RMS Current

$$P(t) = v(t) \cdot i(t)$$


$$P = \frac{1}{T} \int_0^T P(t) dt = \frac{1}{T} \int_0^T v(t) i(t) dt$$

For Pure resistive load.

$$P = \frac{1}{T} \int_0^T i^2 R dt = \frac{R}{T} \int_0^T (i(t))^2 dt$$

$$= RI^2 \Rightarrow I = \sqrt{\frac{1}{T} \int_0^T (i(t))^2 dt} \Rightarrow \text{"rms current"}$$


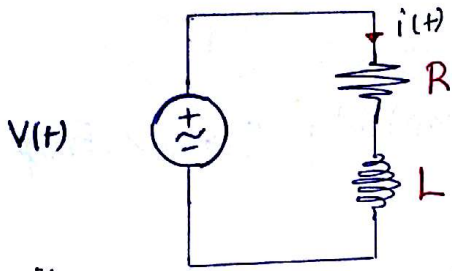
\* Steady-State ac waveforms with sinusoidal voltages and currents.



(( لازم يكون ال V(t) و I(t) نفس Freq نفس Period ))

$$V(t) = \sqrt{2} V \cos \omega t$$
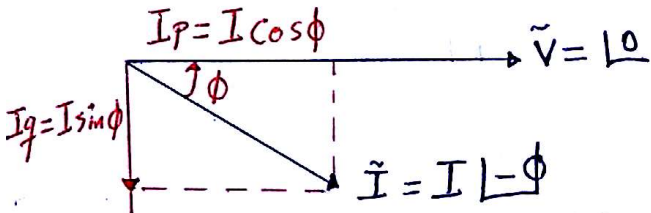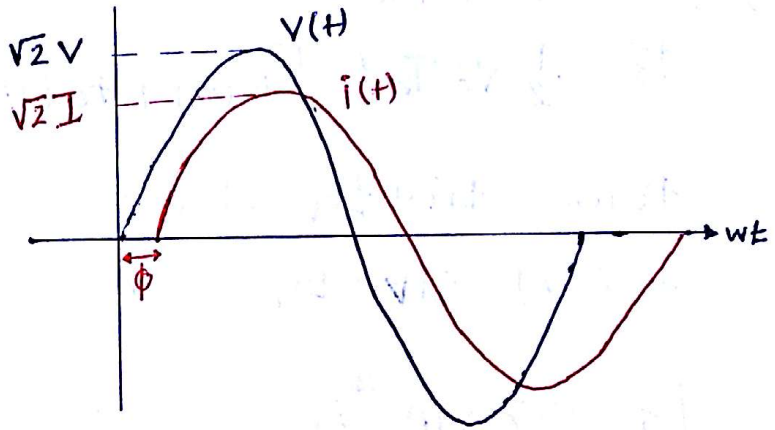
$$i(t) = \sqrt{2} I \cos(\omega t - \phi)$$



$$\tilde{V} = V e^{j0}, \quad \tilde{I} = I e^{-j\phi} = I \cos(-\phi) + j I \sin(-\phi) = I \cos \phi - j I \sin \phi$$

rectangular


$$\Rightarrow V \cos 0 + V \sin 0$$

$$\tilde{Z} = \frac{\tilde{V}}{\tilde{I}} = \frac{V \angle 0}{I \angle -\phi} = \frac{V}{I} \angle \phi = Z \angle \phi$$

$$\tilde{S} = \tilde{V} \tilde{I}^* \rightsquigarrow \text{Complex Power}$$

$$= V \angle 0 (I \angle \phi)$$
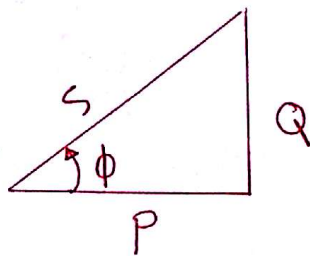
$$= V I \angle \phi = \underbrace{V I \cos \phi}_{\text{active Power}} + j \underbrace{V I \sin \phi}_{\text{reactive Power}}$$



$$i(t) = i_p(t) + i_q(t)$$


$$= (\sqrt{2} I \cos \phi) \cos \omega t + (\sqrt{2} I \sin \phi) \sin \omega t$$

$$PF = \cos \phi$$

$$= \cos \left[ \cos^{-1} \frac{P}{S} \right]$$

$$= \frac{P}{S}$$
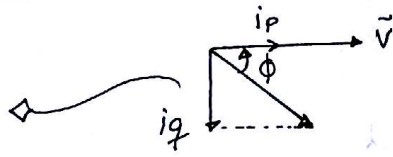
$$= \cos \left[ \sin^{-1} \frac{Q}{S} \right]$$



PF is unity ( $PF=1$ )  $\rightarrow$  R

PF is lagging  $\rightarrow$  RL

PF is leading  $\rightarrow$  RC

Exe-

before C


$$PF = \frac{P}{S} = \frac{1000}{S} = 0.8$$

$$S = 1250 \text{ VA}$$

$$Q = \sqrt{S^2 - P^2} = 750 \text{ VAR}$$

$$\tilde{S} = 1000 + j 750 \text{ VA}$$

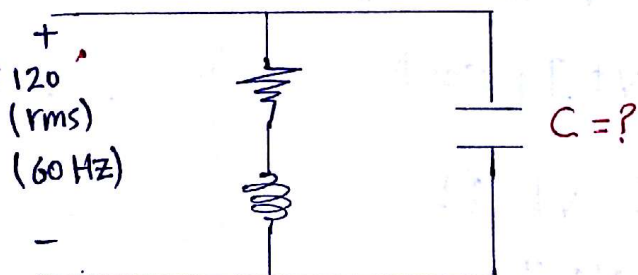$X_C = \frac{1}{\omega C}$
$\omega = 2\pi f$



$P = 1000 \text{ W}$   $0.8 \text{ PF lag}$

$PF = 0.95 \text{ lagging}$

with C

$$0.95 = \frac{P}{S_{\text{new}}} = \frac{1000}{S_{\text{new}}}$$

$$0.95 = \frac{1000}{\sqrt{P^2 + (750 - Q_C)^2}} \rightarrow Q_{\text{new}}$$

$$Q_C = 421.3 \text{ VAR}$$


$$Q_C = \frac{V^2}{X_C} = \frac{V^2}{\frac{1}{\omega C}}$$

$$421.3 = \omega C V^2 = (377) C (120)^2$$

$$C = 77.6 \mu\text{F}$$

# \* Three-Phase Circuits


15

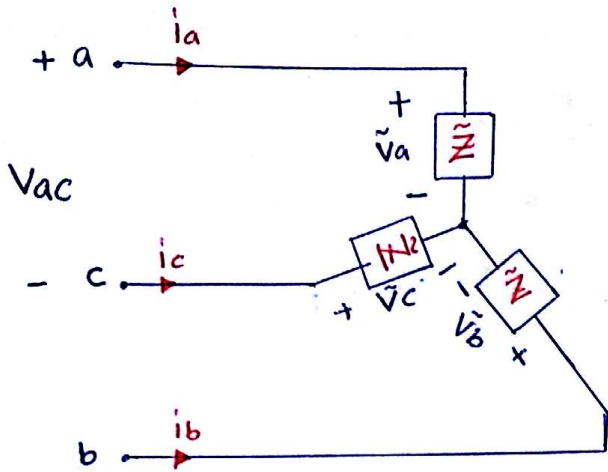

$$\tilde{I}_a = \frac{\tilde{V}_a}{Z} = \frac{V e^{j0}}{Z e^{j\phi}} = \frac{V}{Z} e^{-j\phi}$$

$$\tilde{I}_b = \frac{V}{Z} e^{-j(\phi + 120^\circ)}$$
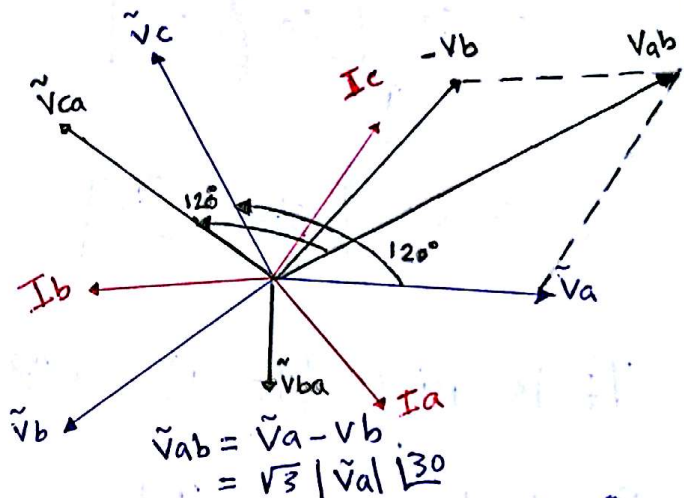
$$\tilde{I}_c = \frac{V}{Z} e^{-j(\phi - 120^\circ)}$$



\* line voltage leads the phase voltage by  $30^\circ + \phi$   
 $V_{LL} = \sqrt{3} V_\phi$

$\Delta$  or  $Y$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$= 3 V_\phi I_\phi \cos \phi$$

$$S = \sqrt{3} V_L I_L$$

$$= 3 V_\phi I_\phi$$

$$Q = \sqrt{3} V_L I_L \sin \phi$$

$$= 3 V_\phi I_\phi \sin \phi$$

$$P_{3-\phi} = 3 P_\phi$$

$$Q_{3-\phi} = 3 Q_\phi$$

$$S_{3-\phi} = 3 S_\phi$$



\* NONsinusoidal waveForm in steady state.

\* The steady state voltage and currents in power electronic systems are normally periodic but not sinusoidal

\* Fouries Analysis OF Repetitive waveForms

\* IF  $f(t)$  is periodic and nonsinusoidal, than

$$f(t) = F_0 + \sum_{h=1}^{\infty} f_h(t) = \frac{1}{2} a_0 + \sum_{h=1}^{\infty} \left\{ a_h \cos(h\omega t) + b_h \sin(h\omega t) \right\}$$

$$F_0 = \frac{1}{2} a_0 \Rightarrow \text{average value of } f(t)$$

$$\rightarrow a_h = \frac{1}{\pi} \int_0^{2\pi} f(t) \cos(h\omega t) d\omega t, \quad h=0, \dots, \infty$$

$$\rightarrow b_h = \frac{1}{\pi} \int_0^{2\pi} f(t) \sin(h\omega t) d\omega t, \quad h=1, \dots, \infty$$


$$F_0 = \frac{1}{2} a_0 = \frac{1}{2\pi} \int_0^{2\pi} f(t) \frac{d\omega t}{d\theta} \Rightarrow \text{average value}$$

$$F_0 = \frac{1}{T} \int_0^T f(t) dt$$

$$* F = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} [f(t)]^2 d\omega t} \Rightarrow \text{rms value of } f(t)$$

$$= \sqrt{F_0^2 + F_1^2 + \dots + F_{\infty}^2}$$

## \* Line Current Distortion

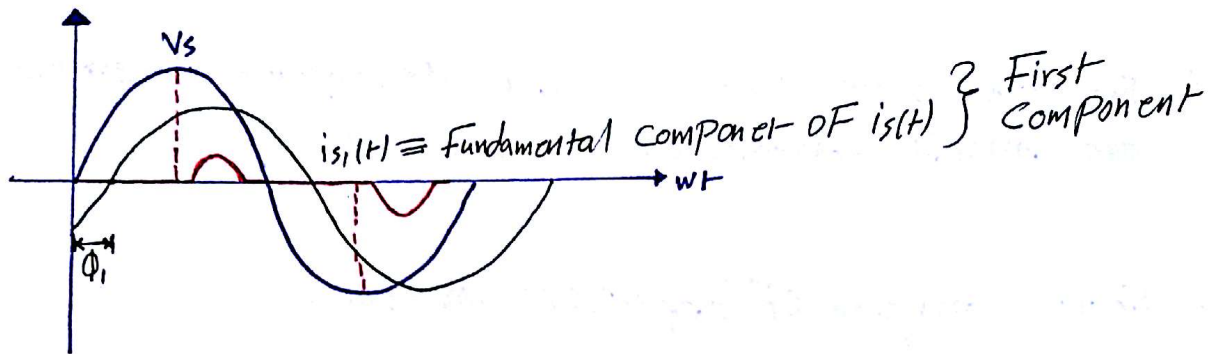

$$V_s(t) = \sqrt{2} V \sin \omega_1 t$$

$$i_s(t) = \underbrace{i_{s1}(t)}_{\text{Fundamental Component}} + \sum_{h \neq 1} \underbrace{i_{sh}(t)}_{\text{harmonic Component}}$$

$$i_s(t) = \sqrt{2} \underbrace{I_{s1}}_{\text{rms value of the Fundamental Component}} \sin(\omega_1 t - \phi_1) + \sum_{h \neq 1}^{\infty} \sqrt{2} \underbrace{I_{sh}}_{\text{rms value of the harmonic Component}} \sin(\omega_h t - \phi_n)$$

$\omega_h t = h \omega t$

\* THD: Total Harmonic Distortion.

$$\text{THD}\% = \frac{\sqrt{I_s^2 - I_{s1}^2}}{I_{s1}} \times 100$$

$\Rightarrow$  indicates how far the signal from sine wave

## \* Power and Power Factor

$$P = \frac{1}{T_1} \int_0^{T_1} P(t) dt$$

$$= \frac{1}{T_1} \int_0^{T_1} v_s(t) i_s(t) dt$$

$$= \frac{1}{T_1} \left[ \int_0^{T_1} [\sqrt{2} V_s \sin \omega_1 t] \left[ \sqrt{2} I_{s1} \sin(\omega_1 t - \phi_1) + \sum_{h \neq 1}^{\infty} \sqrt{2} I_{sh} \sin(\omega_h t - \phi_h) \right] dt \right]$$

$$\Rightarrow \boxed{P = V_s I_{s1} \cos \phi_1} \rightarrow \text{Calculation From the AC Variables}$$

$\Rightarrow$  IF the voltage is sinusoidal and the current not sinusoidal then current component at harmonic freqs do not contribute to the average value of the power

$$S = V_s I_s$$

$$PF = \frac{P}{S} = \frac{V_s I_{s1} \cos \phi_1}{V_s I_s}$$


$$= \frac{I_{s1}}{I_s} \cos \phi_1$$

$$DPF = \cos \phi_1 \Rightarrow \text{Displacement PF}$$



# \* Inductor and Capacitor Responses.

19


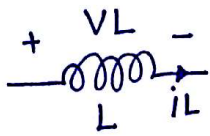


$$V_L = L \frac{di_L}{dt}$$

$$i_L = \frac{1}{L} \int V_L(t) dt + K$$

IF Pure sine waves:-

$$\tilde{V}_L = j\omega L \tilde{I}_L$$

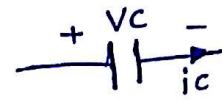
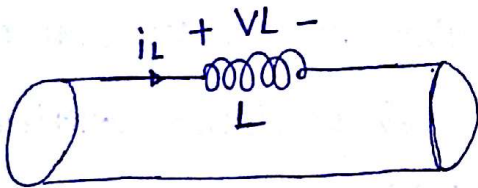


$$i_c = C \frac{dV_c}{dt}$$

$$V_c(t) = \frac{1}{C} \int i_c(t) dt + K$$


IF pure sine waves:-

$$\tilde{I}_c = j\omega C \tilde{V}_c$$

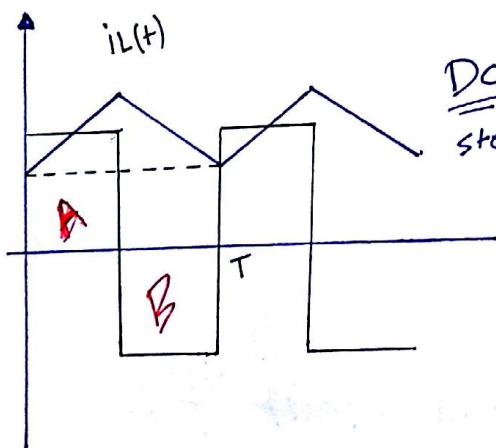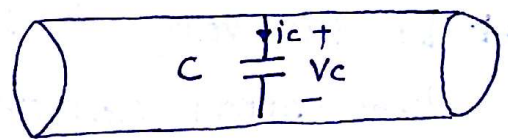

DC steady-state DC waveform

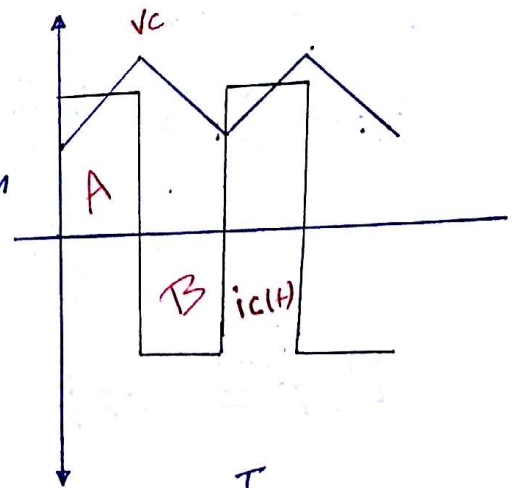
$$V_L = \frac{1}{T} \int_0^T V_L(t) dt = 0 \quad \underline{\underline{A=B}}$$




$$I_c = \frac{1}{T} \int_0^T i_c(t) dt = 0$$



3-6

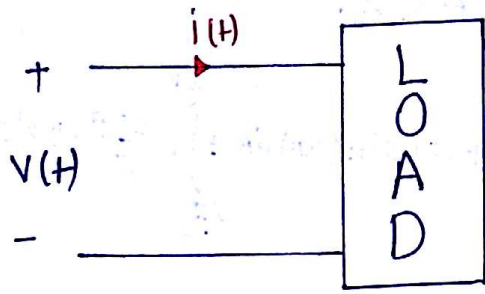

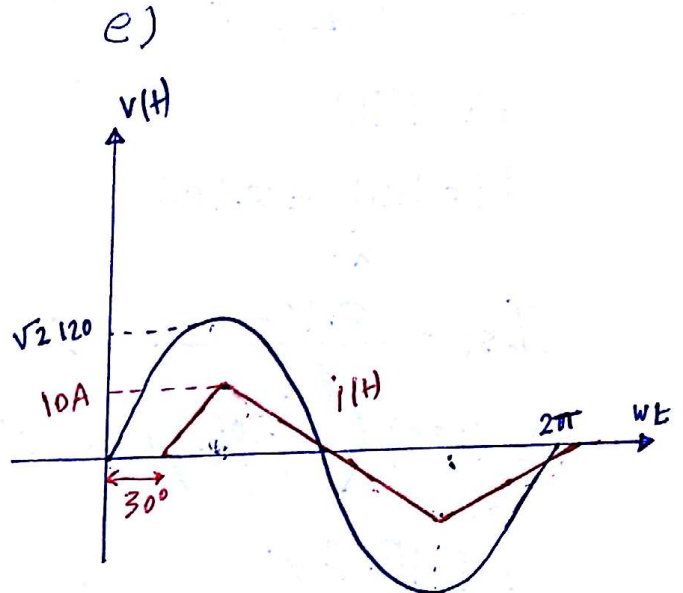- \*  $V(t) = \sqrt{2} V \sin \omega t$
- \*  $i(t) \Rightarrow$  is a triangular wave
- \* With amplitude of 10A
- \*  $i(t)$  lags  $V(t)$  by  $30^\circ$




Find  $\Rightarrow$  P, THD, PF, DPF?

$$P = V I_{s1} \cos \phi$$

\*  $i(t)$  is symmetric on the x-axis

$$a_h = 0, \quad h = 2, 4, 6, \dots, \infty$$
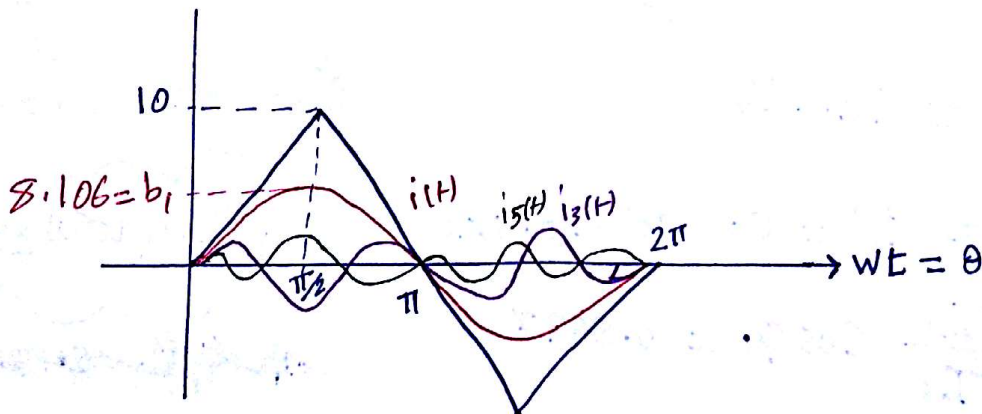
$$b_h = \frac{1}{\pi} \int_0^{2\pi} i(t) \sin(h\omega t) d\omega t$$



$$i(\theta) = \begin{cases} \frac{20}{\pi} \theta & 0 < \theta < \frac{\pi}{2} \\ -\frac{20}{\pi} \theta + 20 & \frac{\pi}{2} < \theta < \frac{3\pi}{2} \\ \frac{20}{\pi} \theta - 40 & \frac{3\pi}{2} < \theta < 2\pi \end{cases} \quad [21]$$

$$b_h = \frac{1}{\pi} \left[ \int_0^{\frac{\pi}{2}} \frac{20\theta}{\pi} \sin(h\theta) d\theta + \int_{\frac{\pi}{2}}^{\frac{3\pi}{2}} \left( -\frac{20\theta}{\pi} + 20 \right) \sin(h\theta) d\theta + \int_{\frac{3\pi}{2}}^{2\pi} \left( \frac{20\theta}{\pi} - 40 \right) \sin(h\theta) d\theta \right]$$

$$b_h = F(h)$$

$$b_1 = b_h \Big|_{h=1} = 8.106$$

$$I_{s1} = \frac{8.106}{\sqrt{2}} = 5.7318 \text{ A rms}$$

$$P = (120) \left( \frac{8.106}{\sqrt{2}} \right) \cos 30^\circ$$

$$= 595.7 \text{ W}$$

$$\text{THD}\% = \frac{\sqrt{I_s^2 - I_{s1}^2}}{I_{s1}} \times 100$$

$$I_s = \sqrt{\frac{1}{2\pi} \left[ \int_0^{\frac{\pi}{2}} \left( \frac{20\theta}{\pi} \right)^2 d\theta + \int_{\frac{\pi}{2}}^{\frac{3\pi}{2}} \left( -\frac{20\theta}{\pi} + 20 \right)^2 d\theta + \int_{\frac{3\pi}{2}}^{2\pi} \left( \frac{20\theta}{\pi} - 40 \right)^2 d\theta \right]}$$

$$= 5.7736 \text{ A}$$

$$\text{THD}\% = \frac{\sqrt{(5.7736)^2 - \left( \frac{8.106}{\sqrt{2}} \right)^2}}{\frac{8.106}{\sqrt{2}}} \times 100$$

$$= 12.1\%$$

$$\text{DPF} = \cos(\phi_1) = \cos(30) = 0.866$$

$$\text{PF} = \frac{I_{s1}}{I_s} \cos \phi_1 = 0.8597$$

\* ارجع لكتاب ص 59

$$I_{s1} = \frac{8.106}{\sqrt{2}} = 5.7318$$

$$I_s = \frac{10}{\sqrt{2}} = 5.7736$$

# \* Matlab :-

22

①

» syms a x

$$\int a \sin x dx$$

» A = int(a \* sin(x), x)

$$A = -a * \cos(x)$$

» B = int(a \* sin(x), a)

$$B = \frac{1}{2} * a^2 * \sin x$$

» C = subs(A, x, (pi/2))

$$C = 0$$

» D = subs(B, a, 2)

$$D = 2 * \sin(x)$$

②

» syms x

» F = exp(x);

» E = int(F, x, 1, 4)

$$E = \dots$$

$$F(x) = e^x$$
$$\int_1^4 e^x dx$$

int :- integration

subs :- substitute

③

» syms a x

» R = a^2 \* exp(x);

» Q = int(R, x, 1, 2)

$$Q = a^2 * \exp(2) - a^2 * \exp(1)$$

» Q1 = vpa(Q, 5)

$$Q_1 = 4.6708 * a^2$$

$$\int_1^2 a^2 e^x dx$$

23

$$b_h = \frac{1}{\pi} \left[ \underbrace{\int_0^{\frac{\pi}{2}} \frac{20\theta}{\pi} \sin(h\theta) d\theta}_{A_1} + \underbrace{\int_{\frac{\pi}{2}}^{\frac{3\pi}{2}} \left( \frac{-20\theta}{\pi} + 20 \right) \sin(h\theta) d\theta}_{A_2} + \underbrace{\int_{\frac{3\pi}{2}}^{2\pi} \left( \frac{20\theta}{\pi} - 40 \right) \sin(h\theta) d\theta}_{A_3} \right]$$

» Syms h th → 0

$$\gg A_1 = \text{int} \left( \left( \frac{20 * th}{\pi} \right) * \sin(h * th), th, 0, (\pi / 2); \right]$$

$$\gg A_2 = \text{int} \left( \left( \frac{-20 * th}{\pi} + 20 \right) * \sin(h * th), th, (\pi / 2), (3 * \pi / 2); \right]$$

$$\gg A_3 = \text{int}$$

$$\gg b_h = (1 / \pi) * (A_1 + A_2 + A_3)]$$

»

$$\gg b1 = \text{subs}(b_h, h, 1)$$

$$b1 = \dots$$

$$\gg b1 = \text{vpa}(b1, 6)]$$

$$\gg b2 = \text{subs}(b_h, h, 2)$$

$$\gg b2 = 1.6 * 10^{-16}$$






\* Line Frequency Diode Rectifiers

✓ Line Frequency ac → uncontrolled dc

line Frequency  $\equiv$  50 or 60 Hz


Rectifiers  $\phi$  - circuits which change from ac into dc

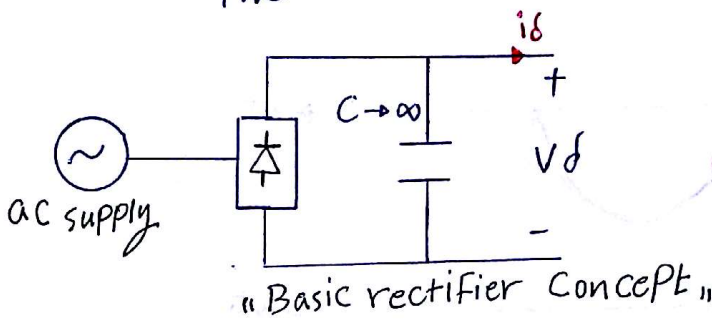UNcontrolled  $\phi$  - the devices are turned on & off by the nature of the power supply.




\* Basic Rectifier concepts  $\phi$  -

II Pure resistive load:-

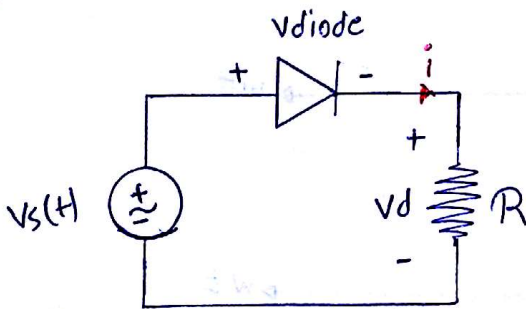


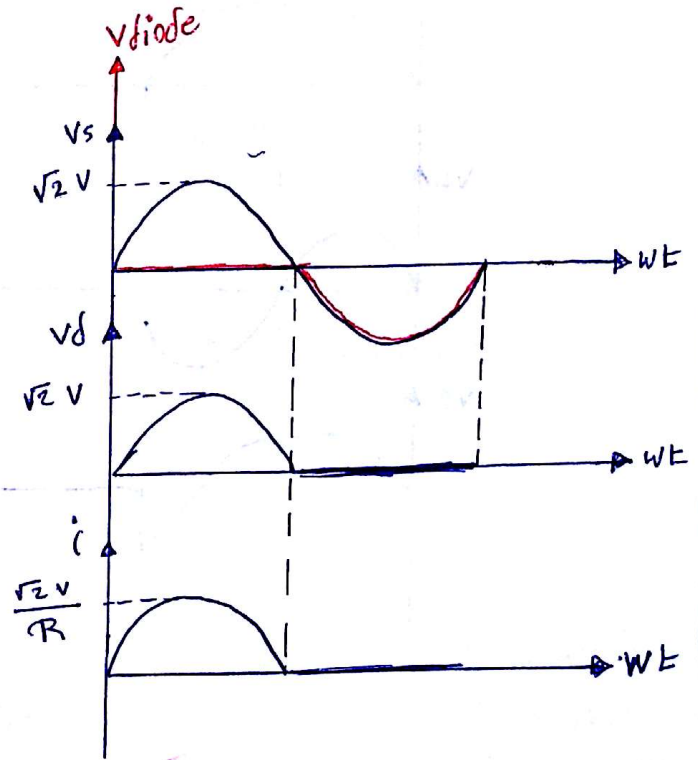half-wave uncontrolled rectifier circuit with pure resistive load



## 2 Inductive load:-


25

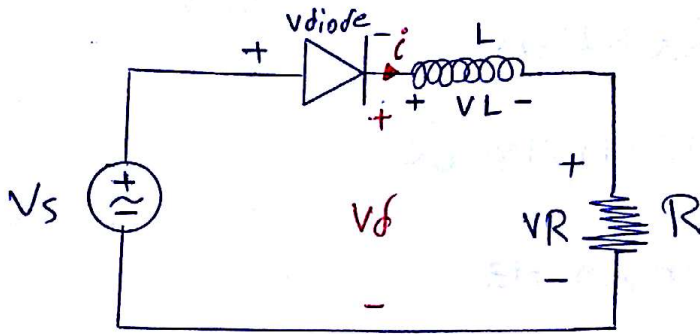

$$-v_s(t) + L \frac{di}{dt} + Ri = 0$$


$$L \frac{di}{dt} + Ri = \sqrt{2} V \sin \omega t$$

$$i(t) = \dots$$

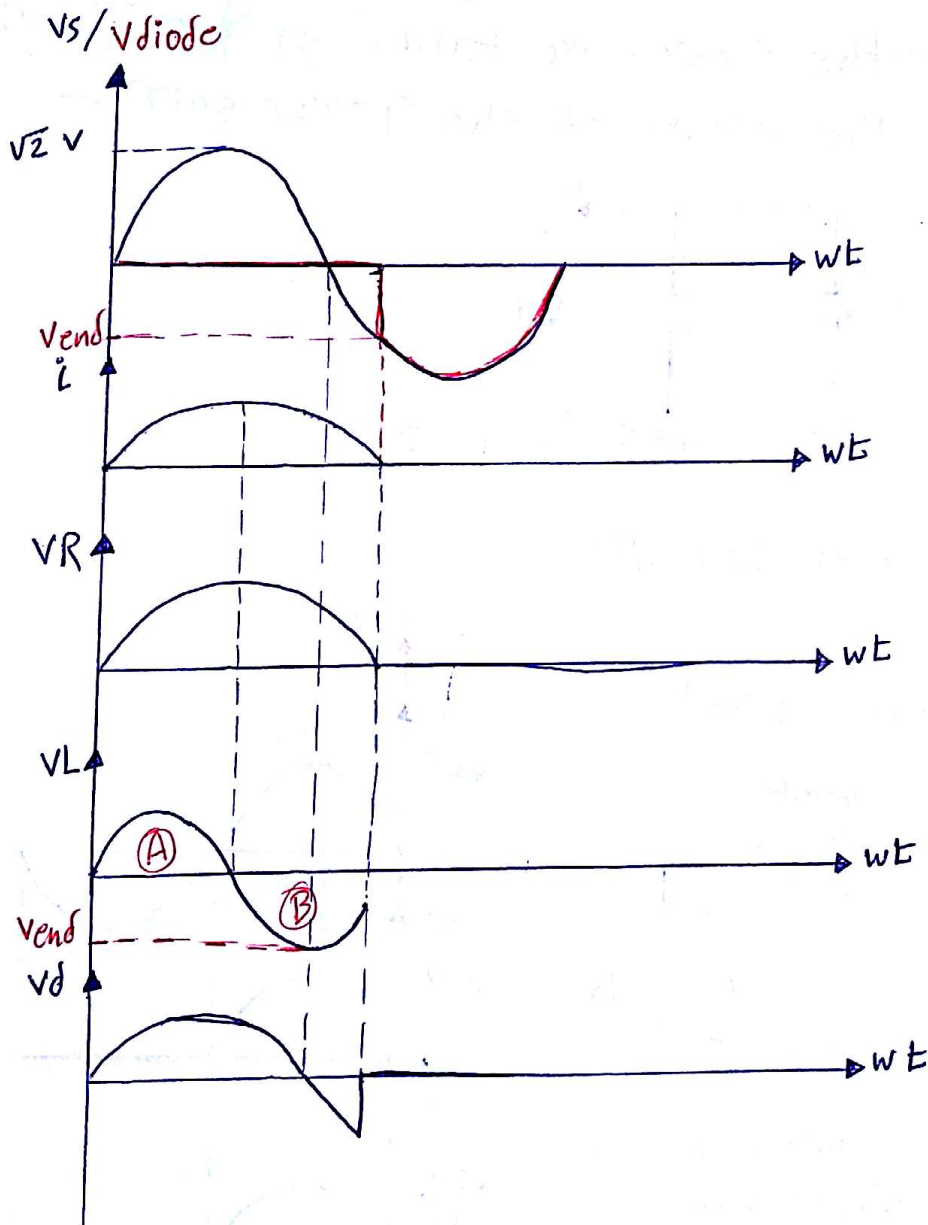

### 3 Load with internal dc voltage:-

26


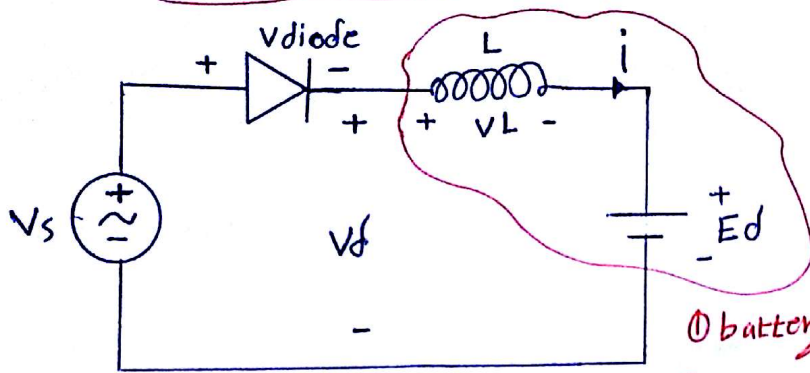


$$-v_s(t) + L \frac{di}{dt} + Ed = 0$$

$$L \frac{di}{dt} = \sqrt{2} V_s \sin \omega t - Ed$$

$$\omega L \frac{di}{d\omega t} = \sqrt{2} \sin \omega t - Ed$$
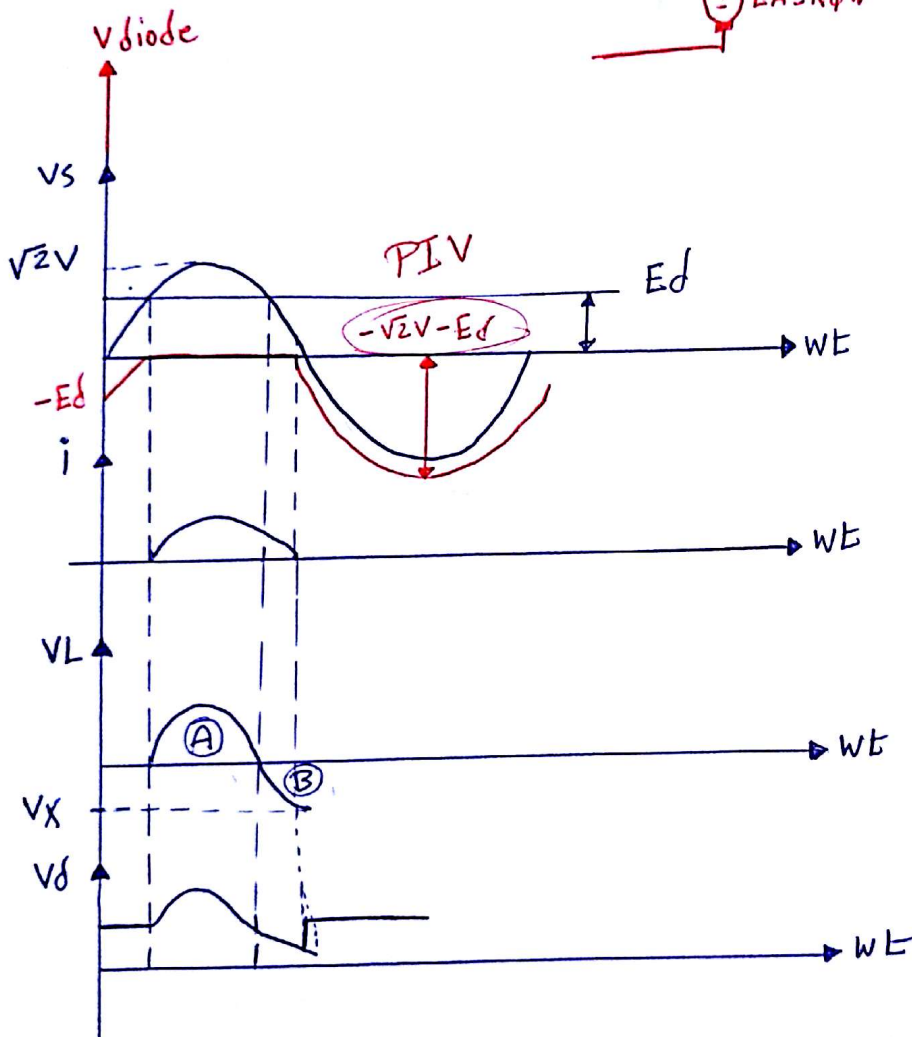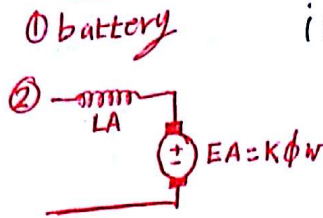
$$i(t) = \left( \frac{1}{\omega L} \right) \int (\sqrt{2} V_s \sin \omega t - Ed) d\omega t + K$$



\*  $v_d = v_s$  if the diode is "ON"

\*  $v_d = E_d$  if the diode is "OFF"

$$-v_s + v_{diode} + v_L + E_d = 0$$

$$v_{diode} = v_s - E_d$$

لعونه القيرست  
1/3/2017  
وقت الحاضرة

\* Power elec

22/2/2017 5:01


27

30mar


AL. Dghelm

\* Single - Phase Diode Bridge Rectifiers -

\* Idealized case ( $L_s = 0$ )

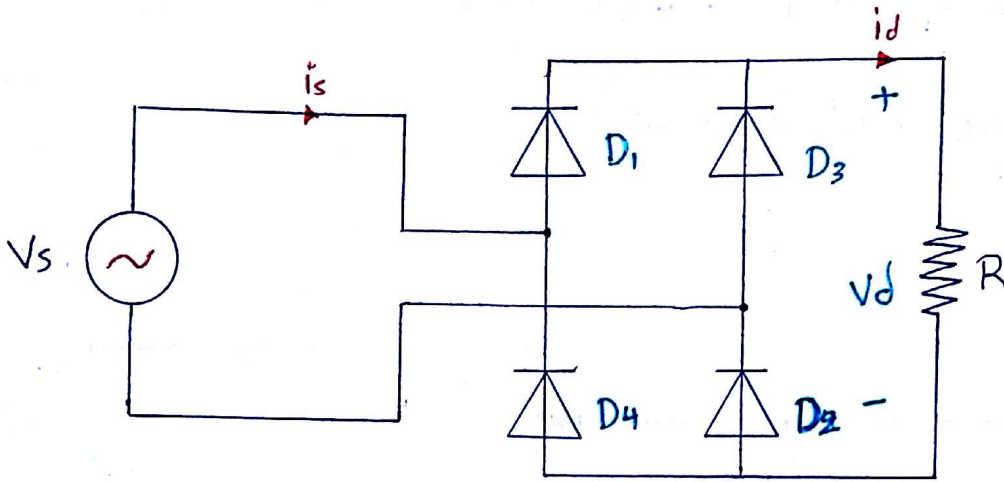


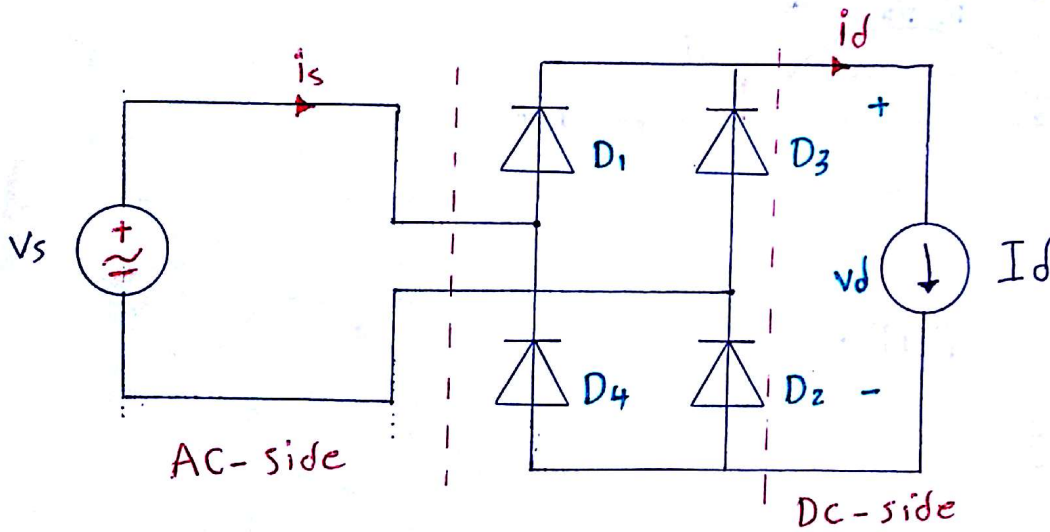Source inductance  
Full-wave uncontrolled rectifier  
Circuit with pure resistive load and zero source inductance



highly inductive load like DC motor

II Pure Resistive Load without  $L_s$  -

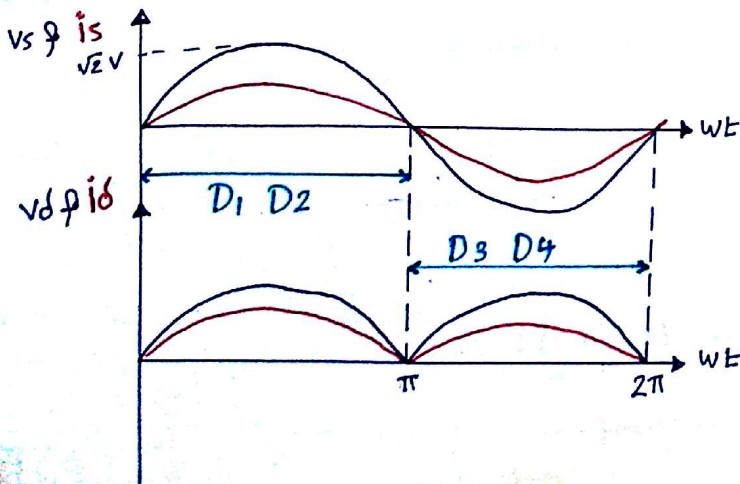


28

$$V_d = \frac{1}{2\pi} \int_0^{2\pi} V_d(t) \cdot d\omega t = \frac{2}{2\pi} \int_0^{\pi} \sqrt{2} V \sin \omega t \, d\omega t = 0.9 V$$

$$I_d = \frac{0.9 V}{R}$$

$$P_d = V_d I_d = 0.81 \frac{V^2}{R} = P_s = I_{s1} V \cos(\theta) = I_{s1}^2 R$$

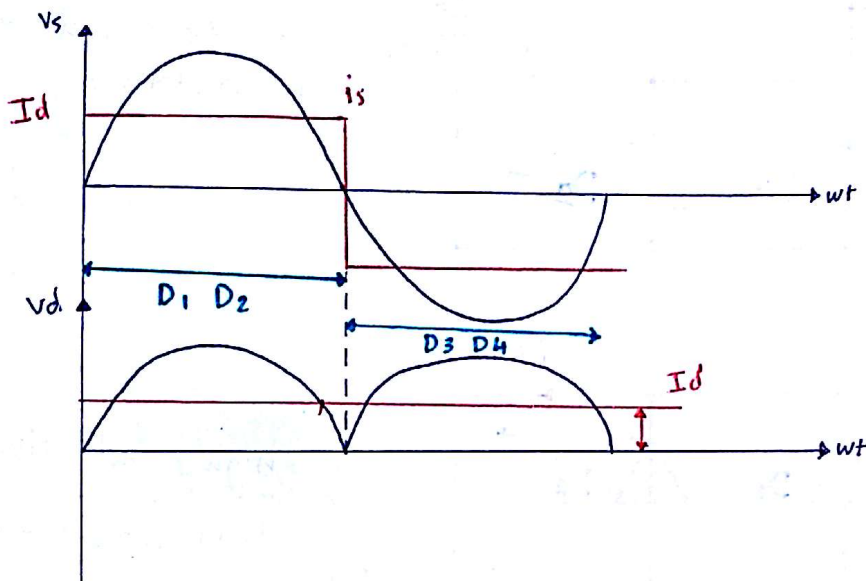12. highly inductive load with  $L_s = 0$



$\Rightarrow P, PF, DPF, THD.$

$$* I_{s1} = I_d$$

$$I_{s1} = 0.9 I_d$$

$$P = V \cdot 0.9 I_d \cos 0$$

$$P_{ac} = 0.9 V I_d \Rightarrow \text{ac side}$$


$$PF = \frac{I_{s1}}{I_s} \quad DPF = 0.9$$

$$DPF = 1$$


$$THD\% = \frac{\sqrt{I_d^2 - (0.9 I_d)^2}}{0.9 I_d} = 48.43\%$$



29

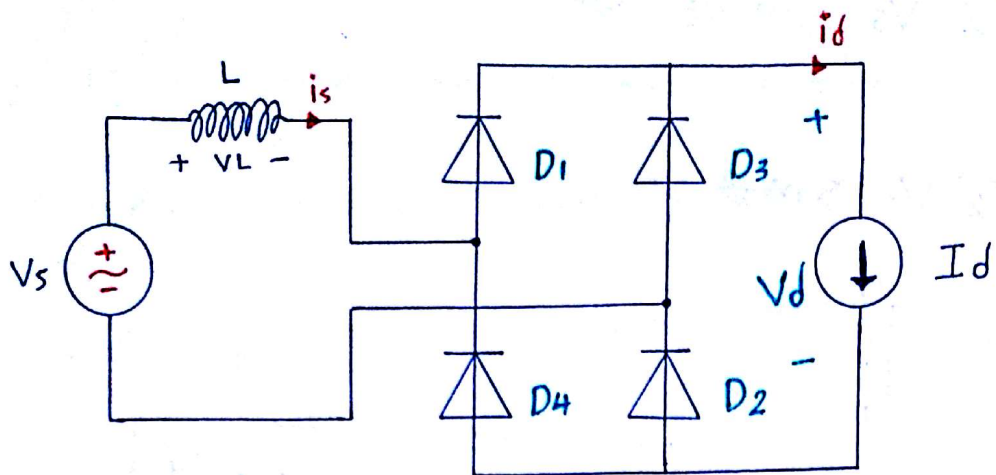


$$V_L = L \frac{di_s}{dt}$$

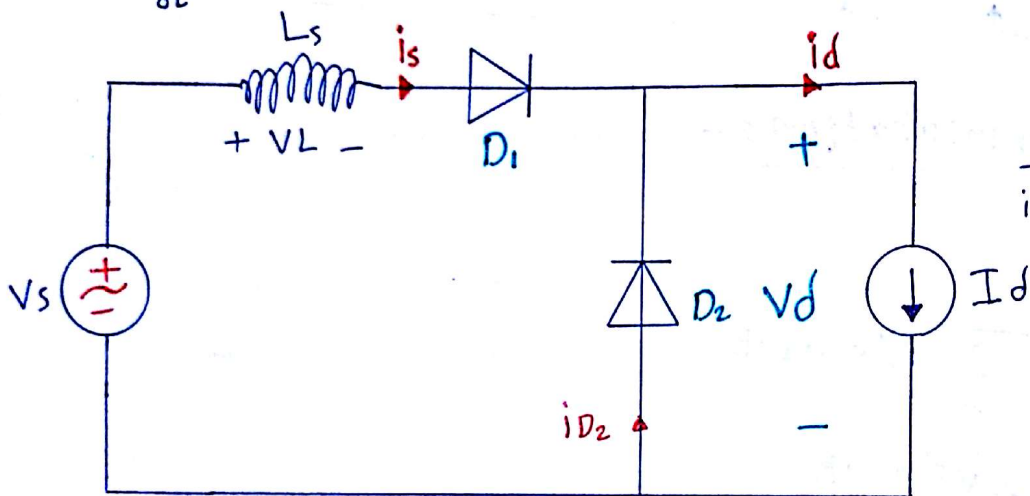

$$-i_s - i_{D2} + I_d = 0$$

$$-i_{D2} = -I_d + i_s \Rightarrow \frac{di_s}{dt} = -\frac{di_{D2}}{dt}$$

$$i_{D2} = I_d - i_s$$

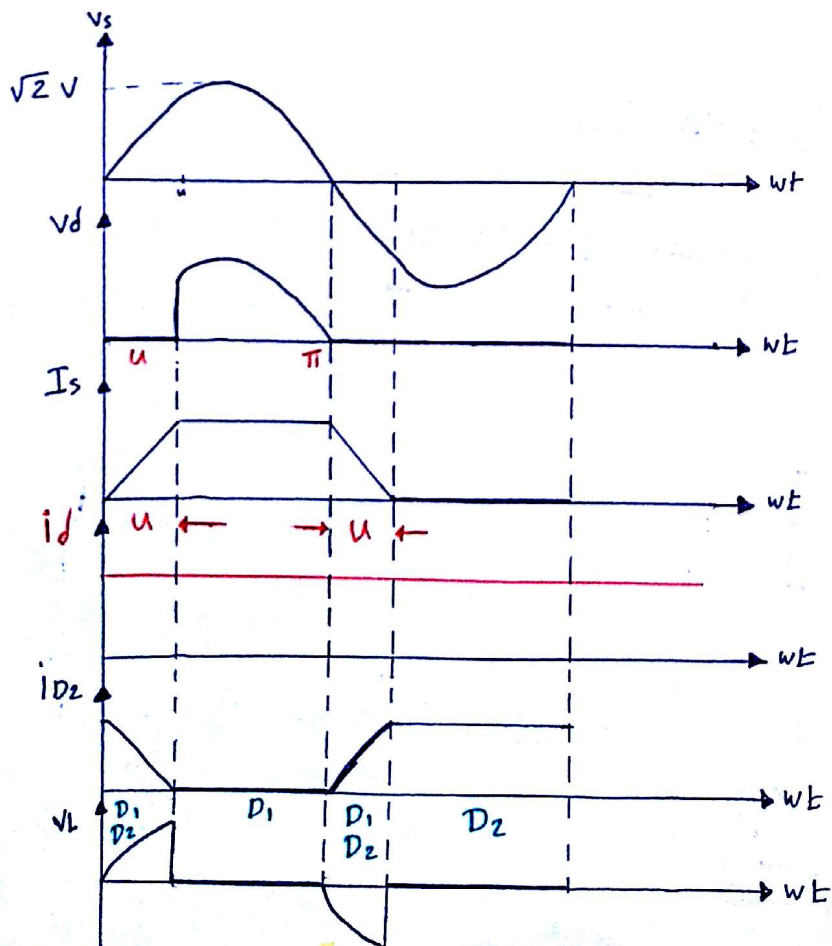

130

$$\begin{aligned}
 * V_d &= \frac{1}{2\pi} \int_0^{2\pi} \sqrt{2} V_s \sin \omega t \, d\omega t \\
 &= \frac{1}{2\pi} \int_u^\pi \sqrt{2} V_s \sin \theta \, d\theta \\
 &= \frac{\sqrt{2} V}{2\pi} \left[ \cos \theta \right]_u^\pi
 \end{aligned}$$

$$V_d = \frac{\sqrt{2} V}{2\pi} [\cos u + 1]$$

$$\Rightarrow V_d = 0.45 V - \frac{\omega L_s I_d}{2\pi}$$

\* During Commutation :-

$$V_L = V_s$$

$$L_s * \frac{di_s}{dt} = \sqrt{2} V \sin \omega t$$

$$\omega L_s \frac{di_s}{d\omega t} = \sqrt{2} V \sin \omega t$$

$$\int_0^{I_d} di_s = \int_0^u \frac{1}{\omega L_s} \sqrt{2} V \sin \omega t \, d\omega t$$

$$I_d = \frac{\sqrt{2} V}{\omega L_s} \left[ \cos \omega t \right]_u^0 = \frac{\sqrt{2} V}{\omega L_s} [1 - \cos u]$$

$$\cos u = 1 - \frac{\omega L_s I_d}{\sqrt{2} V}$$

$$u = \cos^{-1} \left[ \frac{\omega L_s I_d}{\sqrt{2} V} \right]$$

\* If  $L_s = 0$

$$V_d = 0.45 V$$

$$u = 0$$


$$P_d = V_d I_d = 0.45 V I_d$$

\* نتيجة !!!

31

وجود الـ Source Inductance "Ls" effect of "Ls" قلت الـ

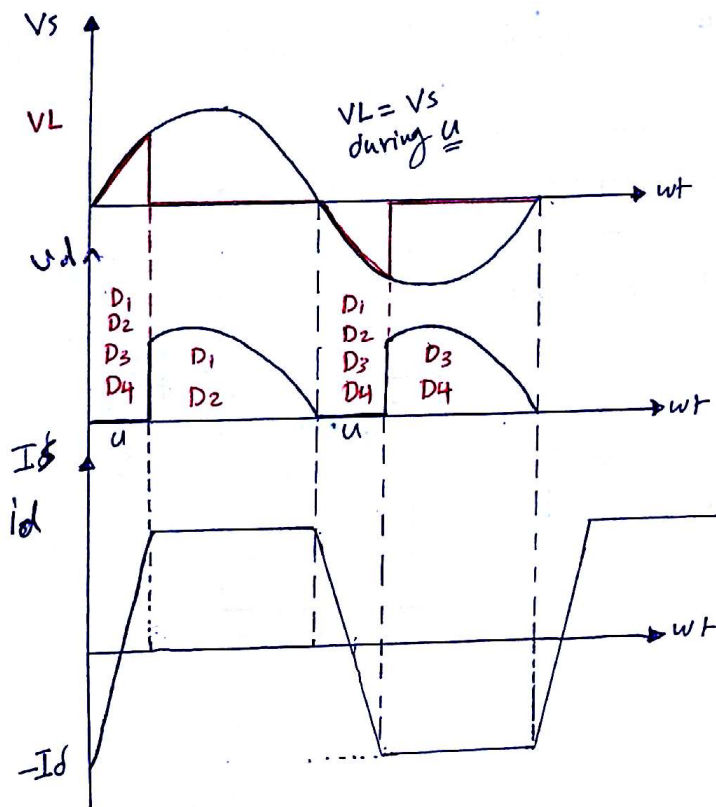- \* reduces the Avg value of the out voltage.
- \* reduces the Avg output power:
- \* introduces the Commutation interval.



Full wave

\* During Commutation :-

$$V_L = V_s$$

$$L_s \frac{di_s}{dt} = \sqrt{2} V \sin \omega t$$

$$\omega L_s \frac{di_s}{d\omega t} = \sqrt{2} V \sin \omega t$$

$$\int_{-I_d}^{I_d} di_s = \int_0^u \frac{1}{\omega L_s} \sqrt{2} V \sin \omega t d\omega t$$

$$2 I_d = \frac{\sqrt{2} V}{\omega L_s} \cos \omega t \Big|_u^0 = \frac{\sqrt{2} V}{\omega L_s} [1 - \cos u]$$

$$\cos u = \dots$$

$$\begin{aligned} V_d &= \frac{1}{2\pi} \int_0^{2\pi} \sqrt{2} V \sin \omega t d\omega t \\ &= \frac{2}{2\pi} \int_0^{\pi} \sqrt{2} V \sin \theta d\theta \\ &= \frac{\sqrt{2} V}{\pi} \cos \omega t \Big|_{\frac{\pi}{2}}^u = \frac{\sqrt{2} V}{\pi} [\cos u + 1] \end{aligned}$$

$$V_d = 0.9 - \frac{2\omega L_s I_d}{\pi}$$



$$P_d = V_d I_d$$







32

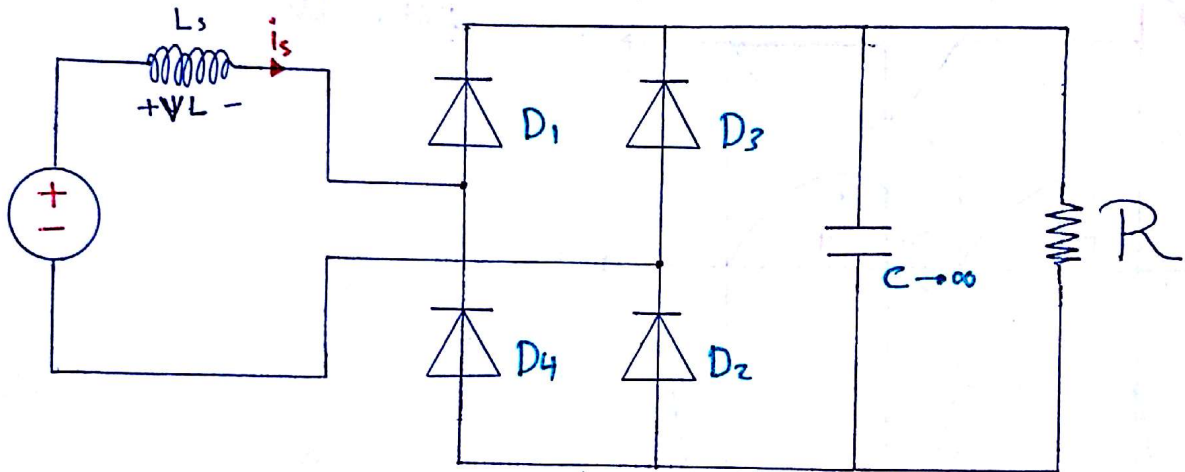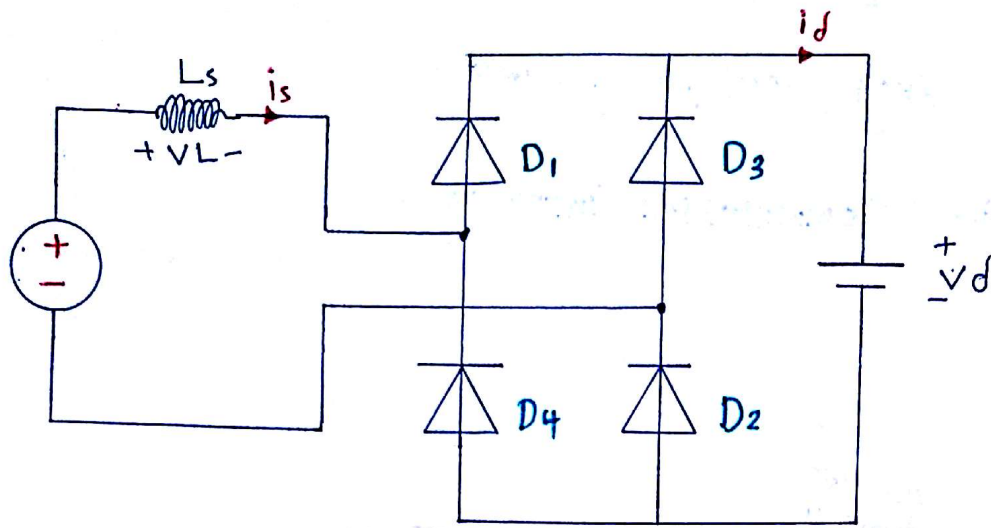\* Constant Dc Voltage across the Load  $v_d(t) = V_d$



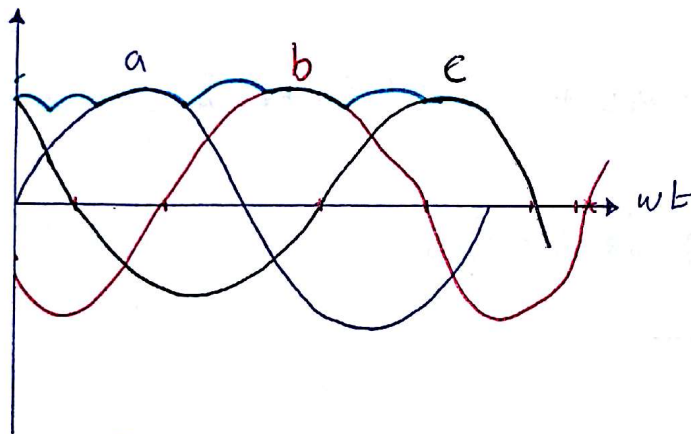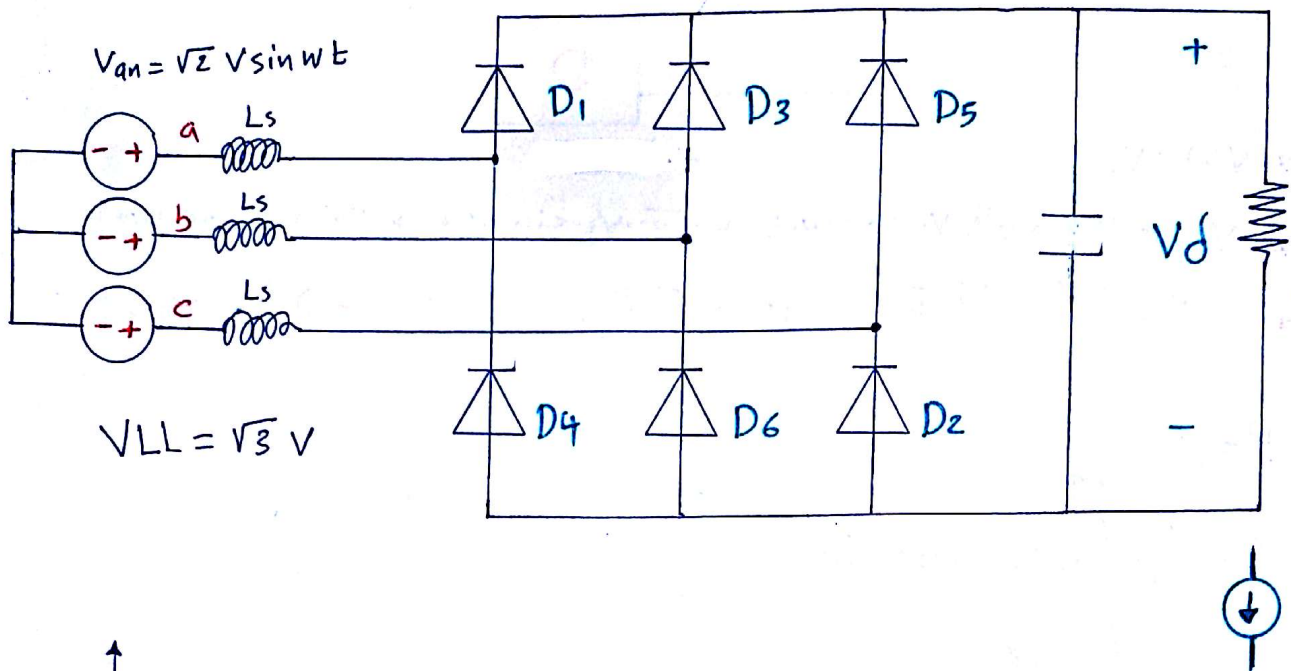\* Three-Phase - Full-Bridge Rectifiers 8-




$$\begin{aligned}
 V_d &= \frac{6}{2\pi} \int_0^{\frac{\pi}{3}} V_d(\theta) d\theta \\
 &= \frac{3}{\pi} \int_0^{\frac{\pi}{3}} \sqrt{2} V \sin \omega t d\omega t \\
 &= 1.35 V_{LL} \text{ rms value of the line input voltage}
 \end{aligned}$$

$$P_d = V_d I_d$$

$$P_d = 1.35 V_{LL} I_d$$

Exe- 5-3

39

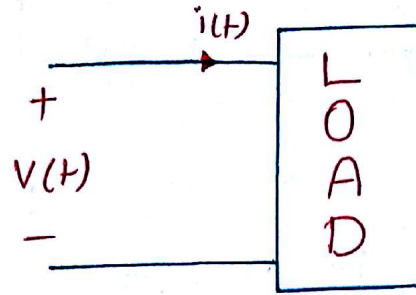

\*  $V(t) = V_d$

\*  $V(t) = V_d + \sqrt{2} V_1 \cos \omega_1 t + \sqrt{2} V_1 \sin \omega_1 t + \sqrt{2} V_3 \cos \omega_3 t$

\*  $i(t) = I_d + \sqrt{2} I_1 \cos \omega_1 t + \sqrt{2} I_3 \cos (\omega_3 t - \phi_3), \omega_3 = 3\omega_1$

a  $P = ??$

$$P = \frac{1}{2\pi} \int_0^{2\pi} V(t) i(t) d\theta$$

$$= \frac{1}{2\pi} \left[ \int_0^{2\pi} (V_d + \sqrt{2} \cos \omega_1 t + \dots) (I_d + \sqrt{2} I_1 \cos \omega_1 t + \dots) d\theta \right]$$

$$P = V_d I_d + V_1 I_1 + V_3 I_3 \cos \phi_3$$

b  $V = \sqrt{V_d^2 + V_1^2 + V_3^2}$

$$I = \sqrt{I_d^2 + I_1^2 + I_3^2}$$

c  $S = V I$



$$PF = \frac{P}{S} = \dots$$



5-4

35

b

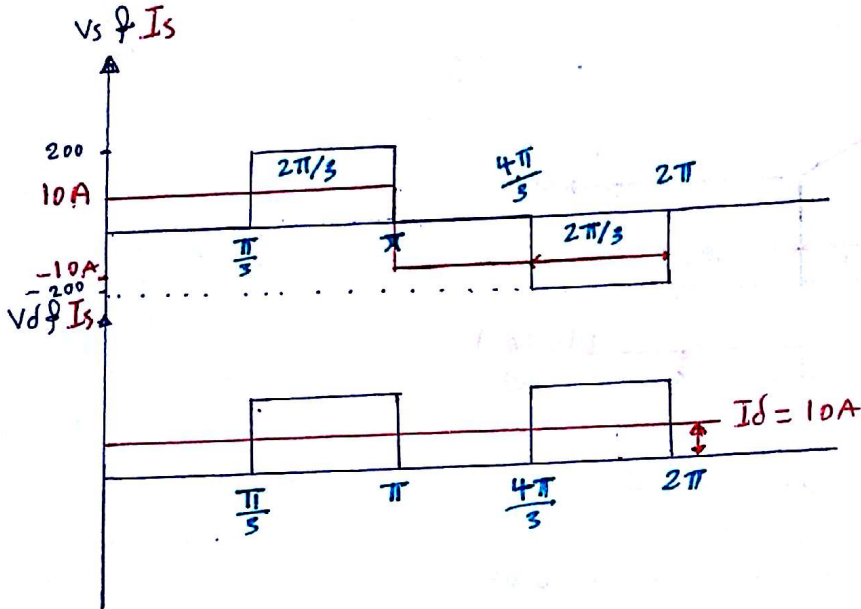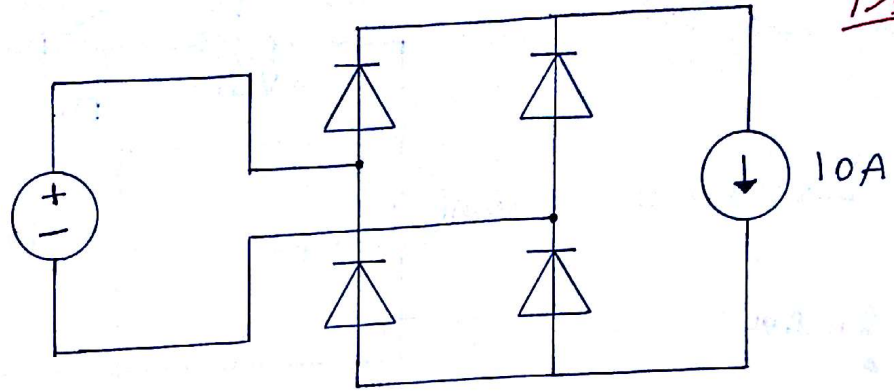



$$\begin{aligned} P_d &= \frac{1}{2\pi} \int_0^{2\pi} v_d(t) i_d(t) d\theta \\ &= \frac{2}{2\pi} \int_{\frac{\pi}{3}}^{\frac{2\pi}{3}} (200)(10) d\theta \\ &= \frac{4000}{2\pi} \left( \pi - \frac{\pi}{3} \right) \\ &= \frac{4000}{3} \text{ W} \end{aligned}$$



5-5

36

c)  $L_s = 5 \text{ mH}$

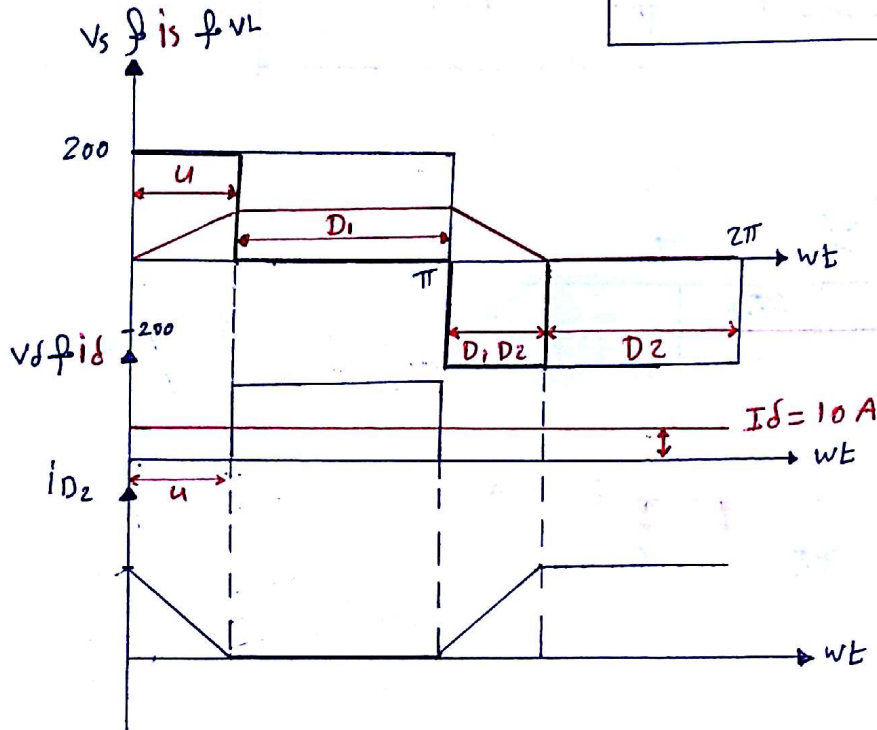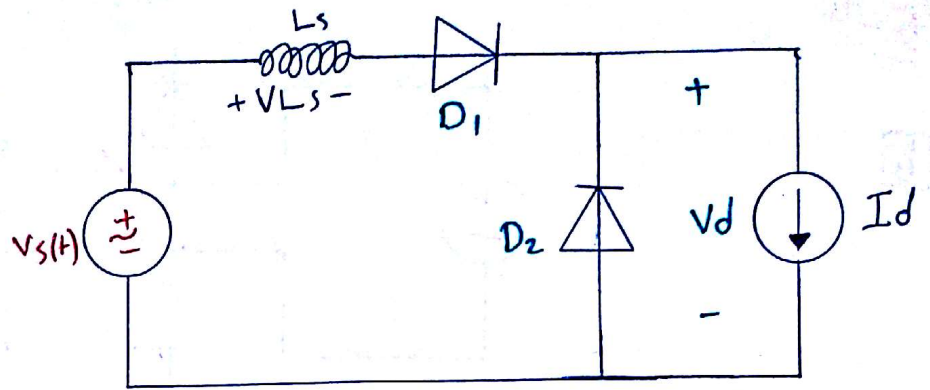

\* During Commutation -

$$V_L = V_s$$

$$\omega L_s \frac{di_s}{d\omega t} = 200$$

$$\omega L_s \int_0^u di_s = \int_0^u 200 d\omega t$$

$$\omega L_s I_d = 200 u$$

$$u = \frac{\omega L_s I_d}{200} = \frac{(377)(5 \times 10^{-3})(10)}{200}$$

$$u = \frac{5.4 * \pi}{180} \text{ rad}$$

$$u = 5.4 \pi$$

$$V_d = \frac{1}{2\pi} \int_u^{\pi} 200 d\theta = \frac{1}{2\pi} 200 (\pi - u)$$


$$= \frac{1}{2\pi} 200 \left[ \pi - \frac{5.4 * \pi}{180} \right] = \dots$$

$$P_d = V_d I_d$$


=

5-11

137

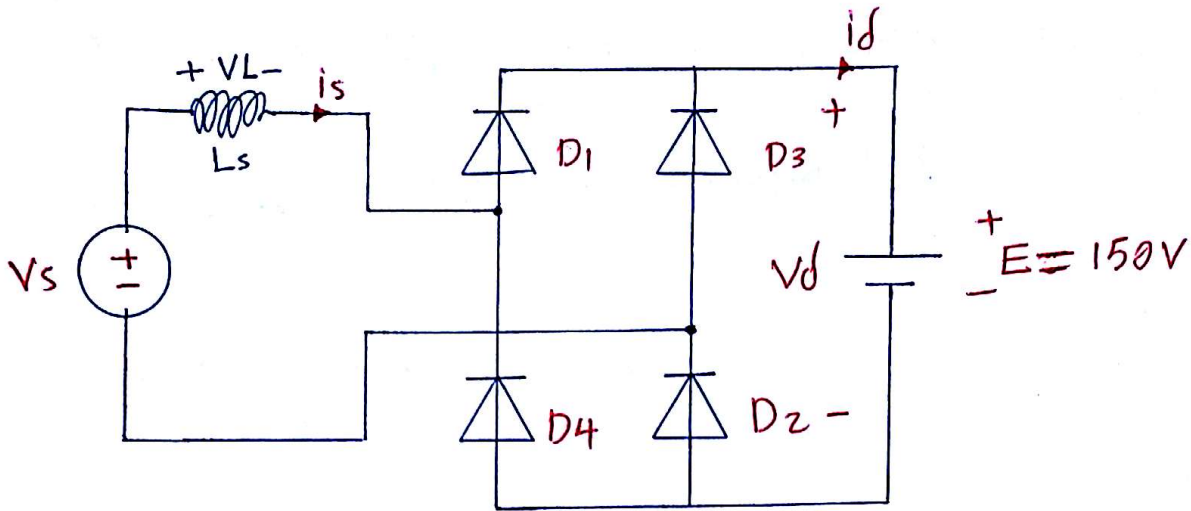
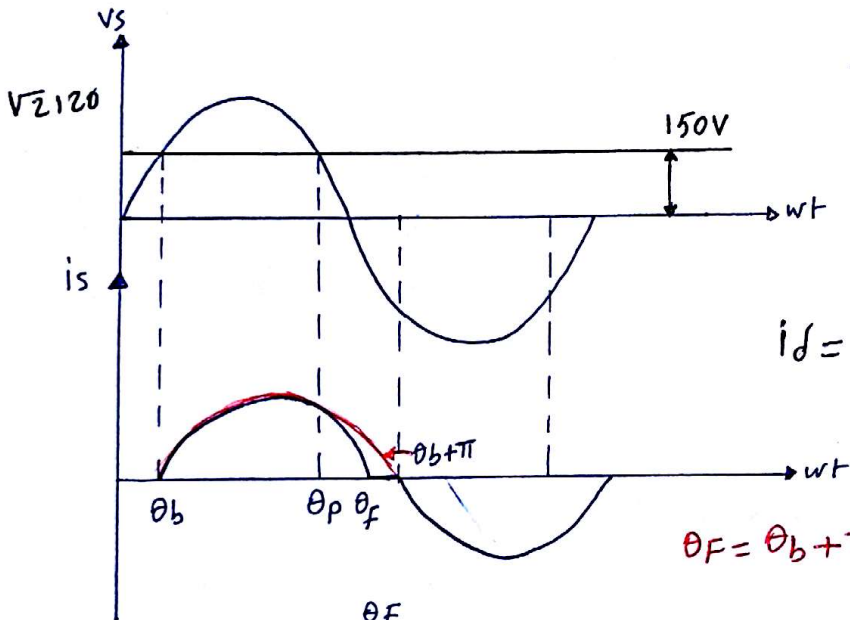
$$V_s = \sqrt{2} V \sin \omega t = \sqrt{2} 120 \sin \omega t$$



$i_d = i_s$  in the first half cycle

$$\theta_f = \theta_b + \pi$$

$$I_d = \frac{1}{\pi} \int_{\theta_b}^{\theta_f} i_d(\theta) d\theta$$

$$i_d(\theta) = \square \cos \theta - \square \theta + \square$$

$$i_d(\theta_f) = 0 = \square \cos \theta_f - \square \theta_f + \square$$

$\theta_f = \dots$  Trial & Error

$$\theta_b = \sin^{-1} \left( \frac{150}{\sqrt{2} \cdot 120} \right) =$$

$$\theta_p = \pi - \theta_b$$

$$\theta_f = ? \quad i_d(\theta_f) = 0$$

$$-V_s(t) + L_s \frac{di_d}{dt} + E = 0$$

$$\omega L_s \frac{di_d}{d\theta} = \sqrt{2} V \sin \theta - E$$

$$di_d = \left( \frac{1}{\omega L_s} \sqrt{2} V \sin \theta - \frac{1}{\omega L_s} E \right) d\theta$$

$$i_d(\theta) = -\frac{1}{\omega L_s} \sqrt{2} V \cos \theta - \frac{1}{\omega L_s} E \theta + K$$

$$i_d(\theta_b) = 0 = \frac{-\sqrt{2}V}{\omega L_s} \cos \theta_b - \frac{E}{\omega L_s} \theta_b + K$$


$$K = \dots$$



\* Controlled Rectifiers And Inverters :-


line Frequency Ac  $\rightarrow$  Controlled Dc.

\* Basic Thyristor circuits :-

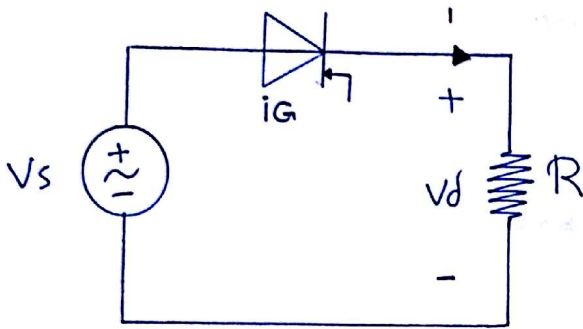



$\alpha$ : Firing angle

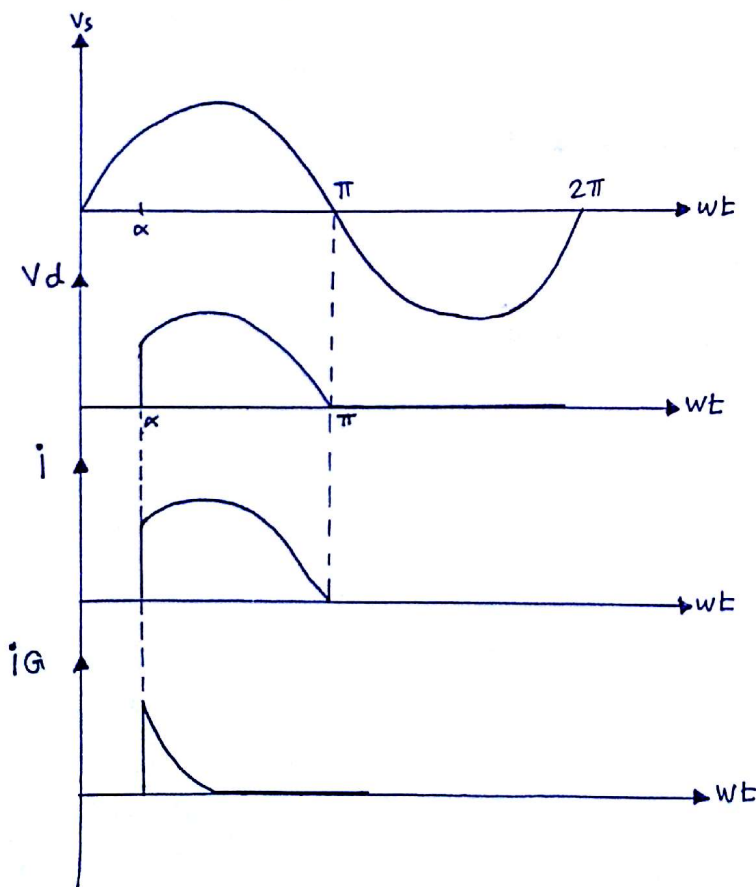half-wave controlled rectifier  
CCT with pure resistive





$$\begin{aligned}
 V_d &= \frac{1}{2\pi} \int_{\alpha}^{\pi} \sqrt{2} V_s \sin \omega t \, d\omega t \\
 &= \frac{\sqrt{2} V}{2\pi} \left[ \cos \omega t \right]_{\alpha}^{\pi} \\
 &= \frac{\sqrt{2} V}{2\pi} [\cos \alpha + 1]
 \end{aligned}$$

139

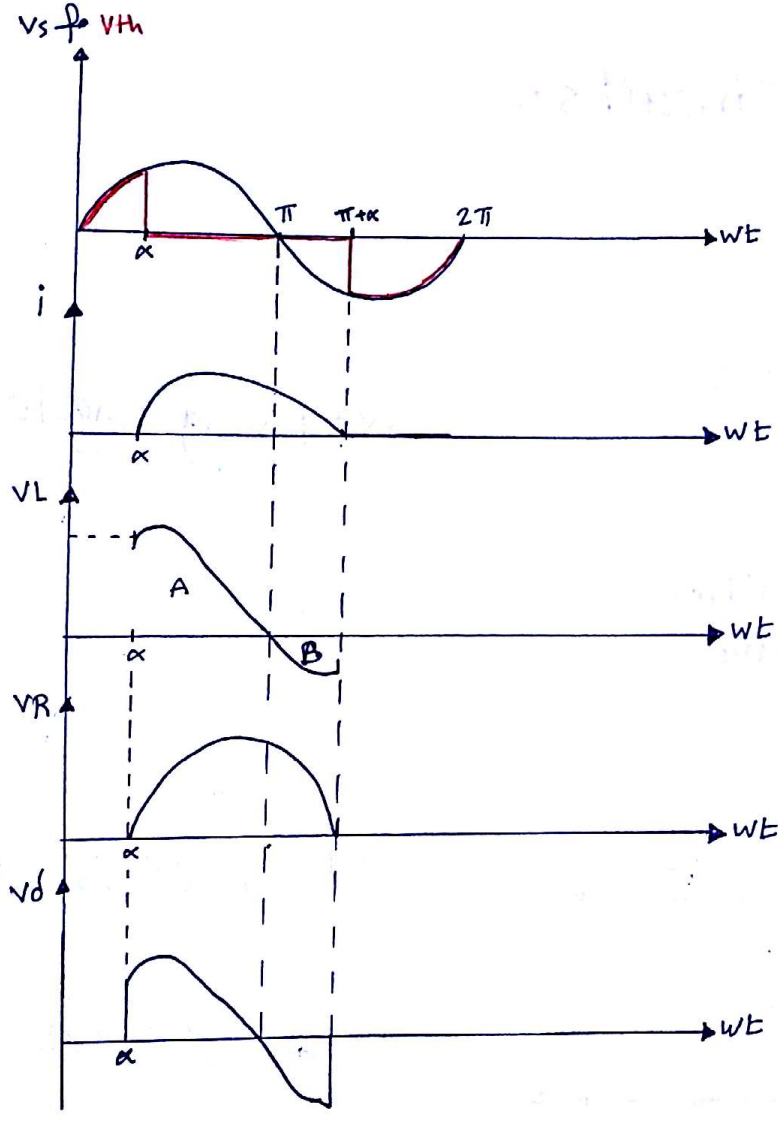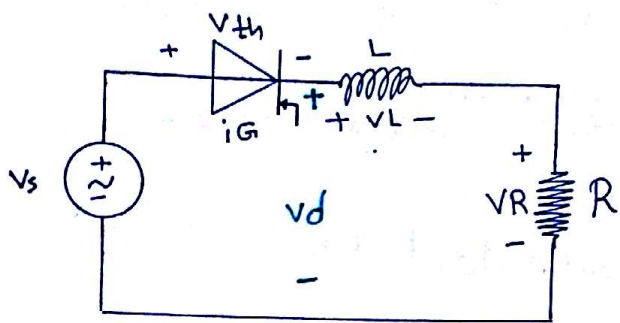



140

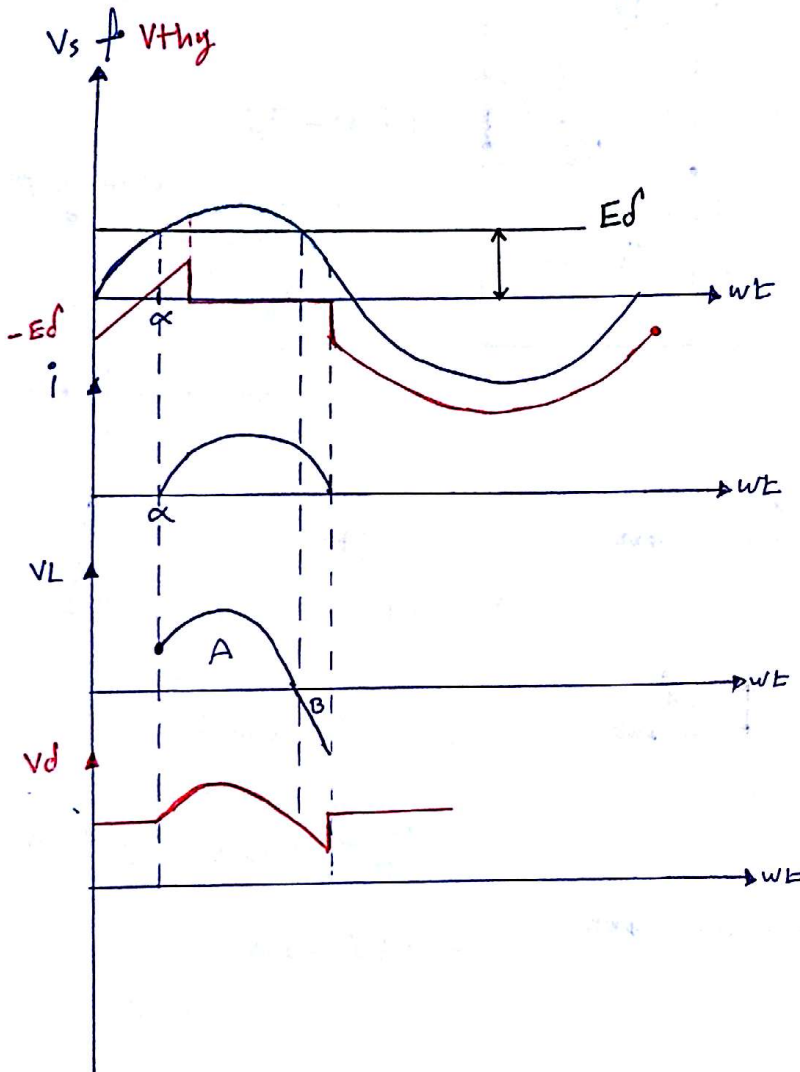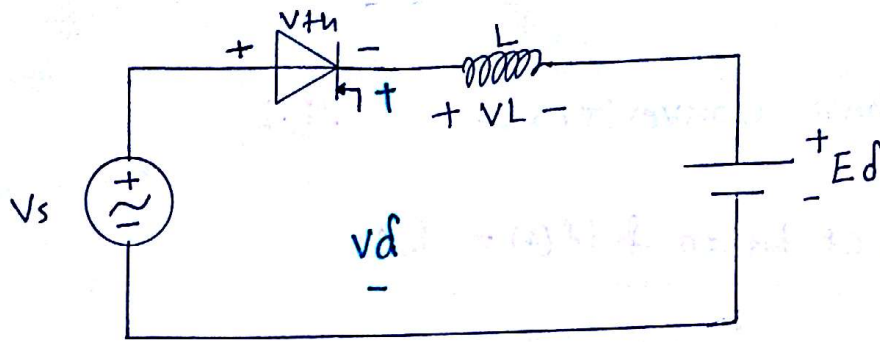

$$-V_s(t) + L \frac{di}{dt} + E_d = 0$$

$$V_L = V_s(t) - E_d$$

\*


# \* Single - Phase Converters :-

41



\* Idealized ckt  $L_s = 0$  &  $i_d(t) = I_d$

ex:-

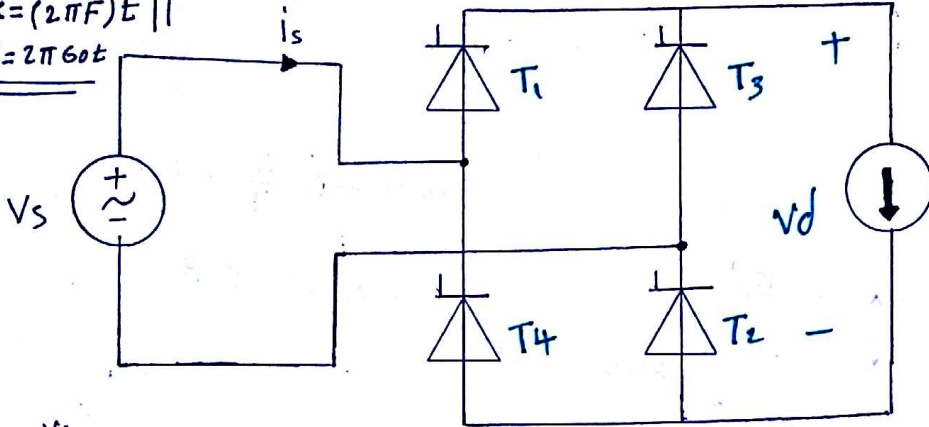$\alpha = \omega t$   
 $\alpha = (2\pi F)t$   
 $45 = 2\pi 60 t$



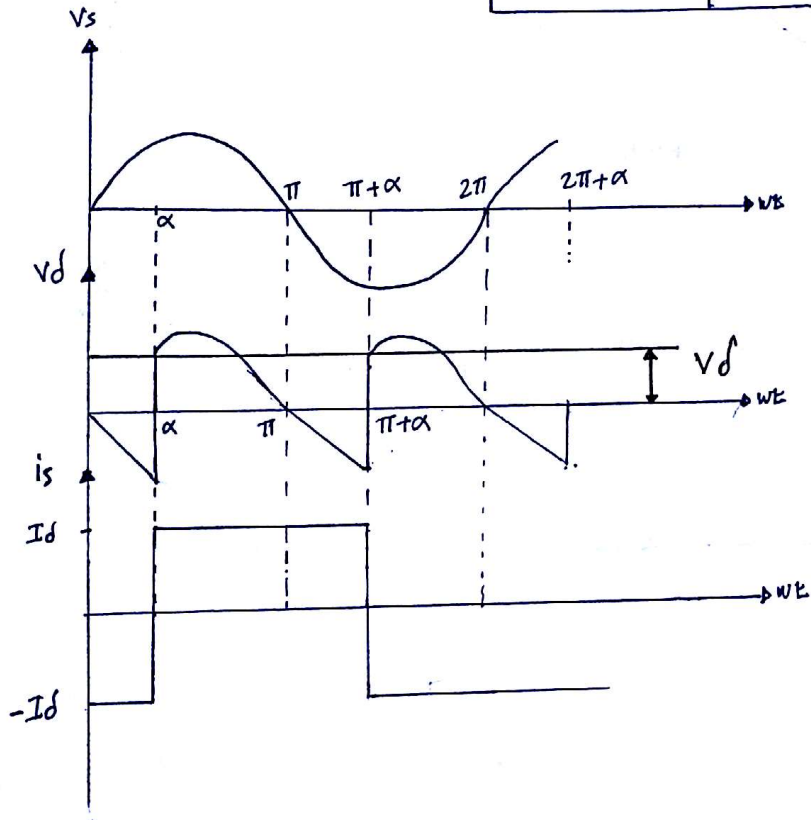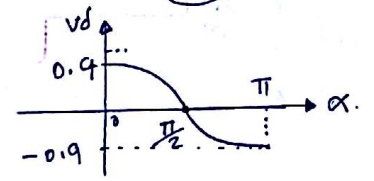$i_d(t) = I_d$   
 (highly inductive) DC Motor load




$$V_d = \frac{2}{2\pi} \int_{\alpha}^{\pi+\alpha} \sqrt{2} V_s \sin \omega t \, d\omega t$$

$$= \frac{\sqrt{2} V}{\pi} \left[ \cos \omega t \right]_{\alpha}^{\pi+\alpha}$$

$$= \frac{\sqrt{2} V}{\pi} \left[ \cos \alpha - \cos(\pi + \alpha) \right]$$

$$= 0.9 V \cos \alpha$$

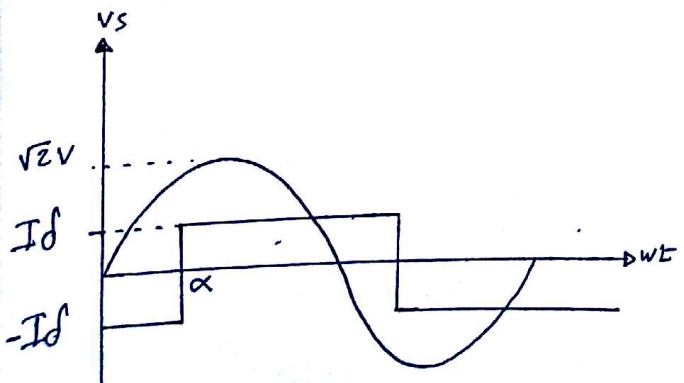

$$P = V I_{s1} \cos \alpha$$

$$= V 0.9 I_d \cos \alpha$$

$$PF = \frac{I_{s1}}{I_s} \text{DPF} = 0.9 \cos \alpha$$

$$\text{DPF} = \cos \alpha$$


$$I_s = I_d$$

$$I_{s1} = 0.9 I_d$$


$$\text{THD} = 48.43\%$$



\* Effect of  $L_s$  :-

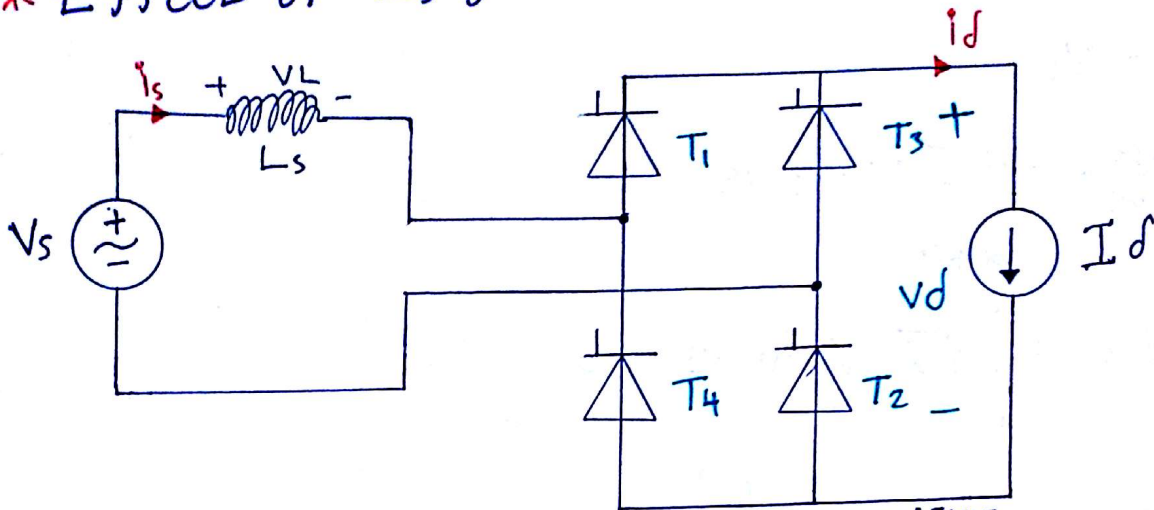

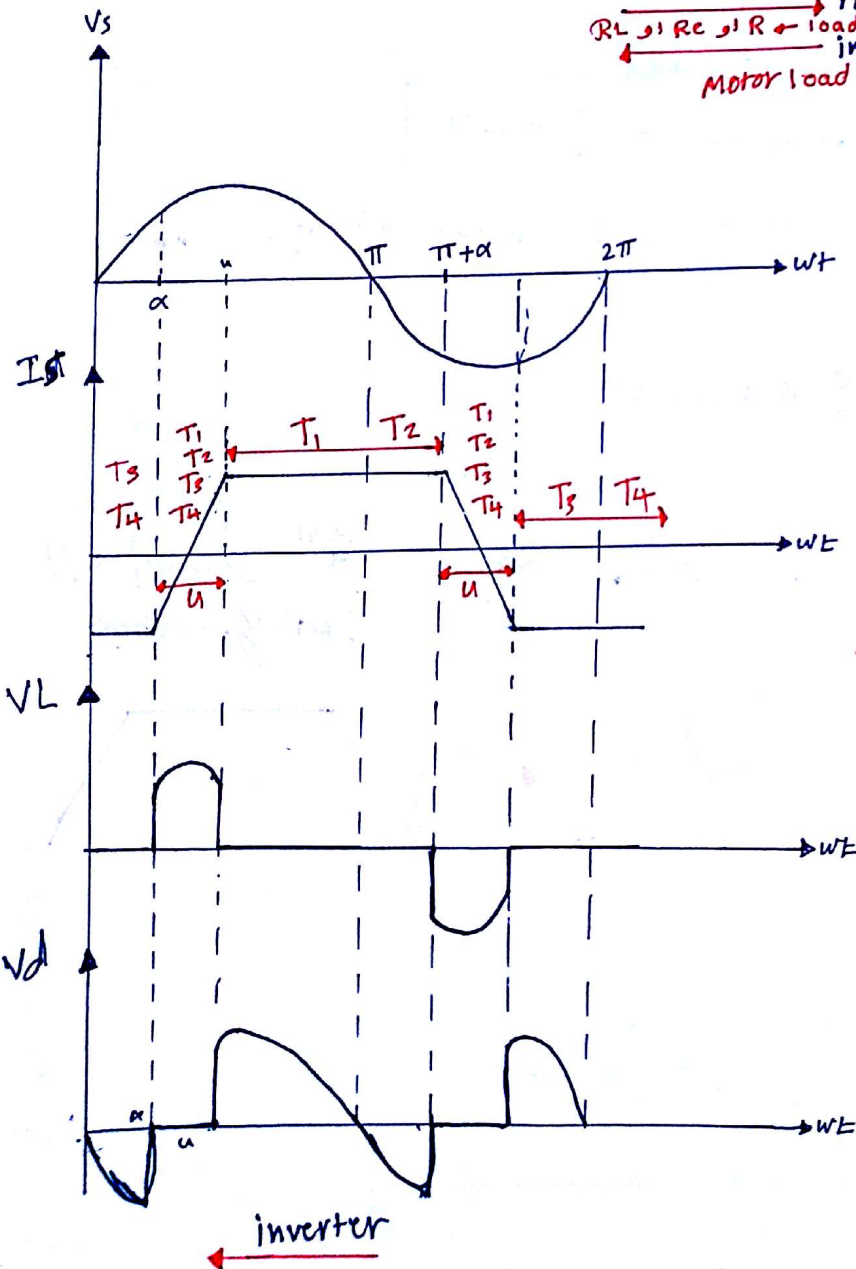$R_L$  و  $R_e$  و  $R$  ← load جى 0 لى جى  
 ← Rectifier  
 ← inverter  
 ← Motor load جى 0 لى جى



$$V_d = \frac{2}{2\pi} \int_{\alpha+u}^{\pi+\alpha} \sqrt{2} V \sin \omega t d\omega t$$

$$= \frac{\sqrt{2} V}{\pi} \cos \omega t \Big|_{\pi+\alpha}^{\alpha+u}$$

$$V_d = \frac{\sqrt{2} V}{\pi} [\cos(\alpha+u) - \cos(\pi+\alpha)]$$

$$= \frac{\sqrt{2} V}{\pi} [\cos(\alpha+u) - \cos \pi \cos \alpha + \sin \pi \sin \alpha]$$

$$= \frac{\sqrt{2} V}{\pi} [\cos(\alpha+u) + \cos \alpha]$$

$$V_d = 0.9 V \cos \alpha - \frac{2 \omega L_s I_d}{\pi}$$

\*\*

regenerative braking.



# During Commutation

143

$$V_L = V_s$$

$$\omega L_s \frac{di_s}{dt} = \sqrt{2} V \sin \omega t$$

$$\omega L_s \int_{-I_d}^{I_d} di_s = \int_{\alpha}^{\alpha+\mu} \sqrt{2} V \sin \omega t dt$$

$$2\omega L_s I_d = \sqrt{2} V \cos \omega t \Big|_{\alpha+\mu}^{\alpha}$$

$$2\omega L_s I_d = \sqrt{2} V [\cos \alpha - \cos(\alpha + \mu)]$$

$$\cos(\alpha + \mu) = \dots \dots \dots (*) \text{نعوضها بمعادلة}$$


$$\omega L_s \int di_s = \int \sqrt{2} V \sin \omega t dt$$

$$\omega L_s i_s(\theta) = -\sqrt{2} V \cos \theta + K$$


$$i_s(\theta) = \dots \dots \dots$$

$$i_s(\alpha) = \dots \dots \dots = -I_d'$$

إيجاد التيار في حالة  
During Comm

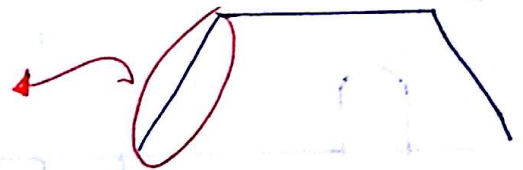


\* Inverter Mode of operation :-

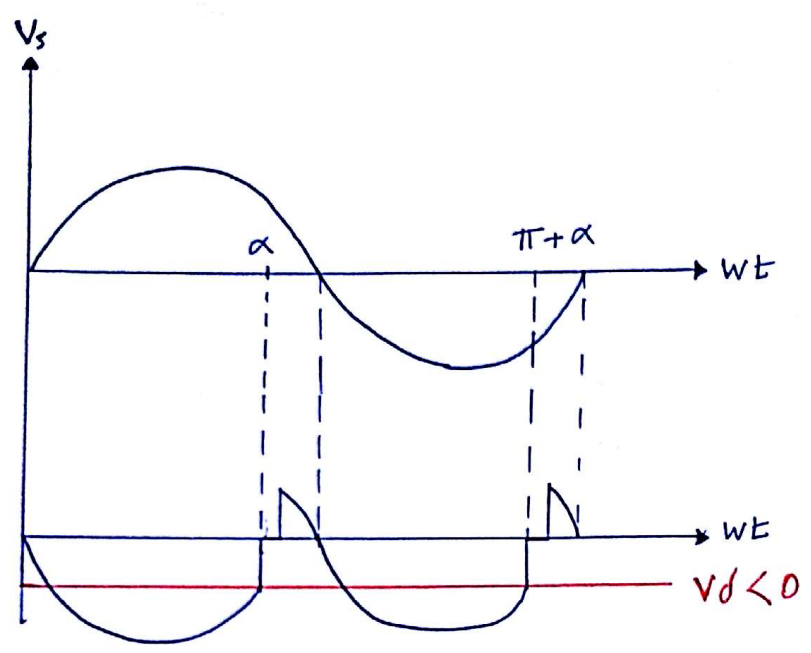

$$V_d = 0.9 V \cos \alpha - \frac{2 \omega L_s I_d}{\pi} < 0$$

- ①  $\alpha < 90$
- ② storage element

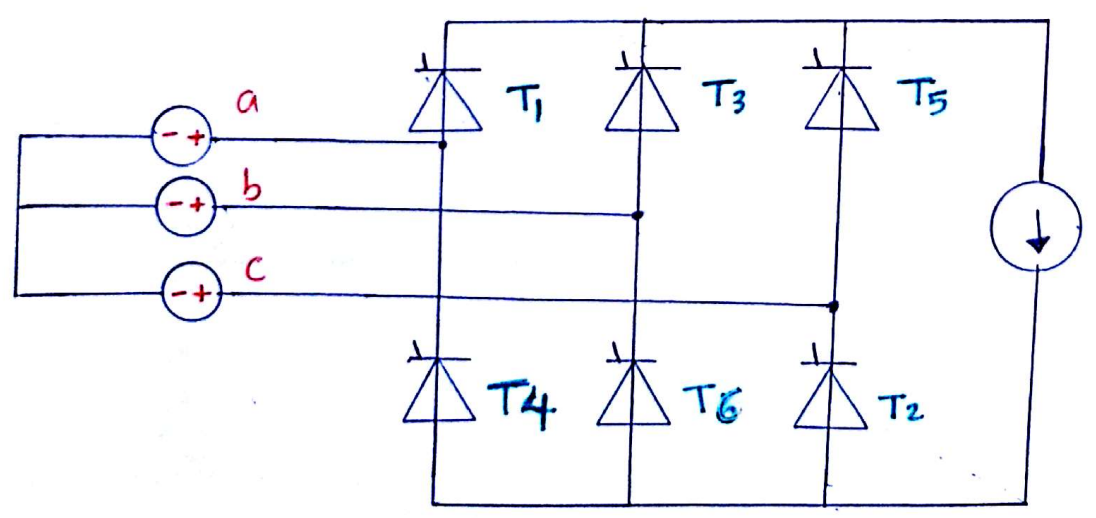
\* Three-Phase Controlled rectifier Circuit :-



$$V_d = 1.35 V_{LL} \cos \alpha$$



rms value  
of line-line voltage

P. 6-1

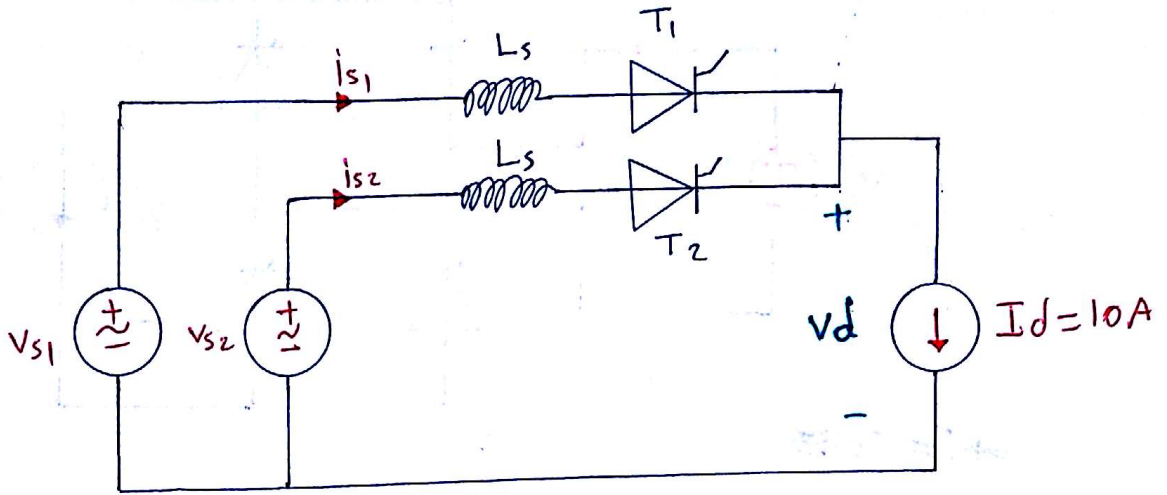

$V_{s1} = V_{s2} = 120V$ ,  $60\text{ Hz}$  (out of phase by  $180^\circ$ ),  $L_s = 5\text{ mH}$

a)  $\alpha = 45^\circ$

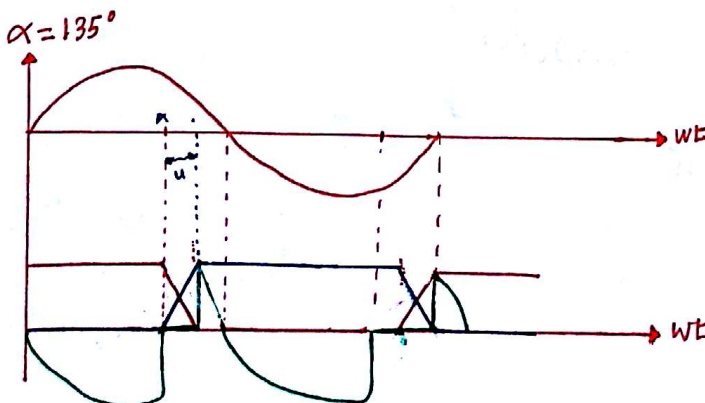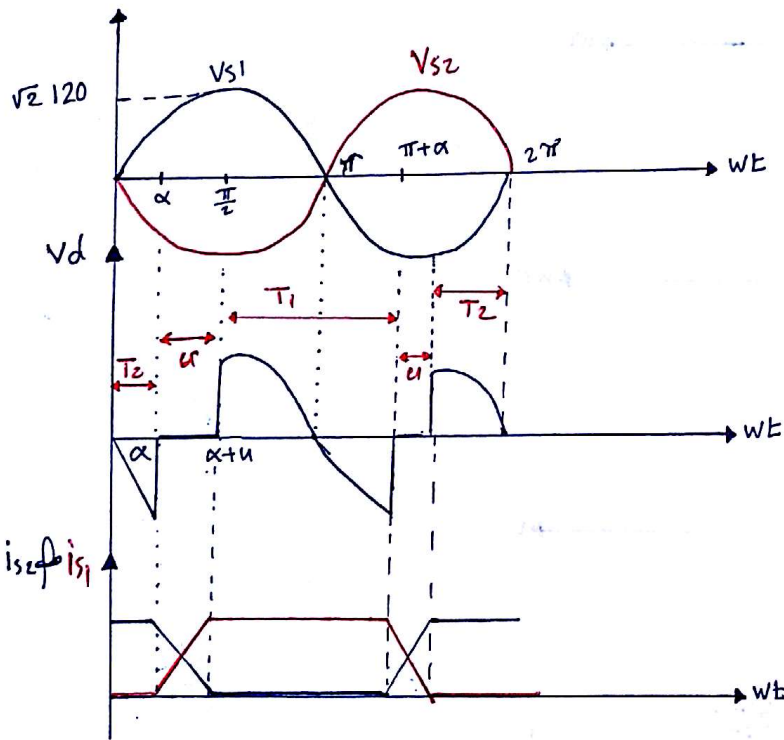

During Commutation

$$V_L = V_s$$

$$\omega L_s \frac{di_s}{dt} = \sqrt{2} V_s \sin \omega t$$

$$\int_0^{I_d} di_s = \int_{\alpha}^{\alpha+u} \frac{1}{\omega L_s} \sqrt{2} V_s \sin \omega t d\omega t$$

$$\Downarrow$$

$$\pi + \alpha + u = ?$$


$$V_d = \frac{2}{2\pi} \int_{\alpha+u}^{\pi+\alpha} \sqrt{2} V_{s1} \sin \omega t d\omega t$$

$$= \dots \dots V$$



6-3


146

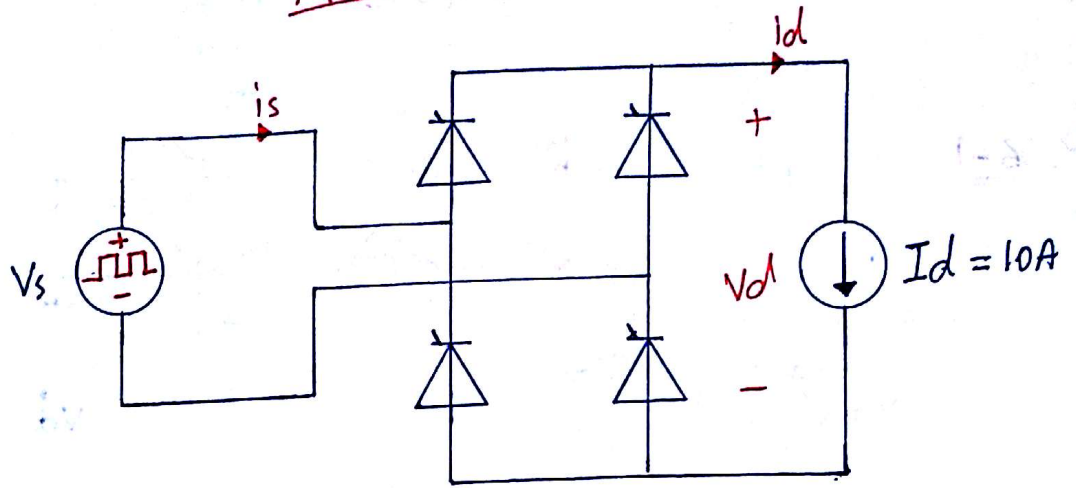

$\rightarrow F = 60 \text{ Hz}$

$\rightarrow V_s$  is a square waveform with a peak of 200 V.

$\alpha = 45^\circ$

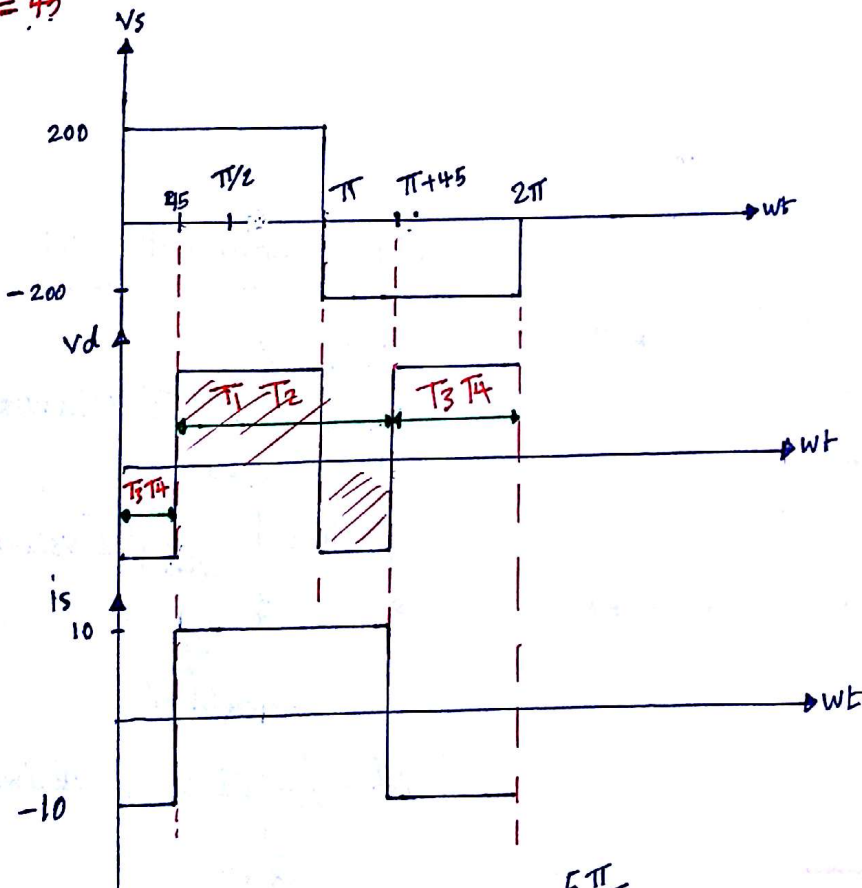



$$V_d = \frac{1}{\pi} \left[ \int_{\frac{\pi}{4}}^{\pi} 200 d\theta + \int_{\pi}^{\frac{5\pi}{4}} -200 d\theta \right]$$



P-6-4

$F = 60 \text{ Hz}$   
 $L_s = 3 \text{ mH}$

47

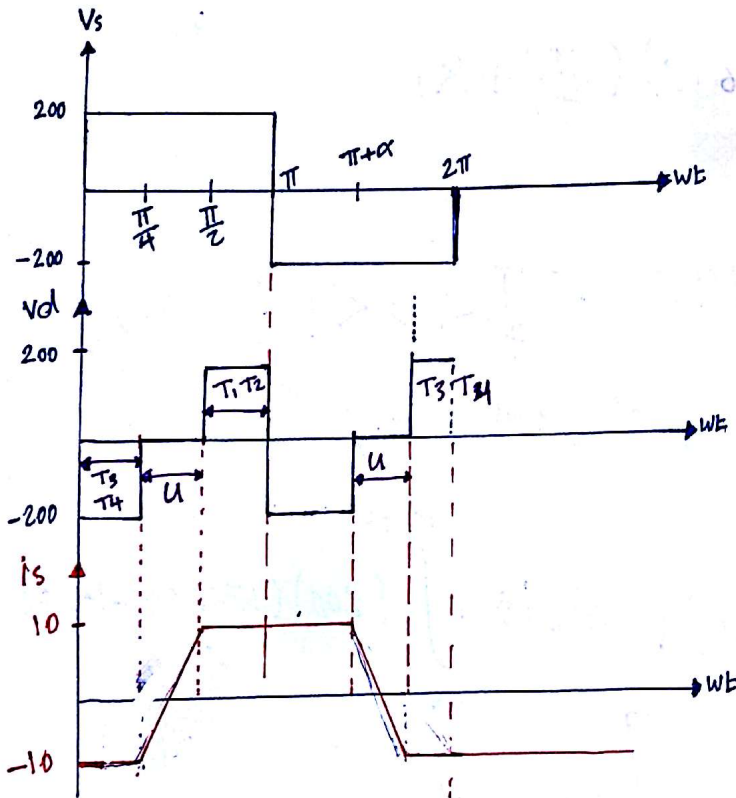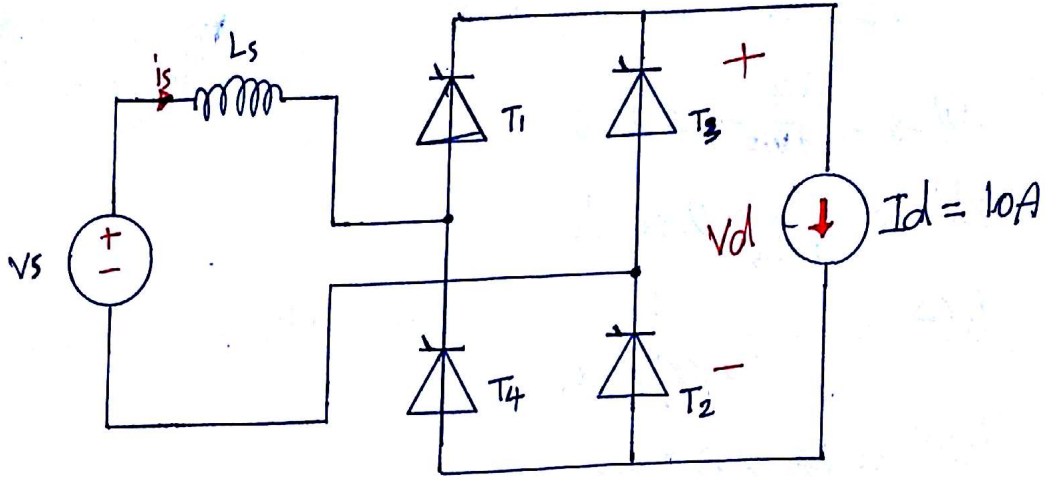

$$V_d = \frac{1}{\pi} \left[ \int_{\alpha+u}^{\pi} 200 d\theta + \int_{\pi}^{\pi+\alpha} -200 d\theta \right]$$

$$P_d = \underline{V_d} I_d$$

During Commutation:-

$$V_L = V_s$$

$$\omega L_s \frac{di_s}{d\omega t} = 200$$

$$\int_{-10}^{10} di_s = \int_{\alpha}^{\pi/4 + u} \frac{1}{\omega L_s} 200 d\theta$$

$$20 = \frac{200 (u)}{(377)(3 \times 10^{-3})} \quad \rightarrow \quad u = 0.11 \text{ rad} = 6.3^\circ$$





\* Mathematical expression of  $i_s$  during commutation

$$V_L = V_s$$

148

$$\omega L_s \frac{di_s}{d\omega t} = 200$$

$$di_s = \frac{1}{\omega L_s} 200 d\theta$$

$$i_s(\theta) = \frac{1}{(377)(30 \times 10^{-3})} 200 \theta + K_1$$

$$i_s(\theta) = 176.8 \theta + K_1$$

$$i_s\left(\frac{\pi}{4}\right) = -10 = (176.8)\left(\frac{\pi}{4}\right) + K_1$$

$$K_1 = -148$$

$$i_s(\theta) = 176.8 \theta - 148 \quad \frac{\pi}{4} < \theta < \left(\frac{\pi}{4} + \alpha\right)$$

$$P_s = \frac{1}{2\pi} \int_0^{2\pi} v_s(\theta) i_s(\theta) d\theta$$

$$= \frac{1}{2\pi} \left[ \int_0^{\alpha} (200)(-10) d\theta + \int_{\alpha}^{\alpha+\mu} (200)(176.8\theta - 148) d\theta + \int_{\alpha+\mu}^{\pi} (200)(10) d\theta \right]$$



\* Dc - Dc Switch Mode Converters :-


→ Applications :-

- 1] Dc Motor drive applications.
- 2] regulated Power supply.

→ Types :-

- 1- step down (Buck)
- 2- step up (Boost)
- 3- step up down (Buck-Boost)
- 4- Full bridge Converter.

\* Dc - Dc Converter system :-

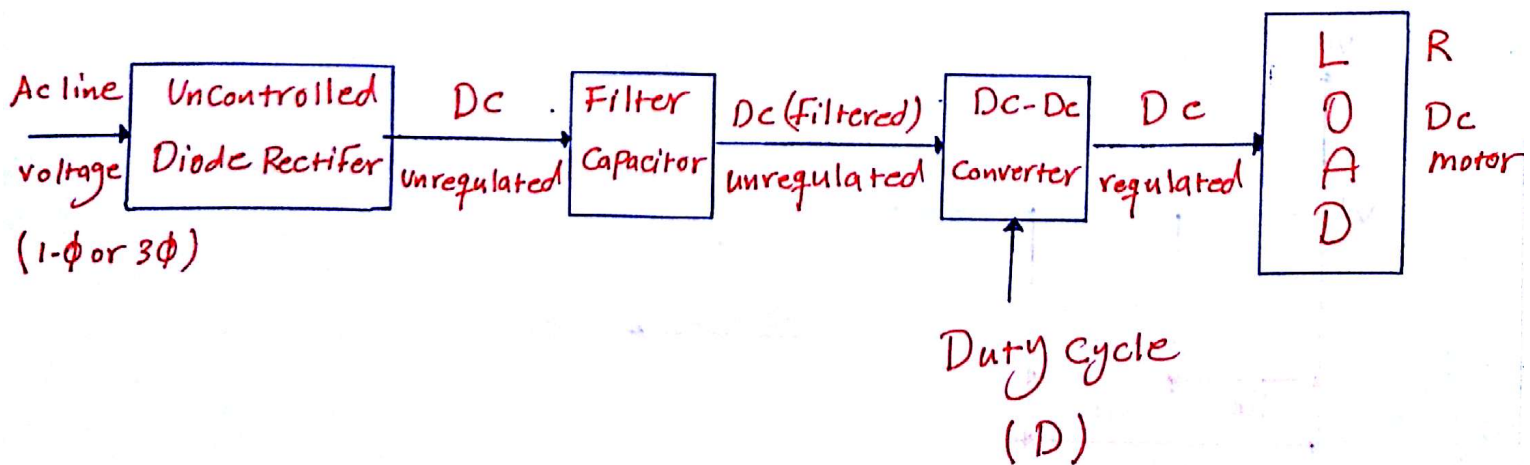


Note

\* The Converter

\*


\*

\* Control of DC-DC Converters :-

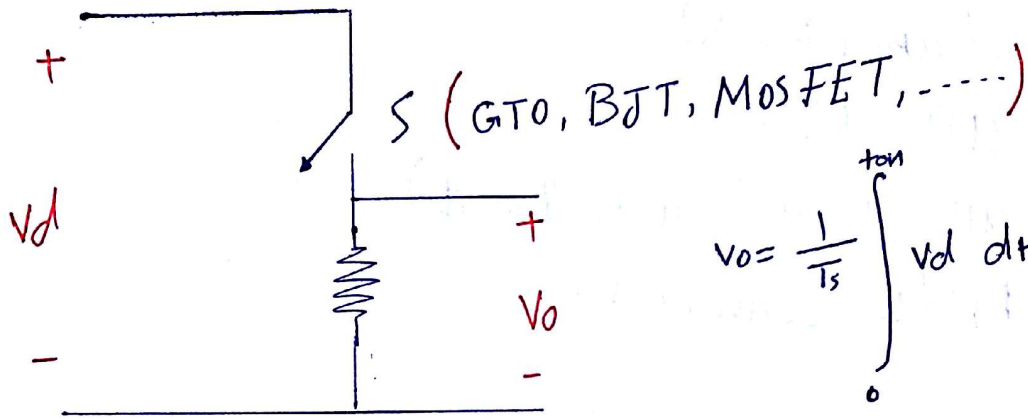



$$V_o = \frac{1}{T_s} \int_0^{t_{on}} v_d dt$$

$$= \frac{t_{on}}{T_s} v_d = D V_d$$

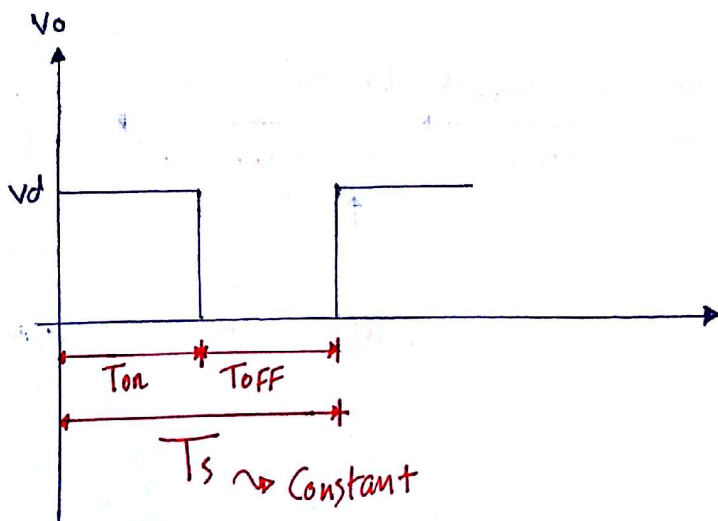

51
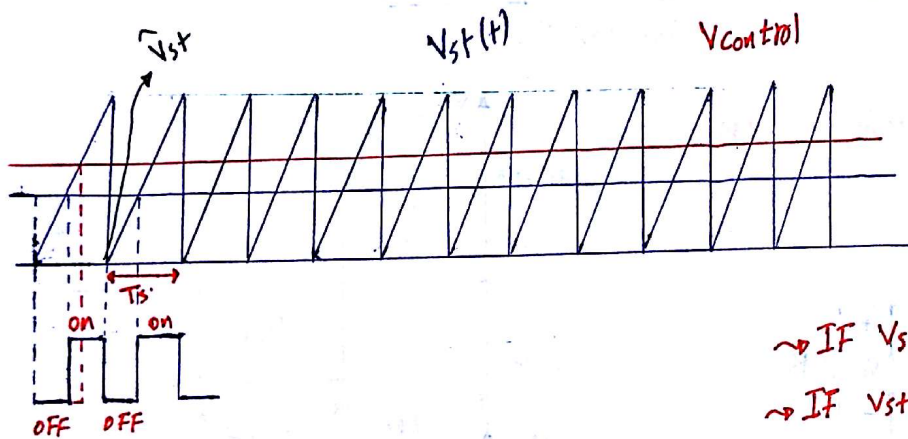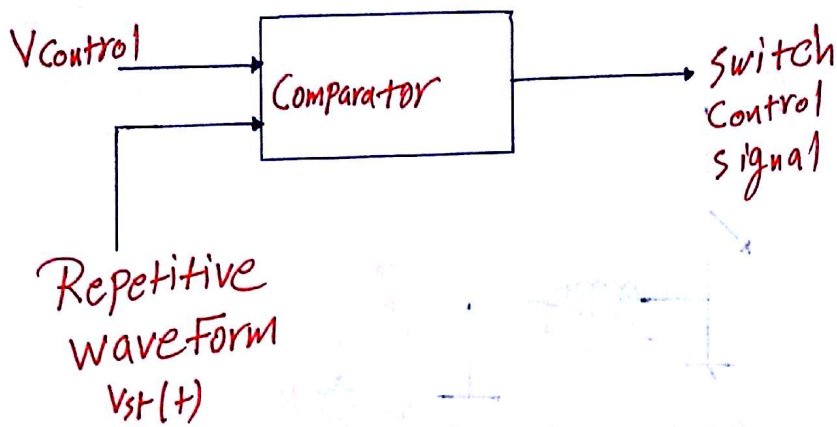
# \* Pulse width Modulation (PWM) Technique :-




→ IF  $V_{st}(t) > V_{control}$  (ON)  
→ IF  $V_{st}(t) < V_{control}$  (OFF)

$$\Rightarrow D = \frac{t_{on}}{T_s} = \frac{V_{control}}{\hat{V}_{st}}$$


Note in Dc - Dc converters there are two modes of operation :-

- 1] Continuous conduction mode.
- 2] discontinuous conduction mode.


\* Step down (Buck) Converter :-

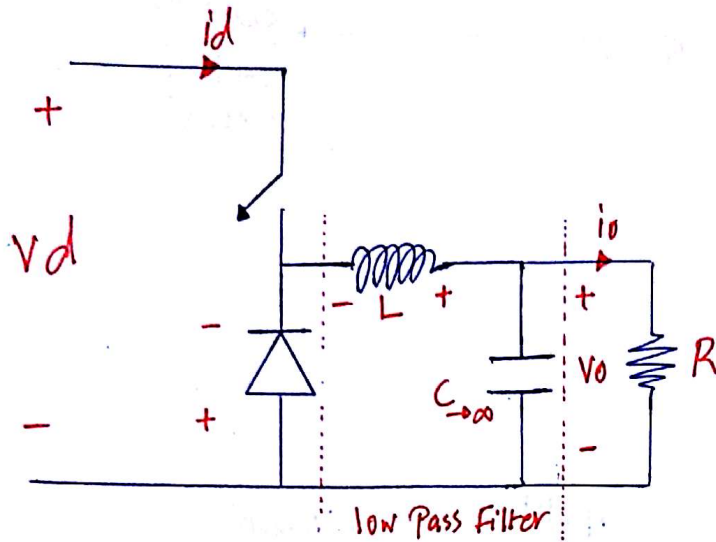


\* If the Switch is "ON" :-

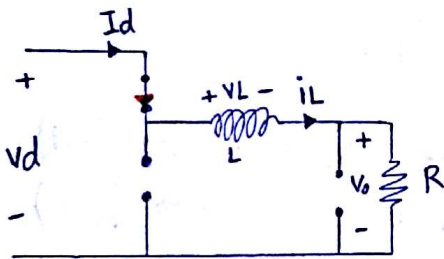

$$V_L = V_d - V_o$$

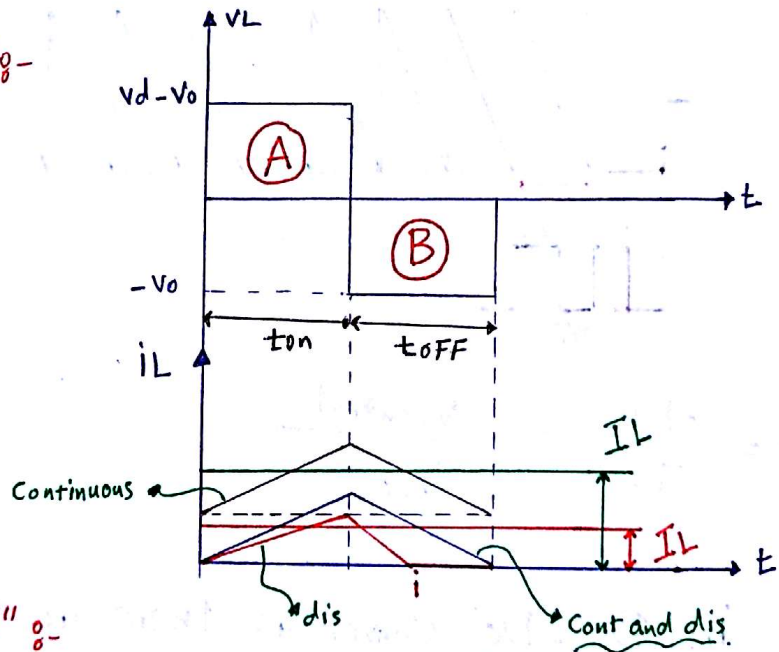

\* If the Switch is "OFF" :-

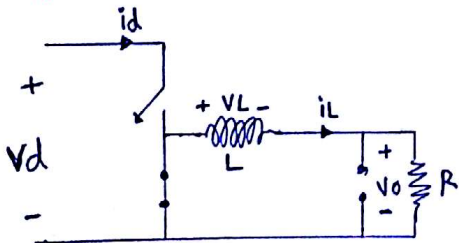

$$V_L = -V_o$$

$$t_{on} + t_{off} = T_s$$

$$D = \frac{t_{on}}{T_s}$$

$$V_L = 0 = \frac{1}{T_s} \left[ \int_0^{t_{on}} (V_d - V_o) dt + \int_{-t_{on}}^{T_s} -V_o dt \right]$$

$$0 = (V_d - V_o)t_{on} - V_o(T_s - t_{on})$$

$$V_d t_{on} - V_o t_{on} - V_o T_s + V_o t_{on} = 0$$

$$V_d t_{on} = V_o T_s$$


$$\frac{V_o}{V_d} = \frac{t_{on}}{T_s} = D$$

$$V_o = D V_d$$

$$\frac{V_o}{V_d} = \frac{I_d}{I_o} = D$$

Continuous + Boundary

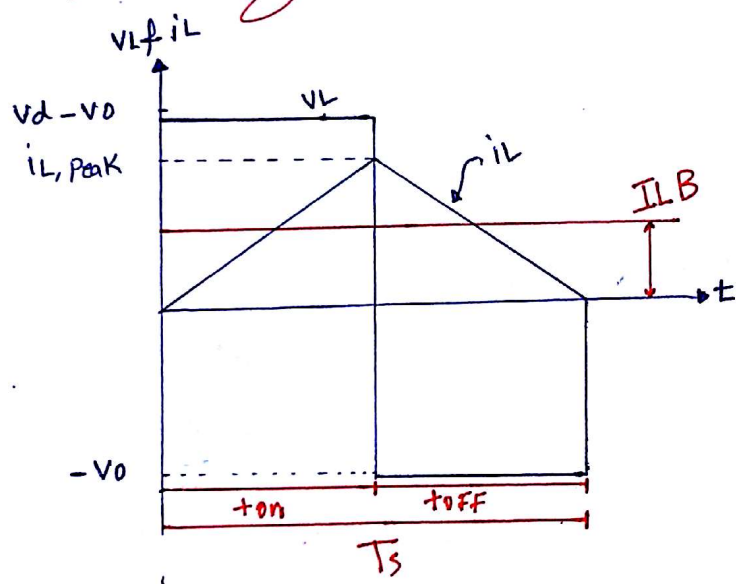\* Boundary Between Continuous & Discontinuous



$$I_{LB} = \frac{1}{T_s} \left[ \frac{1}{2} t_{on} i_{L,Peak} + \frac{1}{2} t_{off} i_{L,Peak} \right]$$

$$= \frac{1}{2} i_{L,Peak}$$

$$i_{L,Peak} = \frac{1}{L} (V_d - V_o) t_{on}$$


$$I_{LB} = \frac{1}{2} \frac{1}{L} (V_d - V_o) t_{on}$$

$$= \frac{t_{on}}{2L} (V_d - V_o)$$


$$I_{LB} = \frac{D T_s}{2L} (V_d - V_o)$$

$$= \frac{D T_s}{2L} V_d - \frac{D T_s V_o}{2L}$$
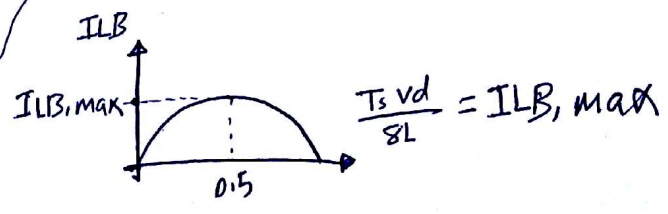
$$= \frac{D T_s}{2L} V_d - \frac{D^2 T_s V_d}{2L}$$



## \* Discontinuous Conduction Mode -

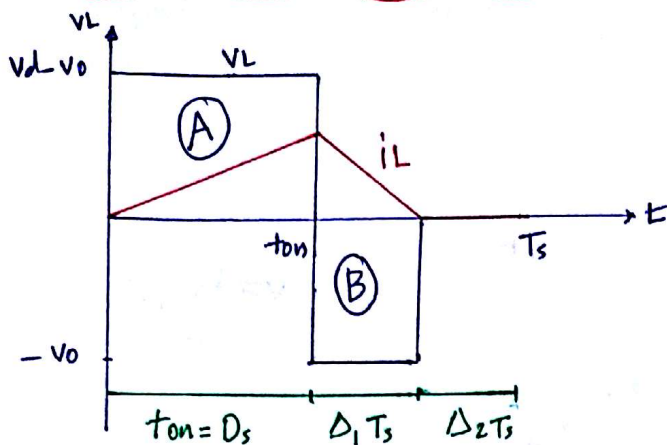

$$A = B$$

$$(v_d - v_o) D T_s = v_o \Delta_1 T_s$$

$$v_d D T_s = v_o \Delta_1 T_s + v_o \Delta_2 T_s$$

$$\frac{v_o}{v_d} = \frac{D}{D + \Delta_1}$$

$$I_L = \frac{1}{T_s} \left[ \frac{1}{2} i_{L, \text{Peak}} D T_s + \frac{1}{2} i_{L, \text{Peak}} \Delta_1 T_s \right]$$

$$I_L = i_{L, \text{Peak}} \left( \frac{D + \Delta_1}{2} \right)$$

$$i_{L, \text{Peak}} = \frac{v_d - v_o}{L} D T_s$$

$$i_{L, \text{Peak}} = \frac{v_o \Delta_1 T_s}{L}$$

$$I_L = \left( \frac{D + \Delta_1}{2} \right) \frac{v_o}{L} \Delta_1 T_s$$

$$= \left( \frac{D + \Delta_1}{2} \right) \frac{1}{L} \Delta_1 T_s \frac{D v_d}{D + \Delta_1}$$


$$I_L = \frac{v_d T_s}{2L} D \Delta_1$$

$$\Delta_1 = \frac{2L I_L}{v_d T_s D}$$

$$\frac{v_o}{v_d} = \frac{D}{D + \frac{2L I_L}{v_d T_s D}}$$

55

# \* Output Voltage Ripple \*

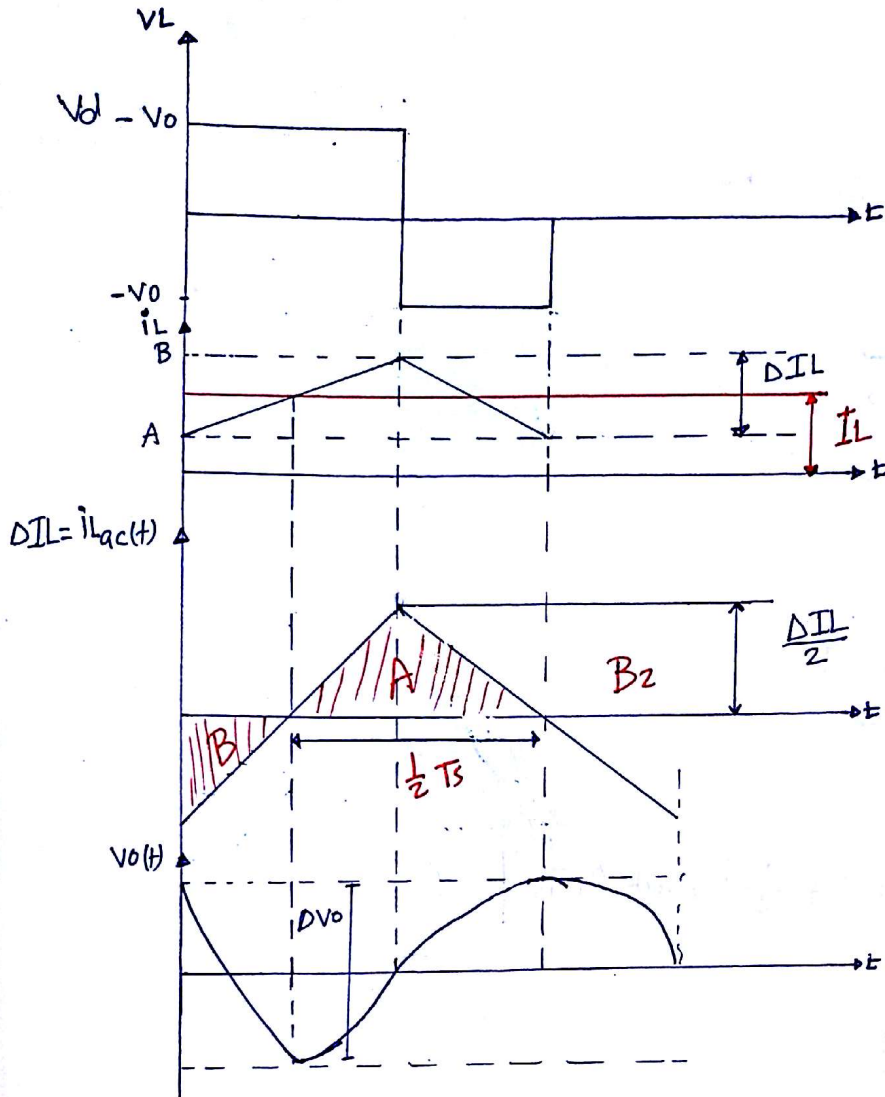

$$V = L \frac{di}{dt}$$

$$i_L(t) = i_{lac}(t) + I_L$$

$$\bar{V}_o = V_o + \underline{V_o(t)}$$

$$\Delta V_o = \frac{\Delta Q}{C} = \frac{1}{C} \cdot \frac{1}{2} T_s \cdot \frac{1}{2} \frac{\Delta I_L}{2}$$

$$\Delta I_L = \frac{V_o}{L} (1-D) T_s \Rightarrow ?$$


$$\Delta V_o = \frac{1}{8} \frac{T_s}{C} \frac{V_o}{L} (1-D) T_s$$

$$\frac{\Delta V_o}{V_o} = \frac{1}{8} \frac{T_s^2 (1-D)}{LC}$$

$$= \frac{1}{8} \frac{(1-D)}{f_s^2 LC}$$



# \* Step-UP (Boost) Converter 8-

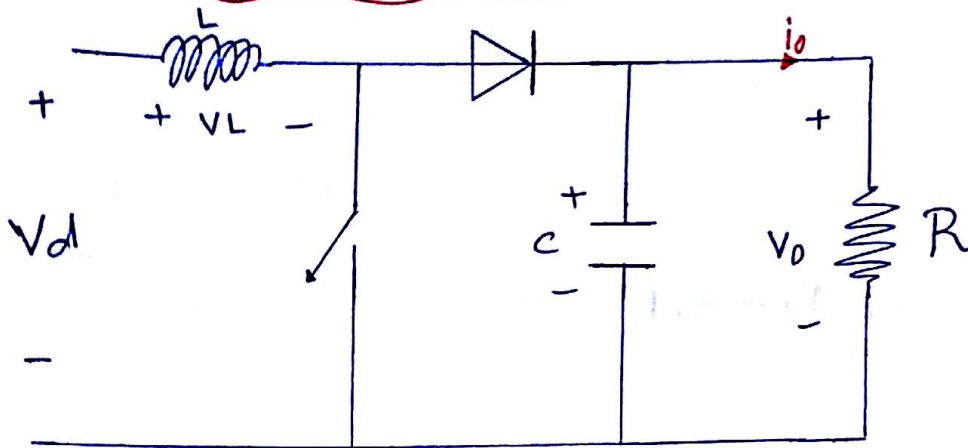


IF the Switch is "ON"

$$-V_d + V_L = 0 \Rightarrow V_L = V_d$$

IF the Switch is "OFF"

$$-V_d + V_L + V_o = 0$$

$$V_L = V_d - V_o$$

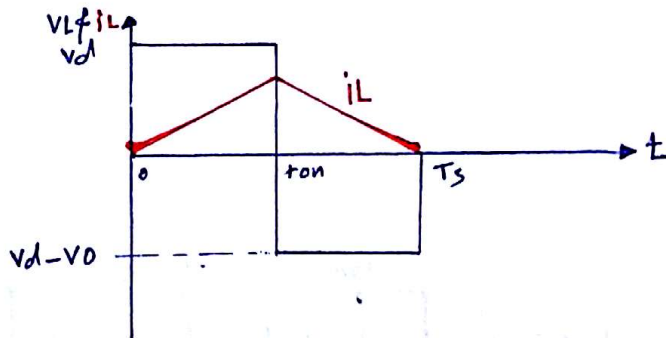

$$V_L = 0 = \frac{1}{T_s} \left[ \int_0^{t_{on}} V_d dt + \int_{t_{on}}^{T_s} (V_d - V_o) dt \right]$$

$$V_d t_{on} + (V_d - V_o)(T_s - t_{on}) = 0$$

$$V_d t_{on} + V_d T_s - V_d t_{on} - V_o T_s + V_o t_{on} = 0$$

$$V_d T_s + V_o (t_{on} - T_s) = 0$$


$$V_d T_s = V_o (T_s - t_{on})$$

$$\frac{V_o}{V_d} = \frac{T_s}{T_s - t_{on}}$$

$$= \frac{T_s}{T_s - DT_s}$$

$$\frac{V_o}{V_d} = \frac{1}{1-D} \geq 1 \quad \rightarrow D = 0.1$$

\* Buck-Boost Converter :-

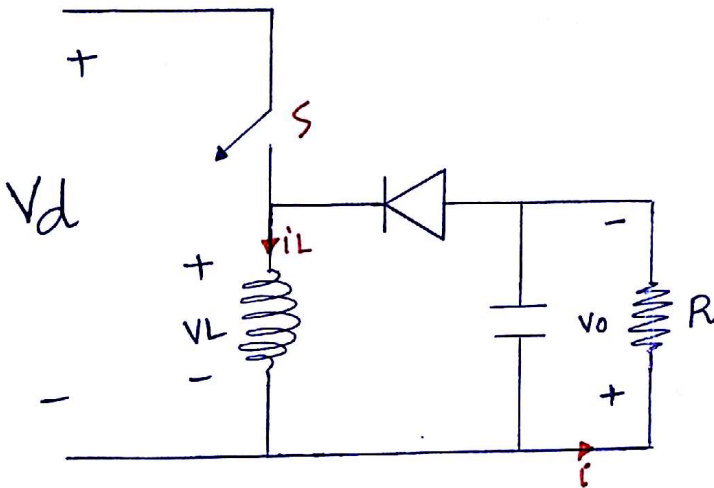


IF "S" "ON"

$$V_L = V_d$$

IF S "OFF"

$$V_L = -V_o$$

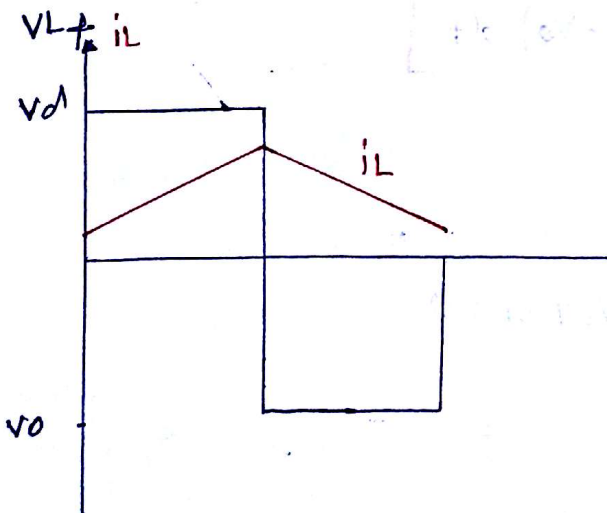

$$V_L = 0 = \frac{1}{T_s} \left[ \int_0^{t_{on}} V_d dt + \int_{t_{on}}^{T_s} -V_o dt \right]$$

$$V_d \cdot t_{on} - V_o (T_s - t_{on}) = 0$$

$$V_d t_{on} = V_o (T_s - t_{on})$$


$$\frac{V_o}{V_d} = \frac{t_{on}}{T_s - t_{on}} = \frac{DT_s}{T_s - DT_s} = \frac{D}{1-D}$$

0 < D ≤ 0.5 down  
0.5 ≤ D < 1 UP
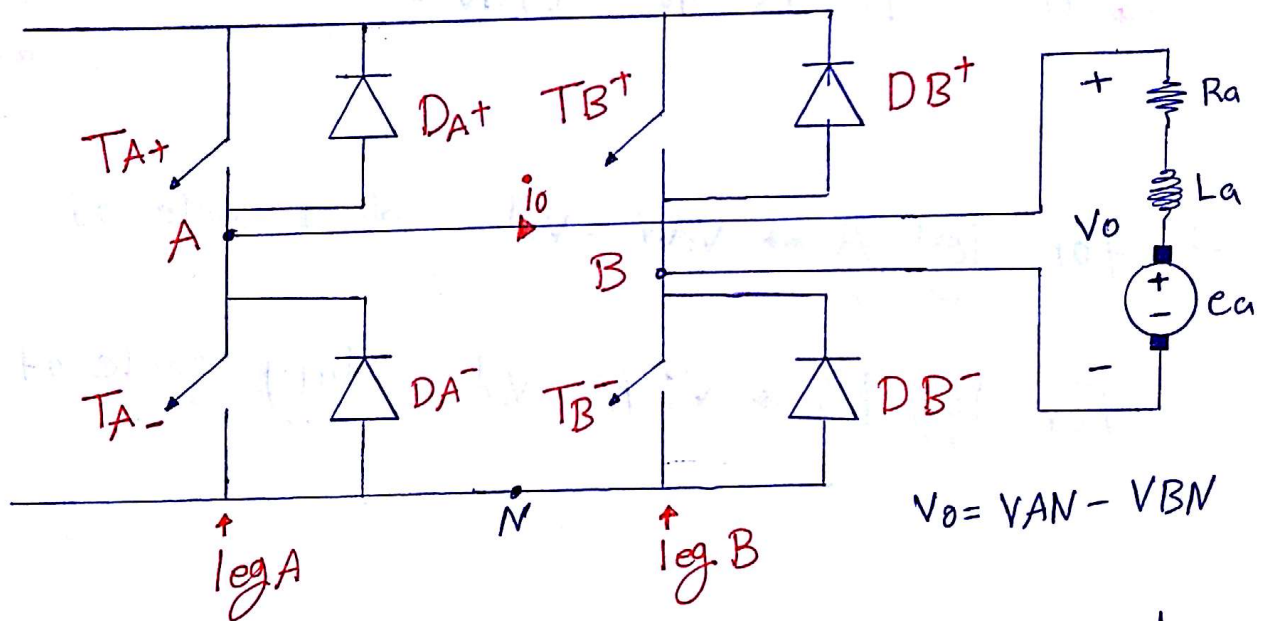
## \* Full - Bridge Dc - Dc Converter :-


→ Application :-

- 1] Dc Motor drives.
- 2] Dc - Ac inverters.
- 3] Renewable energy systems.
- 4] regulated power supplies.



ON state of the switch :- the switches ON and may or may not conduct the current (depending of the direction current)

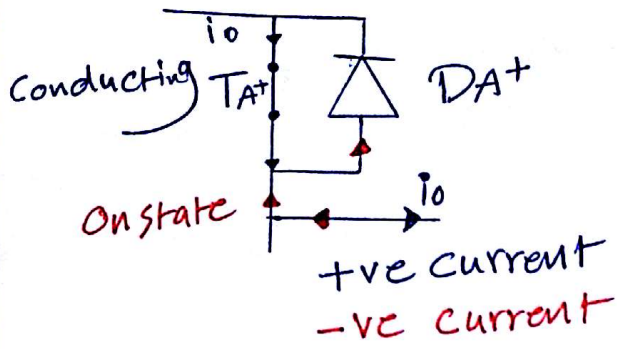conduct state of the switch :- the switch is on and the current flows through it




ONstate = Cond  
 Cond = onstate  
 و SV میں کونڈیشن  
 Cond = onstate

→ IF  $T_{A^+}$  is ON  $V_{AN} = V_d$

→ IF  $T_{B^+}$  is ON  $V_{BN} = V_d$

→ IF  $T_{A^-}$  is ON  $V_{AN} = 0$

→ IF  $T_{B^-}$  is ON  $V_{BN} = 0$

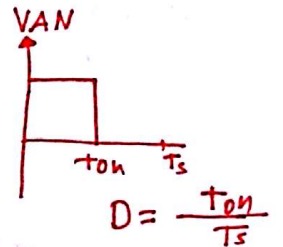

\* For leg A  $\Rightarrow V_{AN} = V_d$  duty cycle of  $T_{A^+}$


For leg B  $\Rightarrow V_{BN} = V_d$  duty cycle of  $T_{B^+}$


\* PWM with "bipolar voltage" Switching

$(T_{A+}, T_{B-})$  ON &  $(T_{B+}, T_{A-})$  ON

1<sup>st</sup> Part of  $T_s$

2<sup>nd</sup> Part of  $T_s$

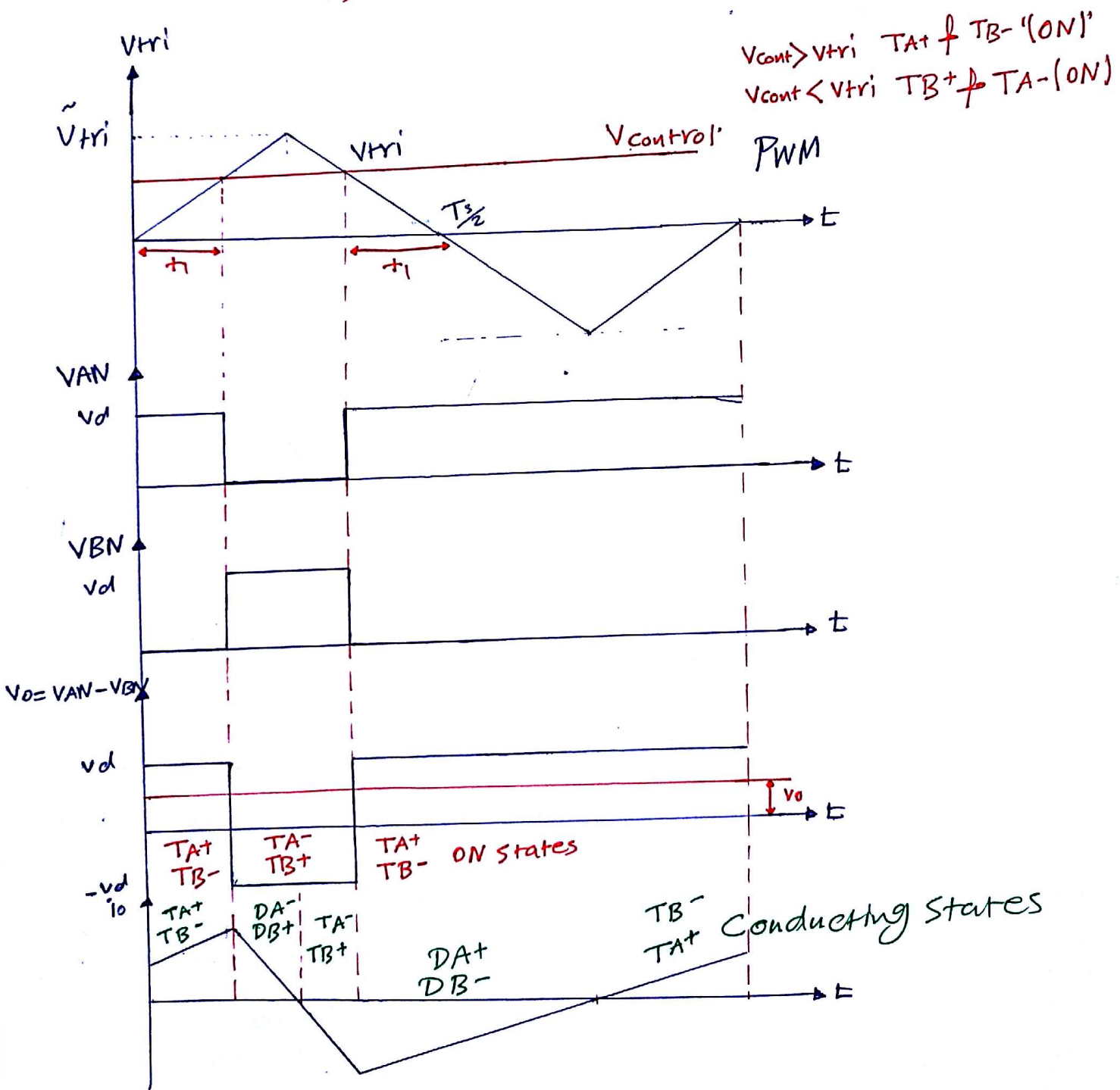

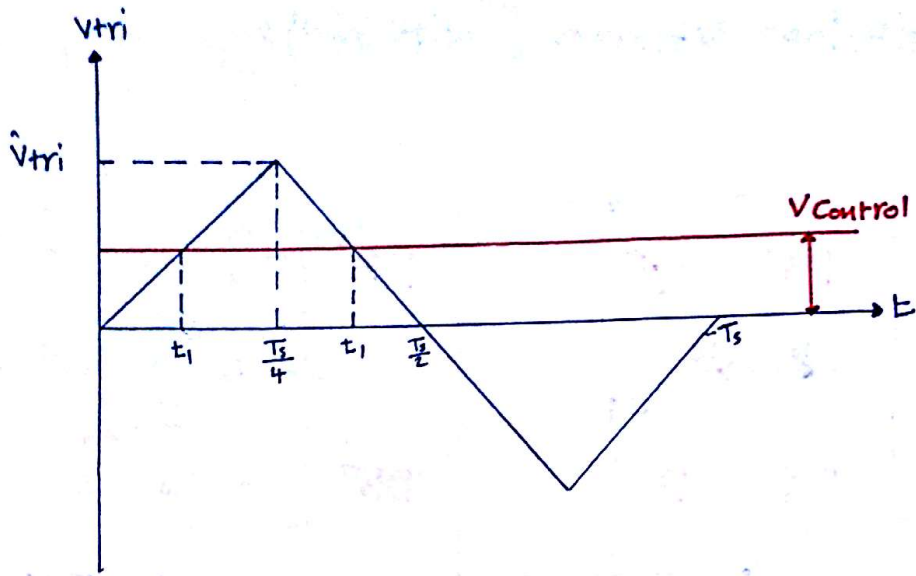

$$v_{tri} = \frac{\hat{v}_{tri}}{\frac{T_s}{4}} t \quad 0 < t < \frac{T_s}{2}$$

$$v_{tri} = \frac{4\hat{v}_{tri}}{T_s} t$$

$$\text{at } t = t_1, V_{control} = \frac{4\hat{v}_{tri}}{T_s} t_1$$

$$t_1 = \frac{V_{control} T_s}{4\hat{v}_{tri}}$$

\* The on duration of  $TA^+$   $TB^-$  is

$$t_{on} = 2t_1 + \frac{1}{2} T_s$$

$$D_1 = \frac{t_{on}}{T_s} = \frac{2t_1 + \frac{1}{2} T_s}{T_s} = \frac{2 \left( \frac{V_{control} T_s}{4\hat{v}_{tri}} \right) + \frac{1}{2} T_s}{T_s}$$

$$D_1 = \frac{1}{2} \left( 1 + \frac{V_{control}}{\hat{v}_{tri}} \right)$$

\* The on duration of  $TB^+$   $TA^-$  is

$$D_2 = 1 - D_1 = 1 - \frac{t_{on}}{T_s}$$

$$= 1 - \frac{1}{2} \left( 1 + \frac{V_{control}}{\hat{v}_{tri}} \right)$$



$$V_o = V_{AN} - V_{BN}$$

$$= D_1 V_d - (1 - D_1) V_d$$

$$= (2D_1 - 1) V_d$$

$$V_o = \frac{V_{control}}{\hat{v}_{tri}} V_d = K V_d$$

# PWM with Unipolar Voltage Switching :-

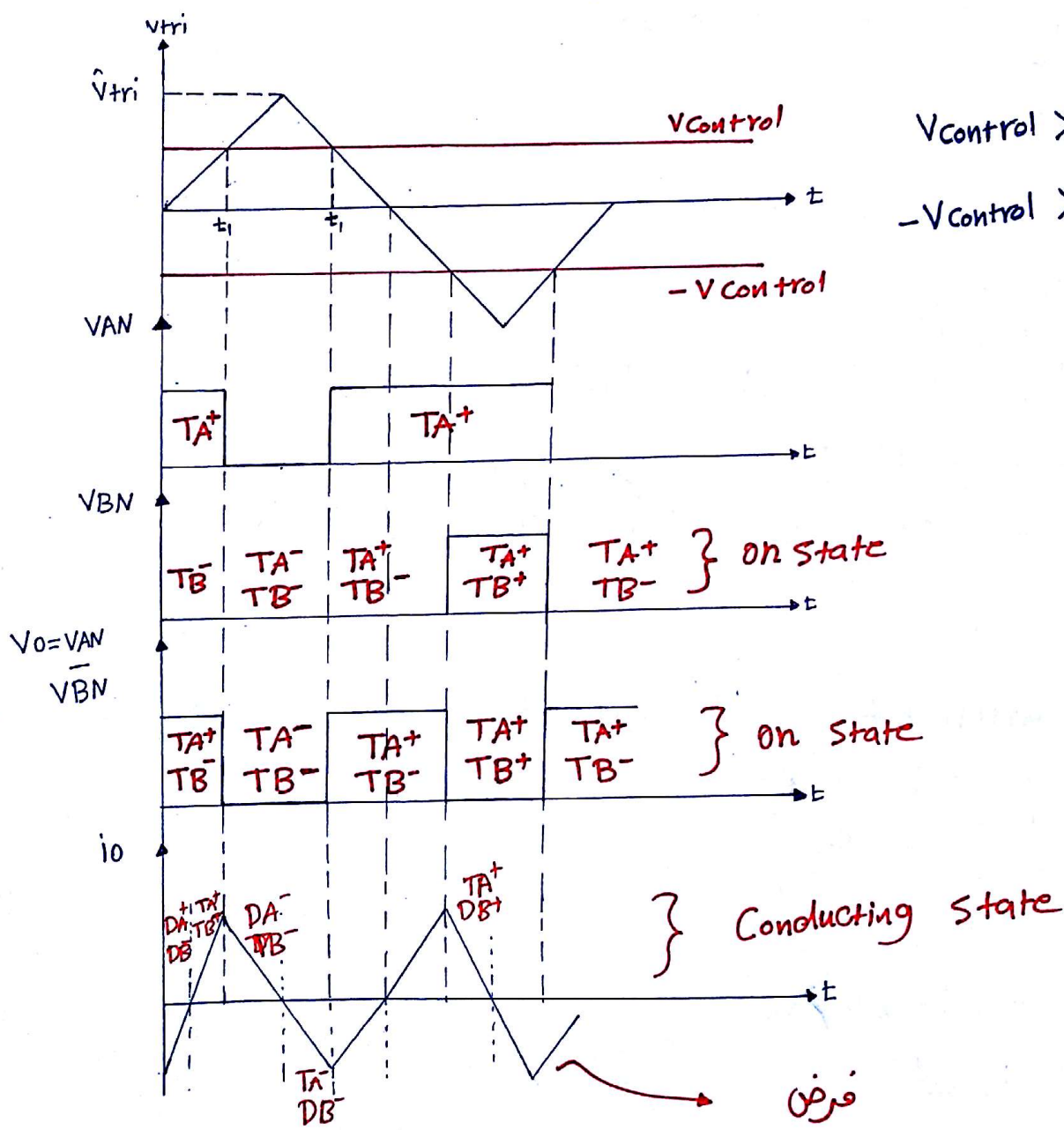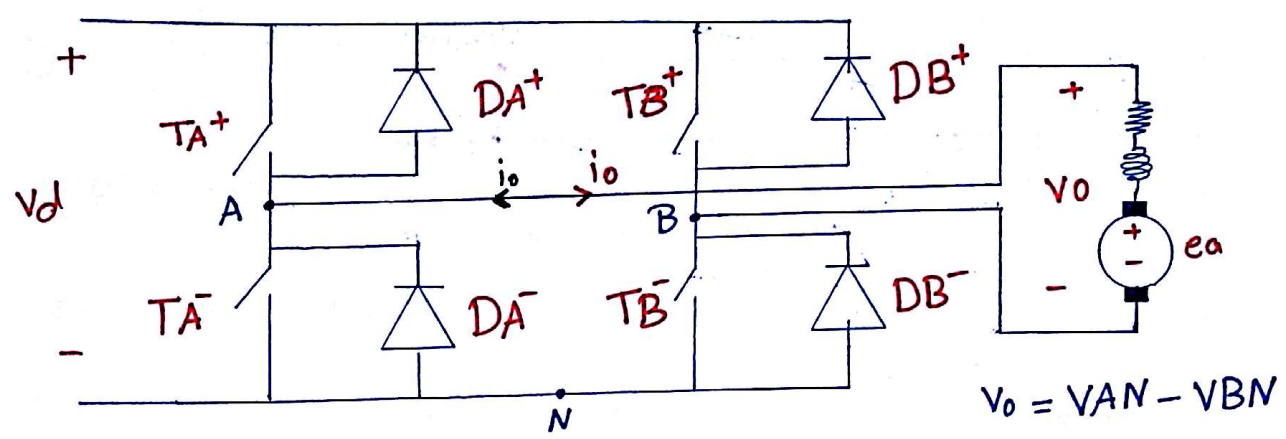

$$V_o = \frac{V_{control}}{V_{tri}} V_{dL} = K V_{dL}$$

# \* Switch Mode Dc - AC Inverters 8-

\* Dc - Sinusoidal AC

\* Applications 8-

a- Ac motor drives.


b- Ups

c- Renewable Energy System

PV





wind

Fc

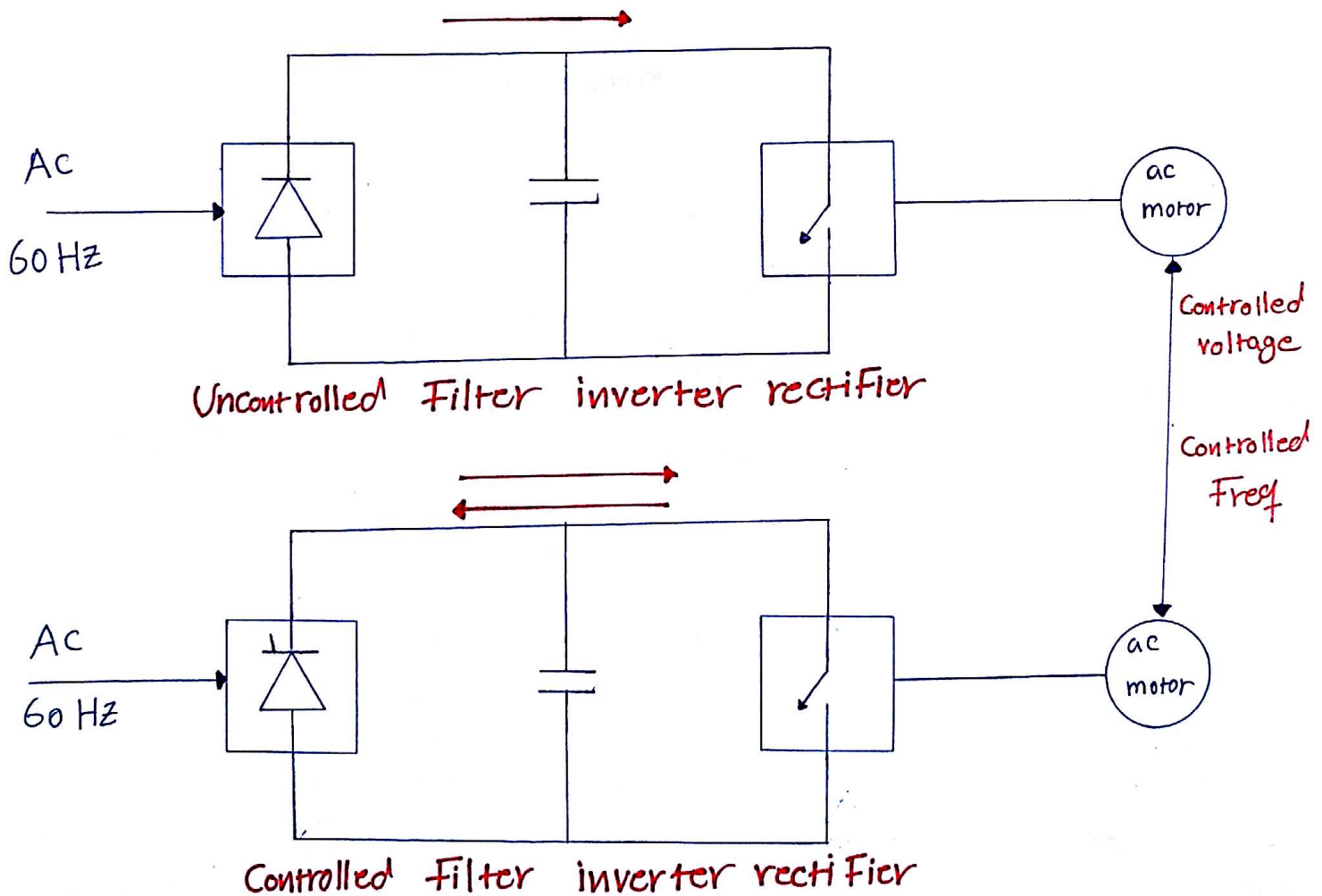




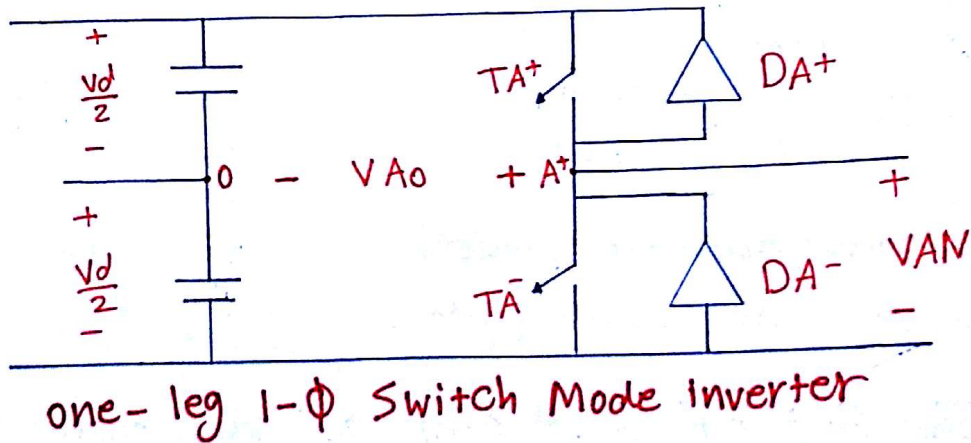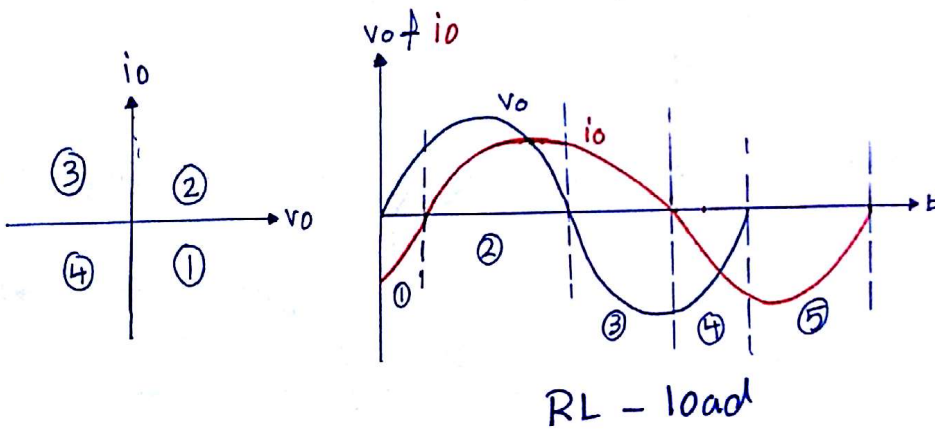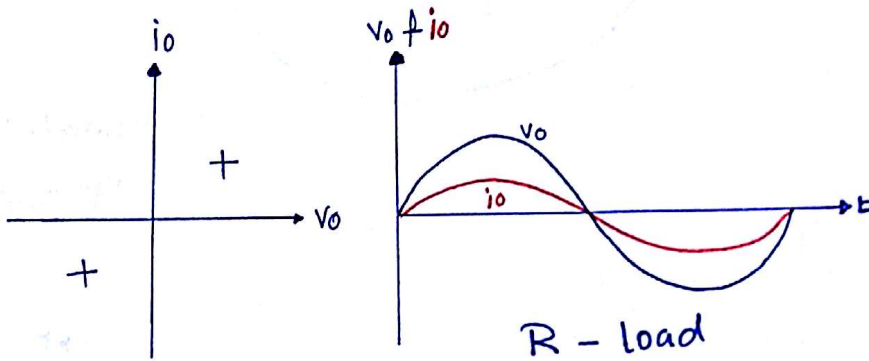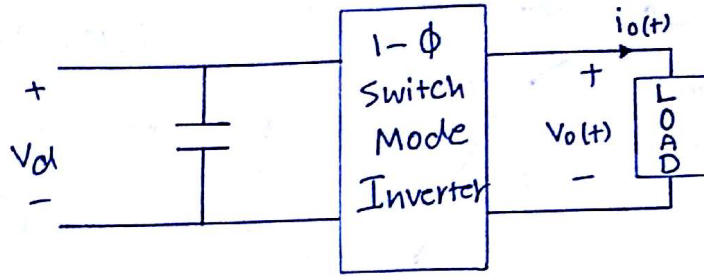\* Basic Concept of Switch Mode Inverters \*


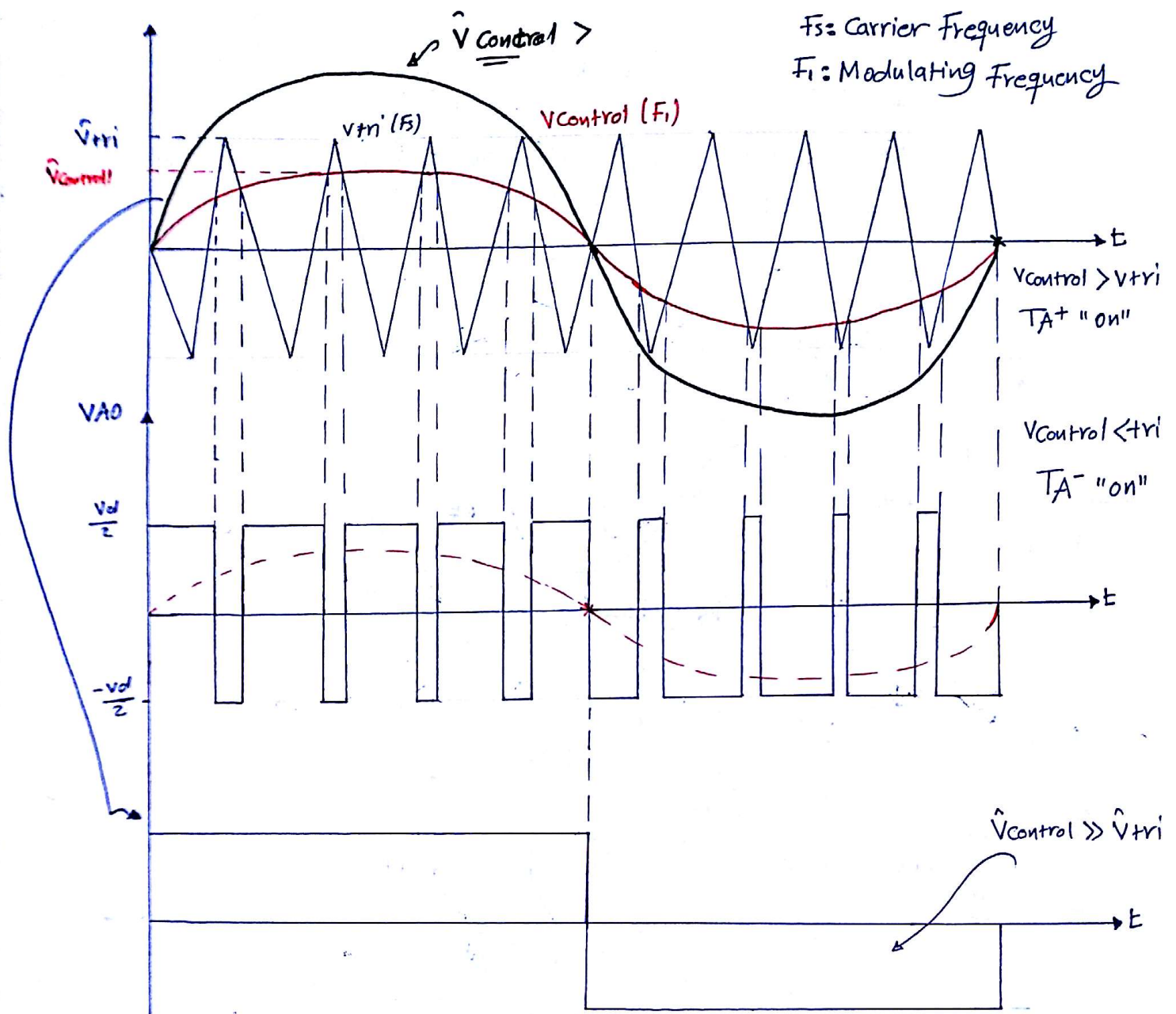
# \* Pulse-Width-Modulated Switching Scheme




$$m_a = \frac{V_{Control}}{V_{tri}}$$

$$MF = \frac{F_s \sim tri}{F_i \sim Control}$$

$m_a$ : amplitude modulation ratio (index)

$MF$ : Frequency modulation ratio (index)

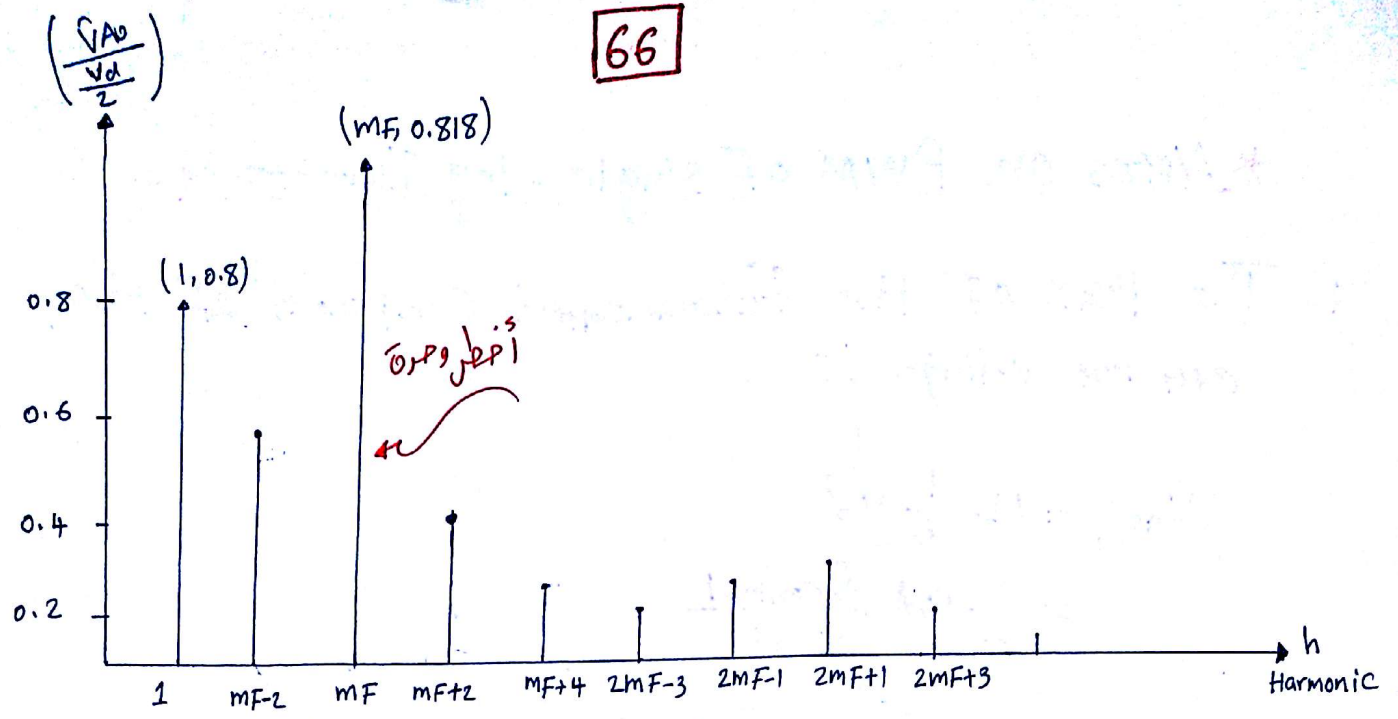Note:- The Freq of Fund Comp of the output voltage  $V_{AO}$  is the Freq of the Control Signal.



### Harmonic Spectrum of VAO for $\alpha = F_1$


$m_a = 0.8 \quad \neq \quad m_F = 15$

$(V_{AO})_1 = 0.8 \frac{V_d}{2}$

$(V_{AO})_1(t) = 0.8 \frac{V_d}{2} \sin \omega_1 t$   $\rightarrow 2\pi F_1$

$(\hat{V}_{AO})_{15} = (0.818) \frac{V_d}{2}$

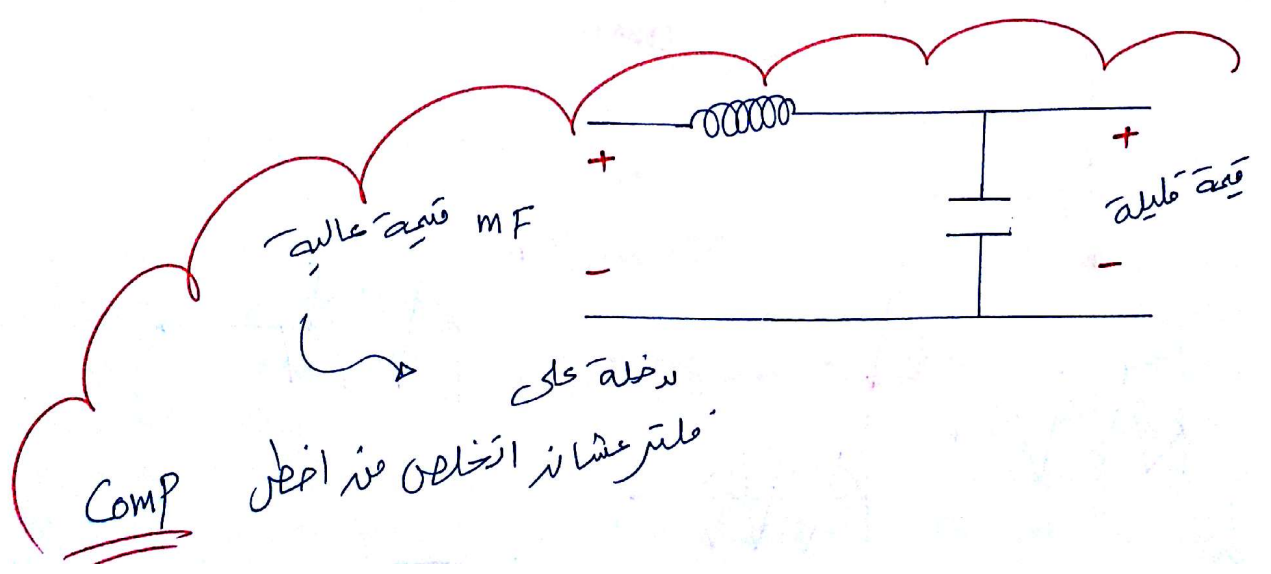$(V_{AO})_{15} = 0.818 \frac{V_d}{2} \sin (15 \omega_1) t$



## \* Notes on PWM of single-leg Inverter :-

- 1- The Peak of the Fundamental Component of the output voltage is

$$\begin{aligned} (\hat{V}_{Ao})_1 &= m_a \frac{1}{2} v_d \\ &= \frac{1}{2} v_d \frac{\hat{v}_{control}}{\hat{v}_{tri}} \end{aligned}$$


$$(V_{Ao})_1(t) = \frac{1}{2} m_a v_d \sin(\omega_1 t), \quad \omega_1 = 2\pi F_1$$


- 2- The harmonics in the inverter output voltage appear as sidebands centered around the switching frequency and its multiples (around  $mF$ ,  $2mF$ ,  $3mF$ , ...)

- 3- The frequencies at which voltage harmonics occur:


$$F_h = (jmF \pm k) F_1 \quad \begin{array}{l} \text{with odd } j \rightarrow k \text{ is even} \\ \text{with even } j \rightarrow k \text{ is odd} \end{array}$$

over modulation ( $m_a > 1$ )

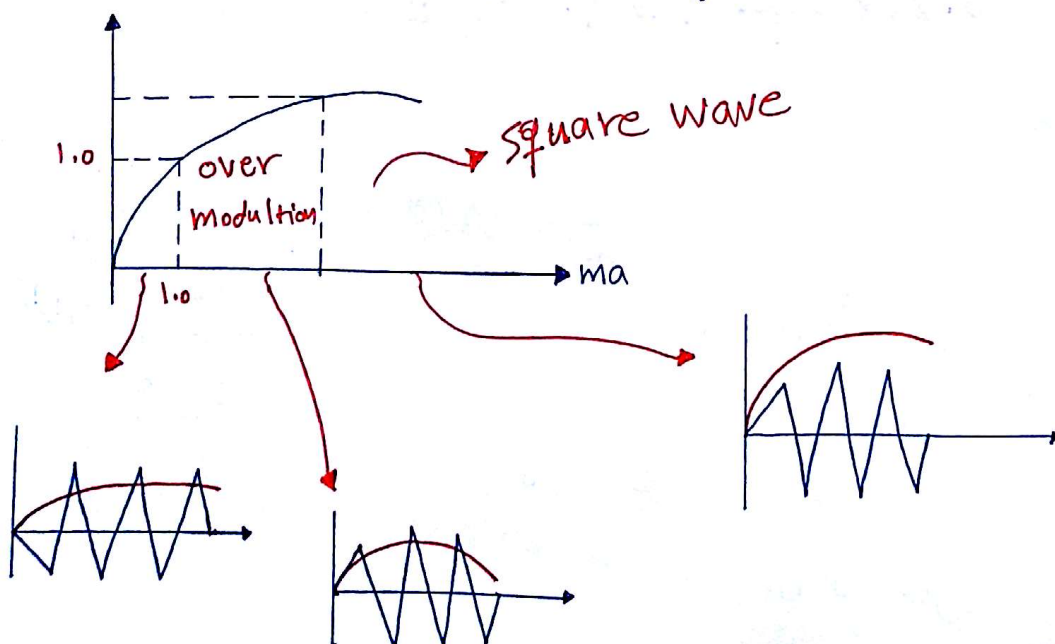

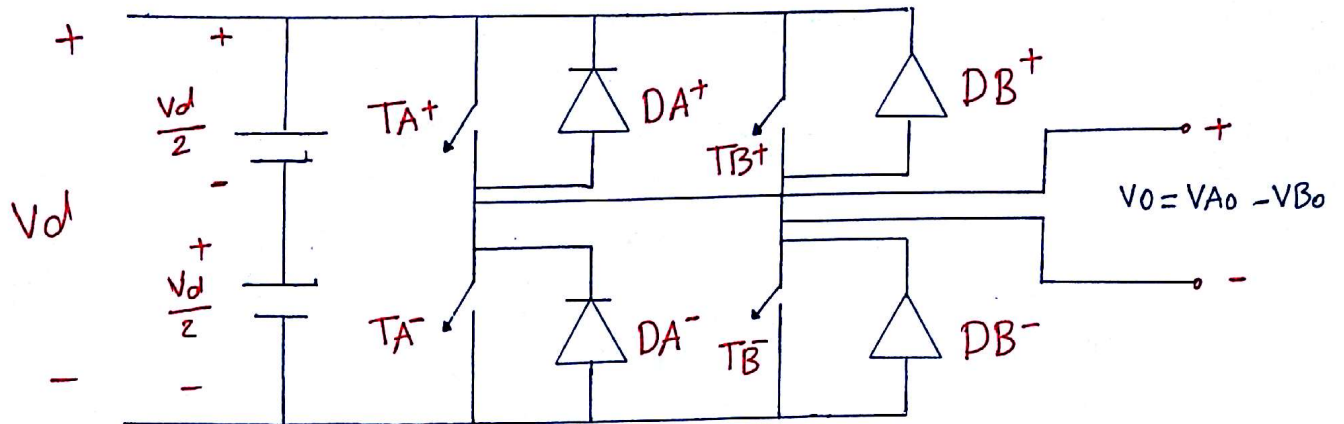

1- $\phi$  Full-Bridge Inverter

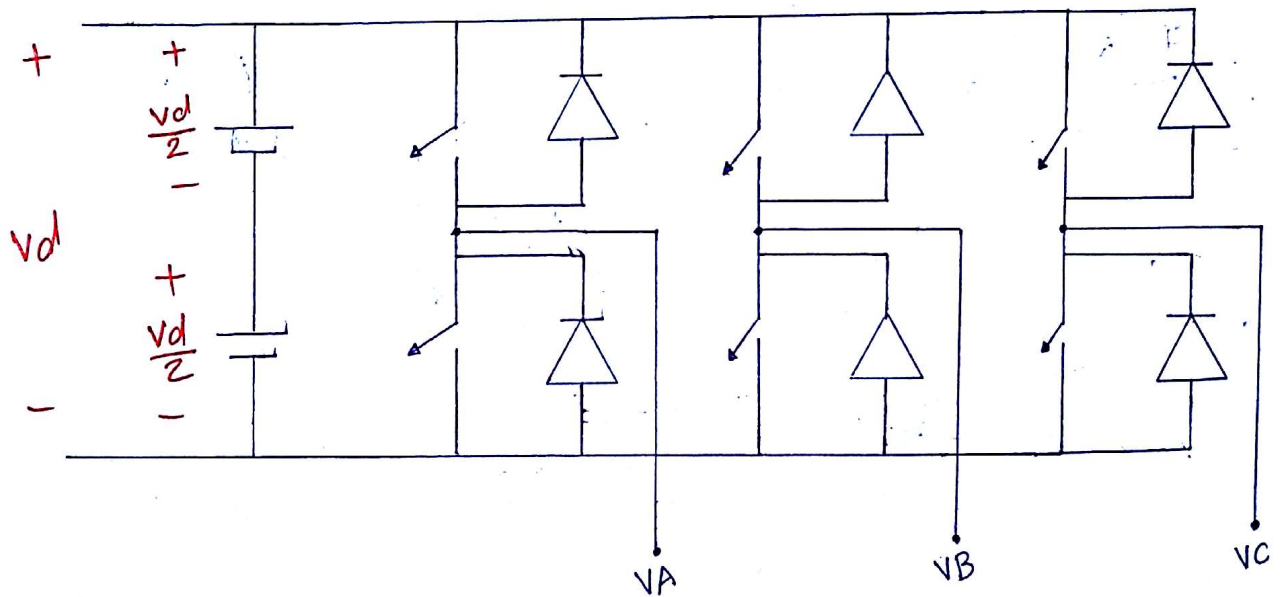

3- $\phi$  Full Bridge Inverter

(3 Control Signals)

⇓  
Sinusoidal Phase Shifted  $120^\circ$