



تقدم لجنة EiCoM الاكاديمية

دفتر لمادة:

الالكترونيات القوى


من شرح:

د. محمد الوديان

جزيل الشكر للطالب:

نمر عودة



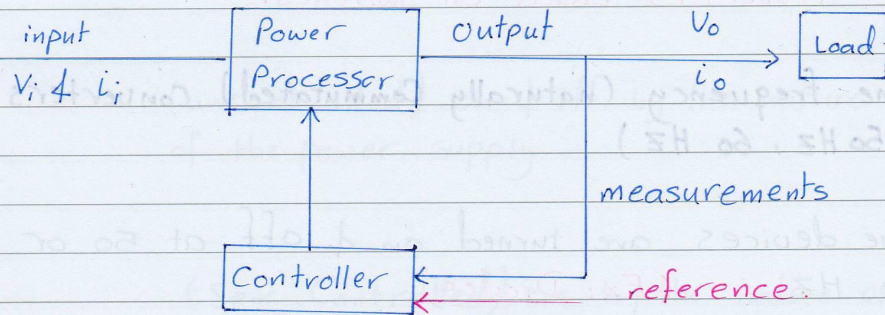

Block diagram of power electronic system (Generic)


Types of Power Processors:

1) DC

- a) regulated magnitude
- b) adjustable magnitude.

2) AC

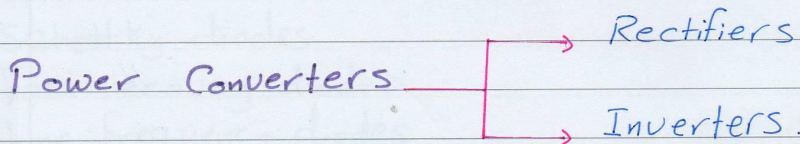
- a) Constant frequency adjustable magnitude.
- b) adjustable frequency adjustable magnitude.



Converters: 1) $1\phi, 3\phi$ ac to dc \equiv rectifier Controlled
UncOntrolled

2) $1\phi, 3\phi$ dc to ac \equiv inverter

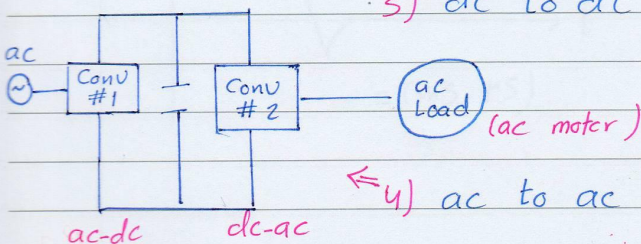3) dc to dc \equiv Converter Step up
Step down
Stepup-Stepdown
full bridge



4) ac to ac \equiv rectifier + inverter

- Types of converters based on switches:-

1) Line frequency (naturally Commutated) converters
(50 Hz, 60 Hz)

The devices are turned on & off at 50 or 60 Hz. (Ex: Diodes)


2) Switched (forced commutated) converters
(15 kHz - 30 kHz)

The devices are turned on & off at frequencies much higher than the line frequency [15kHz-30kHz]

According to the degree of controllability :

- 1) Diodes: (uncontrolled) on & off by the nature of the power supply
- 2) Thyristors: (Semi-Controlled) on by the nature of the power supply + additional control signal and off by the nature of the supply.
- 3) Controllable Switches: (Controlled) on & off by additional control signal (BJT, MOSFET, GTO, IGBT)

1) Diodes


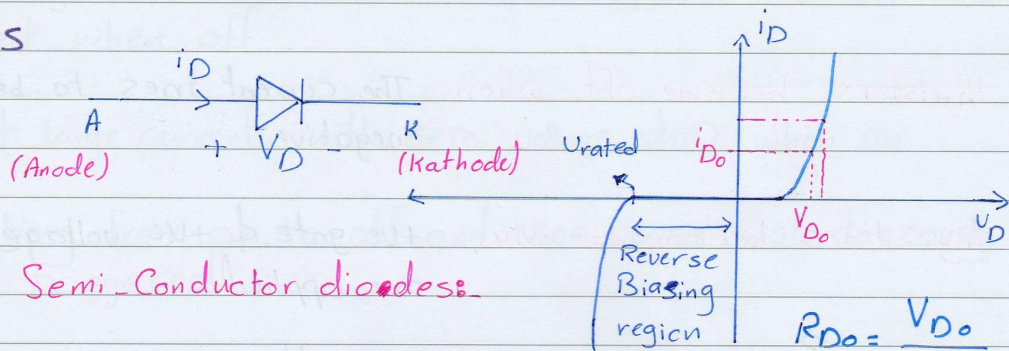


Power Semi-Conductor diodes:



- 1) Schottky diodes $\leftarrow (50-100) V_{rated}$
- 2) Fast recovery diodes
- 3) Line Frequency diodes

*check V_{rated} From the book

$i-v$ Char.



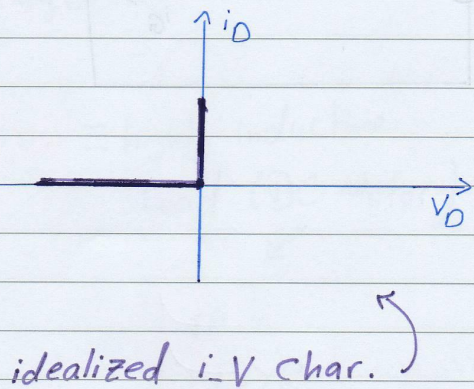
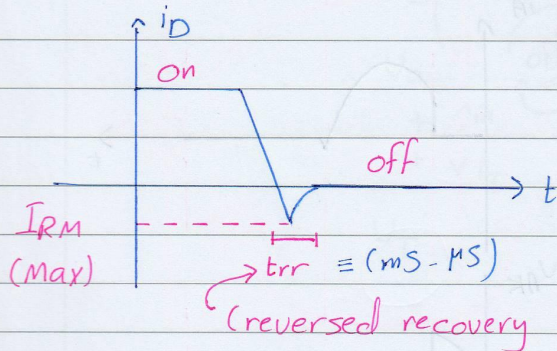



2] Thyristors:

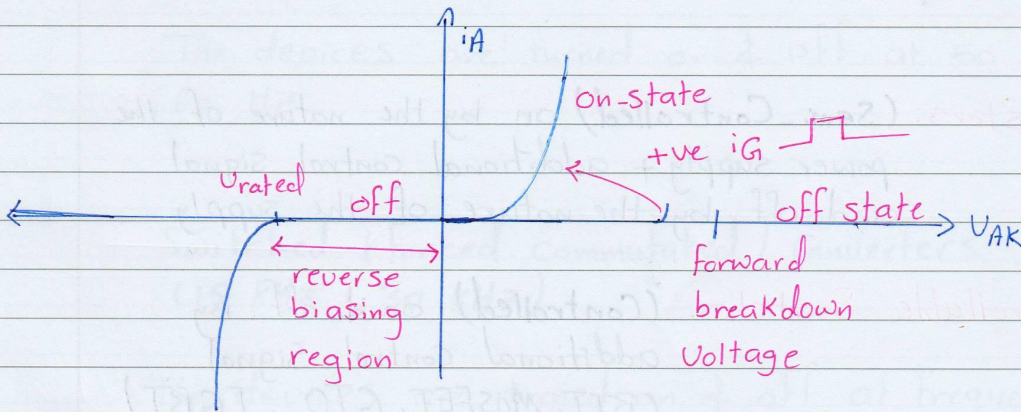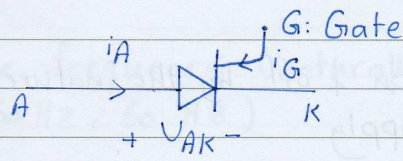

The thyristors become off when: The current tries to be negative

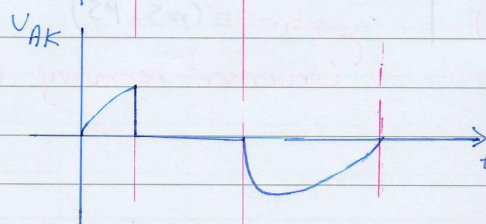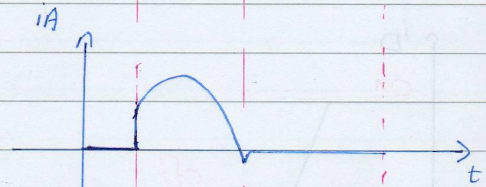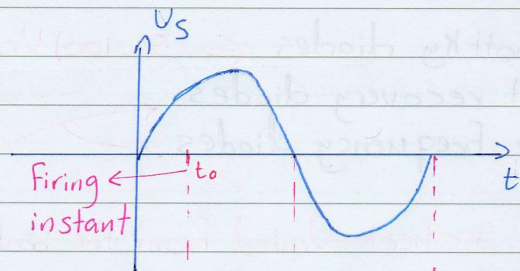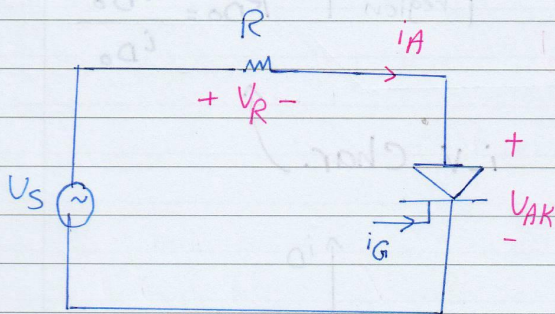The thyristors become on when: +ve gate & +ve voltage are applied.



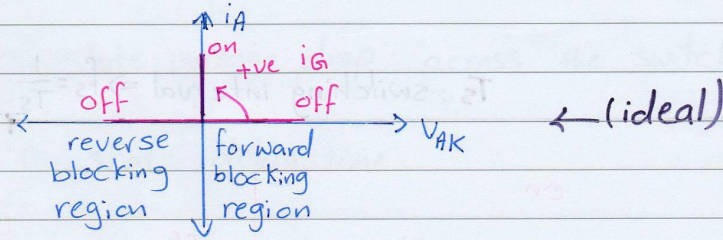


Types of thyristors:-

- 1) Phase Controlled thyristors
- 2) Inverter grid thyristors.
- 3) Light activated thyristors.

Desired characteristics of controllable switches (BJT, MOSFET, IGBT, GTO):




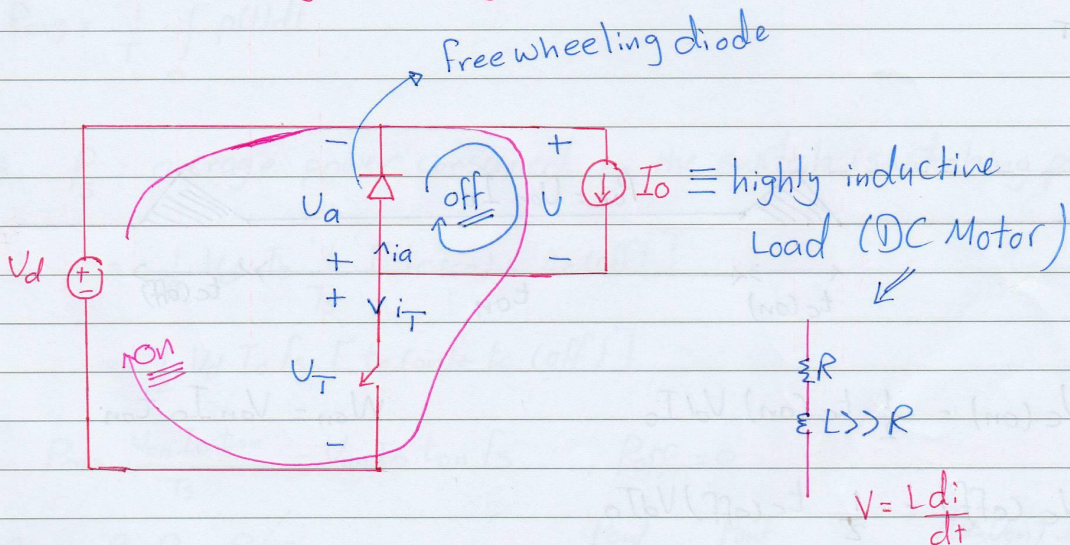
- 1) Block large forward and reverse voltages with zero current when off.
- 2) Conduct large currents with zero voltage drop when on.
- 3) Switching from on to off and vice versa instantaneously when triggered
- 4) Zero power consumption when on, off and during switching

Consider the following commonly encountered circuit in P.E:




Switch control signal

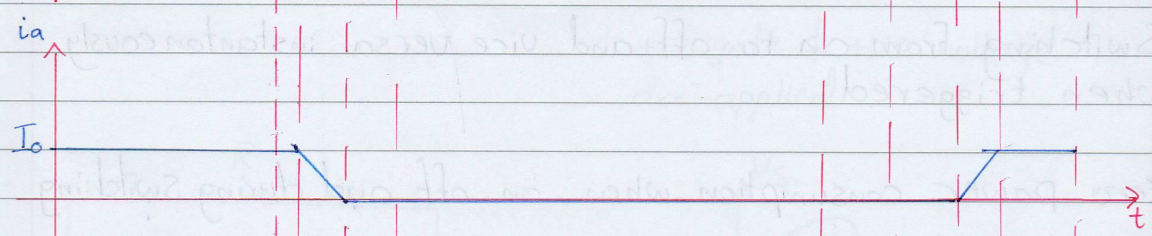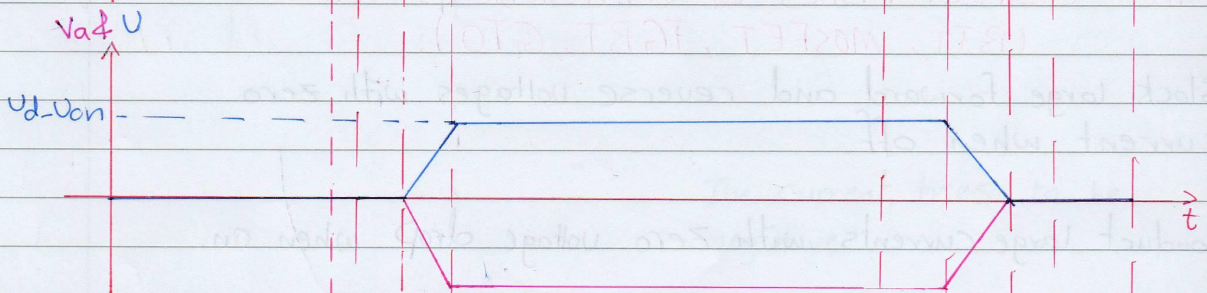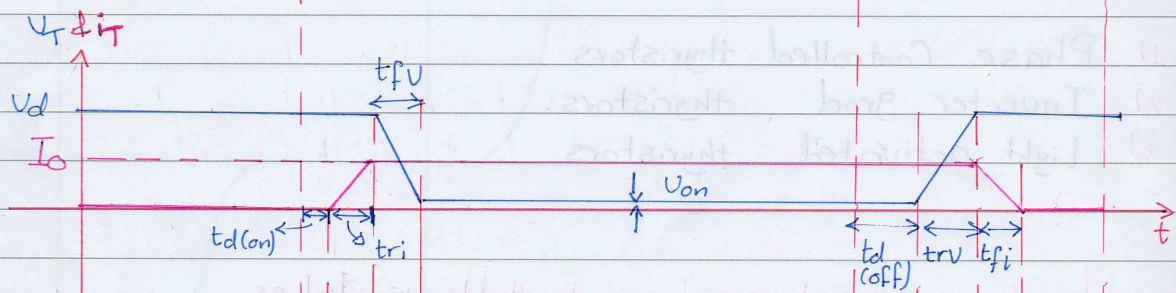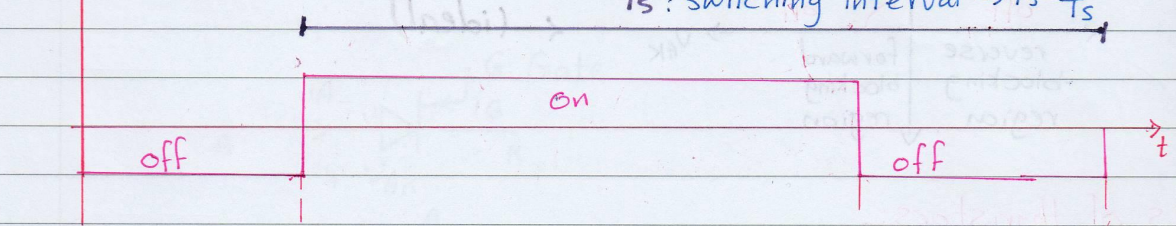T_s : switching interval $\Rightarrow f_s = \frac{1}{T_s}$



$P_T = V_T I_T$

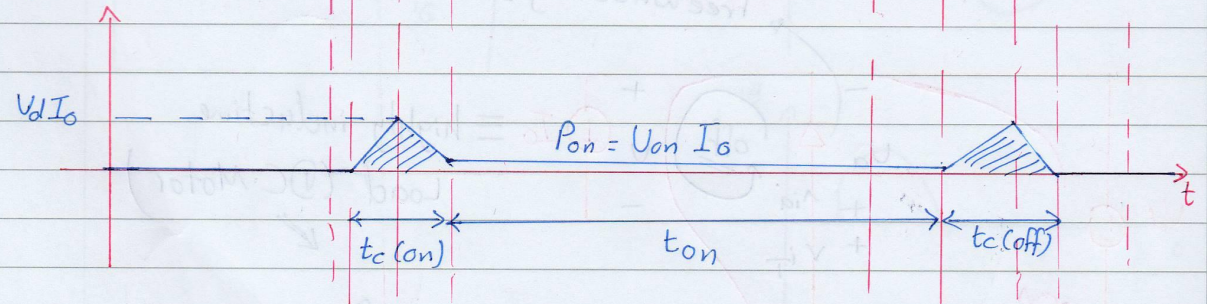

$$W_{c(on)} = \frac{1}{2} t_{c(on)} V_d I_o$$

$$W_{on} = V_{on} I_o t_{on}$$

$$W_{c(off)} = \frac{1}{2} t_{c(off)} V_d I_o$$

V_{on} : On state voltage drop across the switch.

$t_{d(on)}$: On state delay time

t_r : rising time for the current

t_{fv} : falling time for the voltage.

$t_{d(off)}$: Off state delay time

t_{rv} : rising time for the voltage.

t_{fi} : falling time for the current

$$V_d = U + V_T$$

$$\frac{dV_d}{dt} = \frac{dU}{dt} + \frac{dV_T}{dt}$$

$$0 = \frac{dU}{dt} + \frac{dV_T}{dt}$$

$$\frac{dU}{dt} = -\frac{dV_T}{dt}$$

$$I_o = i_a + i_T$$

$$\frac{dI_o}{dt} = \frac{di_a}{dt} + \frac{di_T}{dt} = 0$$

$$\frac{di_a}{dt} = -\frac{di_T}{dt}$$

$$\Rightarrow V_a + U = 0 \Rightarrow V_a = -U$$

$$\Rightarrow P_{avg} = \frac{1}{T} \int_0^T p(t) dt$$

P_s = average power consumed by the switch (switching power)

$$= \frac{1}{2} V_d I_o \frac{1}{T_s} [t_{c(on)} + t_{c(off)}]$$

$$= \frac{1}{2} V_d I_o f_s [t_{c(on)} + t_{c(off)}]$$

$$P_{on} = \frac{V_{on} I_o t_{on}}{T_s} = V_{on} I_o t_{on} f_s, \quad P_{off} = 0 \Rightarrow i_T = 0 \text{ during the off state}$$



$$P_{total} = P_s + P_{on} + P_{off} \Rightarrow \eta_{switch} \% = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{total}} \times 100 = \frac{(V_d - V_{on}) I_o}{(V_d - V_{on}) I_o + P_s + P_{on}}$$

P.7


* From the above discussions, the following cha. in the controllable ~~switches~~ switches are desired.

- 1) Small Leakage (Reversed) current in the off state.
- 2) Small on state voltage drop.
- 3) Short turn on & turn off time intervals. ($P_{sw} < 0$)
- 4) High on state current rating.
- 5) Small power consumed by the control circuit.




3] Bipolar Junction Transistor (BJT)

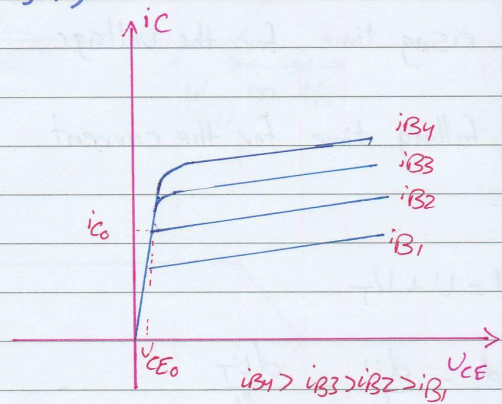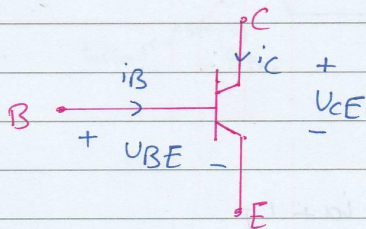

Current controlled device (i_B)

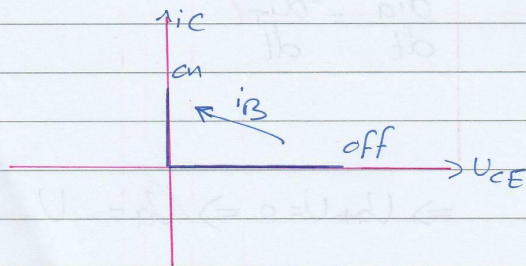


4] MOSFET

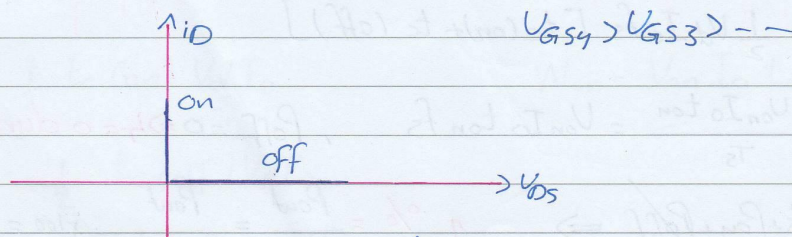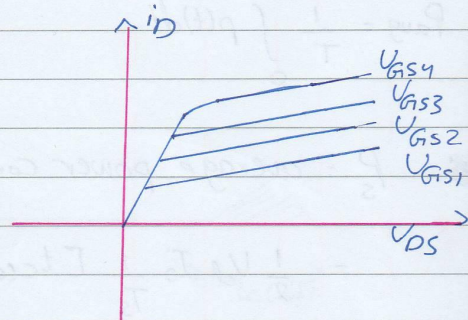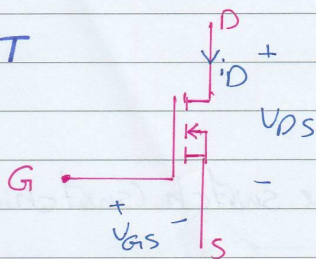

Voltage Controlled device.

5] Gate-Turn-Off Thyristors

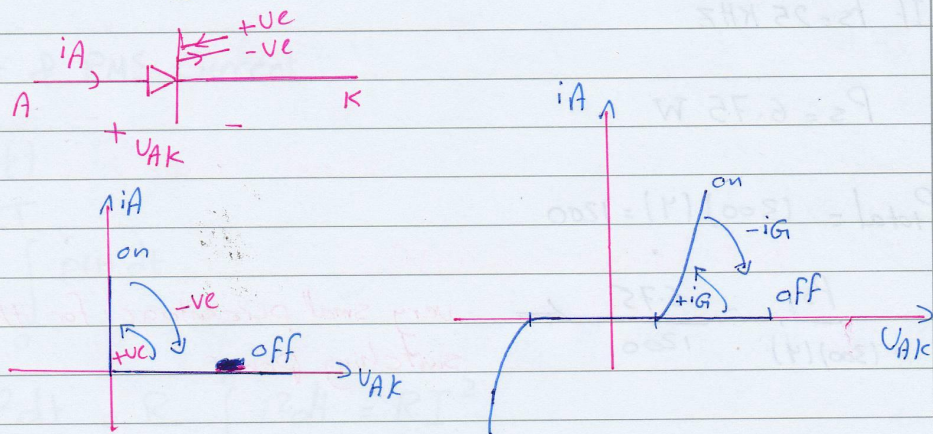

Description: Like the thyristor, GTO is turned on by +ve gate pulse. Unlike the thyristor, GTO is turned off by -ve gate pulse.

Idealized Cha. of controllable switches:

- 1] Zero on-state voltage drop.
- 2] Zero reversed current in the off-state.
- 3] Zero time duration for switching.
- 4] Power required for the control circuit is zero.

$$\begin{bmatrix} P_{on} = \text{Zero} \\ P_{off} = \text{Zero} \\ P_s = \text{Zero} \end{bmatrix}$$

Note: The switches will be treated in this course as ideal, because:

- 1] On-state voltage drop is very small compared with the operating voltage.
- 2] Off-state reversed current is very small compared with rated current.
- 3] Switching time is very small compared with the switching frequency.

P. 2.1 $t_{ri} = 100 \text{ ns}$, $t_{fv} = 50 \text{ ns}$, $t_{rv} = 100 \text{ ns}$, $t_{fi} = 200 \text{ ns}$.
 $V_d = 300 \text{ V}$, $I_o = 4 \text{ A}$, $P_s = ?$

$$P_s = \frac{1}{2} V_d I_o f_s [t_{c(on)} + t_{c(off)}] = \frac{1}{2} (300)(4) f_s [t_{ri} + t_{fv} + t_{rv} + t_{fi}]$$

$$P_s = 2.7 \times 10^{-4} f_s \Rightarrow P_s \propto f_s$$



⇒ If $f_s = 25 \text{ KHz}$

$$P_s = 6.75 \text{ W}$$

$$P_{\text{total}} = (300)(4) = 1200$$

$$\frac{P_s}{(300)(4)} = \frac{6.75}{1200} \leftarrow \text{very small percentage for the switching power.}$$

P.2.2

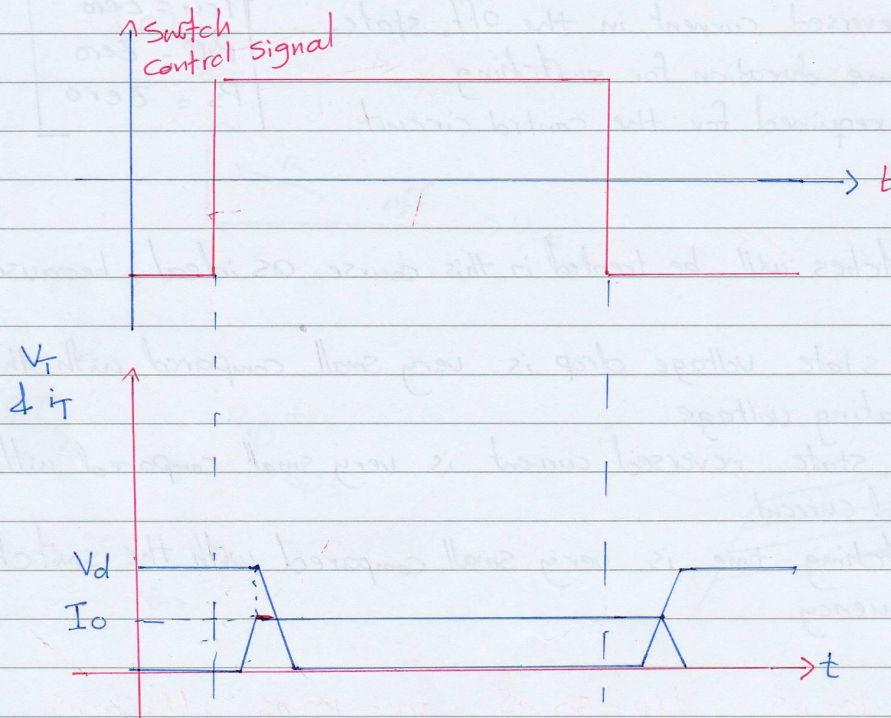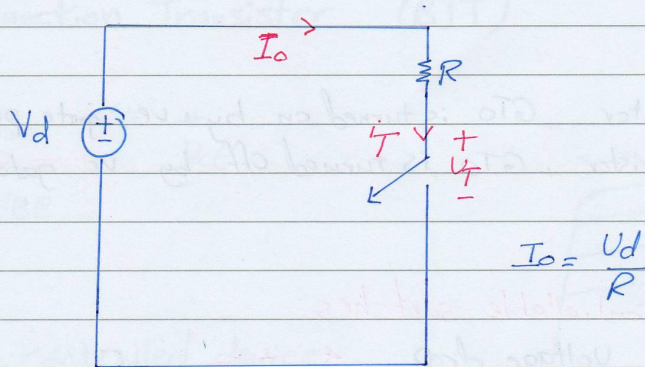

Chp3: Review of Basic Electrical Circuits Concepts

Lml
28-5-2017

Average Power & RMS Current


$P(t) = V(t)i(t) \Rightarrow$ instant. Power.

$P_{avg} = P = \frac{1}{T} \int_0^T p(t) dt$, $P = P(t) \Rightarrow$ in case of 3- ϕ system.

$P_{avg} = \frac{1}{T} \int_0^T R i^2 dt = \frac{R}{T} \int_0^T i^2 dt = R I^2$



$\Rightarrow I = \sqrt{\frac{1}{T} \int_0^T (i(t))^2 dt}$ rms.

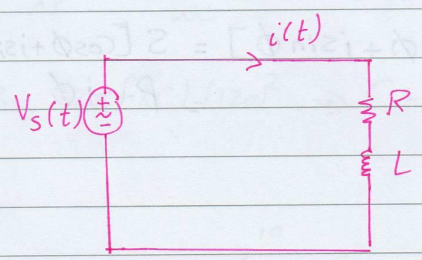Steady-State ac waveforms with sinusoidal voltages & currents.



$v_s(t) = \sqrt{2} V \cos(\omega t)$

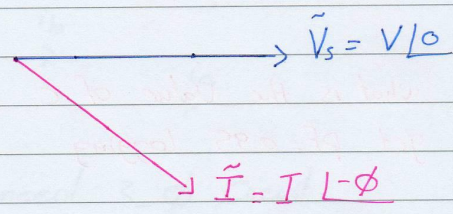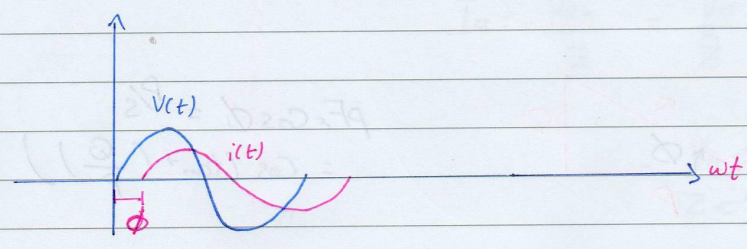$i(t) = \sqrt{2} I \cos(\omega t - \phi)$



$\tilde{V} = V e^{j0} = V \cos(0) + j V \sin(0)$, $\tilde{I} = I e^{-j\phi} = I \cos\phi + j I \sin(-\phi)$

$$\tilde{Z} = \frac{\tilde{V}}{\tilde{I}} = \frac{V e^{j\phi}}{I e^{-j\phi}} = \frac{V}{I} e^{j\phi} = \frac{V}{I} [\cos\phi + j\sin\phi]$$

↗
rectangular form

$$\tilde{Z} = Z e^{j\phi} \leftarrow \text{Exponential form.}$$

Power, Active power, Reactive power, Apparent power and Complex Power.

$$\tilde{S} = \tilde{V} \tilde{I}^* \Rightarrow \text{Complex power}$$


$$= V e^{j\phi} (I e^{-j\phi})^* = VI e^{j\phi}$$

$$= VI [\cos\phi + j\sin\phi] = S [\cos\phi + j\sin\phi]$$

$$= P + jQ$$

$$|\tilde{S}| = VI \Rightarrow \text{apparent power.}$$
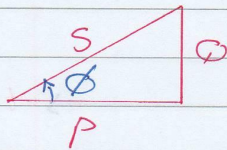
$$P = VI \cos\phi \quad Q = VI \sin\phi$$




$$\text{PF} = \cos\phi = P/S$$

$$= \cos(\tan^{-1}(\frac{Q}{P}))$$

Ex]

$$V = 120 \text{ rms}$$

$$60 \text{ Hz}$$

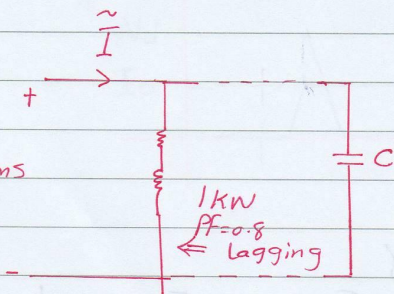

what is the value of C to get $\text{PF} = 0.95$ lagging.

Solution:- $PF = \frac{P}{S} \Rightarrow S = \frac{P}{PF} = \frac{1000}{0.8} = 1250 \text{ VA}$ before "C"

$$Q = \sqrt{S^2 - P^2} = \sqrt{1250^2 - 1000^2} = 750 \text{ VAR}$$

$$\tilde{S} = 1000 + j750 \text{ VA}$$

with C:-


$$\tilde{S} = P + jQ - jQ_c$$

$$0.95 = \frac{P}{S} = \frac{1000}{\sqrt{1000^2 + (750 - Q_c)^2}} \Rightarrow Q_c = 421.3 \text{ VAR}$$

$$Q_c = \frac{U^2}{X_c} = \frac{V^2}{\frac{1}{\omega C}} = \omega C V^2$$

$$421.3 = (2\pi f)(C)(120)^2 \Rightarrow C = 77.6 \text{ }\mu\text{F}$$

Three-phase Circuits.

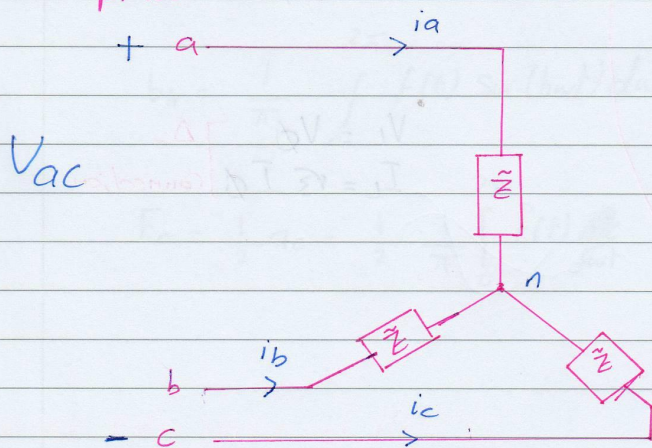

$$\tilde{I}_a = \frac{\tilde{V}_{an}}{\tilde{Z}} = \frac{\tilde{V}_a}{\tilde{Z}}$$


$$= \frac{V_a e^{j\phi}}{Z e^{j\theta}}$$

$$= \frac{V_a}{Z} e^{-j\phi}$$

Balanced 3- ϕ Circuit.

$$\tilde{I}_b = \frac{V_a}{Z} e^{-j(\phi+120^\circ)}$$
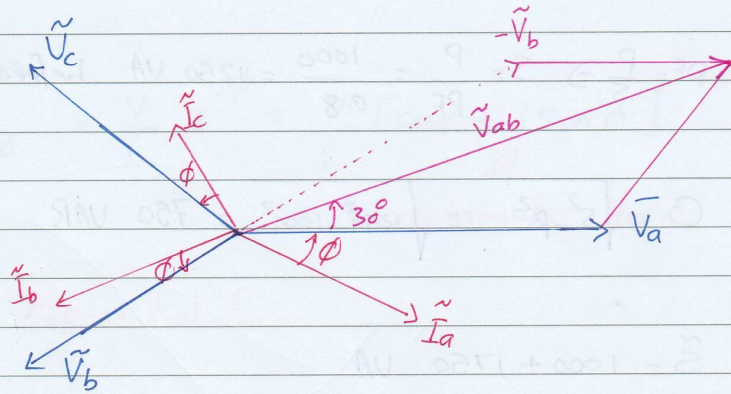
$$\tilde{I}_c = \frac{V_a}{Z} e^{-j(\phi-120^\circ)}$$



$$\tilde{V}_{ab} = \tilde{V}_a - \tilde{V}_b$$

$$= V_a e^{j0} - V_b e^{j(0-120^\circ)} = V_a e^{j0} - V_b e^{-j120^\circ}$$

$$= V \angle 0^\circ - V \angle -120^\circ$$

$$= \sqrt{3} V \angle 30^\circ$$

$$P_{3-\phi} = 3 V_\phi \bar{I}_\phi \cos \phi \quad \leftarrow \text{Y } \Delta$$

$$Q_{3-\phi} = 3 V_\phi \bar{I}_\phi \sin \phi$$

$$S_{3-\phi} = 3 V_\phi \bar{I}_\phi$$

$$P_{3-\phi} = \sqrt{3} V_L \bar{I}_L \cos \phi$$

$$Q_{3-\phi} = \sqrt{3} V_L \bar{I}_L \sin \phi$$

$$S_{3-\phi} = \sqrt{3} V_L \bar{I}_L$$

$$\left. \begin{aligned} V_L &= \sqrt{3} V_\phi \\ \bar{I}_L &= \bar{I}_\phi \end{aligned} \right\} \text{Y-connection}$$

$$\left. \begin{aligned} V_L &= V_\phi \\ \bar{I}_L &= \sqrt{3} \bar{I}_\phi \end{aligned} \right\} \Delta\text{-connection}$$

Non-Sinusoidal waveforms in steady state.

⇒ The steady state voltages and currents of power electronics are usually periodic but not sinusoidal.

Fourier Analysis of Repetitive wave forms.

* A non sinusoidal wave $f(t)$ repeating with an angular frequency ω can be expressed as:-

$$f(t) = F_0 + \sum_{h=1}^{\infty} f_h(t)$$

$$= \frac{1}{2} a_0 + \sum_{h=1}^{\infty} [a_h \cos(h\omega t) + b_h \sin(h\omega t)]$$

$$F_0 = \frac{1}{2} a_0 \Rightarrow \text{average value of } f(t)$$

$$a_h = \frac{1}{\pi} \int_0^{2\pi} f(t) \cos(h\omega t) d\omega t, \quad h = 0, 1, 2, \dots, \infty$$

$$b_h = \frac{1}{\pi} \int_0^{2\pi} f(t) \sin(h\omega t) d\omega t, \quad h = 1, 2, \dots, \infty$$


$$F_0 = \frac{1}{2} a_0 = \frac{1}{2} \frac{1}{\pi} \int_0^{2\pi} f(t) d\omega t = \frac{1}{2\pi} \int_0^{2\pi} f(t) d\omega t$$

* The RMS value of $f(t)$:-

$$F = (F_0^2 + F_1^2 + \dots + F_{\infty}^2)^{1/2}$$

$$F = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (f(t))^2 d\omega t}$$

Line Current Distortion

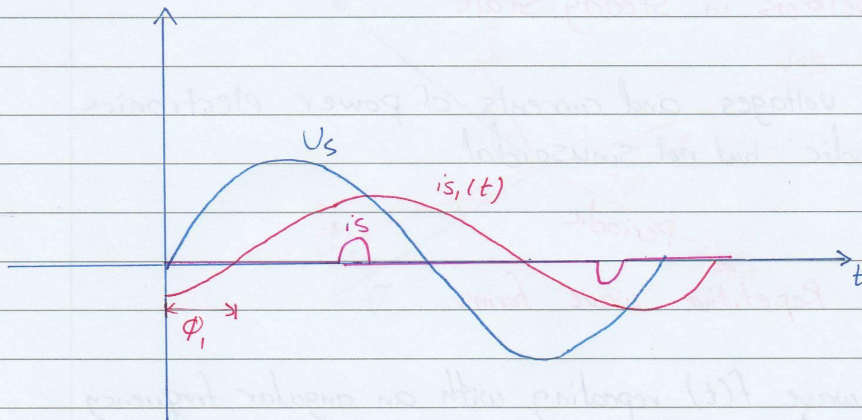

$$V_s = \sqrt{2} V_s \sin \omega t$$

$$i_s(t) = i_{s1}(t) + \sum_{h \neq 1}^{\infty} i_{sh}(t)$$

$i_{s1}(t)$: fundamental component of $i_s(t)$ ω_1

$i_{sh}(t)$: The component at h harmonic ($f_h = h f_1$)

$$i_s(t) = \sqrt{2} I_{s1} \sin(\omega_1 t - \phi_1) + \sum_{h \neq 1}^{\infty} \sqrt{2} I_{sh} \sin(\omega_h t - \phi_h)$$

ϕ_1 : phase shift between V_s & i_{s1}

$$I_s = \sqrt{\frac{1}{T_1} \int_0^{T_1} (i_s(t))^2 dt} \equiv \text{rms value of } i_s(t)$$

$$= \sqrt{I_{s1}^2 + \sum_{h \neq 1}^{\infty} I_{sh}^2}$$

rms value of the fundamental (first component)

THD: Total Harmonic Distortion

$$\text{THD \%} = \frac{\sqrt{I_s^2 - I_{s1}^2}}{I_{s1}} \times 100 \%$$

$$\int_0^T \sin x \sin 2x dx = 0$$

$$\int_0^T \sin x \sin 3x dx = 0$$

Power and Power factor.

$$P = \frac{1}{T_1} \int_0^{T_1} V_s(t) i_s(t) dt = \frac{1}{T_1} \int_0^{T_1} \sqrt{2} V_s \sin \omega t * [\sqrt{2} I_{s1} \sin(\omega t - \phi_1) + \sum_{h \neq 1}^{\infty} \sqrt{2} I_{sh} \sin(\omega_h t - \phi_h)] dt$$

$$\Rightarrow P = V_s I_{s1} \cos \phi_1 \Leftarrow$$

The current components at harmonic frequencies do not contribute to the average power of pure sine voltage and not sinusoidal current.


$S = V_s I_s \Rightarrow$ Definition

$$\text{PF} = \frac{P}{S} = \frac{V_s I_{s1} \cos \phi_1}{V_s I_s} = \frac{I_{s1}}{I_s} \cos \phi_1$$

DPF = Displacement PF = $\cos \phi_1$



"Inductor & Capacitor responses"

Sinusoidal


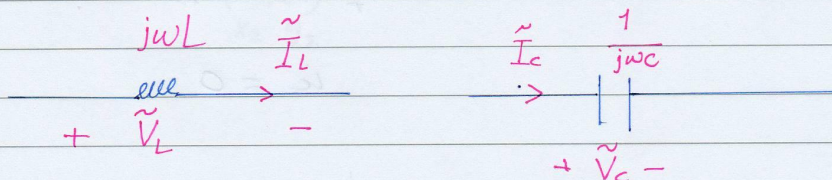


$$\tilde{V}_L = jwL \tilde{I}_L$$

$$\tilde{I}_C = jwC \tilde{V}_C$$

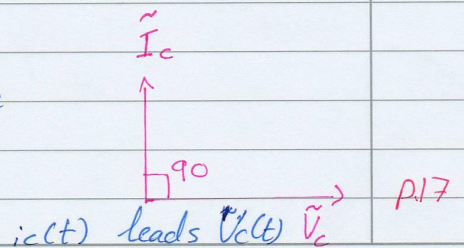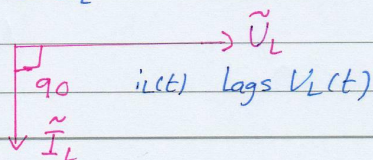





Non-Sinusoidal

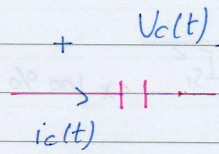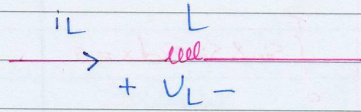

$$V_L(t) = L \frac{di_L(t)}{dt}$$

$$i_C(t) = \frac{C dV_C(t)}{dt}$$
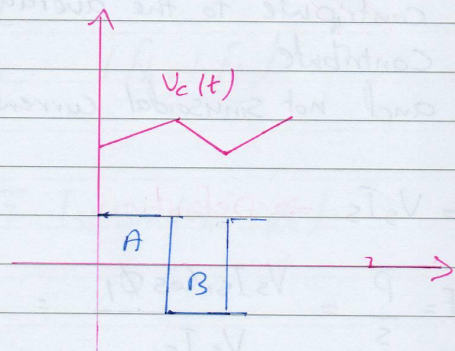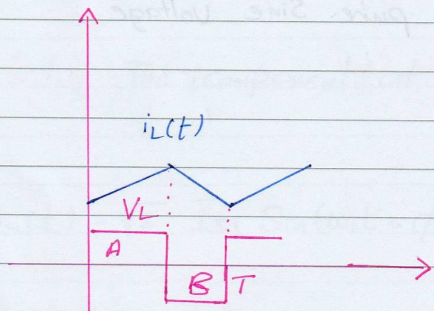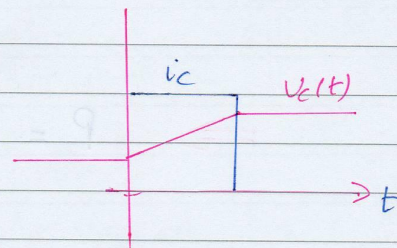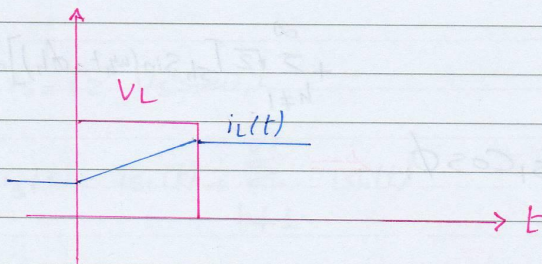
$$V_C(t) = \frac{1}{C} \int i_C(t) dt + K$$




$$V_L = 0$$

average value of the voltage across the inductance in the steady state

The average value of the capacitor current in steady state equals zero

$$i_C = 0$$


P-3-6, pp. 58

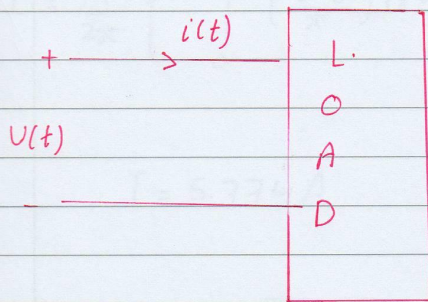

$$v(t) = \sqrt{2} V \sin \omega t, \quad V = 120$$


$i(t)$ is a triangular wave with an amplitude of 10A. also $i(t)$ lags $v(t)$ by 30°

find: P , DPF , THD , $PF = ?$

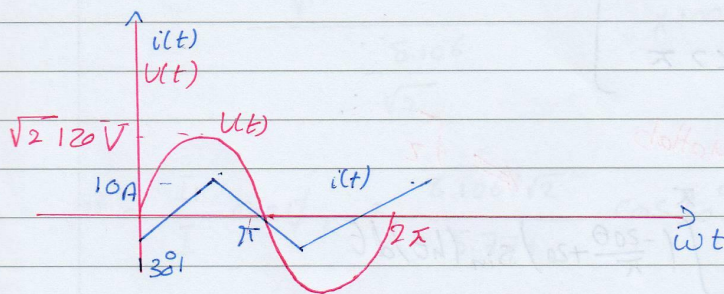

because $i(t)$ is symmetric on the x-axis, all even components of b_n are zero, also all a_n equals zero:
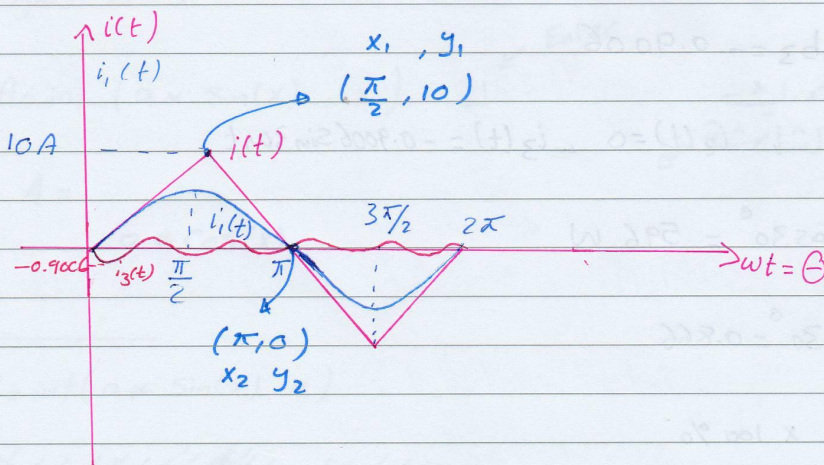
$$P = VI_1 \cos \phi = 120 I_1 \cos 30^\circ$$



$$a_n = 0$$

$$b_n = 0, \quad \text{for } n: \text{even.}$$

$$b_1, b_3, b_5, \dots$$

$$b_h = \frac{1}{\pi} \int_0^{2\pi} i(t) \sin(h\omega t) d\omega t$$

$$b_h = \frac{1}{\pi} \int_0^{2\pi} i(\theta) \sin(h\theta) d\theta$$

$$i(\theta) = \begin{cases} \frac{20}{\pi} \theta, & 0 < \theta < \pi/2 \\ -\frac{20}{\pi} \theta + 20, & \pi/2 < \theta < 3\pi/2 \\ \frac{20}{\pi} \theta - 40, & 3\pi/2 < \theta < 2\pi \end{cases}$$

$$b_h = \frac{1}{\pi} \left[\int_0^{\pi/2} \frac{20\theta}{\pi} \sin(h\theta) d\theta + \int_{\pi/2}^{\pi} \left(-\frac{20\theta}{\pi} + 20\right) \sin(h\theta) d\theta + \int_{3\pi/2}^{2\pi} \left(\frac{20\theta}{\pi} - 40\right) \sin(h\theta) d\theta \right]$$

↙ f1 Matlab
↙ f2
↙ f3

$$b_1 = 8.106, \quad b_3 = -0.9006$$

$$\Rightarrow i_1(t) = 8.106 \sin \omega t, \quad i_2(t) = 0, \quad i_3(t) = -0.9006 \sin 3\omega t$$

$$P = (120) \left(\frac{8.106}{\sqrt{2}} \right) \cos 30^\circ = 596 \text{ W}$$

$$\text{DPF} = \cos \phi_1 = \cos 30^\circ = 0.866$$

$$\text{THD \%} = \frac{\sqrt{I^2 - I_1^2}}{I_1} \times 100 \%$$

$$I_1 = \frac{8.106}{\sqrt{2}}, \quad I = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (i(\theta))^2 d\theta}$$

$$I^2 = \frac{1}{2\pi} \left[\int_0^{\pi/2} \left(\frac{20\theta}{\pi}\right)^2 d\theta + \int_{\pi/2}^{3\pi/2} \left(-\frac{20\theta}{\pi} + 20\right)^2 d\theta + \int_{\frac{3\pi}{2}}^{2\pi} \left(\frac{20\theta}{\pi} - 40\right)^2 d\theta \right]$$

$$I = 5.774 A$$

$$\therefore \text{THD \%} = \frac{\sqrt{(5.774)^2 - \left(\frac{8.106}{\sqrt{2}}\right)^2}}{\frac{8.106}{\sqrt{2}}} \times 100\% = 12\%$$

$$\text{PF} = \frac{I_1}{I} \cos\phi_1 = \frac{8.106/\sqrt{2}}{5.774} \cos 30^\circ$$

" Symbolic Integration in Matlab "

i.g. $\int a \sin x = -\frac{a}{\omega} \cos ax = -\cos ax$.

Ex) write Matlab command to find $\int a \sin x dx$

>> Syms a x

>> A = int (a * sin(x), x)

↙ Enter

بعد تنفيذ الأمر عليك
أن تطلع عندي بالساعة

A =

$$-a * \cos(x)$$

>> B = int(a * sin(x), a)

~~B = 1/2 * a^2 * sin(x)~~

B =

$$1/2 * a^2 * \sin(x)$$

$$\gg C = \text{subs}(B, a, 2)$$

$$C = 2 * \sin(x)$$

$$\gg F = a^2 * \exp(x)$$

$$\gg R = \text{int}(F, x, 1, 2)$$

$$R = a^2 * \exp(2) - a^2 * \exp(1)$$

$$\gg M = \text{Vpa}(R, 5)$$

$$M = 4.6708 * a^2$$

back to the previous problem:

$$\gg \text{syms } h \text{ th}$$

$$\gg F_1 = ((20 * \text{th}) / \pi) * \sin(h * \text{th});$$

$$\gg F_2 = ((-20 * \text{th}) / (\pi + 20)) * \sin(h * \text{th});$$

$$\gg F_3 = \dots$$

$$\gg V_1 = \text{int}(F_1, \text{th}, 0, (\pi/2));$$

$$V_2 = \text{int}(F_2, \text{th}, (\pi/2), (3 * \pi/2));$$

$$V_3 = \dots$$

$$\gg b_h = (1/\pi) * (V_1 + V_2 + V_3)$$

$$b_h = \dots$$

chp3

31.5.2017

$$\Rightarrow b_1 = \text{subs}(b_h, h, 1) \quad \leftarrow$$

$$b_1 = \dots$$

$$\Rightarrow b_2 = \text{subs}(b_h, h, 2)$$

$$b_2 = 1.7 \times 10^{-16} \approx 0$$


p.23

CHP5: Line Frequency Diode Rectifiers:

1.6.2017

Line Frequency ac \rightarrow uncontrolled dc.






Line Frequency \equiv 50 or 60 Hz.

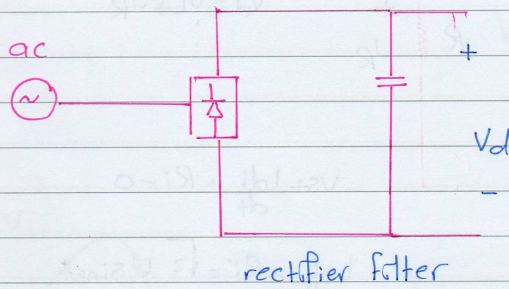







"Block diagram of a rectifier."

"Basic rectifier concepts"

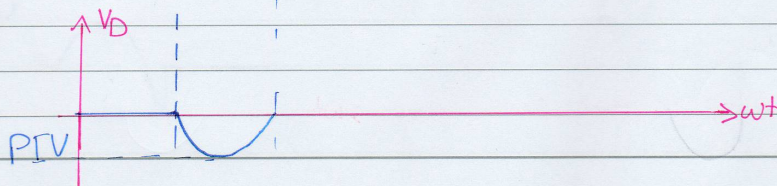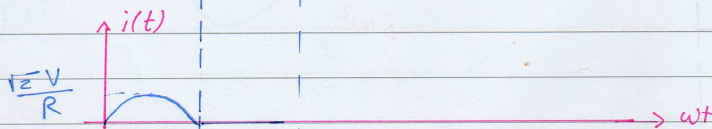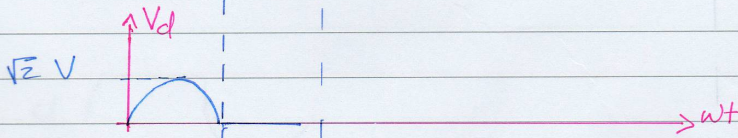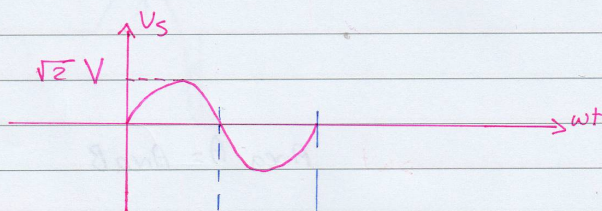
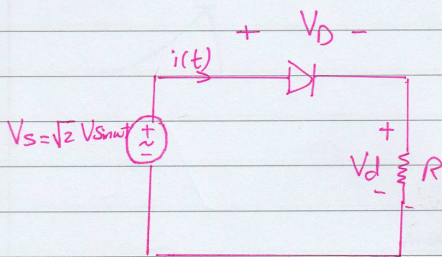
1) Half wave rectifier circuit with pure resistive load.



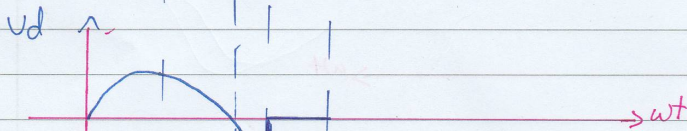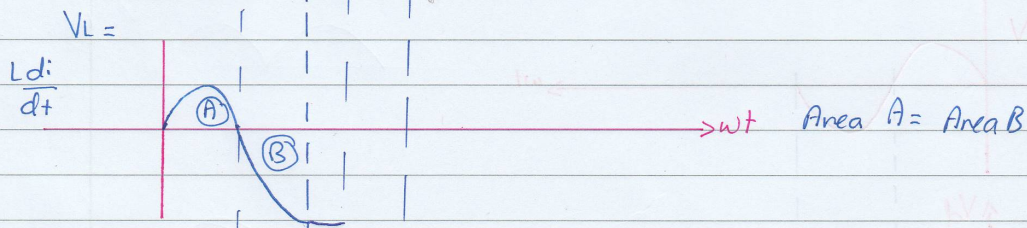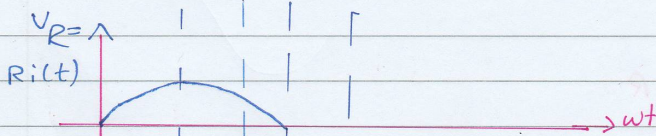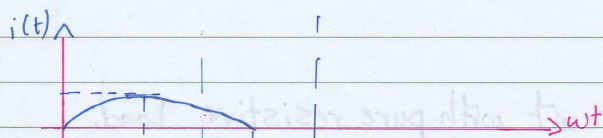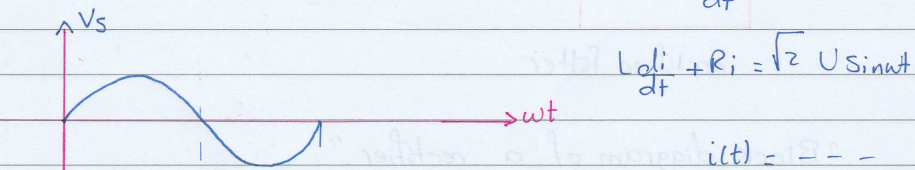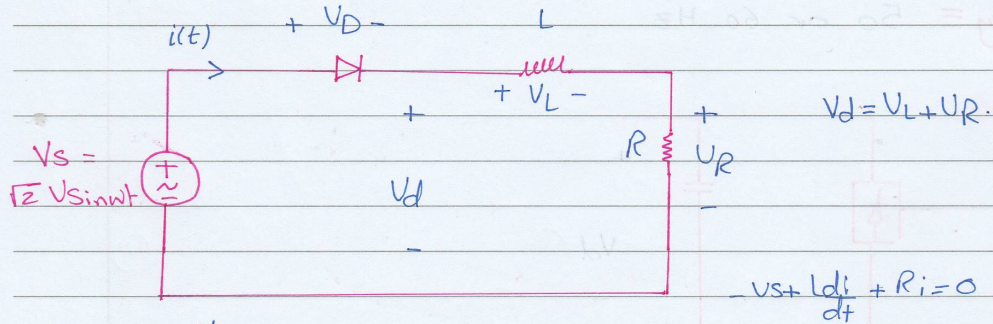2] Half_Wave rectifier circuit with inductive load.



3) Load with internal dc voltage:

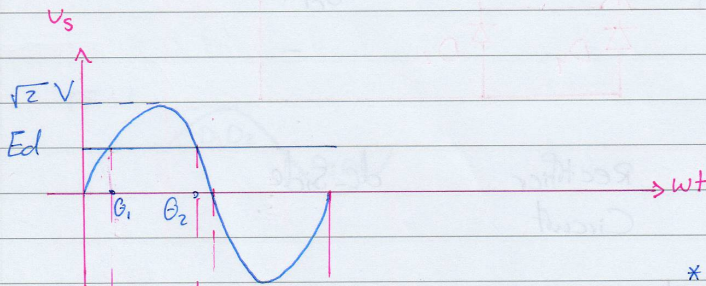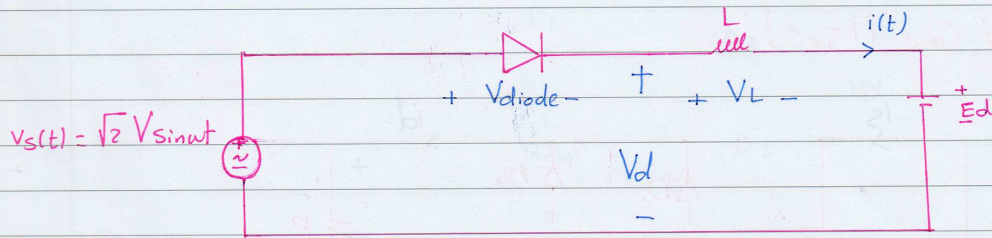

$$L \frac{di}{dt} = \sqrt{2} V \sin \omega t - E_d$$

$$\Rightarrow -v_s(t) + v_{diode} + E_d = 0$$



$$\Rightarrow \text{at } v_s = E_d$$

$$\sqrt{2} V \sin \theta = E_d$$



$$\theta_1 = \sin^{-1} \left[\frac{E_d}{\sqrt{2} V} \right]$$

$$\theta_2 = \pi - \theta_1$$

where $\theta = \omega t$.

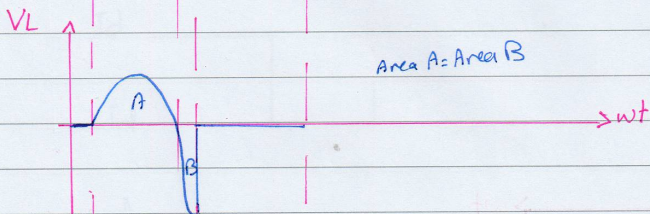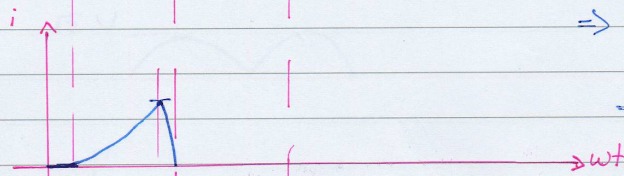


Area A = Area B

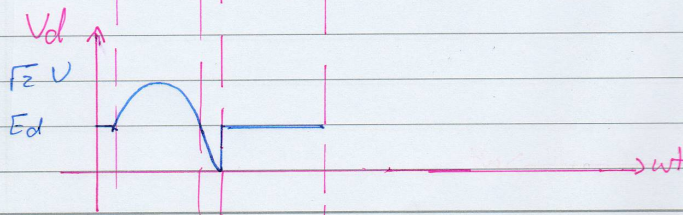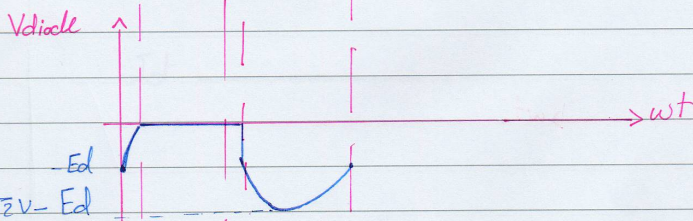

"Single Phase Diode Bridge Rectifiers"

1) Idealized Case ($L_s=0$)

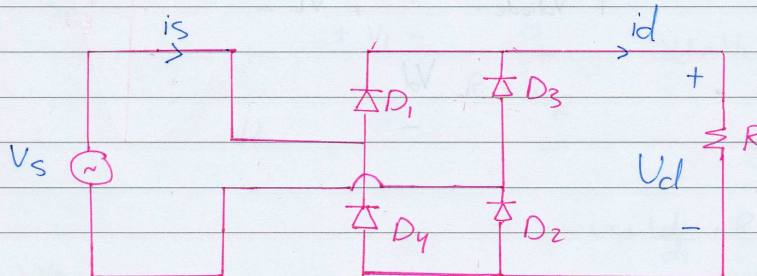



ac-Side

Rectifier
Circuit




dc-Side


(Pure Resistive Load)

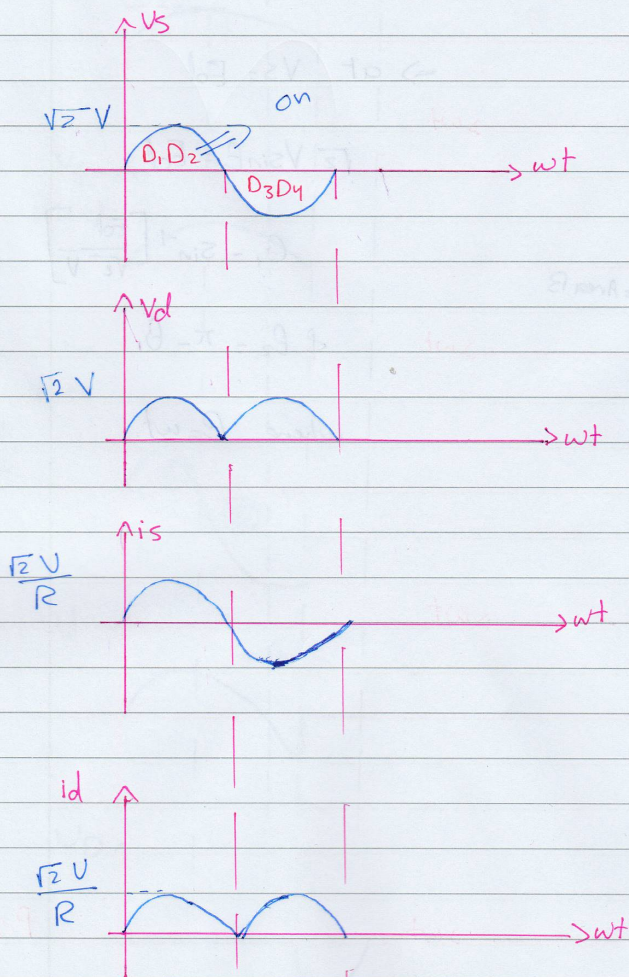

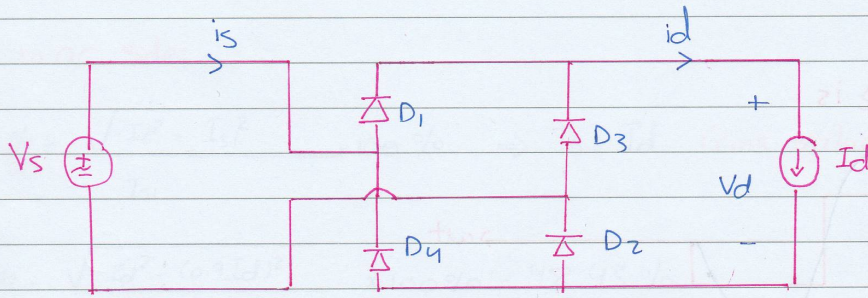

(Highly inductive load)

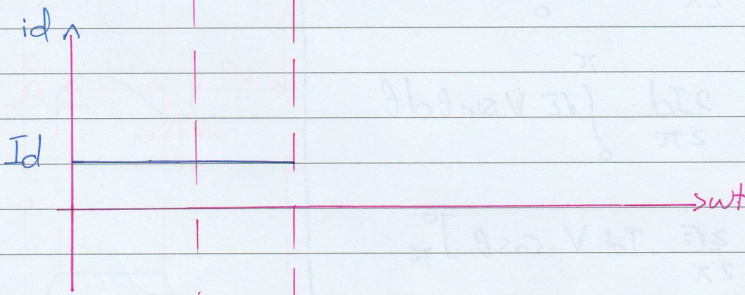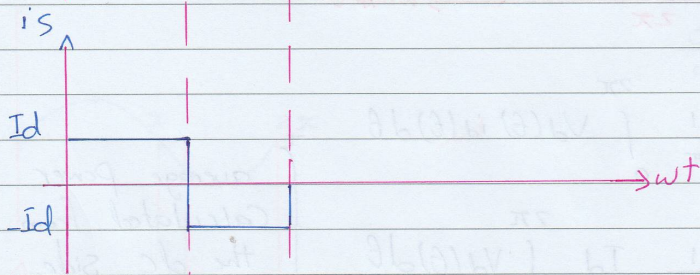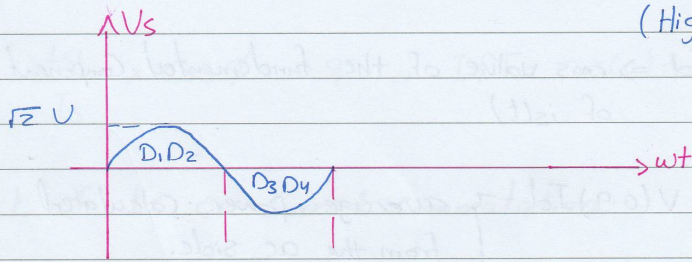


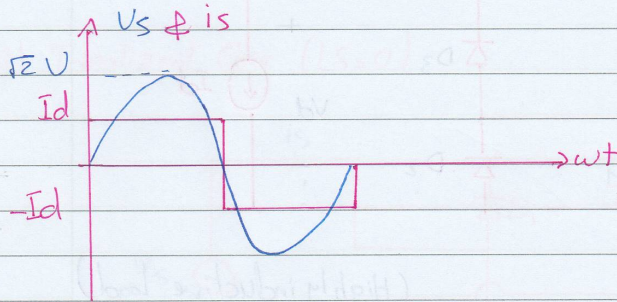

$I_{s1} = 0.9 I_d \Rightarrow$ rms value of the fundamental component of $i_s(t)$

$$P = V I_{s1} \cos \phi_1 = V (0.9) I_d \quad \left. \begin{array}{l} \text{average power calculated} \\ \text{from the ac side.} \end{array} \right\}$$

$$P = 0.9 V I_d$$

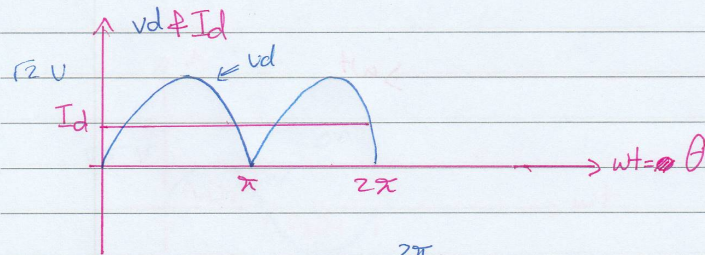

$$P = \frac{1}{2\pi} \int_0^{2\pi} v_d(\theta) i_d(\theta) d\theta$$

$$= \frac{1}{2\pi} I_d \int_0^{2\pi} v_d(\theta) d\theta$$

$$= \frac{2 I_d}{2\pi} \int_0^{\pi} \sqrt{2} V \sin \theta d\theta$$

$$= \frac{2\sqrt{2}}{2\pi} I_d V \cos \theta \Big|_{\pi}^0$$

$$P = 0.9 V I_d$$

average power calculated from the dc side.


Back to ac side:

$$THD\% = \frac{\sqrt{I_s^2 - I_{s1}^2}}{I_{s1}} \times 100\% \Rightarrow I_s = I_d \text{ (rms value)}$$

$$THD\% = \frac{\sqrt{I_d^2 - (0.9I_d)^2}}{0.9I_d} \times 100\% = 48.43\%$$

$$PF = \frac{I_{s1}}{I_s} \times \cos\phi = 0.9, \quad DPF = \cos(0) = 1$$


2) Effect of L_s on current commutation.

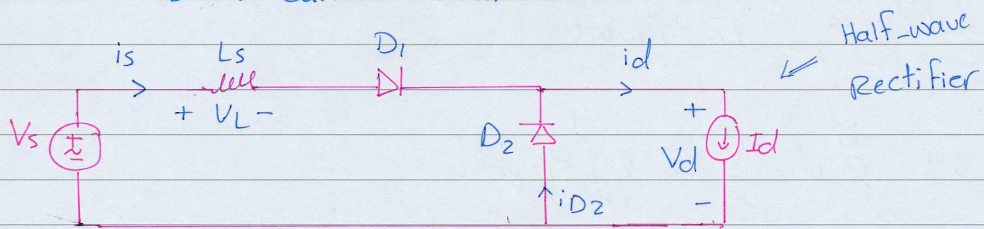

$$i_s + i_{D2} + I_d = 0$$

$$i_s + i_{D2} = I_d$$
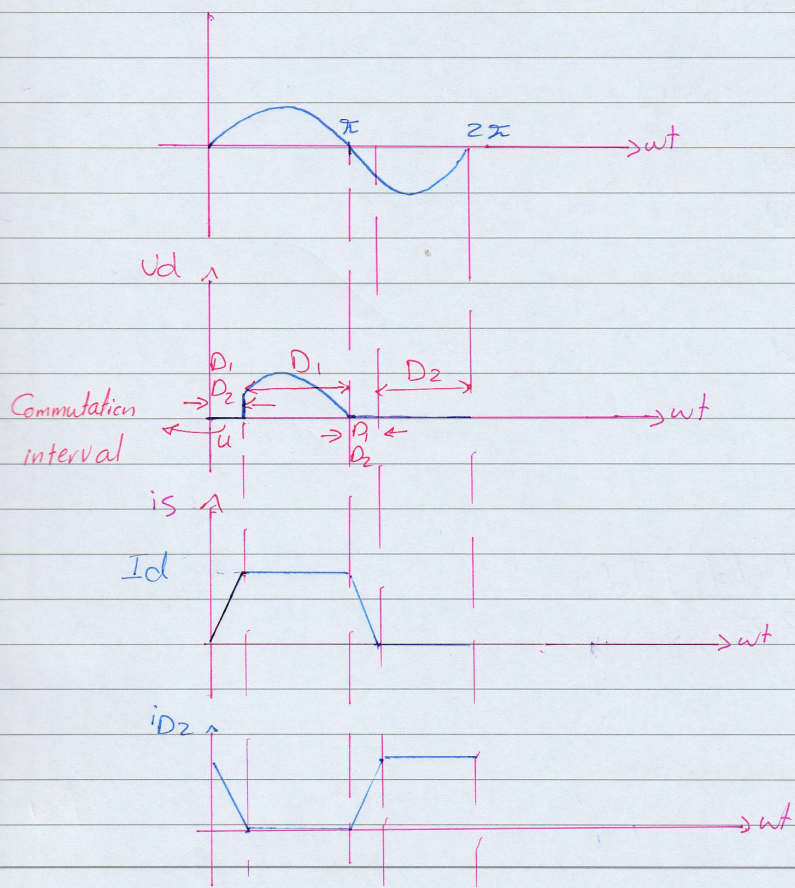
$$\frac{di_s}{dt} = -\frac{di_{D2}}{dt}$$



$$V_d = \frac{1}{2\pi} \int_0^{2\pi} v_d(\theta) d\theta = \frac{1}{2\pi} \int_0^{\pi} \sqrt{2} V \sin \theta d\theta$$

$$V_d = \frac{\sqrt{2} V}{2\pi} [\cos u + 1]$$

During Commutation.

$$V_L = V_s$$

$$L_s \frac{di_s}{dt} = \sqrt{2} V \sin \omega t$$

$$\omega L_s \frac{di_s}{d\omega t} = \sqrt{2} V \sin \omega t$$

$$\omega L_s \int_0^{I_d} di_s = \sqrt{2} V \int_0^u \sin \theta d\theta$$

$$\omega L_s I_d = \sqrt{2} V [\cos \theta]_0^u$$


$$\omega L_s I_d = \sqrt{2} V [1 - \cos u]$$

$$\cos u = 1 - \frac{\omega L_s I_d}{\sqrt{2} V} \Rightarrow u =$$

$$V_d = 0.45 V - \frac{\omega L_s I_d}{2\pi}$$

$$P_d = V_d I_d$$
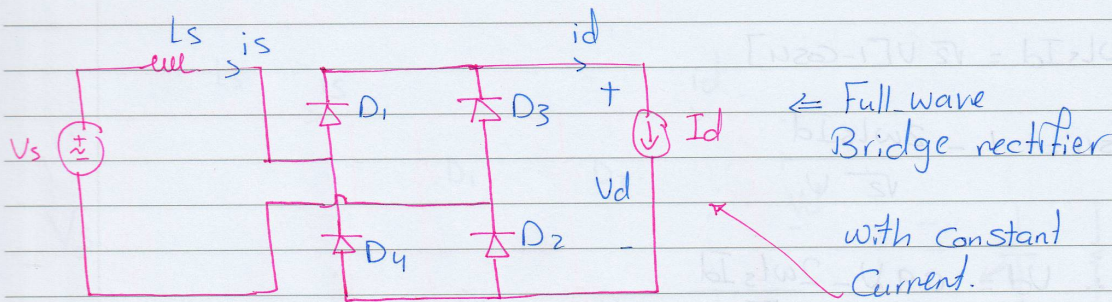
$$\Rightarrow P_d = \left(0.45 V - \frac{\omega L_s I_d}{2\pi} \right) I_d$$



Effects:

- 1] Commutation interval with all diodes are on in it and $V_d = 0$
- 2] Reduce average power and voltage.


average voltage $\frac{2\pi}{2\pi}$

$$V_d = \frac{1}{2\pi} \int_0^{2\pi} V_d(\theta) d\theta$$

$$V_d = \frac{1}{2\pi} \times 2 \int_0^{\pi} \sqrt{2} V \sin\theta d\theta$$

$$= \frac{\sqrt{2} V}{\pi} \cos\theta \Big|_0^{\pi}$$
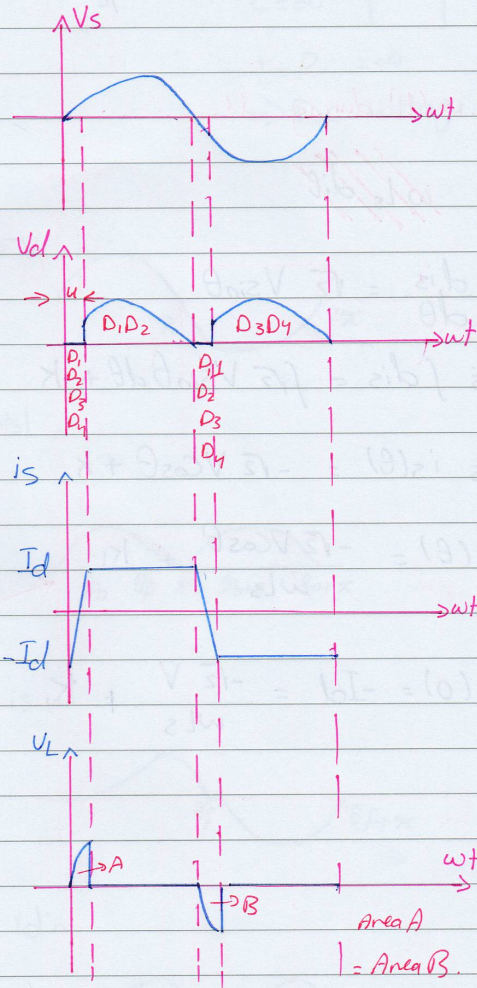
$$= \frac{\sqrt{2} V}{\pi} (\cos\pi + 1)$$



. During Commutation:-

$V_L = V_s$ $L_s \frac{di_s}{dt} = \sqrt{2} V \sin\omega t$ $\omega L_s \frac{di_s}{dt} = \sqrt{2} V \sin\omega t$	$\omega L_s \frac{di_s}{dt} = \sqrt{2} V \sin\theta$ $\omega L_s \int_{-I_d}^{I_d} di_s = \int_0^{\pi} \sqrt{2} V \sin\theta d\theta$ $2\omega L_s I_d = \sqrt{2} V \cos\theta \Big _0^{\pi}$
--	---

$$2\omega L_s I_d = \sqrt{2} V [1 - \cos u]$$

$$\cos u = 1 - \frac{2\omega L_s I_d}{\sqrt{2} V}$$

$$\therefore V_d = 0.9 V - \frac{2\omega L_s I_d}{\pi}$$

$i_s(t)$ during u .

~~$\omega L_s \frac{di_s}{dt}$~~

$$\omega L_s \frac{di_s}{d\theta} = \sqrt{2} V \sin \theta$$


$$\omega L_s \int di_s = \int \sqrt{2} V \sin \theta d\theta + K$$

$$\omega L_s i_s(\theta) = -\sqrt{2} V \cos \theta + K$$

$$i_s(\theta) = \frac{-\sqrt{2} V \cos \theta}{\omega L_s} + K_1$$

$$i_s(0) = -I_d = \frac{-\sqrt{2} V}{\omega L_s} + K_1, \quad K_1 =$$

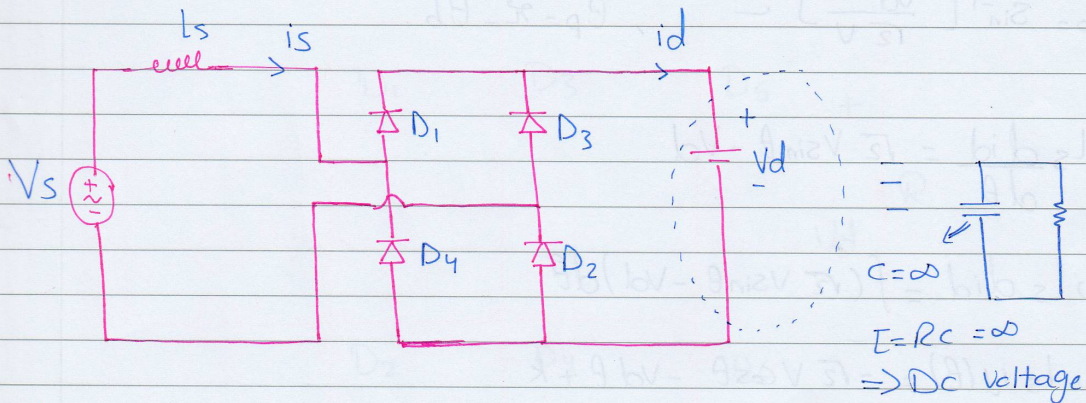Constant dc Side voltage $\Rightarrow V_d(t) = V_d$



at:

$$V_d = V_s$$

$$V_d = \sqrt{2} V_s \sin \theta_b$$

$$\theta_b = \sin^{-1} \left[\frac{V_d}{\sqrt{2} V_s} \right]$$

$$\theta_p = \pi - \theta_b$$

$$\theta_f \gg \theta_p$$






$$\Rightarrow -V_s + L_s \frac{di_s}{dt} + V_d = 0$$

$$L_s \frac{di_s}{dt} = V_s - V_d$$

$$\omega L_s \frac{di_s}{dt} = \sqrt{2} V_s \sin \omega t - V_d$$

$$I_d = \frac{1}{2\pi} \int_0^{2\pi} i_d(\theta) d\theta$$
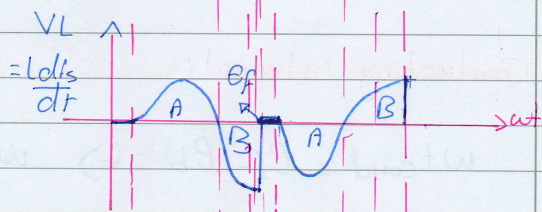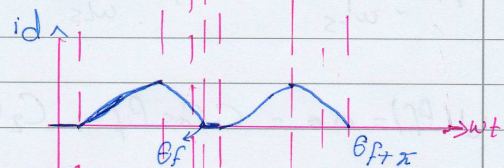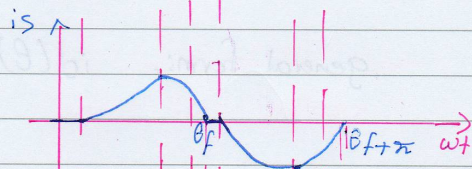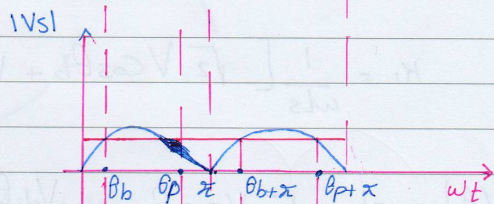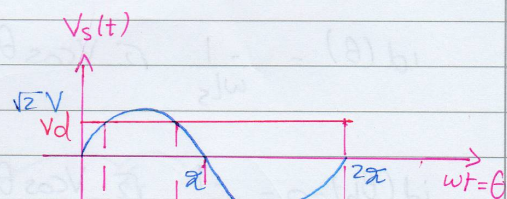
$$= \frac{2}{2\pi} \int_{\theta_b}^{\theta_f} i_d(\theta) d\theta$$



$$\theta_b = \sin^{-1} \left[\frac{V_d}{\sqrt{2} V} \right] \quad , \quad \theta_p = \pi - \theta_b$$

$$\omega L_s \frac{di_d}{dt} = \sqrt{2} V \sin \theta - V_d$$

$$\int \omega L_s di_d = \int (\sqrt{2} V \sin \theta - V_d) dt$$

$$\omega L_s i_d(t) = -\sqrt{2} V \cos \theta - V_d t + k$$

$$i_d(\theta) = \frac{-1}{\omega L_s} \sqrt{2} V \cos \theta - \frac{V_d t}{\omega L_s} + k_1$$

$$i_d(\theta_b) = 0 = \frac{-1}{\omega L_s} \sqrt{2} V \cos \theta_b - \frac{V_d \theta_b}{\omega L_s} + k_1$$

$$k_1 = \frac{1}{\omega L_s} \left[\sqrt{2} V \cos \theta_b + V_d \theta_b \right]$$

$$i_d(\theta) = \frac{-1}{\omega L_s} \sqrt{2} V \cos \theta - \frac{V_d t}{\omega L_s} + \frac{1}{\omega L_s} \sqrt{2} V \cos \theta_b + \frac{1}{\omega L_s} V_d \theta_b$$

general form:- $i_d(\theta) = G_1 \cos \theta + G_2 \theta + C_3$



$$i_d(\theta_f) = \frac{-1}{\omega L_s} \sqrt{2} V \cos \theta_f - \frac{1}{\omega L_s} V_d \theta_f + \frac{1}{\omega L_s} \sqrt{2} V \cos \theta_b + \frac{1}{\omega L_s} V_d \theta_b$$

$$i_d(\theta_f) = 0 = G_1 \cos \theta_f + G_2 \theta_f + C_3 \quad \rightarrow \text{radian}$$

\Rightarrow we find θ_f by Trial and error.


\Rightarrow Conduction interval:-
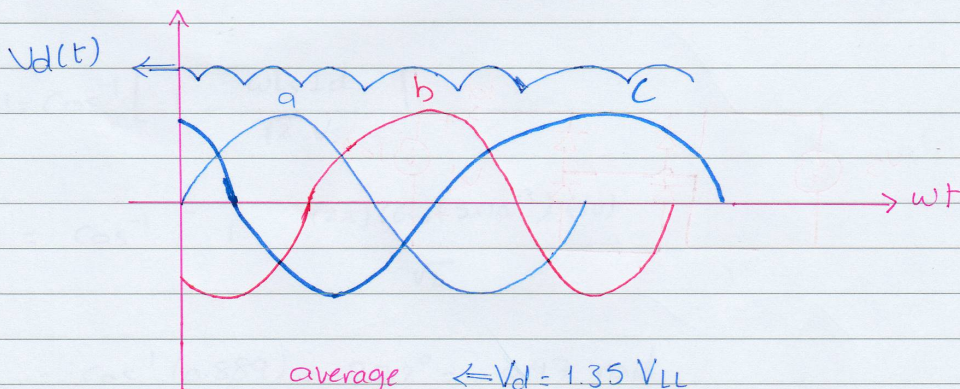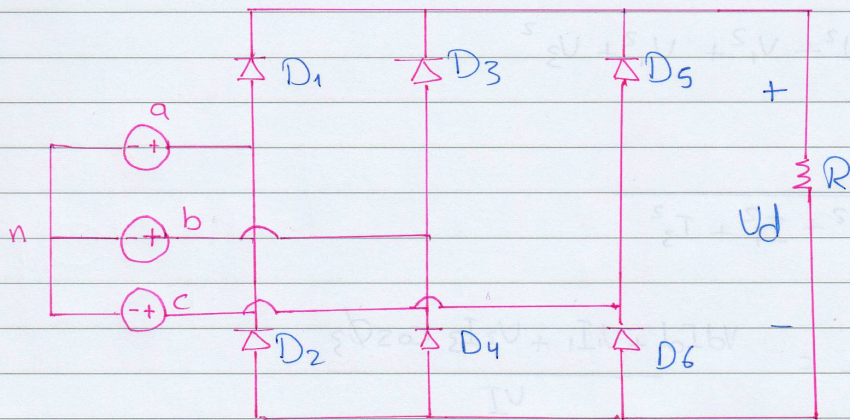
$$\omega t_{\text{cond}} = \theta_f - \theta_b \quad \Rightarrow \quad \omega = 2\pi f$$



average $\leftarrow V_d = 1.35 V_{LL}$
value of the c/p voltage

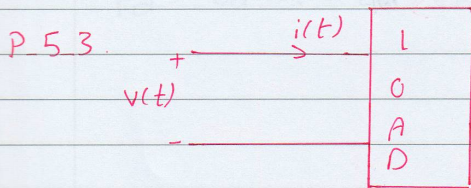rms value of the three phase line voltage.



$$v(t) = V_d + \sqrt{2} V_1 \cos \omega_1 t + \sqrt{2} V_1 \sin \omega_1 t + \sqrt{2} V_3 \cos (\omega_3 t) \quad \text{Volts}$$

$$i(t) = I_d + \sqrt{2} I_1 \cos \omega_1 t + \sqrt{2} I_3 \cos (\omega_3 t - \phi_3) \quad \text{A}$$

$$a) p = \frac{1}{T} \int_0^T v(t) i(t) dt = \frac{1}{T} \int_0^T (\quad) * (\quad) dt$$


$$= V_d I_d + V_1 I_1 + V_3 I_3 \cos \phi_3$$

$$b) V = \sqrt{V_d^2 + V_1^2 + V_2^2 + V_3^2}$$

$$I = \sqrt{I_d^2 + I_1^2 + I_3^2}$$


$$c) PF = \frac{P}{S} = \frac{V_d I_d + V_1 I_1 + V_3 I_3 \cos \phi_3}{VI}$$

5.41

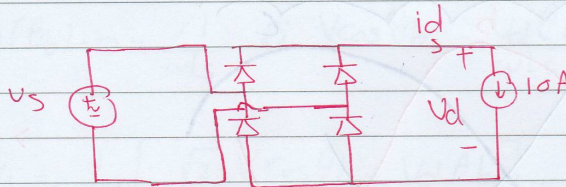


a) if v_s is sinusoidal

b) if v_s is

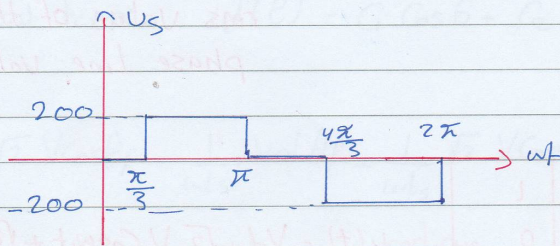

$P = ?$

$v_d \& I_d$

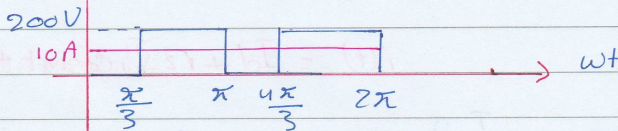


$$P = \frac{1}{2\pi} \int_0^{2\pi} v_d(t) i_d(t) dt = \frac{1}{\pi} \int_{\pi/3}^{\pi} (200)(10) dt = \frac{1}{\pi} (2000 \frac{2\pi}{3})$$

$$= \frac{4000}{3} W$$

P-37

5.5)

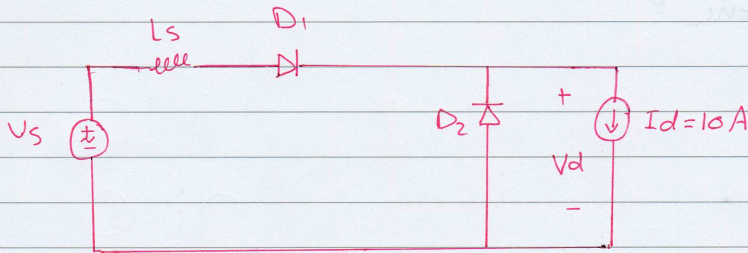

$L_s = 5 \text{ mH}$, $f = 60 \text{ Hz}$, $V_s = 120 \text{ V}$

P_d , V_d , $\alpha = ?$

نصف موجات ال Half wave


$$\alpha = \cos^{-1} \left[1 - \frac{\omega L_s I_d}{\sqrt{2} V_s} \right]$$

$$= \cos^{-1} \left[1 - \frac{(2\pi)(60)(5 \times 10^{-3})(10)}{\sqrt{2}} \right]$$

$$= \cos^{-1}(0.889) = 27.2^\circ = 0.47 \text{ rad.}$$

$$V_d = 0.45 V_s - \frac{\omega L_s I_d}{2\pi} = 54 - 3 = 51 \text{ V}$$
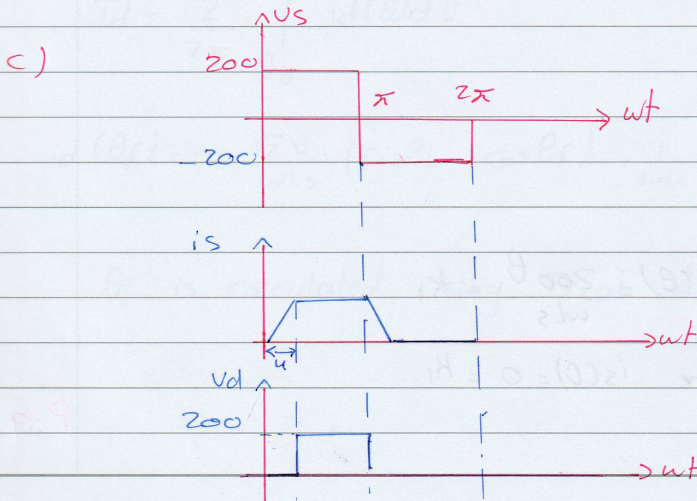
$$P_d = V_d I_d = (51)(10) = 510 \text{ W}$$



During commutation:

$$V_L = V_s$$

$$L_s \frac{di_s}{dt} = 200$$

$$\omega L_s \frac{di_s}{d\omega t} = 200$$

$$\omega L_s \int_0^{i_0} di_s = 200 \int_0^u d\omega t$$

$$\omega L_s (i_0) = 200 u \Rightarrow u = \frac{\omega L_s (i_0)}{200} = 0.094 \text{ rad} = 5.4^\circ$$

$$V_d = \frac{1}{2\pi} \int_u^\pi 200 d\theta$$

$$= \frac{200}{2\pi} [\pi - u]$$

$$= \frac{200}{2\pi} [\pi - 0.094] = 97 \text{ V}$$



$$P_d = V_d I_d = 97 (10) = 970 \text{ W}$$

$i_s(\theta)$ due commutation:

$$\omega L_s di_s = 200 d\omega t$$

$$\omega L_s i_s(\theta) = 200 \theta + K \Rightarrow i_s(\theta) = \frac{200 \theta}{\omega L_s} + K_1$$

$$\text{where } i_s(0) = 0 = K_1$$

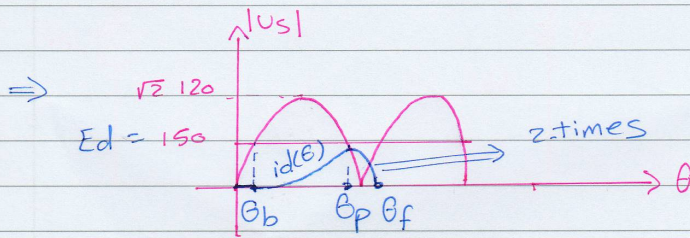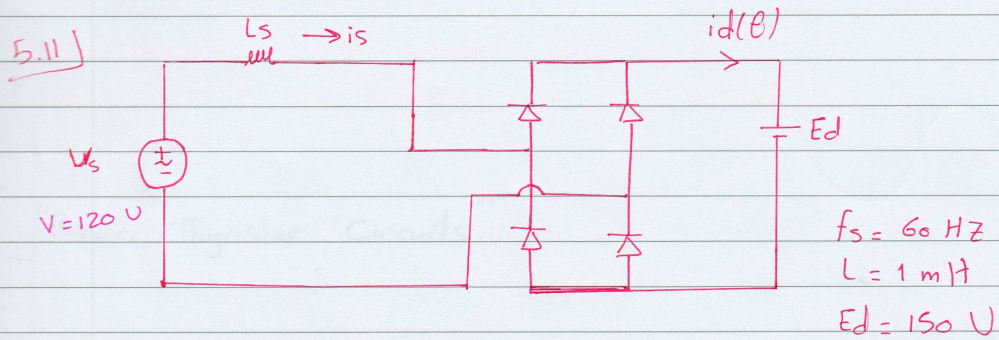

$$\theta_b = \sin^{-1}\left(\frac{150}{\sqrt{2} \cdot 120}\right) = 1.0841\text{ rad} = 62.1144^\circ$$

$$\theta_p = \pi - \theta_b = 180 - 62.1144 = 117.8856^\circ = 2.0558\text{ rad}$$

$$i_d(\theta) = \frac{\sqrt{2}V}{\omega L_s} (\cos\theta_b - \cos\theta) - \frac{1}{\omega L_s} V_d \theta + \frac{1}{\omega L_s} V_d \theta_b$$

$$i_d|_{\text{Peak}} = i_d|_{\theta=\theta_p} = \frac{\sqrt{2}V}{\omega L_s} (\cos\theta_b - \cos\theta_p) - \frac{1}{\omega L_s} V_d \theta_p + \frac{1}{\omega L_s} V_d \theta_b$$

[rad]


$$I_d = \frac{2}{2\pi} \int_{\theta_b}^{\theta_f} i_d(\theta) d\theta$$

$$i_d(\theta_f) = 0 = \frac{\sqrt{2}V}{\omega L_s} (\cos\theta_b - \cos\theta_f) - \frac{1}{\omega L_s} V_d \theta_f + \frac{1}{\omega L_s} V_d \theta_b$$


⇒ θ_f is calculated using Trial & Error.

"Line frequency phase-controlled Rectifiers and inverters: Line-frequency ac \rightarrow controlled dc."


"Basic Thyristor Circuits."

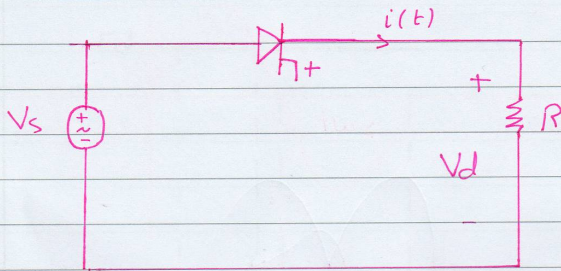

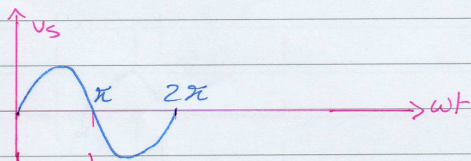Half-wave controlled rectifier circuit with pure resistive load.



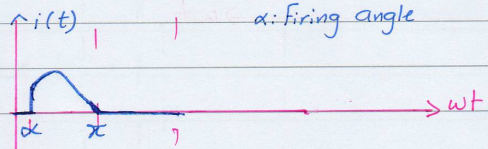
$$V_d = \frac{1}{2\pi} \int_{\alpha}^{\pi} \sqrt{2} V_m \sin \omega t \, d\omega t$$




α : firing angle
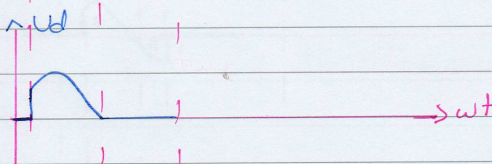
$$V_d = \frac{\sqrt{2} V_m}{2\pi} [\cos \omega t]_{\alpha}^{\pi}$$










$$= \frac{\sqrt{2} V_m}{2\pi} [\cos(\alpha) + 1]$$



\Rightarrow

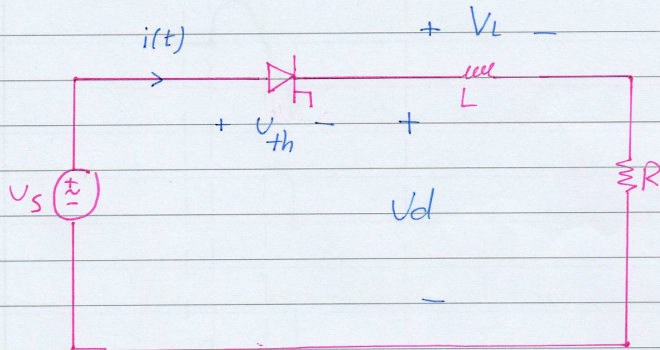


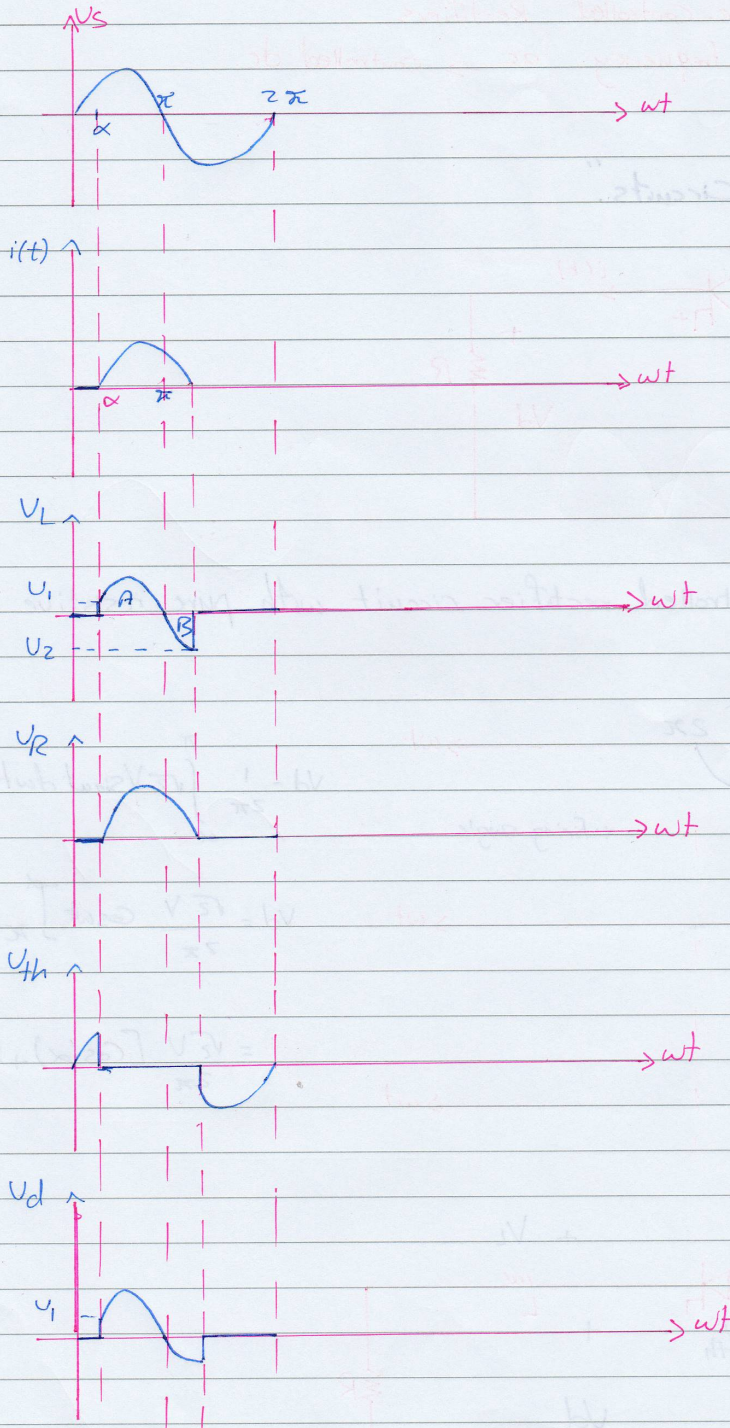
Half-wave controlled rectifier circuit with inductive load.



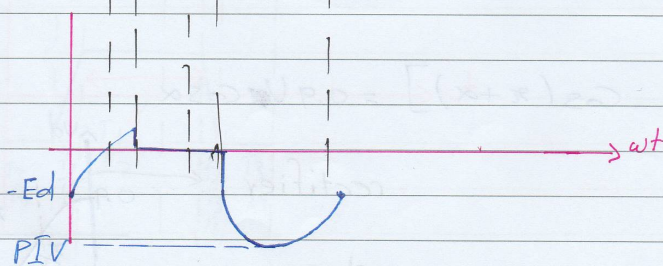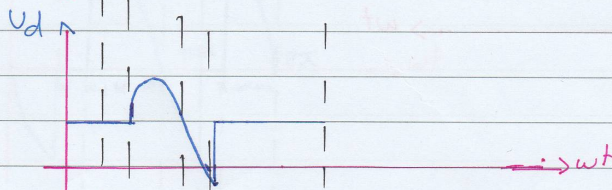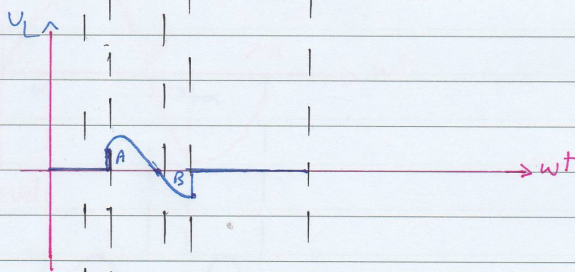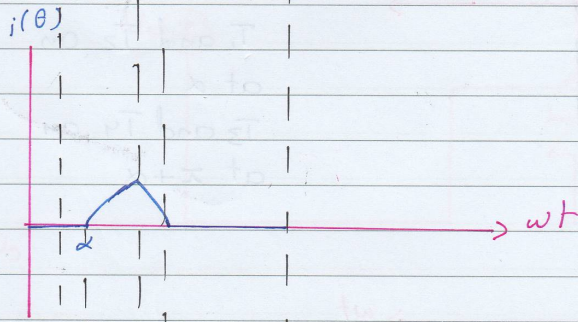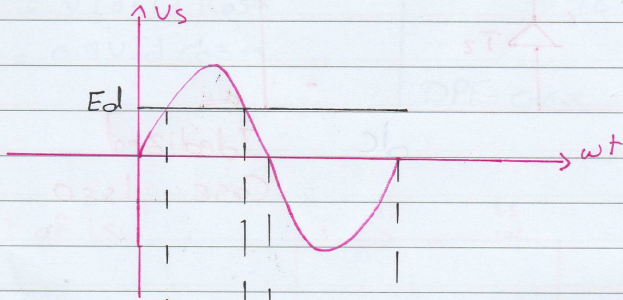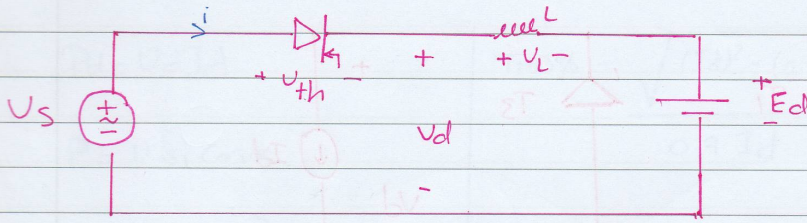

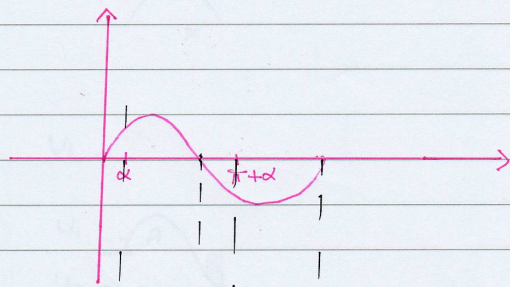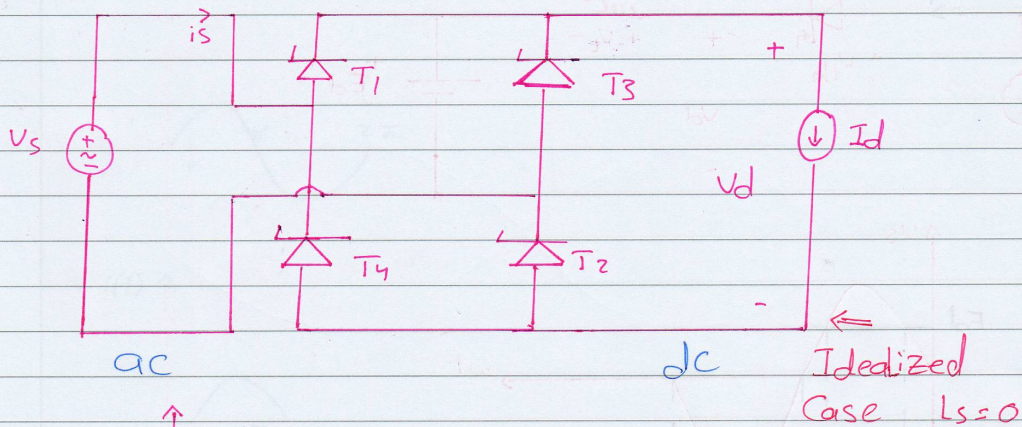


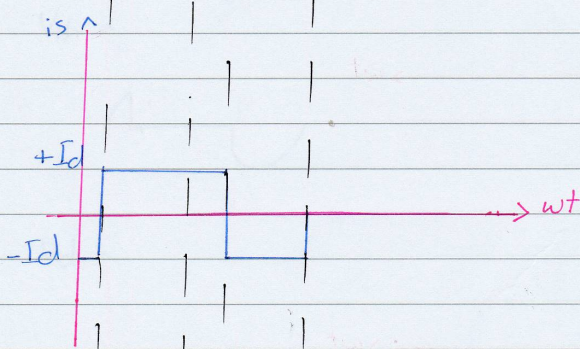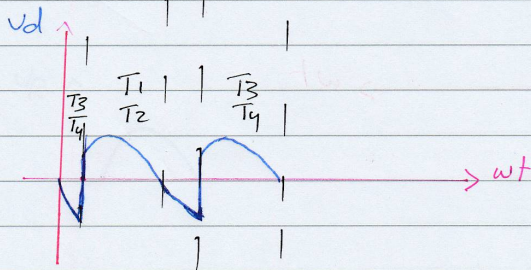\$T_1\$ and \$T_2\$ on
at \$\alpha\$
\$T_3\$ and \$T_4\$ on
at \$\pi + \alpha\$





$$V_d = \frac{2}{2\pi} \int_{\alpha}^{\pi+\alpha} \sqrt{2} V_s \sin \theta d\theta = \frac{\sqrt{2} V}{\pi} \cos \theta \Big|_{\pi+\alpha}^{\alpha}$$
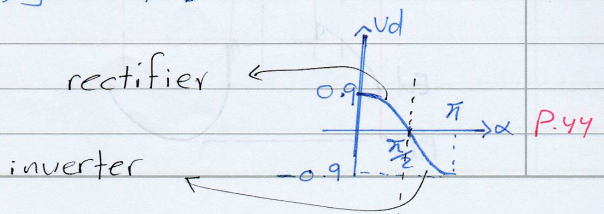
$$= \frac{\sqrt{2} V}{\pi} [\cos \alpha - \cos(\pi + \alpha)] = 0.9 V \cos \alpha$$



$P_d = U_d I_d$ $P = U \bar{I}_s \cos \alpha$ $= U [0.9 I_d] \cos \alpha$ $P = 0.9 U I_d \cos \alpha$	$THD\% = \frac{\sqrt{(I_d)^2 - (0.9 I_d)^2}}{0.9 I_d} \times 100\%$ $= 48.43$ $DPF = \cos \alpha, \quad PF = 0.9 \cos \alpha$
---	---

Effect of L_s :-

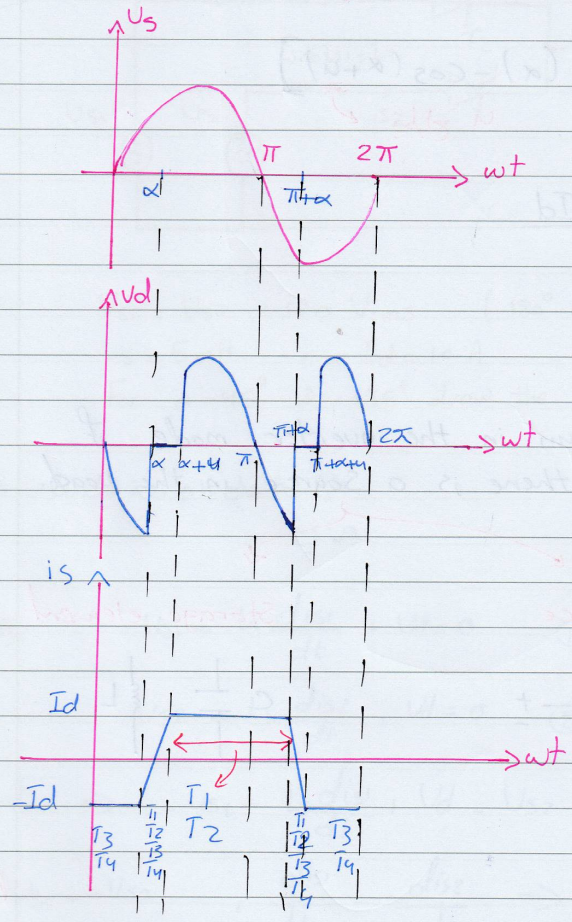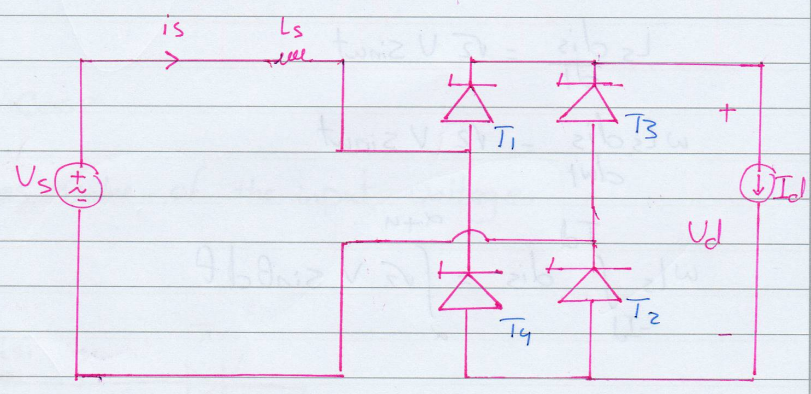

$$V_d = \frac{2}{2\pi} \int_{\alpha+\pi}^{\alpha+\pi} \sqrt{2} V \sin \theta d\theta = \frac{\sqrt{2} V}{\pi} \cos \theta \Big|_{\alpha+\pi}^{\alpha+\pi}$$

$$= \frac{\sqrt{2} V}{\pi} [\cos(\alpha+\pi) - \cos(\alpha+\pi)]$$

During Commutation:-

$$V_L = V_s$$

$$L_s \frac{dis}{dt} = \sqrt{2} V \sin \omega t$$

$$\omega L_s \frac{dis}{dt} = \sqrt{2} V \sin \omega t$$

$$\omega L_s \int_{-I_d}^{I_d} dis = \int_{\alpha}^{\alpha+\pi} \sqrt{2} V \sin \theta d\theta$$


$$2 \omega L_s I_d = \sqrt{2} V [\cos(\alpha) - \cos(\alpha+\pi)]$$

u zlye


$$V_d = 0.9 V \cos \alpha - \frac{2 \omega L_s I_d}{\pi}$$

→ Inverter Mode of Operation:-

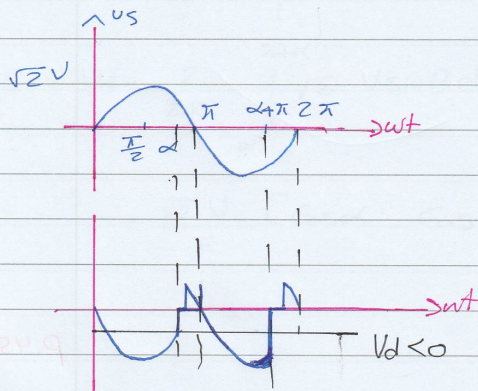
Controlled Rectifier ccts can run in the inverter mode if α is greater than 90° and there is a Source in the Load.




Source

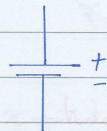

Storage element

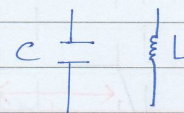


"Three phase Converter"

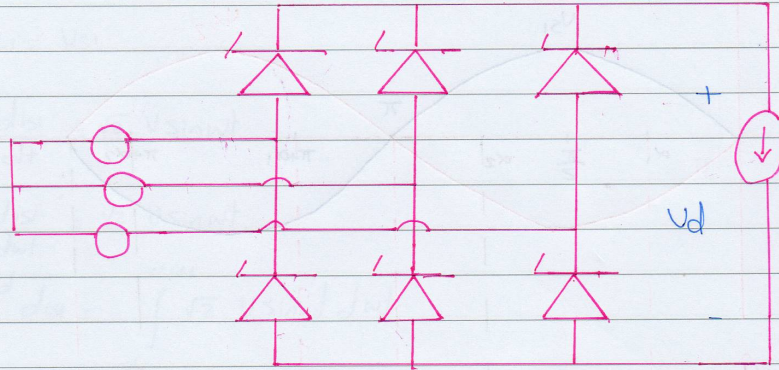

$$V_d = 1.35 V_{LL} \cos \alpha$$

Line-Line rms value of the input voltage.

"Problems"

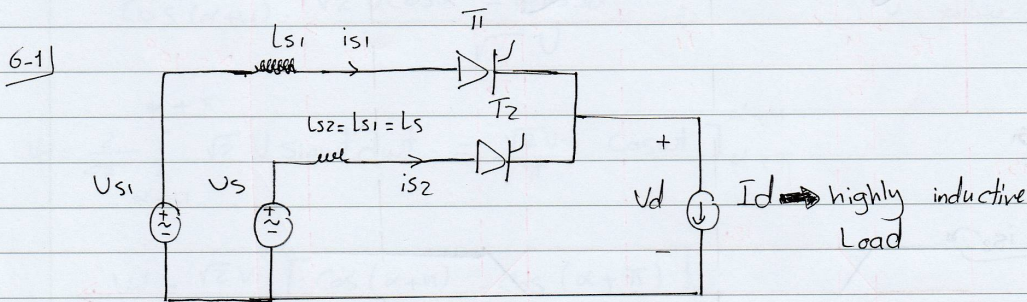

$$V_{s1} = V_{s2} = 120 \text{ V}_{rms} \quad (180^\circ \text{ out of Phase})$$

$$L_s = 5 \text{ mH}, \quad I_d = 10 \text{ A}, \quad 60 \text{ Hz}$$

For $\alpha = 45^\circ$ & 135° draw the wave forms

الرسالة على الصفحة التي بعد
ما

$$\Rightarrow -V_{s1} + L_s \frac{di_{s1}}{dt} + V_d = 0 \quad \text{--- (1)}$$


$$-V_{s2} + L_s \frac{di_{s2}}{dt} + V_d = 0 \quad \text{--- (2)}$$

$$\text{--- (1) + (2) } \Rightarrow -V_{s1} + L_s \frac{di_{s1}}{dt} + V_d - V_{s2} + L_s \frac{di_{s2}}{dt} + V_d = 0$$

$$V_{s1} = -V_{s2}, \quad \frac{di_{s1}}{dt} = -\frac{di_{s2}}{dt} \Rightarrow 2V_d = 0 \Rightarrow V_d = 0$$

during commutation only

during commutation.

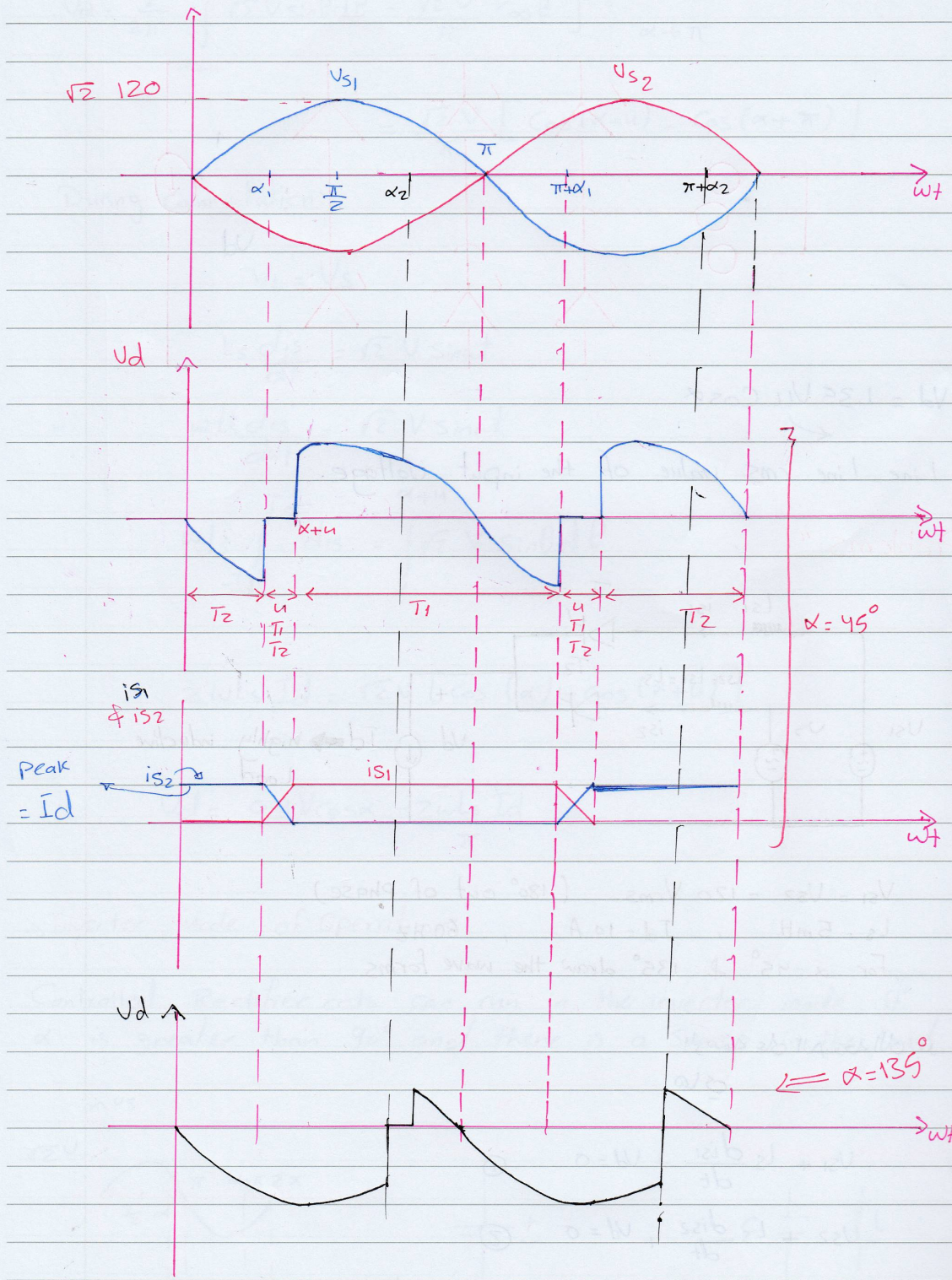

During commutation:-

$$V_{L1} = V_{s1}$$

$$\omega L_s \frac{di_{s1}}{dt} = \sqrt{2} V \sin \omega t$$

$$\omega L_s \frac{di_{s1}}{d\omega t} = \sqrt{2} V \sin \omega t$$

$$\omega L_s \int_0^{I_d} di_{s1} = \int_{\alpha}^{\alpha+\mu} \sqrt{2} V \sin \omega t d\omega t$$


$$\omega L_s I_d = \sqrt{2} V [\cos \alpha - \cos(\alpha + \mu)]$$

$$\omega L_s I_d = \sqrt{2} V \cos \alpha - \sqrt{2} V \cos(\alpha + \mu)$$

$$\cos(\alpha + \mu) = \frac{\sqrt{2} V \cos \alpha - \omega L_s I_d}{\sqrt{2} V} \Rightarrow \mu \text{ given}$$


$$V_d = \frac{2}{2\pi} \int_{\alpha+\mu}^{\alpha+\pi} \sqrt{2} V \sin \omega t d\omega t = \frac{\sqrt{2} V}{\pi} [\cos \omega t]_{\alpha+\mu}^{\alpha+\pi}$$
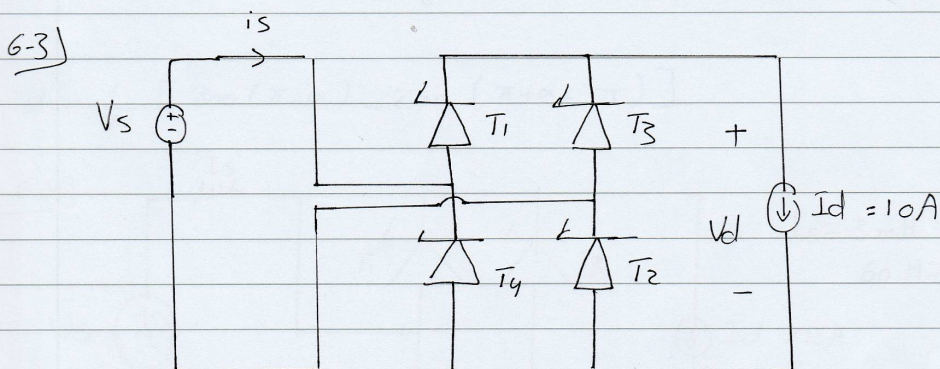
$$V_d = \frac{\sqrt{2} V}{\pi} [\cos(\alpha + \mu) - \cos(\alpha + \pi)]$$



V_s is a square wave with amplitude of 200 V, 60 Hz

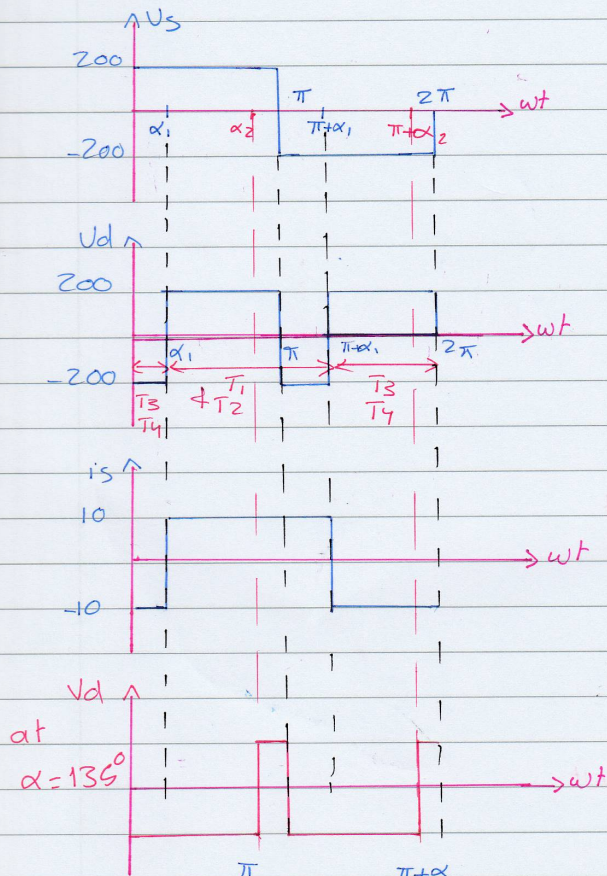
Draw wave-forms at $\alpha = 45^\circ$ & 135°




$$V_d = \frac{2}{2\pi} \left[\int_{\alpha}^{\pi} 200 d\theta + \int_{\pi}^{\pi+\alpha} -200 d\theta \right]$$

$$P_d = V_d I_d \Rightarrow P_d = \frac{1}{2\pi} \int_0^{2\pi} i_d(\theta) v_d(\theta) d\theta = \frac{10}{2\pi} \times 2 \times [\quad]$$
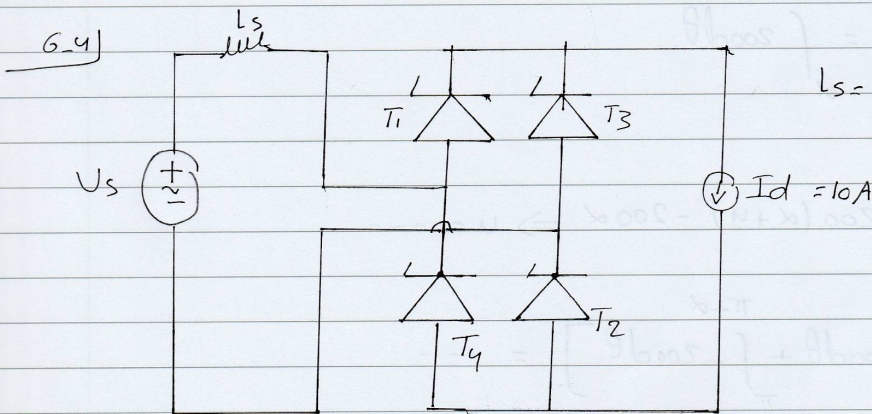
$$V_d = \frac{1}{\pi} [200(\pi - \alpha) - 200(\pi + \alpha - \pi)]$$



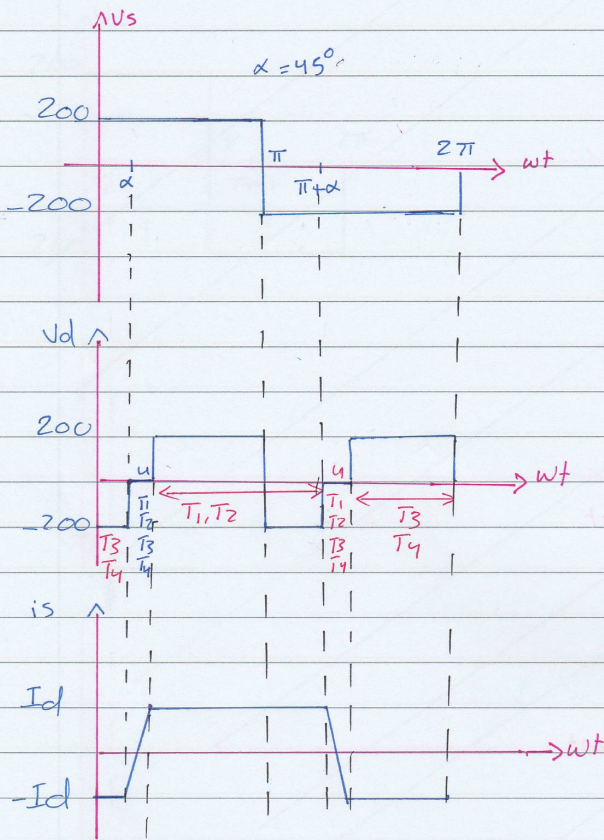

During commutation:-

$$V_L = V_s$$

$$\omega L_s \frac{di_s}{dt} = 200$$

$$\omega L_s \int_{-I_d}^{I_d} di_s = \int_{\alpha}^{\alpha+\pi} 200 d\theta$$

$$2\omega L_s I_d = 200(\alpha + \pi) - 200\alpha \Rightarrow u = \dots$$

$$V_d = \frac{2}{2\pi} \left[\int_{\alpha+\pi}^{\pi} 200 d\theta + \int_{\pi}^{\pi+\alpha} -200 d\theta \right] = \dots$$

Applications:


- 1] Dc motor drive applications.
- 2] Regulated power supplies.

They are used to convert the unregulated dc input into a controlled dc output.

Types:-

- 1] Step-down (buck) converter
- 2] Step-up (boost) converter.
- 3] Step up-stepdown (Buck-Boost) converter.
- 4] Full bridge dc-dc converter.

*Dc-Dc Converter system:


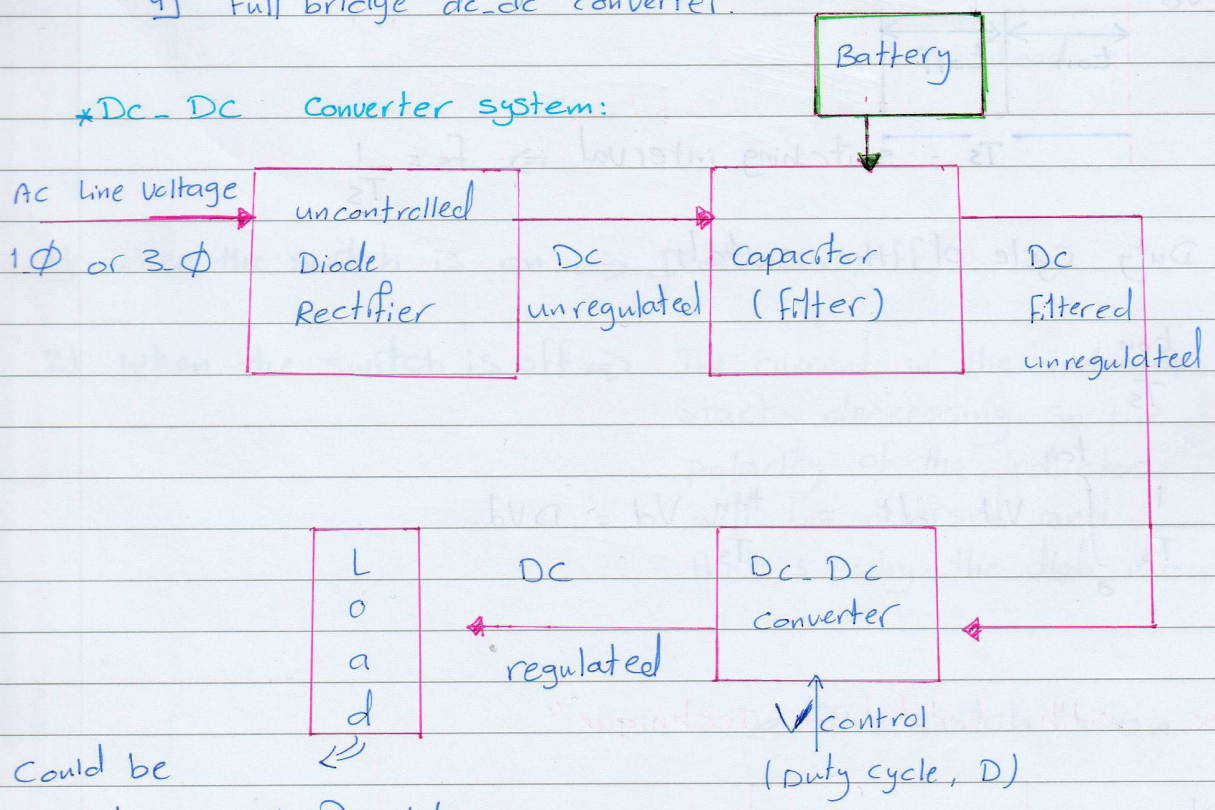


could be resistance or Dc Motor.

In this chapter:

- 1] The converters are analyzed in steady state.
- 2] The switches are ideal (No power loss)
- 3] The losses in the inductive and capacitive part are neglected.

*Control of DC-DC converters:

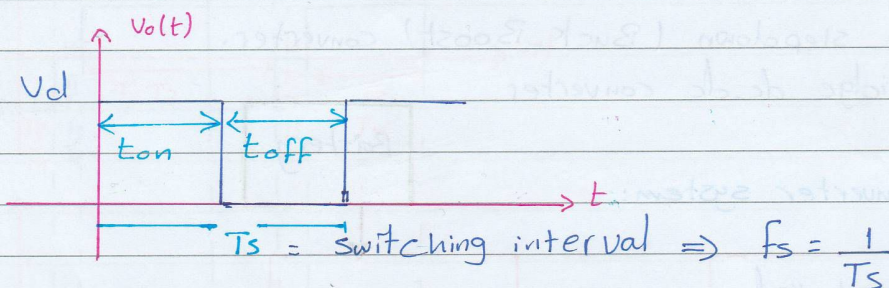
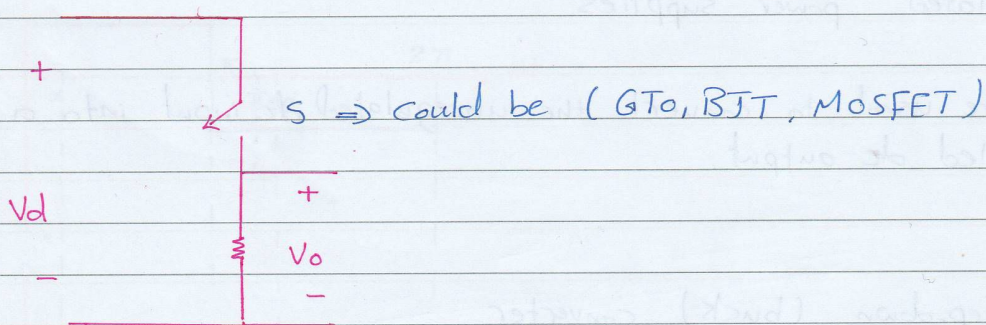


D = Duty cycle of the switch

$$D = \frac{t_{on}}{T_s}$$

$$V_o = \frac{1}{T_s} \int_0^{t_{on}} V_d dt = \frac{t_{on}}{T_s} V_d = D V_d$$


"Pulse width modulation Technique"

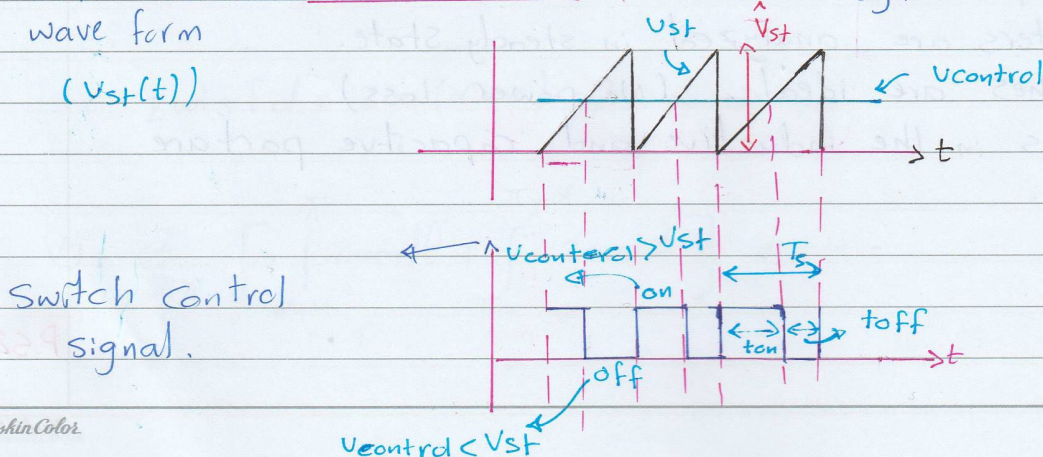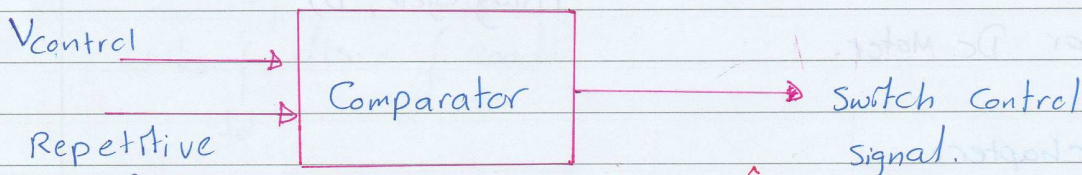

- Dc Dc converters run in:



- 1) Continuous current conduction mode.
- 2) Discontinuous current conduction mode.


"Step down (Buck) converter."

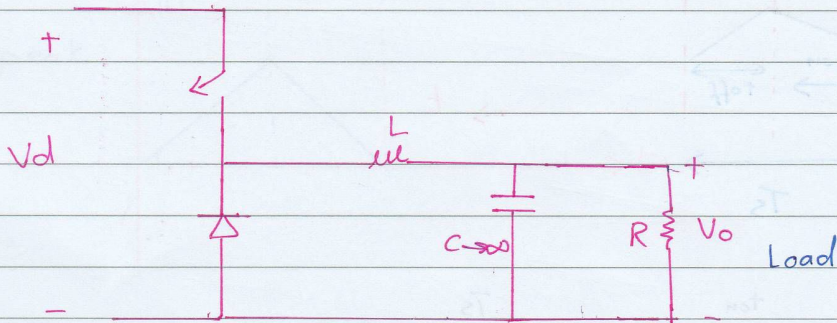

1) when the switch is on \Rightarrow Diode is off.

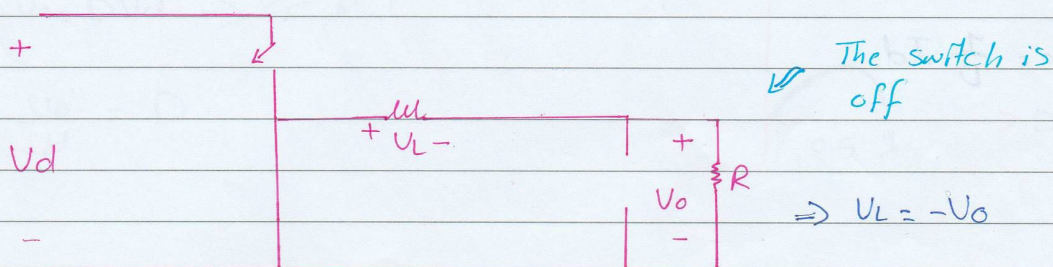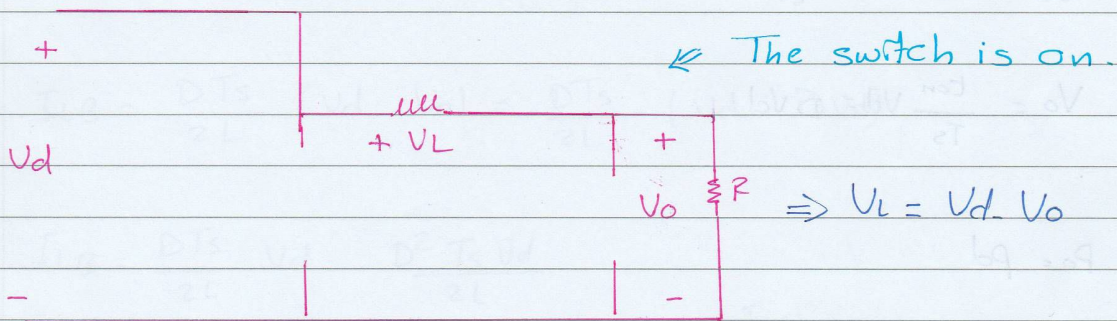2) when the switch is off \Rightarrow The current in the inductor starts decreasing so the polarity of the inductor will be reversed and that is why the diode is on.



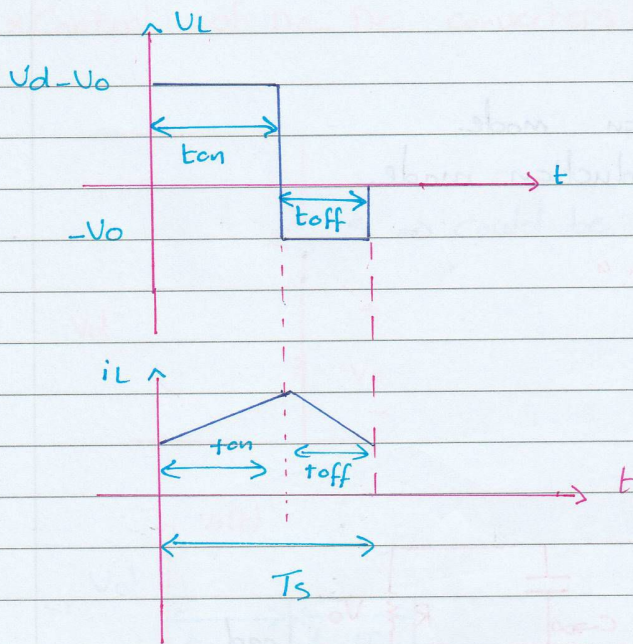

$$V_L = 0 = \frac{1}{T_s} \left[\int_0^{t_{on}} (V_d - V_o) dt + \int_{t_{on}}^{T_s} -V_o dt \right]$$

$$V_L = (V_d - V_o) t_{on} - V_o (T_s - t_{on}) = 0$$

$$V_d t_{on} - V_o t_{on} - V_o T_s + V_o t_{on} = 0$$

$$V_d t_{on} = V_o T_s$$

$$\frac{V_o}{V_d} = \frac{t_{on}}{T_s} = D$$


$$V_o = \frac{t_{on}}{T_s} V_d = D V_d$$

$$P_o = P_d$$

$$V_o I_o = V_d I_d$$

$$I_o = \frac{1}{D} I_d$$

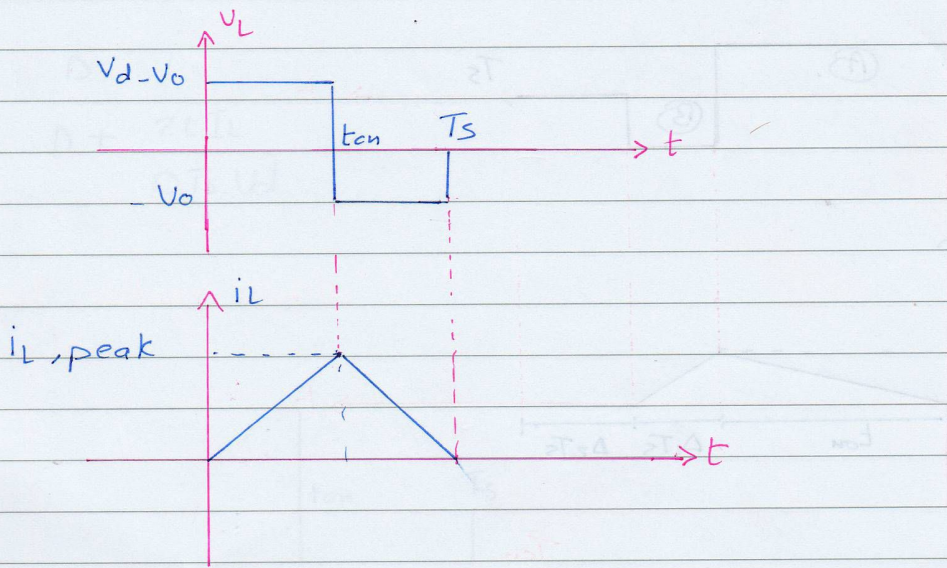1) Cont. mode:- We have current at any instant



$$I_{LB} = \frac{1}{T_s} \left[\frac{1}{2} t_{on} i_{L,peak} + \frac{1}{2} t_{off} i_{L,peak} \right]$$

$$I_{LB} = \frac{1}{2} i_{L,peak}$$

$$i_L(t) = \frac{1}{L} (V_d - V_o) t$$

$$i_{L,peak} = \frac{1}{L} (V_d - V_o) t_{on}$$


$$\therefore I_{LB} = \frac{t_{on}}{2L} (V_d - V_o), \quad D = \frac{t_{on}}{T_s}$$

$$I_{LB} = \frac{DT_s}{2L} (V_d - V_o) = \frac{DT_s}{2L} (V_d - DV_d)$$


$$I_{LB} = \frac{DT_s}{2L} V_d - \frac{D^2 T_s V_d}{2L}$$

$$\Rightarrow V_o = DV_d \Rightarrow C.C.M$$

$$\frac{V_o}{V_d} = D$$

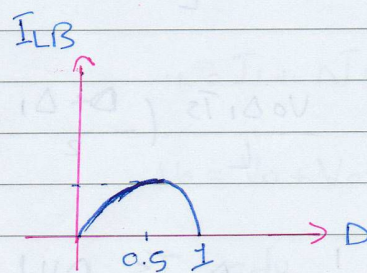

* Discontinuous mode:-

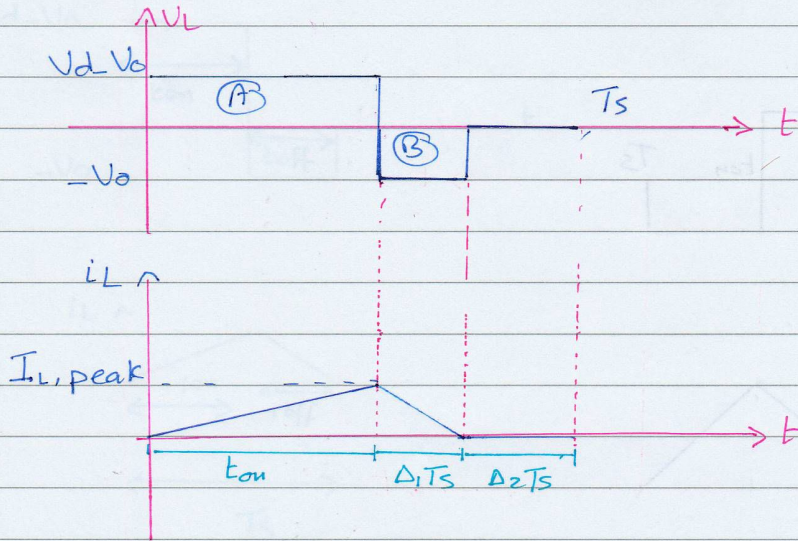

$$\textcircled{A} = \textcircled{B} \Rightarrow (V_d - V_o) \overbrace{D T_s}^{T_{on}} = V_o \Delta_1 T_s$$

$$V_d (D T_s) = V_o \Delta_1 T_s + V_o D T_s$$

$$\frac{V_o}{V_d} = \frac{D}{D + \Delta_1} \Rightarrow \text{not the same ratio}$$

$$\Rightarrow \bar{I}_L = \frac{1}{T_s} \left(\frac{1}{2} i_{L,peak} \overbrace{D T_s}^{T_{on}} + \frac{1}{2} i_{L,peak} \Delta_1 T_s \right)$$

$$\bar{I}_L = i_{L,peak} \left(\frac{D + \Delta_1}{2} \right)$$

$$i_{L,peak} = \frac{(V_d - V_o)}{L} D T_s$$

$$i_{L,peak} = \frac{V_o}{L} \Delta_1 T_s$$





$$\bar{I}_L = \frac{V_o \Delta_1 T_s}{L} \left(\frac{D + \Delta_1}{2} \right) = \left(\frac{D + \Delta_1}{2} \right) \frac{1}{L} \Delta_1 T_s \left(\frac{V_d D}{D + \Delta_1} \right)$$

$$\bar{I}_L = \frac{1}{2L} \cdot \Delta_1 T_s D V_d$$

$$\Delta I_L = \frac{2L \bar{I}_L}{DT_s V_d}$$

$$\frac{V_o}{V_d} = \frac{D}{D + \frac{2L \bar{I}_L}{DT_s V_d}}$$

"Output voltage ripple"

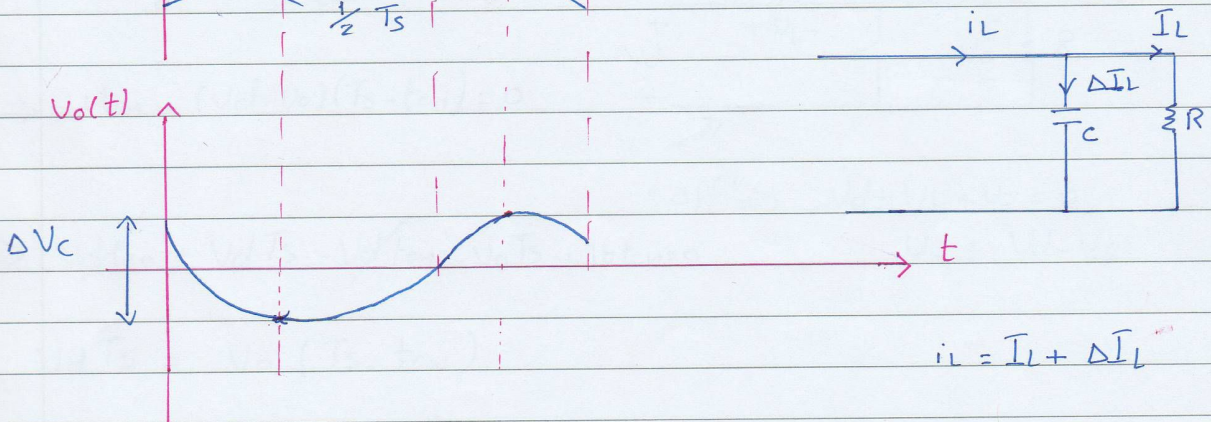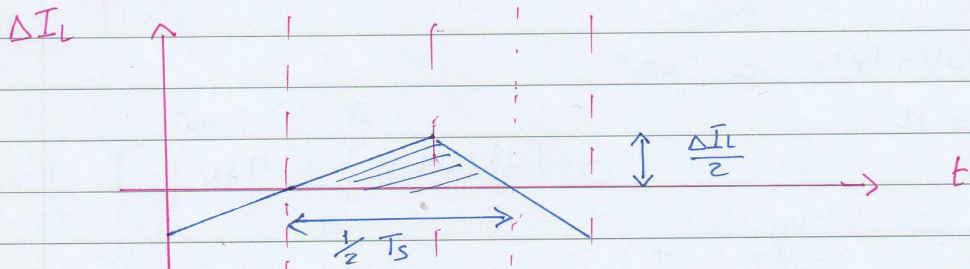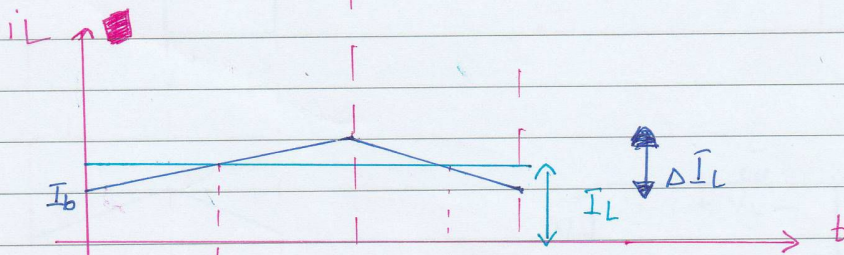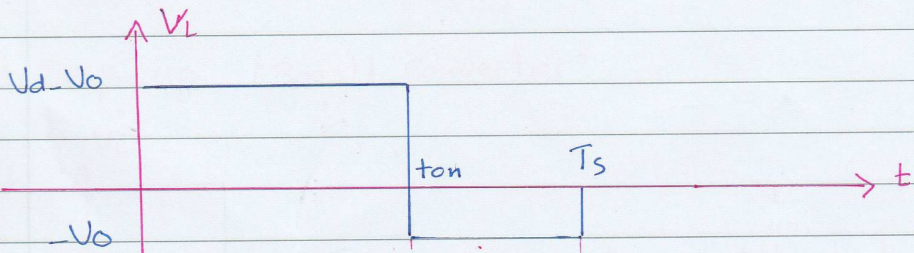

$$i_L = \bar{I}_L + \Delta I_L$$

$$V_o = V_o + V_o(t)$$


$$i = C \frac{dv}{dt}$$

$$\Delta V_o = \frac{\Delta Q}{C} = \frac{1}{C} \times \frac{1}{2} \left(\frac{1}{2} T_s \frac{\Delta I_L}{2} \right)$$

$$\Delta I_L = \frac{V_o}{L} (1-D) T_s$$

$$\frac{\Delta V_o}{V_o} = \frac{1}{8} \frac{T_s^2 (1-D)}{LC} = \frac{1}{8} \frac{(1-D)}{LC f_s^2}$$


"Step-up (Boost) Converter"

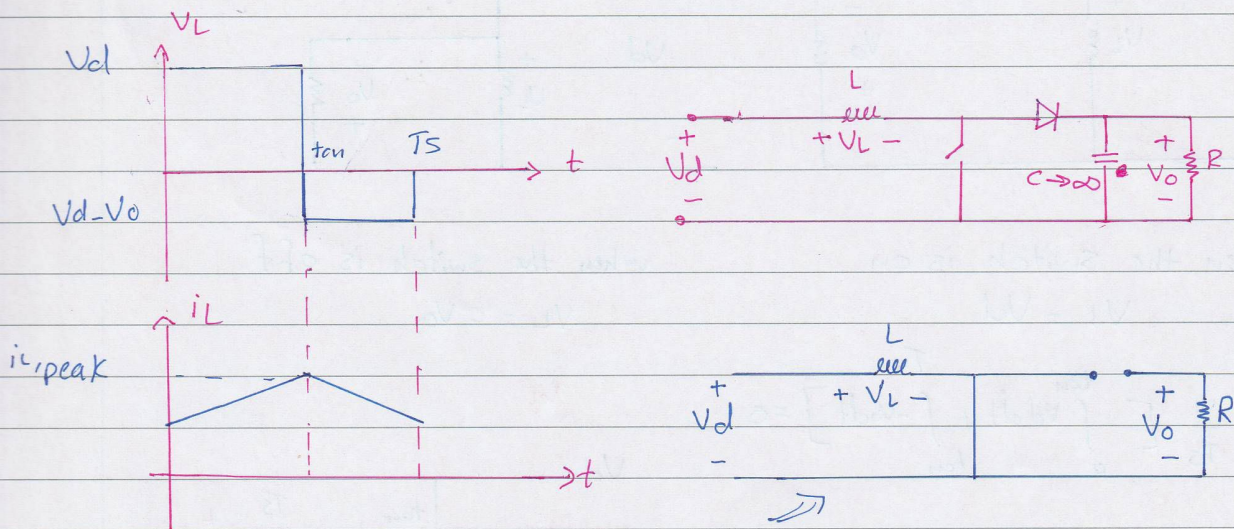

"on" $\Rightarrow -V_d + V_L = 0$
 $V_L = V_d$

$$V_L = \frac{1}{T_s} \left[\int_0^{t_{on}} V_d dt + \int_{t_{on}}^{T_s} (V_d - V_o) dt \right] = 0$$
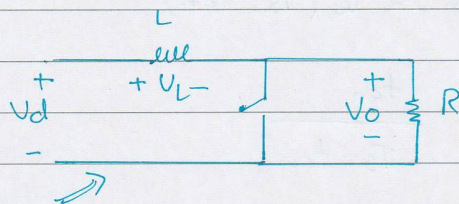
$$\Rightarrow V_d t_{on} + (V_d - V_o)(T_s - t_{on}) = 0$$






"off" $\Rightarrow -V_d + V_L + V_o = 0$
 $V_L = V_d - V_o$

$$\Rightarrow V_d t_{on} + V_d T_s - V_d t_{on} - V_o T_s + V_o t_{on} = 0$$

$$V_d T_s = V_o (T_s - t_{on})$$

$$\frac{V_o}{V_d} = \frac{T_s}{T_s - t_{on}} = \frac{T_s}{T_s - DT_s} = \frac{1}{1-D} \Rightarrow \text{This ratio is always greater than 1.}$$

"Buck-Boost converter"

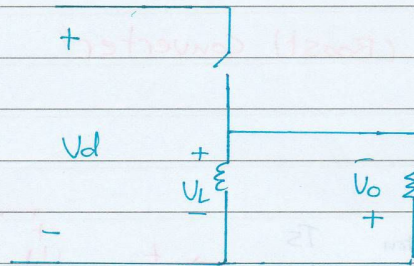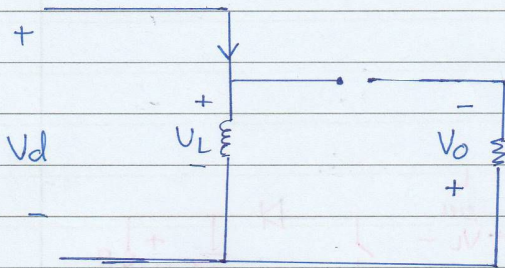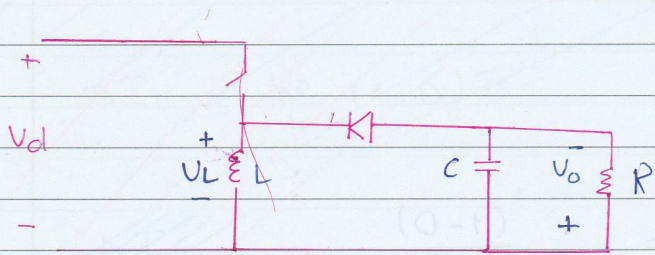

when the switch is on.

$$V_L = V_d$$

when the switch is off

$$V_L = -V_o$$


$$V_L = \frac{1}{T_s} \left[\int_0^{t_{on}} V_d dt + \int_{t_{on}}^{T_s} -V_o dt \right] = 0$$

$$\Rightarrow V_d t_{on} - V_o (T_s - t_{on}) = 0$$

$$V_d t_{on} = V_o (T_s - t_{on})$$

$$\frac{V_o}{V_d} = \frac{t_{on}}{T_s - t_{on}}$$

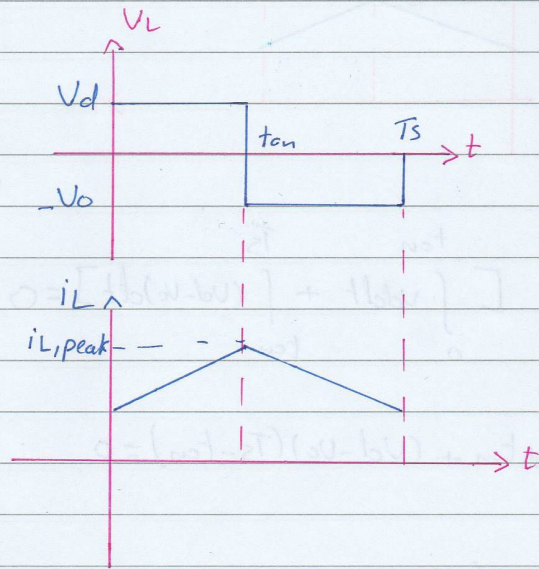
$$\frac{V_o}{V_d} = \frac{DT_s}{T_s - DT_s} = \frac{D}{1-D}$$



"Full-Bridge dc-dc converter"

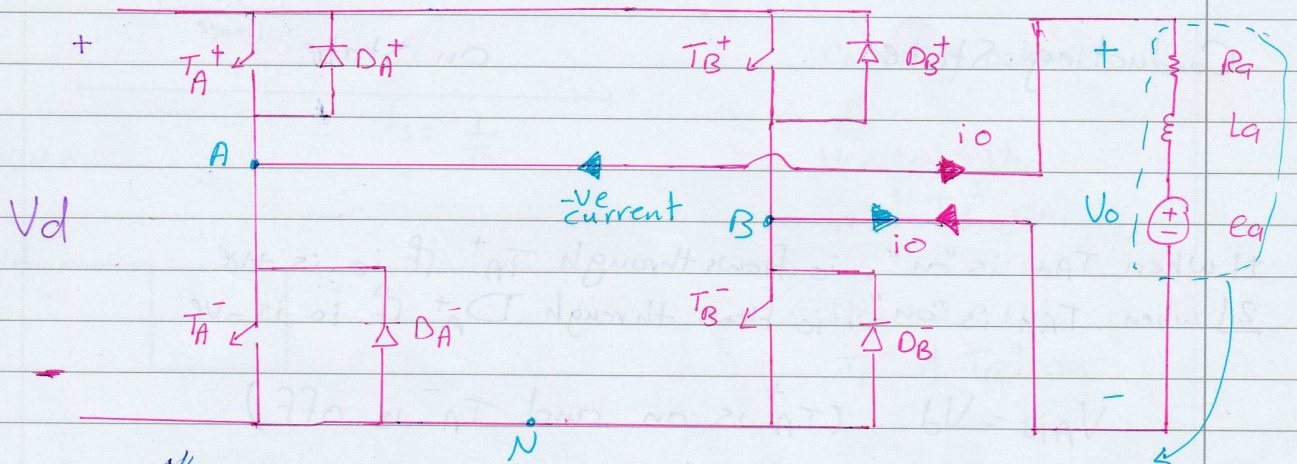- 1) dc motor drive systems.
- 2) regulated power supplies.
- 3) dc-ac conversion (inverter)


* -ve direction for the current passes through the diodes



T_{A+} & T_{A-} or T_{B+} & T_{B-} can't be open at the same time because of V_d .


Dc Meter
(highly inductive Load)

$$V_o = V_{AN} - V_{BN}$$

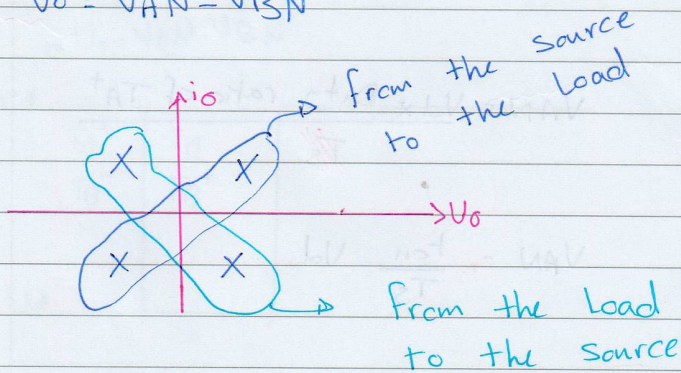


⇒ on-state of the switch:- The switch is on and the current flows through the anti parallel diode

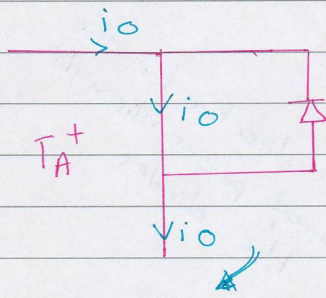⇒ Conducting -state of the switch:- The switch is on and the current flows through it (+ve direction of the current).



Conducting State

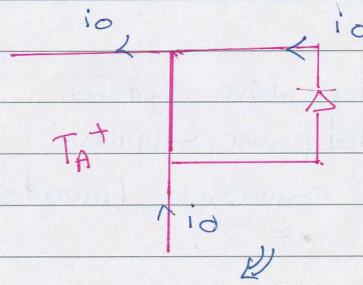


On State

- 1] When T_{A+} is "on", i_o flows through T_{A+} if i_o is +ve
- 2] When T_{A+} is "on", i_o flows through D_{A+} if i_o is -ve

$$V_{AN} = V_d \quad (T_{A+} \text{ is on and } T_{A-} \text{ is off})$$

- 1] when T_{A-} is "on", i_o flows through T_{A-} if i_o is -ve
- 2] when T_{A-} is "on", i_o flows through D_{A-} if i_o is +ve

$$V_{AN} = 0$$

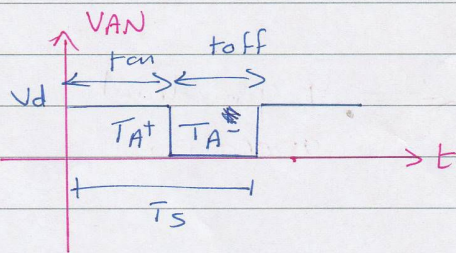


$$V_{AN} = V_d * \text{Duty ratio of } T_{A+}$$

$$V_{AN} = \frac{t_{on}}{T_s} V_d$$

$$V_{BN} = V_d * \text{Duty ratio of } T_{B+} \Rightarrow \frac{t_{on}}{T_s}$$

and these two are independent of the direction of i_o .





"PWM with Bipolar voltage switching"

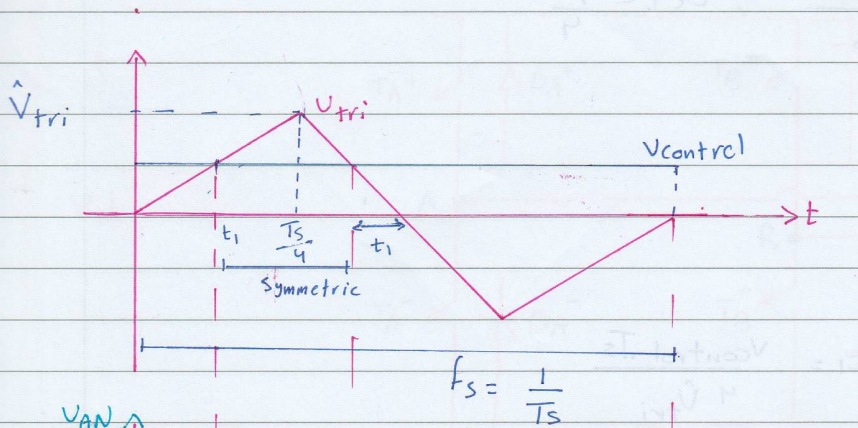

Controlling scheme:

$V_{control} > U_{tri}$
 T_A^+ & T_B^- on

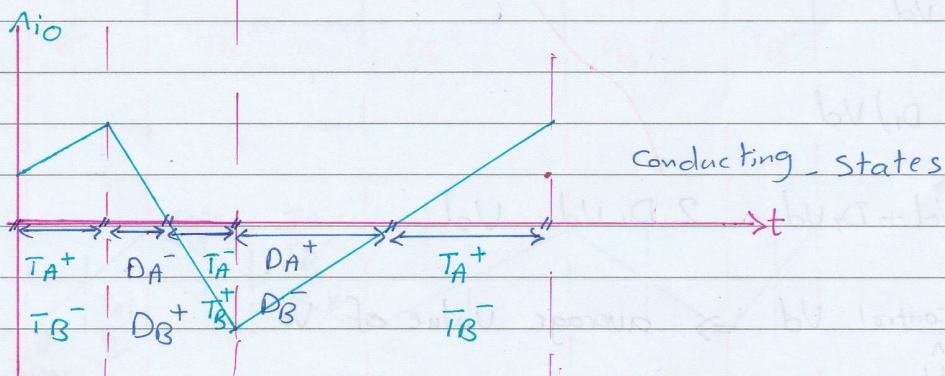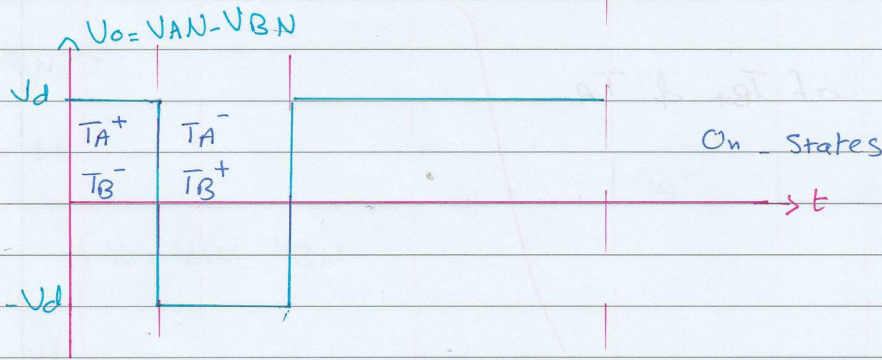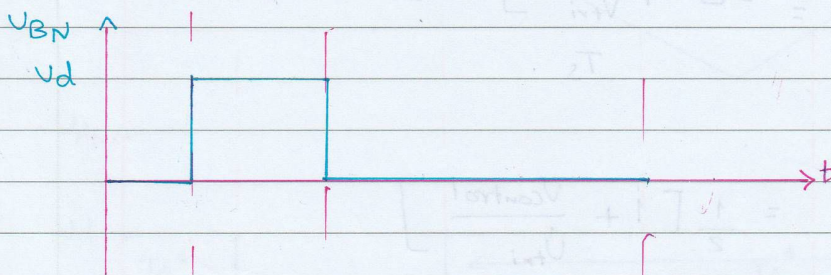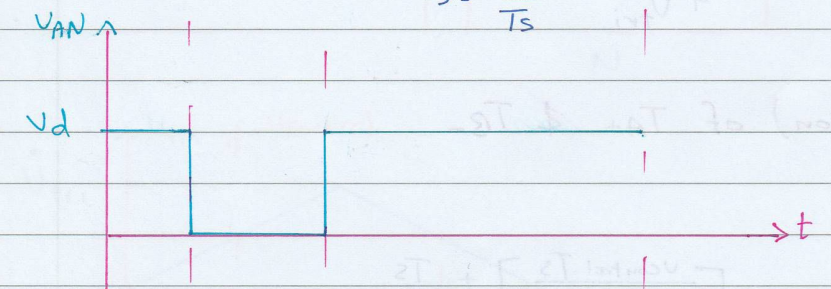$V_{control} < U_{tri}$
 T_A^- & T_B^+ on



4 quadrants.

$$V_{tri} = \hat{V}_{tri} \frac{t}{T_s/4} = \frac{4 \hat{V}_{tri} t}{T_s}, \quad 0 < t < \frac{T_s}{4}$$

at $t = t_1$

$$V_{tri} = V_{control}$$

$$V_{control} = \frac{4 \hat{V}_{tri} t_1}{T_s} \Rightarrow t_1 = \frac{V_{control} T_s}{4 \hat{V}_{tri}}$$

\Rightarrow The on duration (t_{on}) of T_{A+} & T_{B-}

$$t_{on} = 2t_1 + \frac{1}{2} T_s$$

$$D_1 = \frac{t_{on}}{T_s} = \frac{2t_1 + T_s/2}{T_s} = \frac{2 \left[\frac{V_{control} T_s}{4 \hat{V}_{tri}} \right] + \frac{T_s}{2}}{T_s}$$

$$D_1 = \frac{1}{2} \left[1 + \frac{V_{control}}{\hat{V}_{tri}} \right]$$

\Rightarrow The on duration of T_{B+} & T_{A-}

$$D_2 = 1 - D_1$$

$$V_o = V_{AN} - V_{BN}$$


$$V_o = D_1 V_d - D_2 V_d$$

$$= D_1 V_d - (1 - D_1) V_d$$


$$= D_1 V_d - V_d + D_1 V_d = 2 D_1 V_d - V_d$$

$$V_o = K V_d = \frac{V_{control}}{\hat{V}_{tri}} V_d \Rightarrow \text{average value of } V_o$$

"PWM with uni-polar voltage switching"

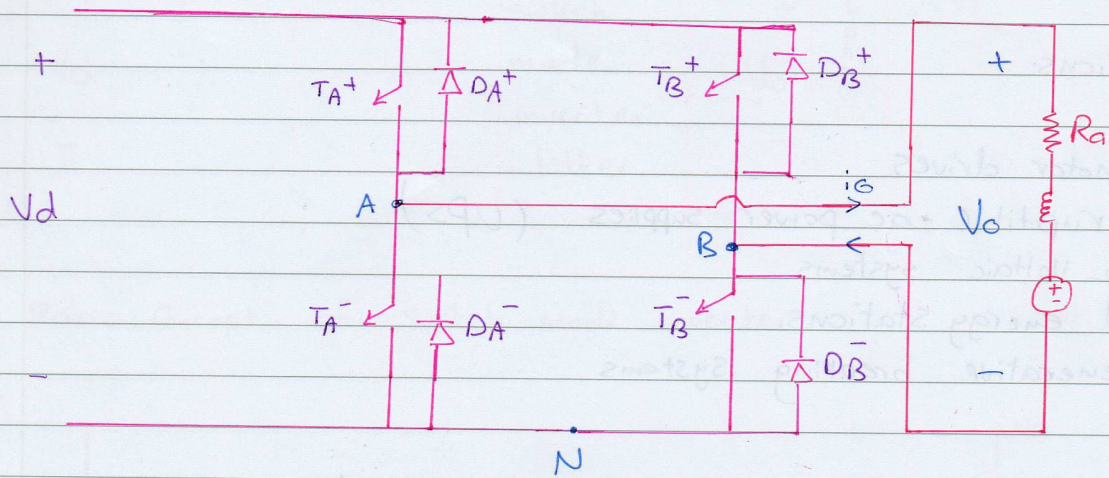

Control scheme:-

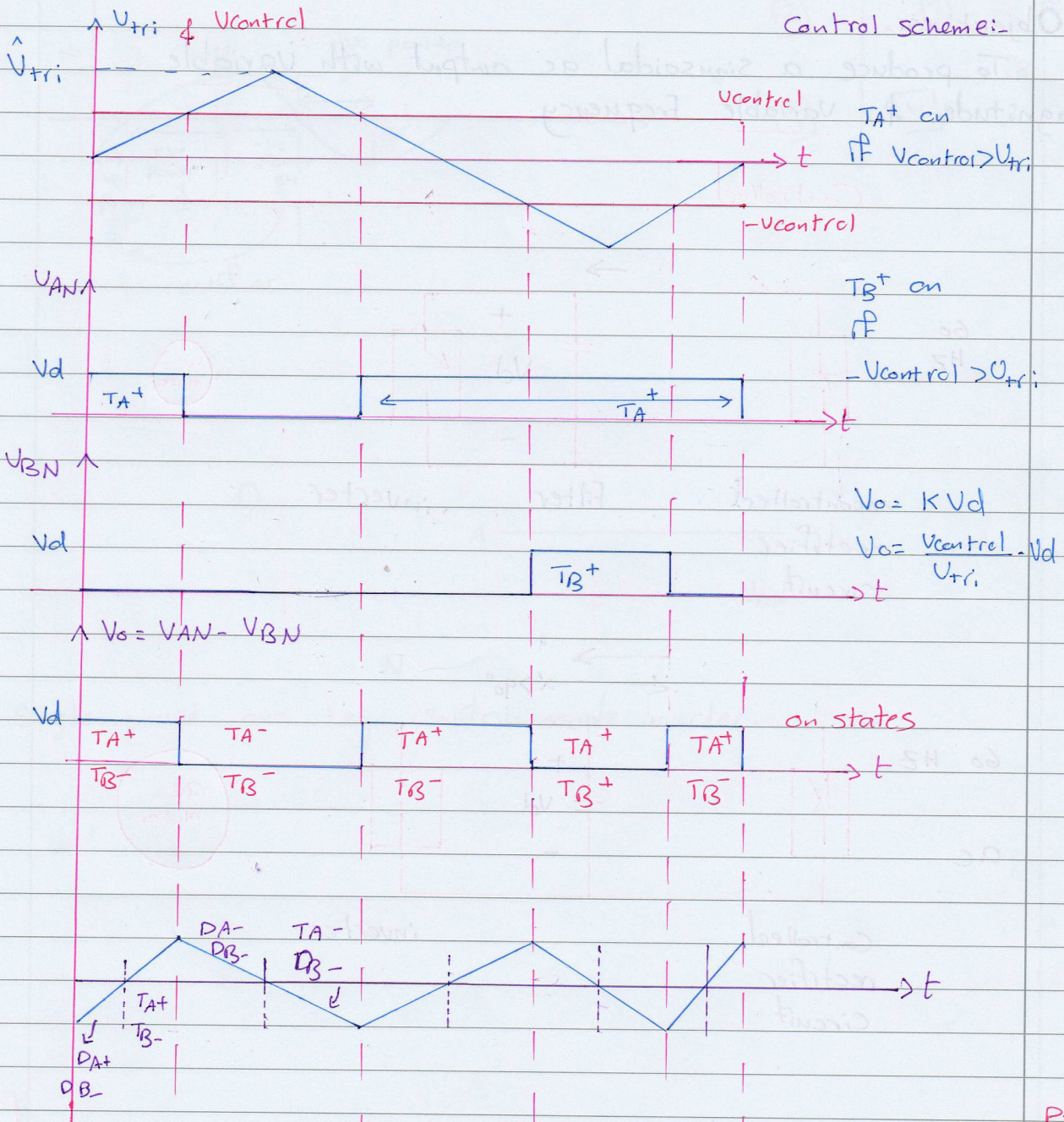

dc \leftrightarrow sinusoidal ac



Applications:-


- 1) ac motor drives
- 2) uninterruptible ac power supplies (UPS)
- 3) Photo-voltaic systems
- 4) Wind energy stations
- 5) regenerative braking systems.

Objectives:-



To produce a sinusoidal ac output with variable magnitude & variable frequency

Controlled

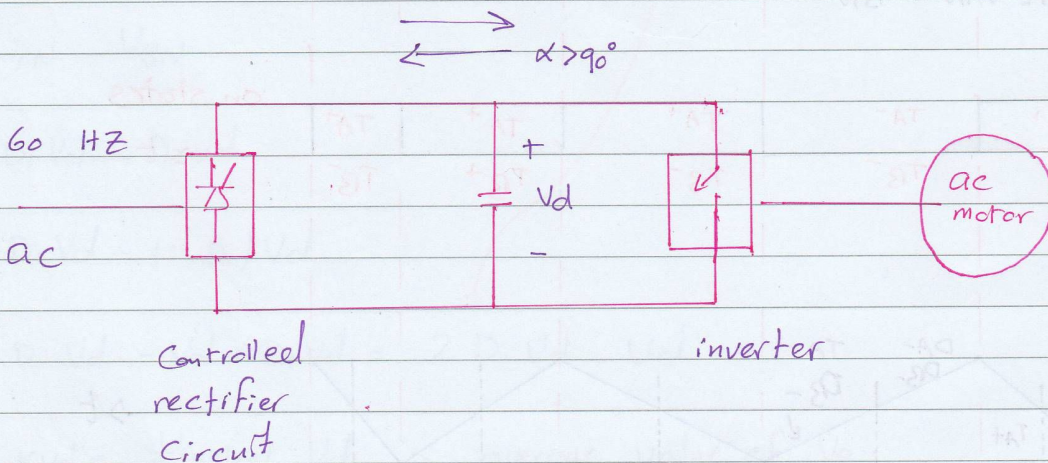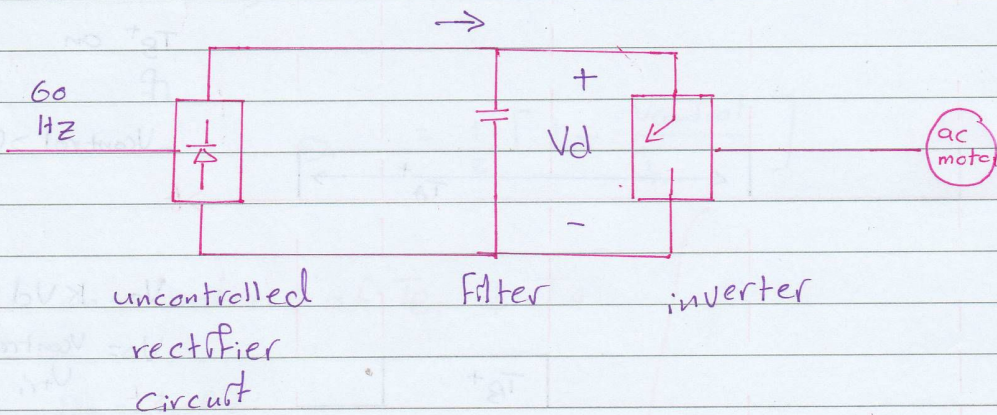


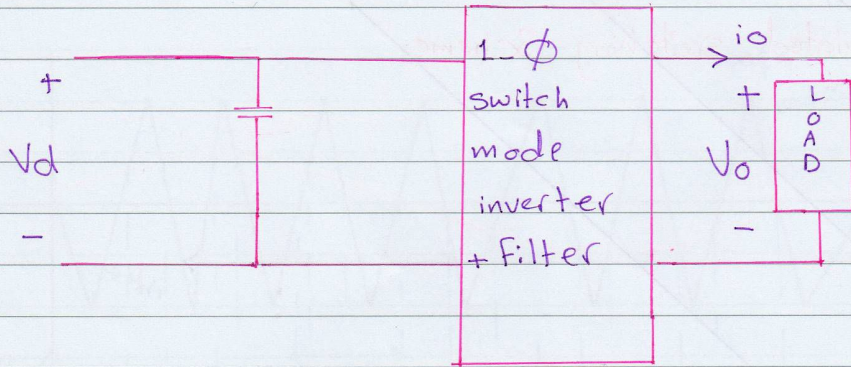


Basic Concept of Switch-Mode Inverters

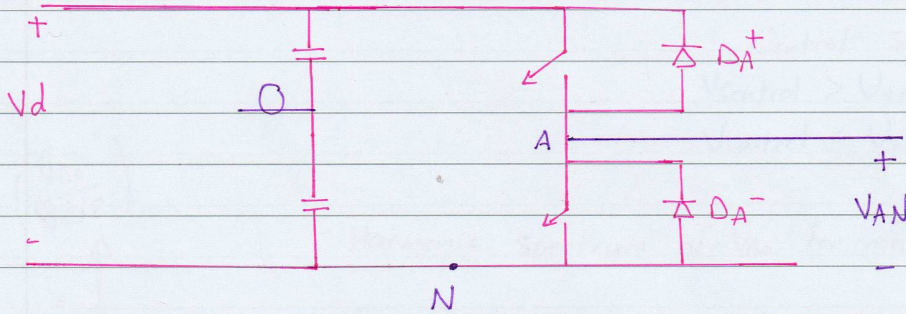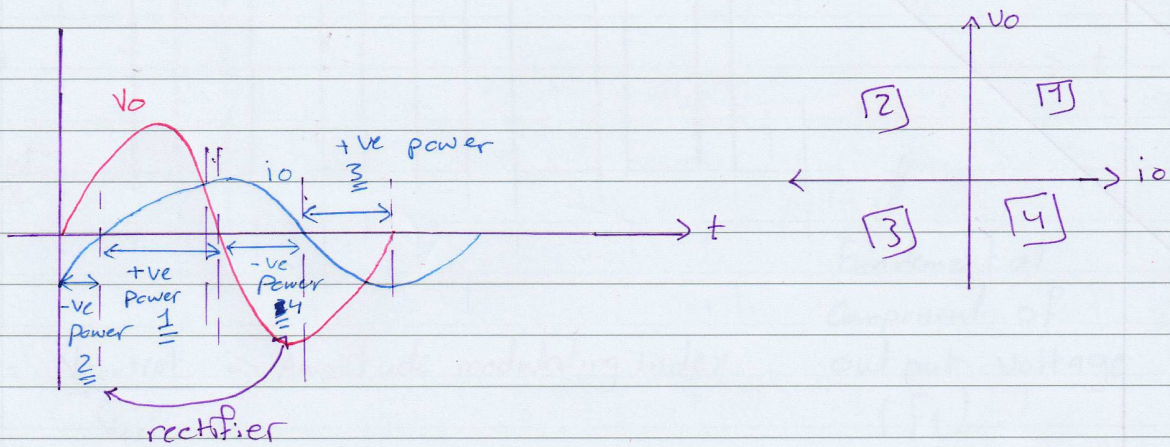

Single phase one-leg switch mode inverter.


"Pulse Width Modulated switching"

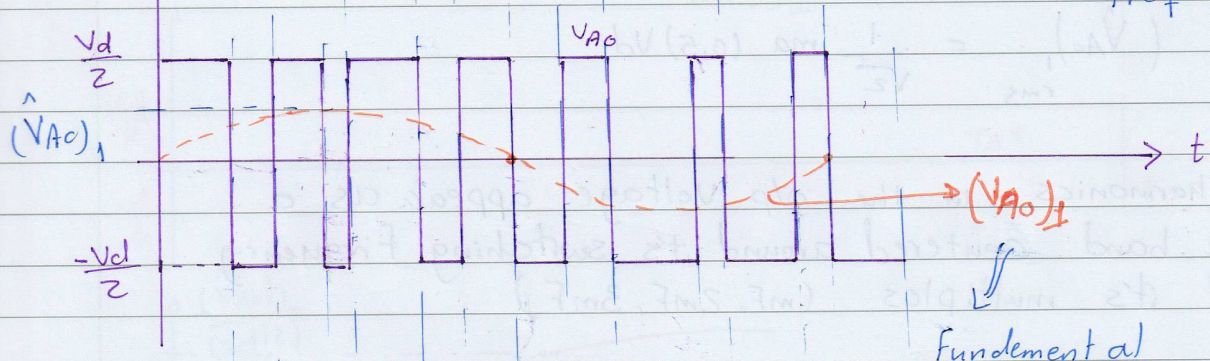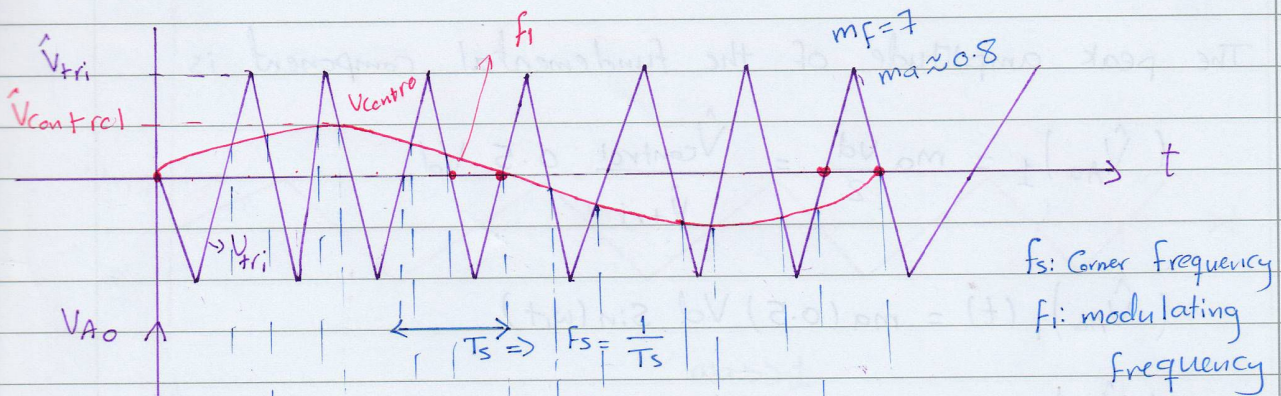

$m_a = \frac{\hat{V}_{control}}{\hat{V}_{tri}} \Rightarrow$ Amplitude modulating index

$m_f = \frac{f_s}{f_i} \Rightarrow$ Frequency modulating index

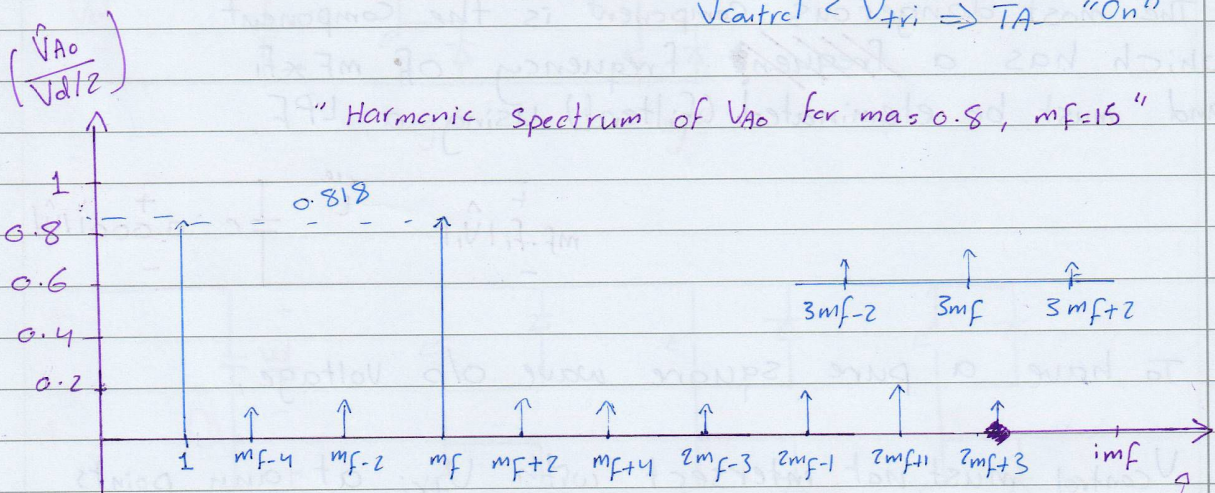Control scheme -
 $V_{control} > V_{tri} \Rightarrow TA$ "On"
 $V_{control} < V_{tri} \Rightarrow TA$ "On"



$\hat{V}_{Ao} = 0.8 \frac{V_d}{2}$

$\Rightarrow (\hat{V}_{Ao})_{mf} = (\hat{V}_{Ao})_{15} = 0.818 \frac{V_d}{2}$

$\hat{V}_{Ao} = m_a \frac{V_d}{2}$

(15 x f_i Hz)

"Notes on PWM":-

1] The peak amplitude of the fundamental component is

$$(\hat{V}_{Ao})_1 = m_a \frac{V_d}{2} = \frac{\hat{V}_{control}}{\hat{V}_{tri}} 0.5 V_d$$

$$(\hat{V}_{Ao})_1(t) = m_a (0.5) V_d \sin(\omega t)$$

$$(\hat{V}_{Ao})_{1,rms} = \frac{1}{\sqrt{2}} m_a (0.5) V_d$$

2] The harmonics in the o/p voltage appear as a side band centered around its switching frequency and its multiples ($mF, 2mF, 3mF$)


3] The frequencies at which harmonic occurs :-

$$f_n = (jmF \pm k) f_1 = hf_1$$

if j is odd, k is even

if j is even, k is odd

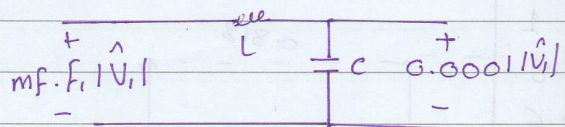4] The most dangerous component is the component which has a ~~frequency~~ frequency of $mF \times f_1$ and must be eliminated (filtered) using a LPF.






5] To have a pure square wave o/p voltage,

$V_{control}$ must not intersect with V_{tri} at any points


except the zero crossing

"chps"

4-7-2017

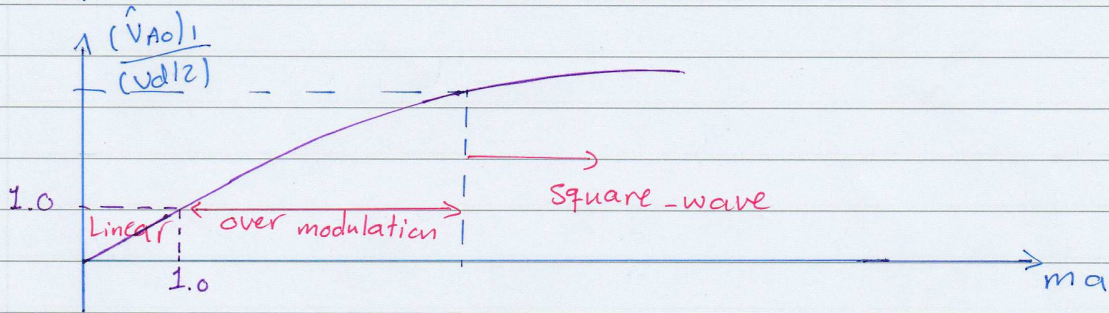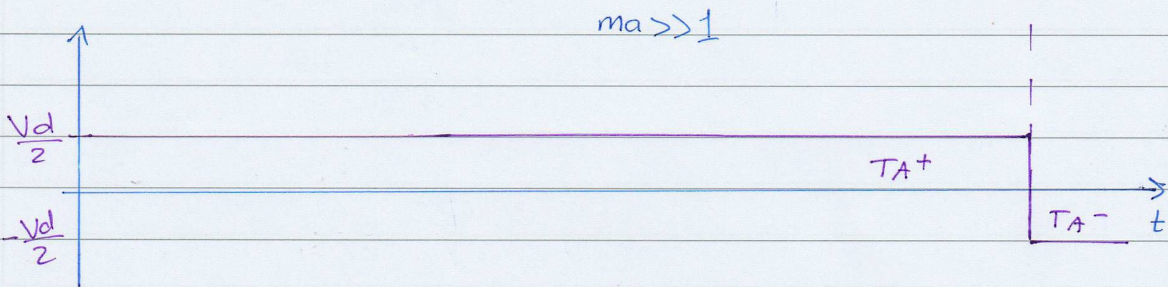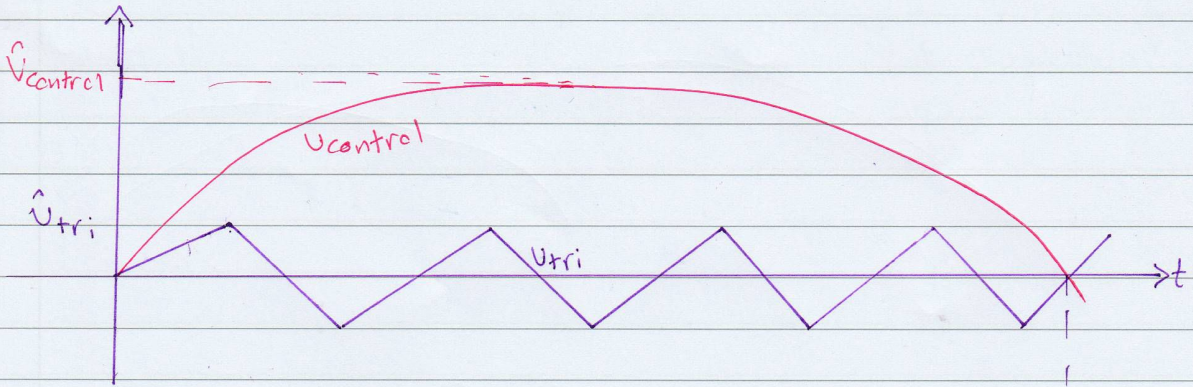

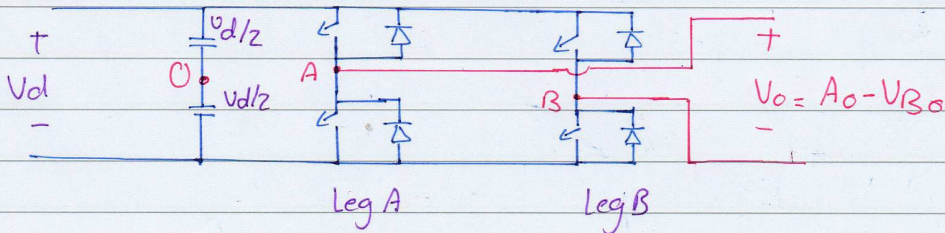" 1- ϕ full bridge switch mode inverter "



" 3- ϕ inverter "

