



تقدم لجنة EiCoM الاكاديمية

تلخيص لمادة:

انظمة قوة كهربائية

جزيل الشكر للطالب:


اسامة هيكل



Power system

* Ac circuits:-

A sinusoidal voltage or current has

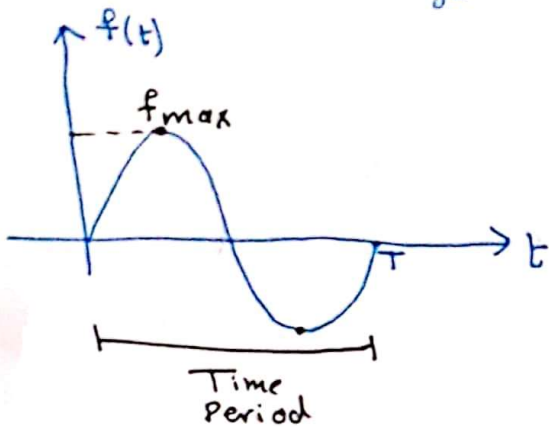

- maximum value
- Time period
- Constant frequency
- phase shift
- sine or cosine

$$f(t) = F_{max} \cos(\omega t + \delta)$$

* $\omega = 2\pi f$ ($\frac{\text{rad}}{\text{s}}$): angular frequency

* $f = \frac{1}{T}$ ($\text{Hz} \equiv \text{s}^{-1}$): number of repeating wave per second

* $T = \frac{1}{f}$ (s): time to complete one full-wave

The reasons of using Ac in Power systems :-

- ⊗ To transmit power we use high voltage, But at the load you need to low voltages, And the Ac is easy to raise and lower. ⇒ Being ABle to convert voltage levels with transformer




⊗ Benefits :- high power efficiency
low current (less heat)
high voltage

* $v(t) = V_m \cos(\omega t + \phi)$ → time-domain Form (instantaneous value)

$V = V_{rms} \angle \phi$ → Polar Form



$V = V_{rms} e^{j\phi}$ → exponential Form

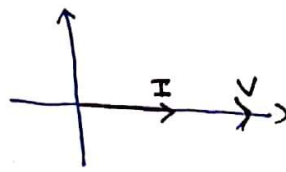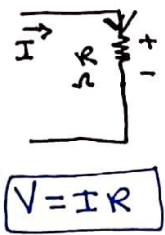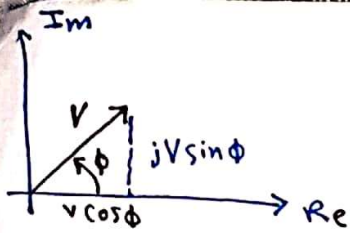$V = V \cos \phi + j \sin \phi$ → rectangular Form





⊗ Inphase
(Resistive)

$$V = j\omega L I$$

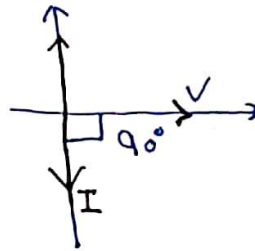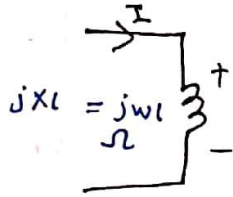

⊗ I lag V
By 90
(Inductive)

$$V = \frac{X_c}{j} I$$

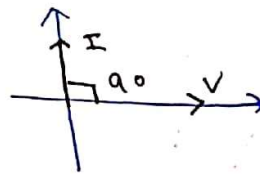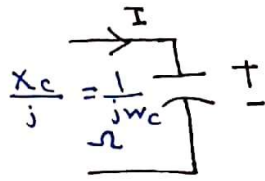


⊗ I lead V
By 90
(capicitive)

Average (mean) value and Root mean Value Square :-

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt$$
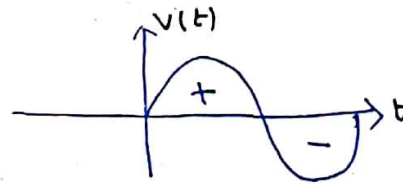
$$= \frac{1}{T} \int_0^T V_m \cos(\omega t) dt = 0$$



$$V_{avg}^2 = \frac{1}{T} \int_0^T V_m^2 \cos^2(\omega t) dt$$

$$= \frac{1}{T} \int_0^T \left(\frac{V_m^2}{2} + \frac{V_m^2}{2} \cos(2\omega t) \right) dt$$

$$V_{avg}^2 = \frac{T V_m^2}{2T} \Rightarrow V_{rms} = \sqrt{V_{avg}^2} = \frac{V_m}{\sqrt{2}}$$

DC Value
Rms Value

As we see the avg of sinusoid is zero effective value
and the avg power is proportional to avg voltage square ($P = \frac{V^2}{R}$) then the Rms is useful

⊗ The Rms gives the DC Value

2.2 Power is The rate of change of energy respect to time. $P = \frac{dE}{dt}$ $\frac{\text{joule}}{\text{sec}} \equiv \text{Watt}$

⊗ Purely Resistive load (I(t) in phase with V(t))

The instan. power absorbed by the resistor has an (avg value) = (RMS) and AC term with zero avg

$$\begin{aligned} P_R(t) &= v(t) i(t) = V_{\max} \cos(\omega t + \phi) I_{\max} \cos(\omega t + \phi) \\ &= V_{\max} I_{\max} \cos^2(\omega t + \phi) \\ &= \frac{V_{\max} I_{\max}}{2} + \frac{V_{\max} I_{\max}}{2} \cos(2\omega t + 2\phi) \end{aligned}$$

$$\frac{V^2}{R} \leftarrow P_R = \underbrace{V_{\text{rms}} I_{\text{rms}}}_{\leftarrow} + V_{\text{rms}} I_{\text{rms}} \cos(2\omega t + 2\phi) \quad (W)$$

⊗ Purely Inductive load (I lag V by 90)

The instan power absorbed by inductor is a double freq sinusoid without any avg value ~~(RMS)~~ for inductor

$$\begin{aligned} P_L(t) &= V_{\max} \cos(\omega t + \phi) I_{\max} \cos(\omega t + (\phi - 90^\circ)) \\ &= \underbrace{+}_{\oplus} V I_L \sin(2\omega t + \phi) \quad , I_L = I_{\text{rms}} \sin(\phi - (\phi - 90)) = I_{\text{rms}} \xrightarrow{\text{pure}} \end{aligned}$$

$$\otimes \cos(\theta - 90) = \sin(\theta)$$

$$\sin(\theta + 90) = \cos(\theta)$$

$$\cos(\theta + 90) = -\sin(\theta)$$

$$\sin(\theta - 90) = -\cos(\theta)$$

$$\otimes \sin(\theta \pm 180) = -\sin(\theta)$$

$$\otimes \cos(\theta \pm 180) = -\cos(\theta)$$

⊗ Purely Capacitive load (I leads V by 90)

Same as inductor

$$P_C(t) = v(t) i(t)$$

$$= \ominus V I_C \sin(2\omega t + 2\phi) \quad , I_C = I_{\text{rms}} \sin(\phi - (\phi + 90)) = -I_{\text{rms}} \xrightarrow{\text{pure}}$$

⊗ For general load

$$P(t) = v(t) i(t)$$

$$= V_{\max} \cos(\omega t + \delta) I_{\max} \cos(\omega t + \beta)$$

$$= \frac{V_{\text{rms}} I_{\text{rms}}}{2} [\cos(\delta - \beta) + \cos(2\omega t + \delta + \beta)]$$

$$= \frac{V_{\text{rms}} I_{\text{rms}}}{2} [\cos(\delta - \beta) + \cos(\underbrace{2\omega t + \delta + \delta}_{A} - \underbrace{(\delta - \beta)}_B)]$$

$$= V_{\text{rms}} I_{\text{rms}} [\cos(\delta - \beta) + \cos(2\omega t + 2\delta) \cos(\delta - \beta) + \sin(2\omega t + 2\delta) \sin(\delta - \beta)]$$

$$= \underbrace{VI \cos(\delta - \beta)}_{\text{instantaneous power absorbed by resistor}} + \underbrace{VI \cos(2\omega t + 2\delta) \cos(\delta - \beta) + VI \sin(\delta - \beta) \sin(2\omega t + 2\delta)}_{\text{instantaneous power absorbed by reactive load}}$$

⊗ $\cos A \cos B = \frac{1}{2} (\cos(A+B) + \cos(A-B))$

⊗ $\cos(A+B) = \cos A \cos B - \sin A \sin B$

~~instantaneous power~~
instantaneous power absorbed by resistor

instantaneous power absorbed by reactive load

* AVG power/Real power/active power in the load is just in the resistor equal $\rightarrow P = VI \cos(\delta - \beta)$

$$= \frac{V_m I_m}{2} \cos(\delta - \beta) = V I \cos(\delta - \beta) = \frac{V^2}{R} W$$

* Reactive Power is the Amplitude of double freq power of reactive load $\Rightarrow Q = VI \sin(\delta - \beta)$ Volt Amper Reactive (Var)

⊗ $\cos(\delta - \beta) \rightarrow$ Power Factor



Power factor lagging: inductive load ($\beta < \delta$) I lag V (تأخر)

Power factor leading: capacitive load ($\beta > \delta$) I lead V (تقدم)

Unity power factor: Resistive load ($\beta = \delta$) I in phase V (متساوية)

P is: Total energy absorbed by load during time



Q is: max value of instan power absorbed by reactive component

⊗ Complex power :-


$$\begin{aligned}
 S &= VI^* = V_{rms} I_{rms} \angle \delta - \beta \\
 &= V_{rms} I_{rms} e^{j(\delta - \beta)} \\
 &= \underbrace{V_{rms} I_{rms} \cos(\delta - \beta)}_P + j \underbrace{V_{rms} I_{rms} \sin(\delta - \beta)}_Q \\
 &= P + jQ
 \end{aligned}$$

|S| is apparent power

$$\begin{aligned}
 |S| &= V_{rms} I_{rms} \\
 &= \frac{P}{PF} \\
 &= \sqrt{Q^2 + P^2}
 \end{aligned}$$

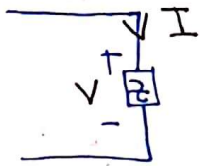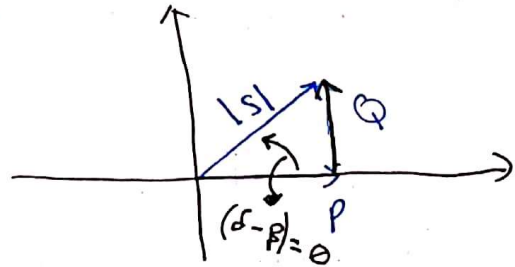

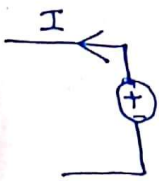- ⊗ P +ve → absorbed real power
- P -ve → delivered real power
- Q +ve → absorbed ~~reactive~~ reactive power
- Q -ve → Delivered reactive power




- P +ve → Delivered real power
- P -ve → absorbed // //
- Q +ve → Delivered react power
- Q -ve → react power is absorbed

$S_R = \frac{V^2}{R}$ $P_R = \frac{V^2}{R}$ W $Q_R = 0$ Absorbed

$S_L = \frac{jV^2}{X_L}$ $P_L = 0$ $Q_L = \frac{V^2}{X_L}$ Absorbed

$S_C = \frac{-jV^2}{X_C}$ $P_C = 0$ $Q_C = \frac{V^2}{X_C}$ Delivered

Ex 2.3 source delivers 100 kW, $P_f = 0.8$ lagging

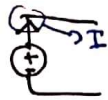⊗ Delivers → 

⊗ $P = 100 \text{ kW} \rightarrow$ absorbed by resistor

⊗ $P_f = 0.8$ lagging → inductive

السور يكمل أو لا يكمل
دائماً تتجمع

$$Q = Q_L + Q_C = Q_L + 0 = Q_L \rightarrow \text{قبل إضافة Cap}$$

$$Q = Q_L + Q_C + Q_R = Q_L + Q_C \rightarrow \text{بعد إضافة Cap}$$

$$P = P_R \begin{cases} \rightarrow \text{قبل إضافة} \\ \rightarrow \text{بعد إضافة} \end{cases}$$

So To find $Q(\text{after}) = Q_L + Q_C$

you need to find $Q_L = Q(\text{before})$

$$Q_L = V I \sin(\delta - \beta)$$

$$(\delta - \beta) = \cos^{-1}(0.8) = 36.8$$

$$\sin(\delta - \beta) = 0.6 \quad I = \frac{P}{V \cos(\delta - \beta)}$$

$$Q_L = \frac{P \sin(\delta - \beta)}{\cos(\delta - \beta)}$$

أكد بعد إضافة ربح تتغير زاوية التيار فأنت تاني P_f جديدة

$$(\delta - \beta) = \cos^{-1}(0.95) = 18.19$$

$$I = \frac{P}{V \cos(\delta - \beta)}$$

$$Q_{\text{tot}} = V I \sin(\delta - \beta) = P \tan(\delta - \beta)$$

ملاحظة بعد المثال

$$Q_{\text{tot}} = Q_L + Q_C$$

$$Q_C = Q_{\text{tot}} - Q_L$$

2.5

3 phase circuit give more power at the same amperrage

2 connections $\left\{ \begin{array}{l} \rightarrow Y \text{ connection} \rightarrow 4 \text{ wires} \\ \rightarrow \Delta \text{ connection} \rightarrow 3 \text{ wires} \end{array} \right.$

Balanced connections :

* Balanced Source (Y or Δ) *
 mean : For Y

The phase Voltages
 Same magnitude and 120°
 Phase difference +ve seq



$V_{an} = V_p \angle 0^\circ$ lead

$V_{bn} = V_p \angle -120^\circ$ lead

$V_{cn} = V_p \angle -240^\circ = V_p \angle +120^\circ$

$I_n = I_a + I_b + I_c = 0$

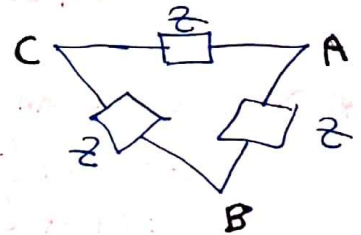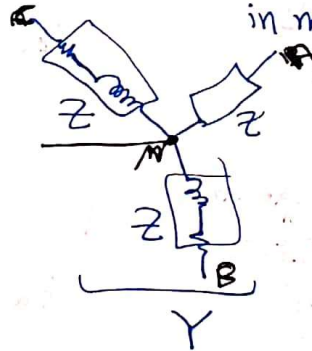* Balanced load (Y or Δ) *
 mean : all loads
 identical
 in mag and phase




and -ve seq if

$V_{an} = V_p \angle 0$

$V_{bn} = V_p \angle -240^\circ = V_p \angle +120^\circ$ lead


$V_{cn} = V_p \angle -120^\circ$ lead

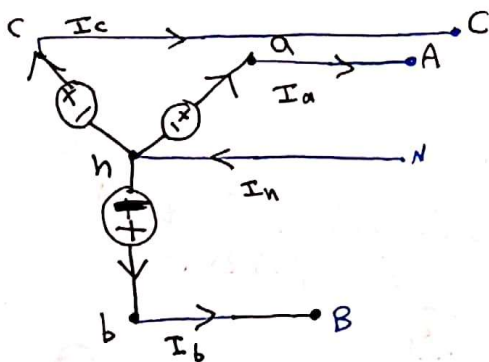

and $V_{an} + V_{bn} + V_{cn} = 0$


and $V_{AB} + V_{BC} + V_{CA} = 0$

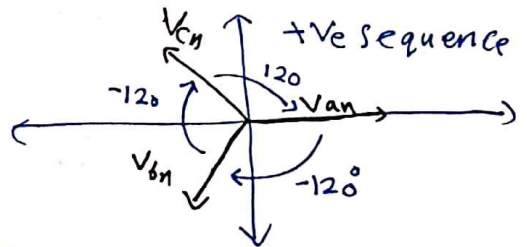The line to neutral
 called phase voltages
 V_{an}, V_{bn}, V_{cn}



- ⊗ V_{an} lead V_{bn} by 120°
- ⊗ V_{an} lead V_{cn} by 240°
- ⊗ V_{bn} lag V_{cn} by 120°
- ⊗ V_{bn} lag V_{cn} by 120°

(ABC)

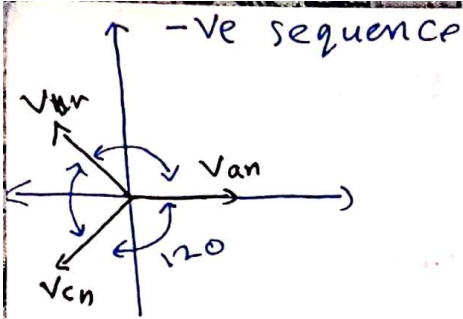

Van leads Vcn by 120
 Van leads Vbn by 240
 Vcn leads Vbn by 120

ACB

Line Voltages → line to line (+ve seq) Vab leads Vbc leads Vca by (20, 120)

$$\textcircled{\otimes} V_{ab} = V_{an} - V_{bn} \quad (V_{ab} \text{ leads } V_{an} \text{ by } 30)$$

$$= \sqrt{3} V_p \angle 30 \quad V_{ab} = \sqrt{3} V_{an} \angle 30$$



$$\textcircled{\otimes} V_{bc} = V_{bn} - V_{cn} = \quad (V_{bc} \text{ leads } V_{bn} \text{ by } 30)$$

$$= \sqrt{3} V_p \angle 30 - 120 \quad V_{bc} = \sqrt{3} V_{bn} \angle 30$$


$$= \sqrt{3} V_p \angle -90$$

$$\textcircled{\otimes} V_{ca} = V_{cn} - V_{an} \quad (V_{ca} \text{ leads } V_{cn} \text{ by } 30)$$


$$= \sqrt{3} V_p \angle -90 - 120 \quad V_{ca} = \sqrt{3} V_{cn} \angle 30$$

$$= \sqrt{3} V_p \angle -210$$


$$= \sqrt{3} V_p \angle 150$$

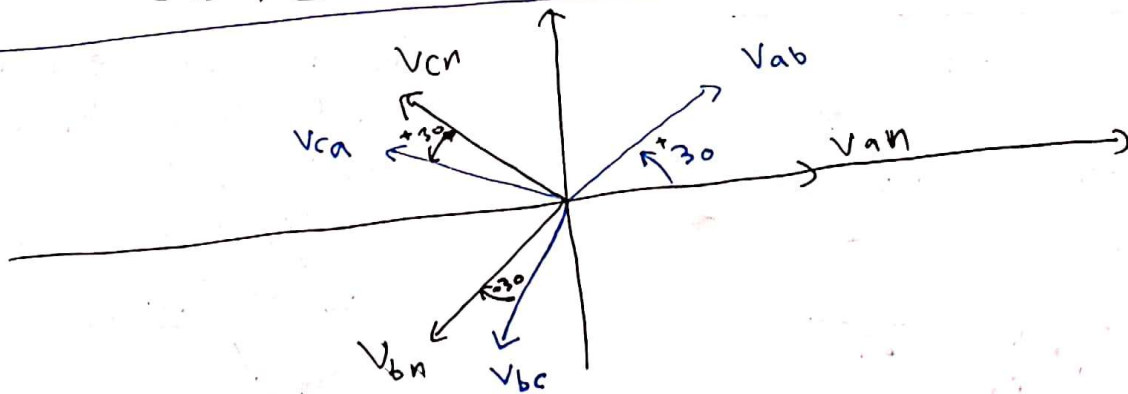

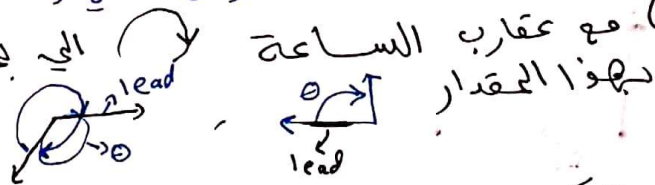الخريطة متحد فيها lead و lag في راحة (phaser)
 ① مع عقارب الساعة إلى يمينه أول هو lead إلى يمينه أول هو lag




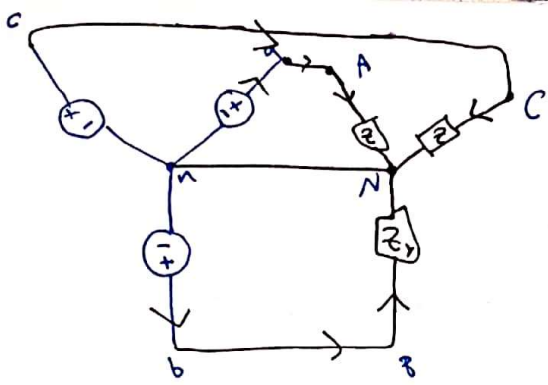② عكس عقارب الساعة إلى يمينه أول هو lag إلى يمينه أول هو lead
 بهذا المقدار بهذا المقدار




Y - Y

The per phase is (line to neutral)

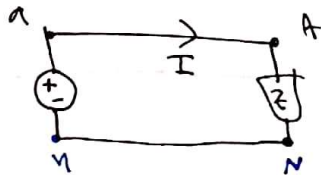

$$I_a = \frac{V_{an}}{Z}$$

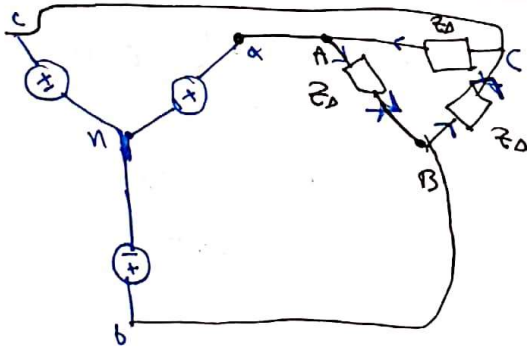

Y - Δ

$$V_{\Delta CA} = V_{Y CA}, \quad V_{\Delta BC} = V_{Y BC}, \quad V_{\Delta AB} = V_{Y AB}$$

$$I_{AB} = \frac{V_{\Delta AB}}{Z_{\Delta}} = \frac{V_{Y AB}}{Z_{\Delta}} = \frac{\sqrt{3} V_{an} \angle 30^\circ}{Z_{\Delta}}$$

$$I_{BC} = \frac{\sqrt{3} V_{bn} \angle -90^\circ}{Z_{\Delta}}$$

$$I_{CA} = \frac{\sqrt{3} V_{cn} \angle 150^\circ}{Z_{\Delta}}$$


phase currents

$$I_a = \sqrt{3} I_{AB} \angle -30^\circ \text{ lag}$$

↙ scale

at 90° w.r. to line current

if convert ~~Δ~~ Δ to Y then

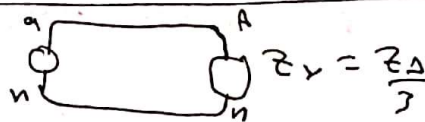

$$I_a = I_A = \frac{V_{an}}{Z_Y} = \frac{V_{AB} \angle -30^\circ}{\sqrt{3} Z_Y}$$

$$V_{an} = \frac{V_{AB} \angle -30^\circ}{\sqrt{3}}$$

Balanced Y currents :-

Phase current = line current

$$I_{an} = I_{aA} \quad I_n = I_{an} + I_{bn} + I_{cn} = 0$$

$I_{bn} = I_{bB}$ and the phase difference at voltage ϕ

$$I_{cn} = I_{cC} \quad * I_{an} = I_a = I \angle 0$$


$$* I_b = I \angle 0 - 120^\circ$$

$$* I_c = I \angle 0 - 240^\circ$$

For Δ :-

Same as Y the sum of line voltages or phase voltages and the sum of line/phase current equal zero.

⊗ Phase Voltage = ~~line~~ line voltage

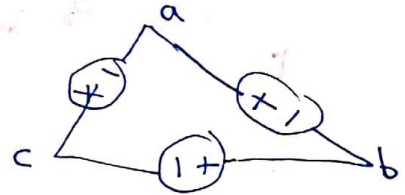

$$V_{ab} = V_p \angle 0$$

$$V_{bc} = V_p \angle -120^\circ$$

$$V_{ca} = V_p \angle +120^\circ$$


line current ~~leads~~ ^{lags} phase current by 30° and a factor $= \frac{1}{\sqrt{3}}$

⊗ Balanced Does not mean that the lines lossless, (without Z)

⊗ To analyze 3 Phase ^{Balanced} System you need to solve it per phase (single phase with singelood) then KVL

if $\Delta - \Delta \rightarrow$ no problems

if $Y - Y \rightarrow$ no problems

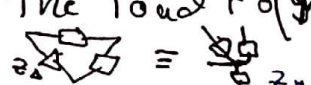if $Y - \Delta \rightarrow$ then convert the load to (Y)
By $Z_y = \frac{Z_\Delta}{3}$ 

* Power in 3 phase Balanced circuits :-

Power in general is Voltage (times) current

Power in general is always Sum

instant
Power in each phase given by

$$P_a(t) = V_{an}(t) i_a(t), \quad P_b(t) = V_{bn}(t) i_b(t), \quad P_c(t) = V_{cn}(t) i_c(t)$$

$$P_{3\phi}(t) = P_a(t) + P_b(t) + P_c(t)$$

$$= 3 V_{\phi} I_{\phi} \cos(\delta - \beta)$$

$$= \sqrt{3} V_{LL} I_{\phi} \cos(\delta - \beta) \text{ (W)}$$

total instantaneous power
Delivered by 3- ϕ Balanced
Condition and constant

دائماً فرقة بین
زاویہ تیار و جہد
ہوتے وہ ما غنشیور
نہ

IF Y
 $V_{\phi} = \frac{V_L}{\sqrt{3}}, \quad 3V_{\phi} = \sqrt{3} V_L$
 $I_{\phi} = I_L$

IF Δ
 $V_{\phi} = V_L$
 $I_{\phi} = \frac{I_L}{\sqrt{3}} \quad 3I_{\phi} = \sqrt{3} I_L$

$$S_{3\phi} = S_a + S_b + S_c$$

$$= 3 V_{Ln} I_L \cos(\delta - \beta) + j 3 V_{Ln} I_L \sin(\delta - \beta)$$

$$= P_{3\phi} + j Q_{3\phi} = 3 V_{Ln} I_L \angle (\delta - \beta)$$

$$|S_{3\phi}| = \sqrt{3} V_{LL} I_L \text{ (VA)}$$

$$= 3 V_{Ln} I_L \text{ (VA)}$$

④ حیت آنہ
دائماً فرقة بین
زاویہ تیار و جہد
ہوتے وہ ما غنشیور
نہ

in 3- ϕ motor the current enter the phase then is absorbed and same equations.

④ And equation of power identical for Δ -loads, Y-loads

Ex 2.5 - 3- ϕ Balanced Source with $V_p = 4160$ V

- two 3- ϕ Balanced motor parallel

First motor :- $P = 400$ kW $P_f = 0.8$ lagging

Second motor :- $S = 150$ kVA $P_f = 0.9$ leading

lagging \rightarrow absorbed (Q) $\rightsquigarrow +ve$

leading \rightarrow delivered (Q) $\rightsquigarrow -ve$

induction motor \rightarrow

$$P = 400 \text{ kW}$$

$$|S| = \frac{P}{P_f} = \frac{400}{0.8} = 500 \text{ kVA}$$

$$Q = \sqrt{S^2 - P^2} = 300 \text{ kVar} \quad \text{absorbed}$$

synchronous motor \rightarrow

$$|S| = 150 \text{ kVA}$$

$$P = |S| \cdot P_f = 135 \text{ kW}$$

$$Q = \sqrt{S^2 - P^2} = 65.4 \text{ kVar} \quad \text{Delivered}$$

$$= -65.4 \text{ kVar}$$

Compound motor \rightarrow total Power in each of \rightarrow induction
 \rightarrow synch


$$P_{com} = P_i + P_{syn} = 535 \text{ kW}$$

$$S_{com} = S_i + S_{syn} \Rightarrow \underline{\underline{S_{in}}}$$

$$Q_{com} = Q_i + Q_{syn}$$

$$= 300 + (-65.4) = \del{504.2} \text{ kVA}$$

$$= 234.6 \text{ kVar absorbed}$$

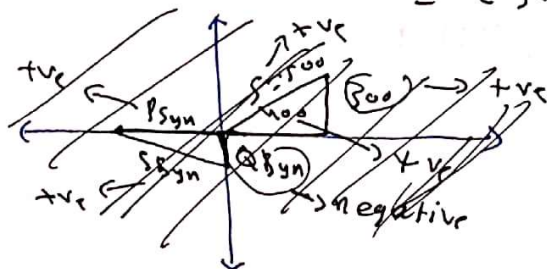


note:-

(+) absorbed + absorbed = absorbed

(-) Delivered + Delivered = Delivered

But
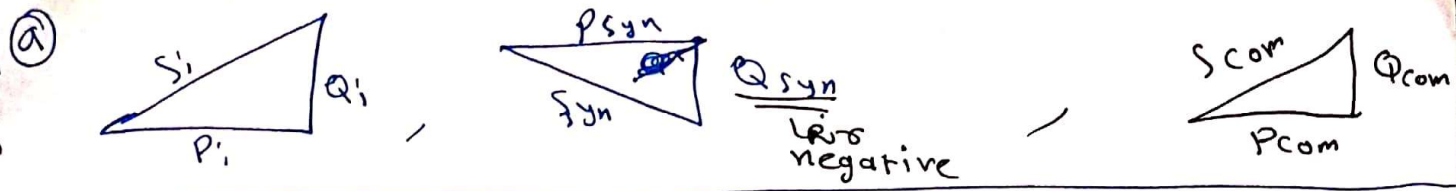
$$\text{absorbed} + \text{Delivered} = \dots$$



② $P_f = \frac{P}{S} = 0.916$ lagging

③ $S_{3\phi} = 3 I_{\phi} V_{\phi}$
 $= \sqrt{3} I_L V_L$

→ $\begin{matrix} 419 \\ 50 \end{matrix}$ $\cos^{-1} 0$

$I_L = \frac{S_{3\phi}}{\sqrt{3} V_L} = \frac{584.7}{(\sqrt{3})(4160)} = I_{\phi} = 81.4 \text{ A}$

④ Power factor unity mean → ~~$\cos 90^\circ = 0$~~
 ~~$\sin 90^\circ = 1$~~
No reactive power

then $Q_{new} = Q_{com} + Q_{add} = 0$

$Q_{add} = Q_{com}$ → if this absorbed then Q_{add} delivered
 لا تلتزم بالمتغير

⑤ $Q_{com} = 234.6 \text{ kVar}$ absorbed
 $Q_{add} = 3 \frac{V^2}{X_c} \Rightarrow X_c = \frac{3V^2}{Q_{com}}$

~~$X_c = \frac{Q_{com}}{3}$~~
 $= 221.3 \Omega$

⑥ line current ~~سأنا~~ Q_{com} $\cos^{-1} 0$ L_d

$P_{3\phi} = 3 I_{\phi} V_{\phi} P_f = 5 P_f$


$S = \sqrt{P^2 + Q^2} = \sqrt{P^2} = P$

$= \sqrt{3} I_L V_{\phi} P_f = 5 P_f$


$I_L = \frac{5 P_f}{\sqrt{3} V_{\phi}} = \frac{P}{\sqrt{3} V_{\phi}} = 74.3 = I_{\phi}$

CH-5 Transmission lines خطوط النقل

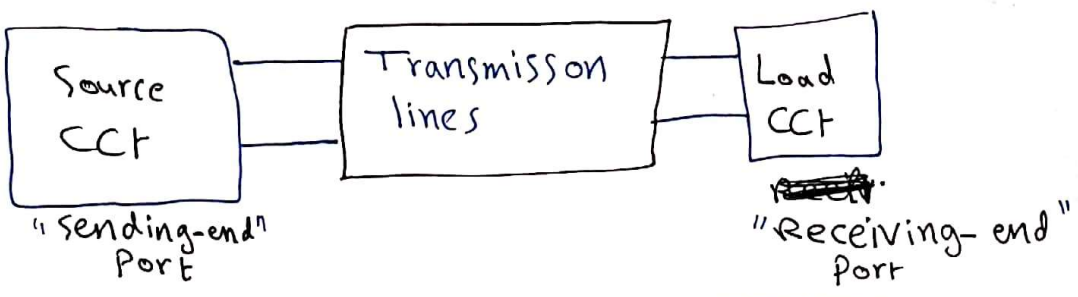- بشكل أساسي يوجد لمريقتين للثبات
- ① بث لاسلكي (wireless) ويكون بالعادة لمجموعة واسعة من الأشكال والنقل بالهواء (free space) ويسمى (unguided)
 - ② بث عن طريق الأسلاك (Transmission Lines) ويجعل على نقل الطاقة من المصدر للـ Load (Guided) "بين نقطتين" من سورس إلى لود



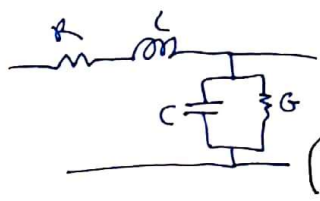لحق يسهل تحليل النظام وحل معادلاته عليه فلازم نعمل (circuit model)
 الـ Transmission lines يتكون من الأسلاك من موصلين بينهم مادة عازلة وتكون من 2 terminals




- ⊗ الموصل له مقاومة R وإذا كان فوهده مثالي $0 = R$
- ⊗ ويوجد تأثير متناهي ~~في~~ هناك (L)
- ⊗ وسبب وجود مادة عازلة بين موصلين ← يوجد (C)
- ⊗ ومادة عازله لها موصلية G وإذا مثالية $0 = G$
- ⊗ بعد تقطيعه في دائرة منقهر نعمل KVL و KCL



⊗ Two Port network

Port : فنقطة : pair of terminals which current enter network and leave from other terminal

Ex: one port network

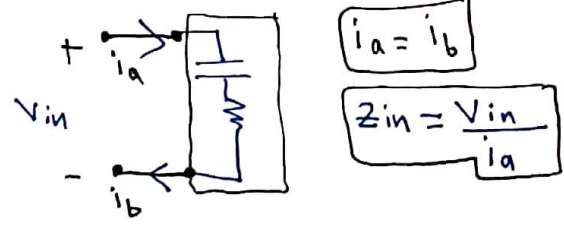

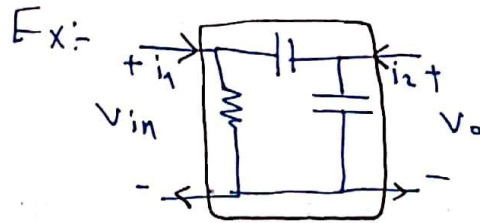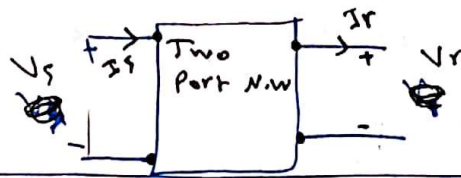* Two Port network :- $\left\{ \begin{array}{l} \text{one pair of input (source} \rightarrow 2 \text{ terminals)} \\ \text{one pair of output (load} \rightarrow 2 \text{ terminals)} \end{array} \right.$



حتى نتحكم بالسيستم (م تعد معادلة بين V_s و V_r و I_s و I_r و اعراف هو تأثير ائنت على اوتنت

⊗ One of the methods to represent relation between input and output is (ABCD) Parameters

السور ائنت لور اوتنت

$$\begin{cases} V_1 = AV_2 + BI_2 \\ I_1 = CV_2 + DI_2 \end{cases}$$

⊗ in matrix Form :

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

⊗ ABCD, Depends on Transmission-lines parameters (R, L, C, G)

⊗ A, D \rightarrow constant (Dimensionless بدون وحدة)

⊗ B \rightarrow ohm

⊗ C \rightarrow (ohm) $^{-1}$ = Simens


⊗ AD - BC = 1


To calculate A, B, C, D

- ① output \rightarrow O.C \rightarrow $i_r = 0$, $A = \frac{V_1}{V_2}$, $C = \frac{I_1}{V_2}$ (ohm $^{-1}$)
- ② output \rightarrow S.C \rightarrow $V_r = 0$, $D = \frac{I_1}{I_2}$, $B = \frac{V_1}{I_2}$ (ohm)
- ③ input \rightarrow S.C \rightarrow $V_s = 0$, $A = \frac{I_2}{I_1}$, $B = \frac{V_2}{I_1}$ (ohm)
out put \rightarrow Source

* Transmission lines models :- (Approximations) *

if T.L length less than 25 Km and 60-Hz

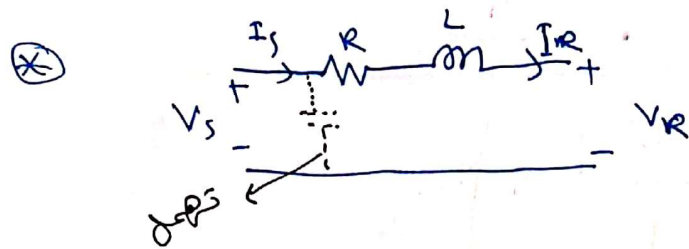Capacitor \parallel ~~inductor~~ , Short T.L \leftarrow 



(*) KVL $\rightarrow V_s = -V_R + I_s Z$, $I_s = I_R$

KCL $\rightarrow I_s = I_R + 0$

Compared to ABCD equation

(*) $A = 1$ (*) $B = Z$ (*) $C = 0$ (*) $D = 1$

OR ~~Output O.C $\rightarrow A = \frac{V_1}{V_2} = \frac{V_s}{V_R} = 1$~~

(*) $V_s = A V_R + B I_R$

(*) $I_s = C V_R + D I_R$

if output O.C $\rightarrow I_R = 0$, $I_s = 0$, $V_R = V_s$

$A = \frac{V_s}{V_R} = 1$, $C = \frac{I_s}{V_R} = 0$

if output S.C $\rightarrow I_R = I_s$, $V_R = 0$

$D = \frac{I_1}{I_2} = 1$, $B = \frac{V_1}{I_2} = Z$

if input S.C $\rightarrow A = \frac{I_2}{I_1} = 1$, $B = \frac{V_2}{I_1} = Z$


IN matrix form

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

* The transmission line have 2 important elements:-

1- series impedance $z = R + j\omega L \quad \Omega/m$

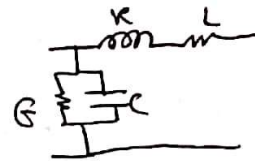2- shunt Admittance $y = G + j\omega C \quad S/m$




* For Transmission lines to overhead 60-Hz
(6) حل

⊗ إذا حول ال T.L من (25 - 250) كم إلى تردد 60 Hz $\frac{60}{50}$ بسعة T.L Lines

ولا نهمل تأثير (Shunt Admittance) و يقسم إلى قسمين $y = \left(\frac{y}{2} + \frac{y}{2}\right)$ جزء بداية

السيركية و جزء نهاية السيركية

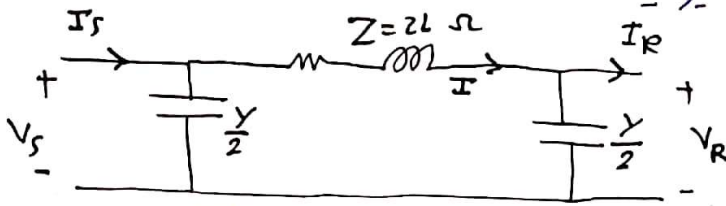

T.L medium model
Normal π model

Recall: For any impedance $Z \quad V = IZ \quad , \quad I = \frac{V}{Z}$

For any Admittance $Y \quad V = \frac{I}{Y} \quad , \quad I = VY$

⊗ method 1 to solve ABCD:-

KVL:- $V_s = IZ + V_R$

to find I:-

$$I = I_R + I_1$$

$$= I_R + V_R \left(\frac{Y}{2}\right)$$


then

$$V_s = I_R Z + V_R \frac{YZ}{2} + V_R$$

$$= V_R \left(1 + \frac{YZ}{2}\right) + I_R Z$$

$$\therefore A = 1 + \frac{YZ}{2}$$

$$\therefore B = Z \quad \Omega$$

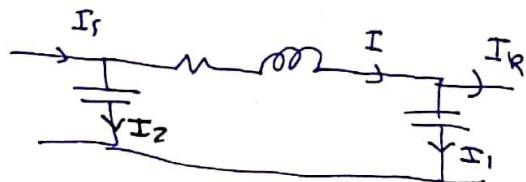

$$* \text{ and } I_s = I_1 + I_2$$

$$= I_1 + I_R + I_2$$

$$* I_s = \frac{V_R Y}{2} + I_R + \frac{V_s Y}{2}, \quad V_s = \left(1 + \frac{YZ}{2}\right) V_R + Z I_R \quad *$$

$$I_s = \frac{V_R Y}{2} + I_R + \left(\left(1 + \frac{YZ}{2}\right) V_R + Z I_R \right) \frac{Y}{2}$$

$$= \frac{V_R Y}{2} + I_R + \frac{Y V_R}{2} \left(1 + \frac{YZ}{2}\right) + \frac{YZ}{2} I_R$$

$$= V_R \frac{Y}{2} + \frac{Y V_R}{2} \left(1 + \frac{YZ}{2}\right) + \left(\frac{YZ}{2} + 1\right) I_R$$

$$= V_R Y (0.5 + 0.5 + 0.25 YZ)$$

$$= Y V_R \left(1 + \frac{YZ}{4}\right) + \left(1 + \frac{YZ}{2}\right) I_R$$

$$\div C = Y \left(1 + \frac{YZ}{4}\right) \quad (-2)$$

$$\div D = \left(1 + \frac{YZ}{2}\right) = A$$

method 2 :-

$$A = \frac{V_s}{V_R} \Big|_{I_R=0}$$

$$* V_s = I(Z) + I\left(\frac{Z}{Y}\right)$$


$$* V_R = \left(\frac{Z}{Y}\right) I$$

$$* \frac{V_s}{V_R} = \frac{I \left(Z + \frac{Z}{Y} \right)}{\frac{Z}{Y}}$$

$$= \frac{\left(\frac{ZY + Z}{Y} \right)}{\frac{Z}{Y}}$$

$$= \frac{ZY^2 + ZY}{ZY}$$

$$A = \left(\frac{ZY}{2} + 1 \right)$$

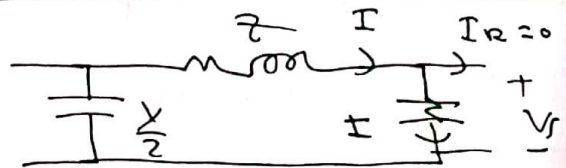

Voltage Regulation

* طريقة لحساب التغير في فولتية (Receiving end) V_R عند (load) نسبة
قبل احماله load و بعد احماله load مع العلم ان V_S ثابتة
 V_{RNL} V_{RFL}

Note at No load $I_R = 0$

$$A V_{RNL} = V_S$$

$$V_{RNL} = \frac{V_S}{A}$$

$$\text{Percent } V_R = \frac{|V_{RNL}| - |V_{RFL}|}{|V_{RFL}|} 100\%$$

التغير من (no load) \rightarrow full load بدون مع بور فاكور معينة

* $|V_{RNL}| > |V_{RFL}| \Rightarrow V_R\% \text{ +ve} \rightarrow$ lagging power factor

* $|V_{RNL}| < |V_{RFL}| \Rightarrow V_R\% \text{ -ve} \rightarrow$ leading load pf

* $|V_{RNL}| = |V_{RFL}| \Rightarrow V_R\% = 0 \rightarrow$ unity power factor (?)

⊛ T.L Voltages decreases when heavily loaded \hat{dies}

⊛ T.L Voltages increases when lightly loaded \hat{dies}

5.1 Three-phase, 60 Hz, 345 kV, 200 km medium

$$z = 0.032 + j0.35 \frac{\Omega}{\text{km}}$$

$$y = j4.2 \times 10^{-6} \frac{\text{S}}{\text{km}}$$

at full load at receiving end $\rightarrow P = 700 \text{ MW}$ ^{current lead (0.99)}

$P_f = 0.99$ leading

$V_R = (0.95)$ of rated
 $= (0.95) (345)$

(A) Z, Y, A, B, C, D

$$A = D = \left(1 + \frac{YZ}{2}\right) =$$

$$\otimes Z = zL = (200)(0.032 + j0.35) = 70.29 \angle 84.78^\circ \Omega$$

$$\otimes Y = yL = (200)(j4.2 \times 10^{-6}) = 8.4 \times 10^{-4} \angle 90^\circ \text{ S}$$

$$\Rightarrow A = D = 1 + 0.0295 \angle 174.78^\circ$$

$$\otimes B = Z = 70.29 \angle 84.78^\circ \Omega$$

$$\otimes C = Y \left(1 + \frac{YZ}{2}\right)$$

$$= 8.277 \times 10^{-4} \angle 90.08^\circ$$

(B) :- $V_S = AV_R + BI_R$, $V_R = (0.95)(345) = 327.8 \text{ kV}$

$$I_S = CV_R + DI_R$$

$$V_S = \dots$$

$$I_S = \dots$$

But note that 345 is line voltage to find phase voltage

$$\tilde{V}_R = \frac{327.8}{\sqrt{3}} = 189.2 \angle 0^\circ$$

$$\text{then } \tilde{I}_R = \frac{\tilde{V}_R}{1} \times \frac{2}{Y}$$

OR:-

$$P_R = 3 \tilde{I} \tilde{V} \cos(\theta)$$

$$\tilde{I}_R = \frac{700 \text{ MVA} (0.99)}{(3)(0.95)(189.2) \text{ kV}} = 1.245 \frac{\text{A}}{\text{kV}}$$

$$\Rightarrow P_S = 3 \tilde{V}_S \tilde{I}_S \cos(\theta_{V_S} - \theta_{I_S})$$

$$= \sqrt{3} V_{SLL} I_{SLL} \cos(\theta_{V_S} - \theta_{I_S})$$

$$= 730.5 \text{ MW}$$

③ Percent VR:

$$V_{RLN} = \frac{V_S}{A} = 356.3 \text{ k(V)} \rightarrow \text{line}$$

$$\text{Percent VR} = \frac{V_{KAK} - V_{KFL}}{V_{KFL}} = \frac{V_R = 0.45 \text{ (SW)}}{\text{line}}$$
$$= 8.7 \%$$

2. $\frac{1.8 \text{ kA}}{2 \times 0.9}$

e. $P_S = P_{MS} + P_R$


$$P_{MS} = 30.5 \text{ MW}$$

$$\text{Percent EFF} = \frac{P_R}{P_S} 100\% = 95.8\%$$

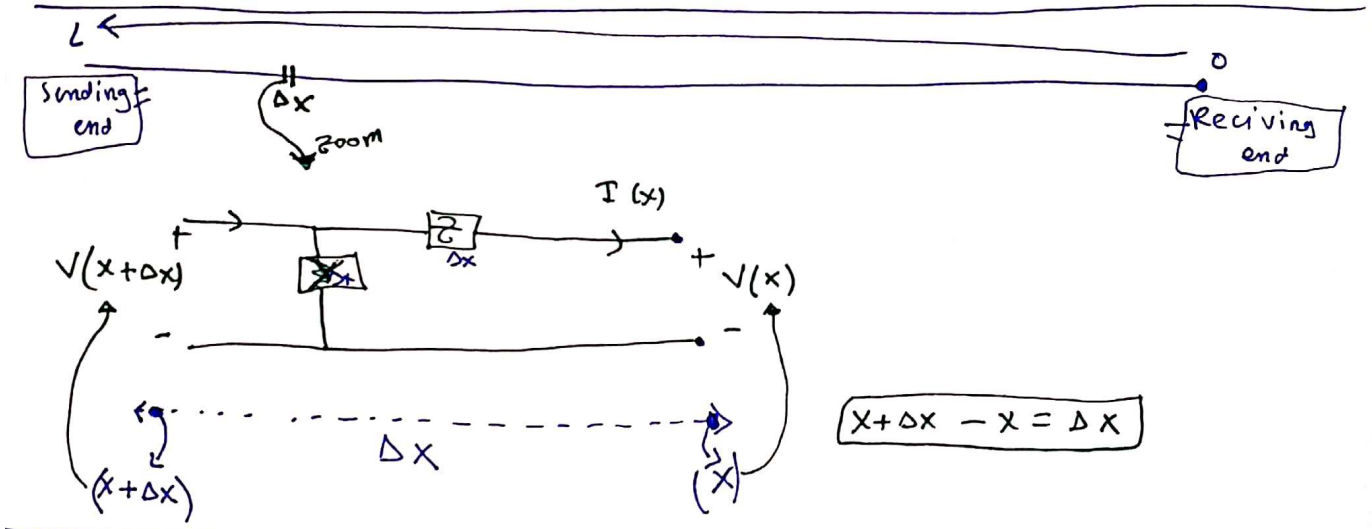5.2 بالنسبة لـ long وهو أكبر من طول medium وروح تقسم السلك
 إلى طول (L) إلى عدد لا نهائي من الأجزاء وكل جزء طول Δx
 وتؤثر Δx إلى زيور وروح نحسب الفولتيج و التيار ومن ثم نجمعهم
 ليصيرو معادلات عامة لحساب الفولتيج أو التيار عند أي نقطة
 و هيك يكون جاهز اعرف كونفولتية ال load عند مسافة (0)
 و كونفولتية ال source عند مسافة (L)

يعني ال Voltage وال Current هما function بالفيذر دومين أما تايم دومين

$\uparrow V(x, r)$
 $\downarrow \tilde{V}(r)$



KVL:-

$$V(x+\Delta x) = I(x) Z_{\Delta x} + V(x)$$

$$\textcircled{1} \frac{V(x+\Delta x) - V(x)}{\Delta x} = Z I(x) \rightarrow \Delta x \rightarrow 0$$

$$\frac{dV(x)}{dx} = \overset{s/m}{Z} I(x) \text{ --- equation (1) } \rightarrow \text{KVL}$$

$$\frac{dI(x)}{dx} = \overset{s/m}{Y} V(x) \text{ --- equation (2) } \rightarrow \text{KCL}$$

لكن بيدي أنا معادلة خاصة بكل منا
 Voltage ←
 Current ←

$$(*) \left(\frac{dV(x)}{dx} = z I(x) \right)$$

$$(*) \frac{d^2 V(x)}{dx^2} = z I'(x), \quad \frac{dI(x)}{dx} = y V(x)$$

leads to \rightarrow

$$(*) \frac{d^2 V(x)}{dx^2} - z(y V(x)) = 0 \rightarrow \text{معادلة تفاضلية تصف معدل تغير الجهد مع}$$

Solution :-

$$(*) V(x) = A_1 e^{\gamma x} + A_2 e^{-\gamma x} \text{ (Volt)}$$

⊗ $A_1, A_2 \rightarrow$ integration constant
unit :- Volt

⊗ γ : Propagation constant (ثابت الانتشار) و يعتمد على $(\sigma, \epsilon, \mu, R)$

$$\begin{aligned} \gamma &= \sqrt{zy} \text{ (m}^{-1}\text{)} \\ &= \sqrt{\frac{j\omega}{\sigma} \frac{j\omega \epsilon}{\mu}} \\ &= \sqrt{\frac{-\omega^2 \epsilon \mu}{\sigma}} \\ \gamma &= \frac{j\omega \sqrt{\epsilon \mu}}{\sigma} = \alpha + j\beta \end{aligned}$$

المسافة و اذا علينا
منكون علينا معادلة
الجهد

$$\text{and } I(x) = \frac{A_1 e^{\gamma x} - A_2 e^{-\gamma x}}{z_c} \Rightarrow \frac{z}{\gamma} = \frac{z}{\sqrt{zy}} = \frac{\sqrt{z} \sqrt{z}}{\sqrt{z} \sqrt{y}} = \frac{\sqrt{z}}{\sqrt{y}} = \sqrt{\frac{z}{y}} = z_c$$

$$\Rightarrow I(x) = B_1 e^{\gamma x} - B_2 e^{-\gamma x} \text{ - Amper}$$

$B_1, B_2 \rightarrow$ unit Amper

⊗ z_c : characteristics impedance (Ω)

و يعتمد على σ, ϵ, μ, R و وحدة أوم و وحدة كبير
و طاقة لكل trans. line و هي $\frac{A}{B_1}$

و أفضل قيمة هي 50Ω يتقبل أقل loss, أقل power

γ يجب قيمة التوازي A_1, A_2 نحتاج معادلتين وحدة من جهد و وحدة من تيار

at $x=0 \rightarrow V_R, I_R$ (Receiving end)

⊗ $V_R = V(0), I(0) = I_R$

$V(0) = V_R = A_1(1) + A_2(1) \quad \text{--- ①}$

$I(0) = I_R = \frac{A_1}{z_c} - \frac{A_2}{z_c} \quad \text{--- ②}$

$A_1 = \frac{V_R + z_c I_R}{2}, \quad A_2 = \frac{V_R - z_c I_R}{2}$

هناك مدار على مدارات جاهزة لا جهد وتيار وبصالح احوال
مسألة بين اياها وبعد السؤال :-

لكن ليس ما وصلت للمعادلة γ \leftarrow ABCD تحت اعرافهم لا long Parameter

$V(x) = A_1 e^{\gamma x} + A_2 e^{-\gamma x} = \frac{V_R e^{\gamma x} + z_c I_R e^{\gamma x}}{2} + \frac{V_R e^{-\gamma x} - z_c I_R e^{-\gamma x}}{2}$

نفس الحل ABCD equation ⊗ $V(x) = V_R \left(\frac{e^{\gamma x} + e^{-\gamma x}}{2} \right) + I_R \left(\frac{e^{\gamma x} - e^{-\gamma x}}{2} \right) z_c$

⊗ $I(x) = \frac{1}{z_c} \left(\frac{e^{\gamma x} - e^{-\gamma x}}{2} \right) V_R + I_R \left(\frac{e^{\gamma x} + e^{-\gamma x}}{2} \right)$
sinh γx cosh γx

$A(x) = \frac{e^{\gamma x} + e^{-\gamma x}}{2} = \cosh \gamma x = D(x)$

$B(x) = \sinh(\gamma x)$

$C(x) = \frac{1}{z_c} \sinh(\gamma x)$

هنا معادلات فوق فما هو؟ لها عبارة عن معادلة القولية والتيار
عند اي مسافة بدلالة تقولية وتيار load فإذا عوضنا $L = x$
صارت معادلة تقولية وتيار ~~source~~ بدلالة تقولية وتيار load

$A = \cosh \gamma L = D$	$V(L) = A V_R + B I_R$
$B = \sinh(\gamma L)$	
$C = \frac{1}{z_c} \sinh(\gamma L)$	$I(L) = C V_R + D I_R$

5.2(Ex) :-

3-phase \rightarrow Line-line 765, 60 Hz
+ve sequence

$$L = \frac{300 \text{ km}}{L_{\text{long}}}$$

$$* z = 0.0165 + j0.3306 = 0.3310 \angle 87.14 \text{ } \Omega/\text{km}$$

$$* y = j4.674 \times 10^{-6} \text{ S/km}$$

calculate ABCD :-

to find ABCD \rightarrow find (γL)

find (z_c)

$$* \gamma = \sqrt{zy} =$$

$$* z_c = \sqrt{\frac{z}{y}} = 266.1 \angle -1.43 \text{ } \Omega$$

$$* \gamma L = (300) \gamma = 0.373 \angle 88.57 \text{ } (\text{m}^{-1} \text{ m}) \rightarrow \text{per unit}$$


بدرج واحد

$$* A = \cosh \gamma L \rightarrow \text{ماتر كوشنجر}$$

ماتر كوشنجر
complex

$$\# \text{ } e^{\gamma L} = 1/\cosh \gamma L$$

5.3: Equivalent π circuit :-

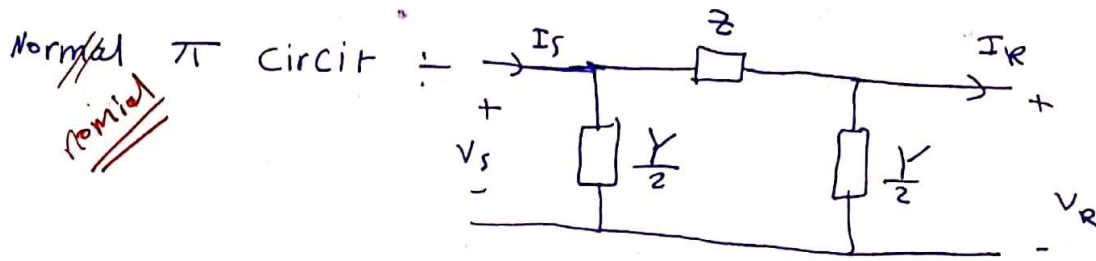

$$A = D = 1 + \frac{YZ}{2}, \quad B = Z (\Omega)$$

$$C = Y \left(1 + \frac{YZ}{4} \right) (S)$$

In equivalent π circuit: Z converted to Z'

$$\frac{Y}{2} \text{ converted to } \frac{Y'}{2}$$

Same ABCD equations


where $Z' = Z_c \sinh(\gamma l) = Z F_1 = Z \frac{\sinh(\gamma l)}{\gamma l}$

where F_1 is correction factor to convert Z from normal (π) to equivalent (π)

where $\frac{Y'}{2} = \frac{Y}{2} F_2 = \frac{Y}{2} \left(\frac{\tanh(\gamma l/2)}{(\gamma l/2)} \right) = \frac{\tanh(\gamma l/2)}{Z_c}$

and F_2 is correction factor to convert $\frac{Y}{2}$ from normal (π) to equivalent (π)

⊛ Equivalent π circuit

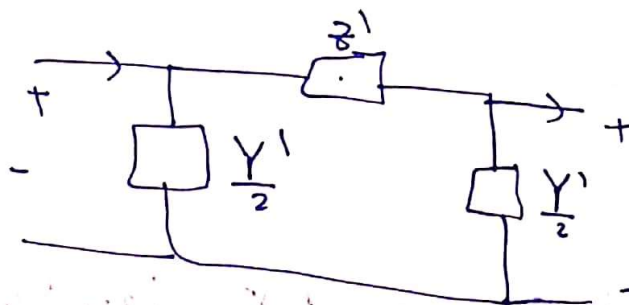

(1)

5.4 lossless lines :-

* حكمينا أنه (α) يتأثر كثير على نوع السلك لأنه يتأثر بـ (R, C, L, G) ^{غاما}
 و (α) يتكون من $(\alpha$ و $\beta)$ واحد يتأثر على Amplitude و واحد يتأثر على phase

زي ما تعرف البور تكسب من ال Amplitude
 حيث لو أرسلت (propagate بيت) فخطيب معين ب Amplitude معين
 وكان $\alpha = 0$ بالتالي رخ تفقد Amplitude مثل ما هي حتى توصل ال مستد
 و هيك فاني أي خسارة بين فرسل و مستقبل و يبقى
 " lossless transmission line "

lossless transmission line :-

* كذلك مند ما لا مهمة و Z_c مهمة لتتس السبب و اذا كانت
 real أو complex يعرف برفو

* احنا نتعرف انه البور الحقيقي تستهلك زي $(R$ و $G)$ حيث حتى
 تكفي انه ما عنا (loss) بالنسبة للأسلاك لازم تكفي انه فتر $(R$ و $G)$

lossless transmission line:

is :- perfect conductor with $R = 0$

perfect dielectric with $G = 0$

$$Z = j\omega L + (0) \quad \frac{\Omega}{m}$$

$$Y = j\omega C + (0) \quad \frac{S}{m}$$

$$Z_c = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{j\omega L}{j\omega C}} = \sqrt{\frac{L}{C}} \Omega \rightarrow \text{Pure real}$$

$$\gamma = \sqrt{ZY} = \sqrt{(j\omega L)(j\omega C)} = j\omega\sqrt{LC} \quad (m^{-1}) \rightarrow \text{pure imaginary}$$

$$\gamma = \alpha + j\beta = 0 + j\omega\sqrt{LC} \quad (m^{-1})$$

← مثل ما قلنا فوتر ما بين (α)

⊗ Z_c in lossless is called surge impedance

* ⊗ ABCD in lossless :-

* ⊗ $A(x) = D(x) = \cosh(\gamma x) = \cosh(j\beta x) = \cos(\beta x)$


$$\frac{e^{j\beta x} + e^{-j\beta x}}{2}$$

* ⊗ $B(x) = Z_c \sinh(\gamma x) = j Z_c \sin(\beta x) = j \sqrt{\frac{L}{C}} \sin(\beta x) \Omega$

$$B(x) = Z_c' = j Z_c \sin(\beta x) = j X' \Omega$$

* ⊗ $\frac{Y'}{Z'}$ in lossless :- $= \left(\frac{j\omega dD}{2} \right) S$ length

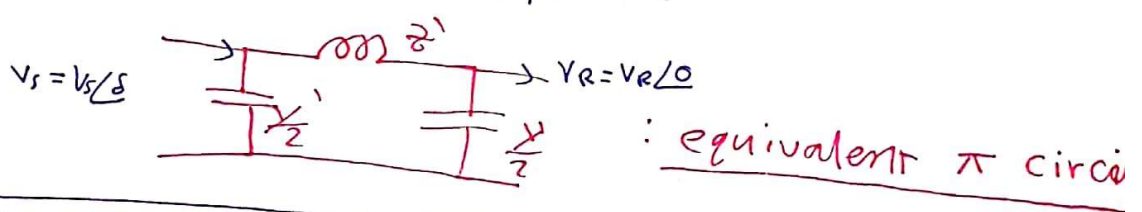Z' : Pure inductive , Y' = Pure Capacitive



* ⊗ Wave length :- (λ)


frequency :- \rightarrow هو عدد تكرار الموجة في الثانية لو اعادة مرة في ثانية * ⊗
 $f = 1 \text{ Hz}$

مربعين في ثانية $f = 2 \text{ Hz}$

* ⊗ الطول الموجي هو مسافة من بداية الموجة لنفسيتها (زي مكانك بولك تاخذ) * ⊗
 أو هو مسافة بين قاعين أو قمميين (time period)

* ⊗ مثلا طول موجي قبل ~~بسط~~ تردد يزيد ويمكن تحريكه

* ⊗ هو مسافة لازمة للموجة تغطي (2λ)

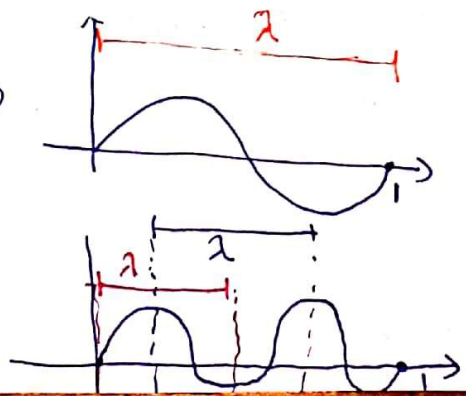

* لكن نرى شيئا مهم زحونة من شرط اذا تغير واحد منهم يتغير الثاني يعني (التردد وطول موجي) لانه في معنا عامل ثالث بانر ويتأثر فيهم
 + هو السرعة الموجية

⊗ $\lambda : m$ ~~3m~~

⊗ $f : \frac{1}{s}$

⊗ $\lambda f = \frac{(m)}{(s)} \rightarrow \underline{\underline{speed}}$

Phase velocity $\rightarrow v_p = \lambda f$

⊗ بالاسلان التردد ما يتغير لكن الأوج سرعة تتغير حسب الوسط بالفوايم سرعة تساوي سرعة الضوء (3×10^8)
 لكن اذا تغير الوسط عندها سرعة تقل بسبب وجود ~~مقاومة~~
 معوقات فلما يتغير السرعة يتأثر طول موجي علما انه التردد ما يتغير لانه مثبت


$v(x) = A(x) V_R + B(x) I_R$

$= \cos(\beta x) V_R + B(x) I_R$

when $\beta x = 2\pi$ then

then $x = \frac{2\pi}{\beta} = \lambda (m)$

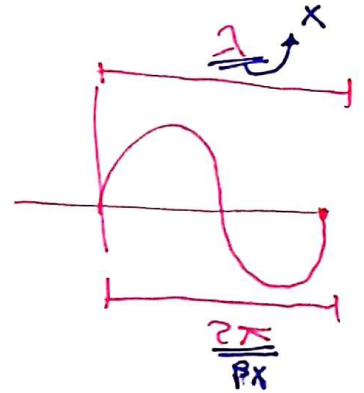(منقدر نوجد x لانها λ لانه قلنا به
 نقيمه λ فنصرونه من
 بيان موجي لانها بيتها
 2π)



⊗ $\lambda = \frac{2\pi}{\omega \sqrt{LC}} = \frac{1}{f \sqrt{LC}} m$

⊗ $v_p = f \lambda = \frac{1}{\sqrt{LC}}$ ⊗ :- velocity of propagation (phase velocity)
 سرعة الموجات (فولتية و تيار)

⊗ for overhead lines $v_p = 3 \times 10^8 \frac{m}{s}$

$\lambda \Rightarrow$ for $f = 60 Hz$ = 5000 Km = 3100 m;

* surge impedance loading (SIL)

⊗ surge impedance يعني Z_c و loading تعني (load نوعه Z_c)

بالختم سببنا load قيمته Z_c وتساوي $\sqrt{\frac{L}{C}}$

بنفس وقت احنا لس بار (lossless) كيف؟ حج درسنا تورج ياتو


⚡ البور التي رح تروح بالسلك شو رح تكون؟
 ① Q absorbed in L (series)
 ② Q generated in C (shunt)

الحالة رح يلغو بعينها وهي حالة خالية عن load مساوي Z_c

* it is also called natural load

* in Surge impedance load ÷ Voltage and Current in phase All points

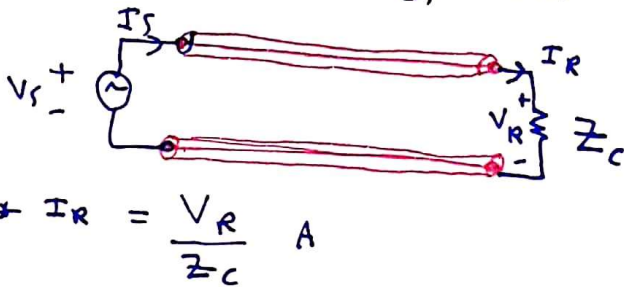* surge impedance load is the ideal load because $I(x)$ and $V(x)$ is uniform along line



⇒ lossless line terminated by resistance = $\sqrt{\frac{L}{C}} = Z_c$

* $I_R = \frac{V_R}{Z_c} A$

SIL ÷ is the power delivered by a lossless line to a load equal to surge impedance $Z_c = \sqrt{\frac{L}{C}}$

$$\begin{aligned}
 U(x) &= \cos(\beta x) V_R + j Z_c \sin(\beta x) I_R \\
 &= \cos(\beta x) V_R + j Z_c \sin(\beta x) \frac{V_R}{Z_c} \\
 &= e^{j\beta x} V_R
 \end{aligned}$$

$|V(x)| = |V_R|$ و $v \rightarrow$? value

$\Delta x = x$
 $|V(0)| = |V_R|$
 $V_s = V_R$

يعني قولية ثابتة على طول line

في حالة الخط المثالي $Z_c = Z_c$ فإن
 لا يتغير تقسيم الجهد $V_d = V_r$



at SIL
 Voltage profile
 is flat

و يسوي الجهد في الطرفين ←

and $I(x) = e^{j\beta x} \frac{V_R}{Z_c}$

$\Rightarrow |I(x)| = \frac{|V_R|}{Z_c}$

القدرة الحقيقية P هي نفسها في الطرفين \Rightarrow Power flow is real
 والقدرة التخيلية Q هي نفسها في الطرفين \Rightarrow Power flow is complex
 $Q_L = Q_c$
 $Q_L - Q_c = 0$

$$S(x) = P(x) + jQ(x) = V(x) I(x)^*$$

$$= (e^{j\beta x} V_R) \left(e^{-j\beta x} \frac{V_R}{Z_c} \right)$$

$$= \frac{|V_R|^2}{Z_c}$$

real \rightarrow $\frac{|V_R|^2}{Z_c}$ \rightarrow ωL \rightarrow ωC

The real power flow along a lossless line at SIL ($Z_L = Z_c$)
 remains constant from sending end \leftrightarrow receiving end
 and reactive power is zero

$SIL = \frac{V_{rated}^2}{Z_c}$ \rightarrow the real power delivered or SIL
 rated voltage

- ⊗ rated voltage used for single phase line
- ⊕ rated line-line used for total power three phase line

Voltage Profiles:-


هناك نوعان من الـ SIL، إما هو ideal load فالجهد العكس يراوح ويكون load سيء SIL
 يمكن يكون أكبر أو أقل سيء اعتماداً على :-

- ① line length
 - ② line compensation , during heavy load conditions
- بالتالي ما زال يكون Flat (constant) الفولتية

1. No load $\rightarrow I_R = 0$, $V_R = \frac{V_S}{A} = \frac{V_S}{\cos(\beta l)}$ $\rightarrow \gamma l < 1$
 يعني $V_S < V_R$ بالتالي الفولتية تالتهما increasing

2. at load = Z_c (SIL) $V_S = V_{R_{SIL}}$ (flat)

3. at load (S.C) $V_{R_{sc}} = 0$, I_R maximum , $V(x_{sc}) = 0 + Z_c \sin \beta x I_{R_{sc}}$

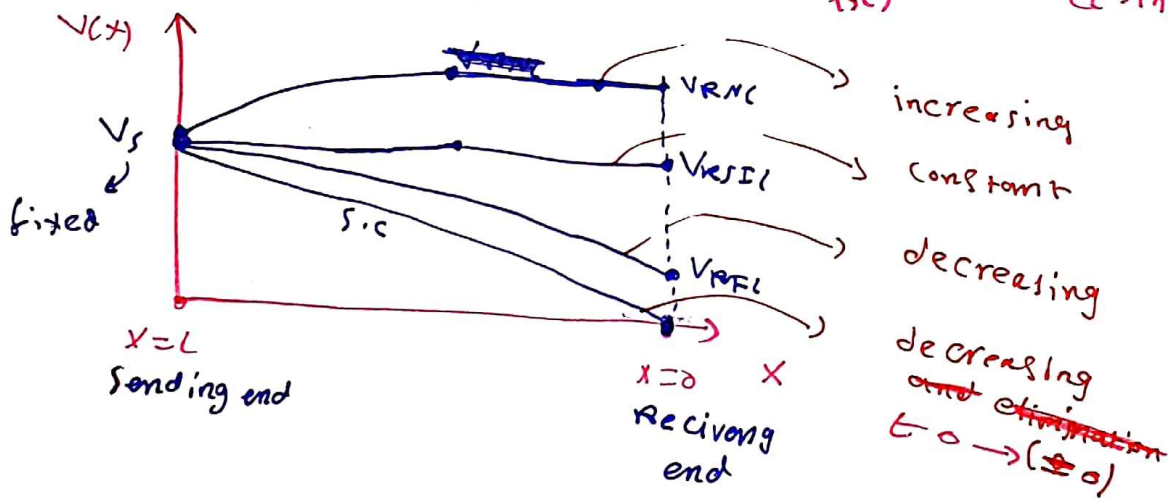


Case 3: V_S decrease to (0) at Receiving-end as (x) varied

The full load voltage depends on the specification of I_{FL} and it's above V_{sc} and less than $V_{R_{SIL}}$

⊗ مثل ما احنا شافيناه عنا فرق بين No load و Full load و V_S و V_R يعني

انه كلما زاد طول المسلك كلما بتكبر نسبة Receiving end regulation Percent (more severe) يعني

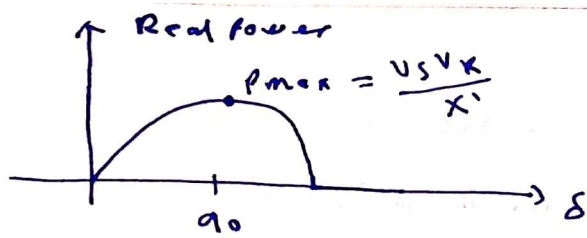والحل لها هو Compensation Methods لتقليل تقلبات (Fluctuations) الفولتية



③ Real power for lossless as δ varying


* Loadability :- is defined as the extent of load ^{مدى} can flow through line without exceeding ^{تجاوز} the limitations.

* Line loadability :- defined as Percentage of SIL

What is the limitations ? :-

- ① Thermal limit :- heating of transmission line
- ② Voltage drop limit
- ③ Steady State Stability limit

* حدود ائى load تا بصير يتجاوز الحد.

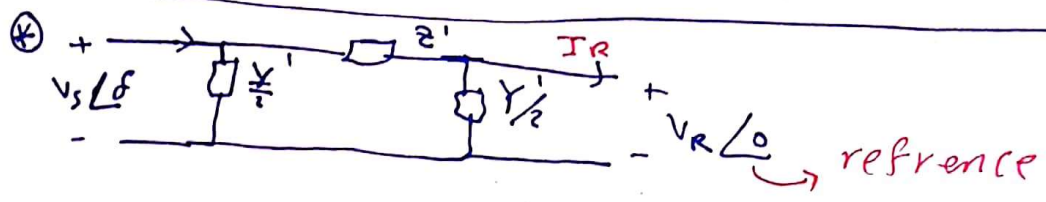

$$* I_R = \frac{V_S - V_R}{Z'} = \frac{V_R e^{j\delta} - V_R}{jX'} - \frac{j\omega C L}{2} V_R$$

$$* S = \frac{j(V_R V_S \cos \delta - V_R^2)}{X'} + \frac{V_R V_S}{X'} + \frac{j\omega C L}{2} V_R^2$$

$$* P = P_S = P_R = \text{Re}(S_R) = \frac{V_R V_S}{X'} \sin \delta$$

lossless

Note at SIL

$$\frac{V_R = V_S, \delta = 90}{P = \frac{V_R^2}{X'}}$$

For fixed V_R, V_S

$$P_{max} \Big|_{\delta=90} = \frac{V_R V_S}{X'} \Rightarrow \text{theoretical steady state stability limit of lossless line}$$

$$P_{min} = 0$$

و ا يمكن تجاوز هالقية ^{و ما عين} بتفقد ^{فزامنتها اذا اعدت}

Power max of 1-5-5 in terms of SIL

$$P = \frac{V_R V_S}{x'} \sin \delta = \frac{V_S V_R}{Z_c \sin \beta l} \sin \delta = \frac{V_S V_R}{Z_c} \frac{\sin \delta}{\sin(\frac{2\pi l}{\lambda})}$$

$$P = \frac{V_{spu} V_{rpu} (\text{SIL}) \sin \delta}{\sin(\frac{2\pi l}{\lambda})}$$

$$P_{\max} |_{\delta=90} = \frac{V_{spu} V_{rpu} (\text{SIL})}{\sin(\frac{2\pi l}{\lambda})}$$

Where V_{spu}, V_{rpu} is rated line voltages in per unit.

Two factors affecting the (S-S-S-limit)


⊛ it increases with the square of line voltage

⊛ it decreasing with line length

For $V_{spu} = 1 = V_{rpu}$, $\lambda = 5000 \text{ km}$

the theoretical steady state stability limit decrease from 4(SIL) to 2(SIL)

from 200 km to 400 km

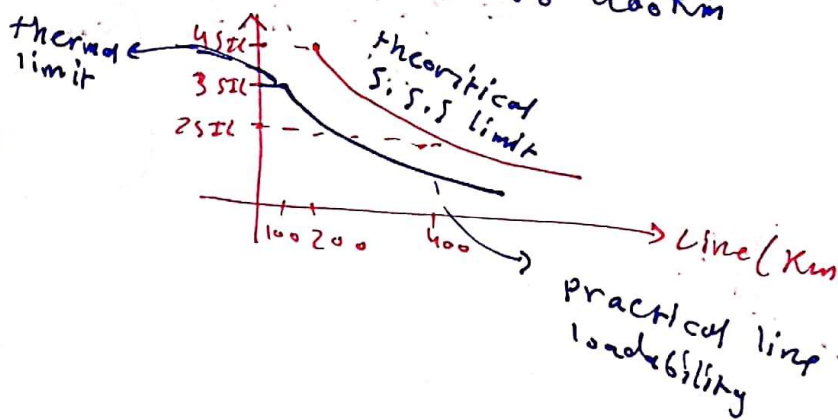

5.5 maximum Power flow \Rightarrow for lossy lines

Let $A = \cosh(\gamma l) = A \angle \theta_A$

$B = Z' = Z' \angle \theta_Z$

$V_S = V_S \angle \delta$

$V_R = V_R \angle 0$

* ~~ABC~~ \rightarrow ABCD equation $\rightarrow I_R = \frac{V_S - V_R}{A} = \frac{V_S e^{j\delta} - V_R e^{j0}}{Z' e^{j\theta_Z}}$

\otimes $S_R = V_R I_R^* = V_R \left(\dots \right)^*$

$= \frac{V_R V_S e^{j(\theta_Z - \delta)}}{Z'} - \frac{A V_R^2}{Z'} e^{j(\theta_Z - \theta_A)}$

Then $P_R = \text{Re}(S_R) = \frac{V_R V_S}{Z'} \cos(\theta_Z - \delta) - \frac{A V_R^2}{Z'} \cos(\theta_Z - \theta_A)$
 (general) \leftarrow يعتبر

$Q_R = \text{Im}(S_R) = \frac{V_R V_S}{Z'} \sin(\theta_Z - \delta) - \frac{A V_R^2}{Z'} \cos(\theta_Z - \theta_A)$

\otimes الشرط الوحيد متغيري المعادلة هو (δ) θ_Z θ_A Z' A V_R V_S Z' $\cos(\theta_Z - \delta) = 1$
 يعني $\theta_Z = \delta$ يكونا مأكس يور

general \leftarrow $P_{Rmax} = \frac{V_R V_S}{Z'} - \frac{A V_R^2}{Z'} \cos(\theta_Z - \theta_A)$
 lossless or not

in lossless $\theta_A = 0$ $\theta_Z = 90$ and $Z' = jX'$
 then equation become for lossless.

$$\textcircled{a} \text{ Percent } V_R = \frac{V_{RFL} - V_{RFL}}{V_{RFL}} \times 100\% = \frac{V_S/A - V_{RFL}}{V_{RFL}} 100\%$$

(line) → V_{RFL} جو سہو

(765) = V_S کے لیے 15

$$= \underline{\underline{12.72\%}}$$

فیصد

② The thermal limit is max rated current

From table = 1.2 kA

and for four conductors

4.8 km

$I_{RFL} < 4.8 \text{ km} \rightarrow \checkmark$ thermal limit

$\frac{V_S}{V_R} \geq 0.95 \rightarrow \checkmark$ Voltage drop limit

Percent $V_R = 12.72\%$

too much

But in 5.7 may be solution to increase loadability

5.7 ^{تعويض} RACTIVE compensation Techniques.

هي طريقة لتعويض وتخوير أداء ال system في AC وذلك في جانبين :

① Load compensation :- and objective is :-

- i) increase the power factor of the system
- ii) balance real power from the system
- iii) Compensate percent VR
- iv) Eliminate current harmonic

② Voltage support :- main purpose to decrease the Voltage fluctuation

* To improve the stability.

And Because reactive power is required to maintain the voltage to deliver Active Power

But when there is not enough reactive power the voltage get down and not possible to re deliver enough active power.

* And required to regulate the power factor of the system we need to compensate REACTIVE Power (VAR)

The methods Are :-

- * Shunt compensation. Device connected in parallel
- * series compensation, Device connected in series
- * Synchronous Condensers.
- * Static VAR Compensators.
- * Static Compensators.

① shunt compensator :- * Shunt reactors (inductor)

* Shunt capacitors

② and it's connected at selected points along EHV lines from each phase to neutral

* Shunt reactors :- absorbs reactive power and

* Reduce over voltages by consuming Q

* Reduce transient over voltages

But * it reduce line loadability if they not removed under full load

* Shunt capacitors :- Deliver reactive power and increase transmission voltages during load conditions (maintain the voltage level)

③ The series compensator can connected anywhere in the line.

2 kinds :- capacitive mode or inductive mode

* series capacitors :- (some times used on long lines to increase line loadability)

* (Reduce net series impedance of line with the capacitor banks, reduce line voltage drop

increase S.S.S. Limit, increase loadability

Disadvantage :- $\left(\frac{V}{f}\right)$ see Book (کتاب)

5: 1 ⇒ shunt inductors → shunt compensation

75% compensation

at full load it's removed

$$I_{FL} = 1.9 \text{ kA} \quad V_{FL} = 730 \text{ kV} \quad \text{PF} = 1$$

A: Find percent VR :-

$$V_{RNL} = \frac{V_S}{A} \quad A \text{ from Ex 5.2} = 0.9713 \angle 0.209^\circ$$

$$V_S = AV_{R1} + BI_R$$

$$= \overleftarrow{A} \overleftarrow{V_{RFL}} + \overleftarrow{B} \overleftarrow{I_{RFL}}$$

$$V_S = 766.0 \text{ kV}_{LL}$$

$$\oplus V_{RNL} = \frac{V_S}{A} = 822.6 \text{ kV}_{LL}$$

$$V_{RFL} = 730 \text{ kV}$$

$$VR\% = \frac{822.6 - 730}{730} \cdot 100 = 12.58\%$$

13) $\frac{Y'}{2} = \frac{3.7}{10^7} + j \frac{7.094}{10^4} \text{ S} \rightarrow$ From previous Example

$$Y' = 2 \left(\frac{3.7}{10^7} + j \frac{7.094}{10^4} \right)$$

$$= 7.4 \times 10^{-7} + j 14.188 \times 10^{-4} \text{ S}$$

with compensation → shunt

$$Y_{req} = Y' - 75\% \dot{Y} = 3.547 \times 10^{-4} \angle 89.88^\circ$$

$\frac{Y'}{2} = \frac{7.4 \times 10^{-7} + j 14.188 \times 10^{-4}}{2}$

So $Z_{eq} = Z' = 97.0 \angle 87.7^\circ$ from 5.2 because no series compensation

14) $A_{eq} = 1 + \frac{Y_{eq} Z_{eq}}{2}$ (compensator) $\oplus V_{RNL} = \frac{V_S}{A} = 779.4 \text{ kV}_{LL}$

$$= 0.98 \angle 28 \angle 0.01^\circ$$

$$\oplus VR\% = 6.77\%$$

(C) →

← $V_{RFL} \rightarrow$ same removed as 1