

Filter Sheet.

Q₁ Design a 1st order HP Filter to have $f_c = 10\text{KHz}$ and a Max. gain of 20dB . draw the cct. diagram and calculate all required components?

Q₂ A filter with a transfer function given by:

$$H(s) = \frac{60S^3}{S^3 + 2S^2 + 3S}$$

identify: filter type, Filter order and Max. gain of the filter?

Q₃ For the cct. shown in Fig.

the transfer function:


$$H(s) = \frac{V_o}{V_i} = \frac{1}{1 + 2RCs + R^2C^2S^2}$$

- Identify type & order.

- derive expression for V_i


the cut off freq (f_c), Max. gain.

- Sketch the frequency response.

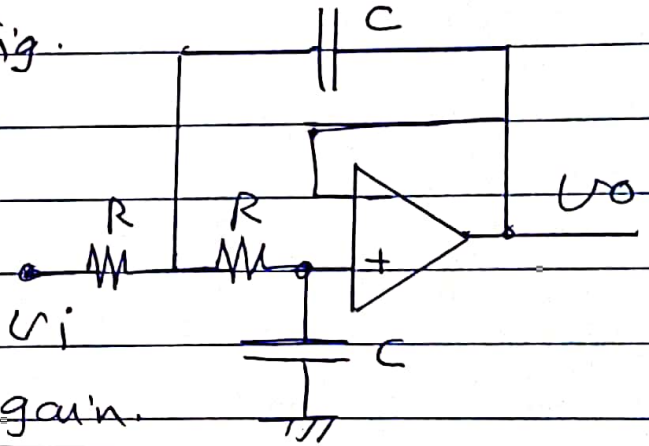

Q₄ For the filter shown
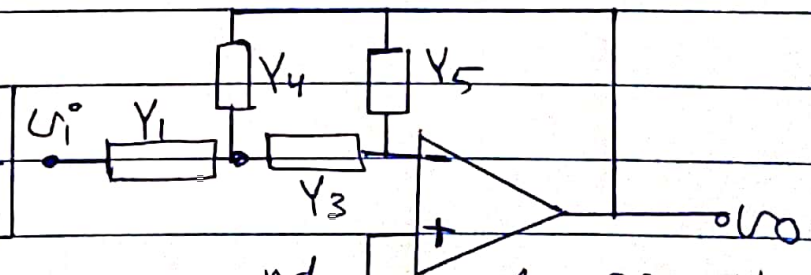
$$H(s) = \frac{-Y_1 Y_3}{Y_5(Y_1 + Y_3 + Y_4) + Y_3 Y_4}$$



1) choose Y 's to make the cct. as 2nd order BPF, then derive expressions for center freq, Selectivity Q and Max. gain?

2) Design the cct. to have $f_c = 10\text{KHz}$, $Q = 10$, $k_{max} = 10$

3) choose Y 's to realize 2nd order HPF

4) " " " " " " " " LPF