
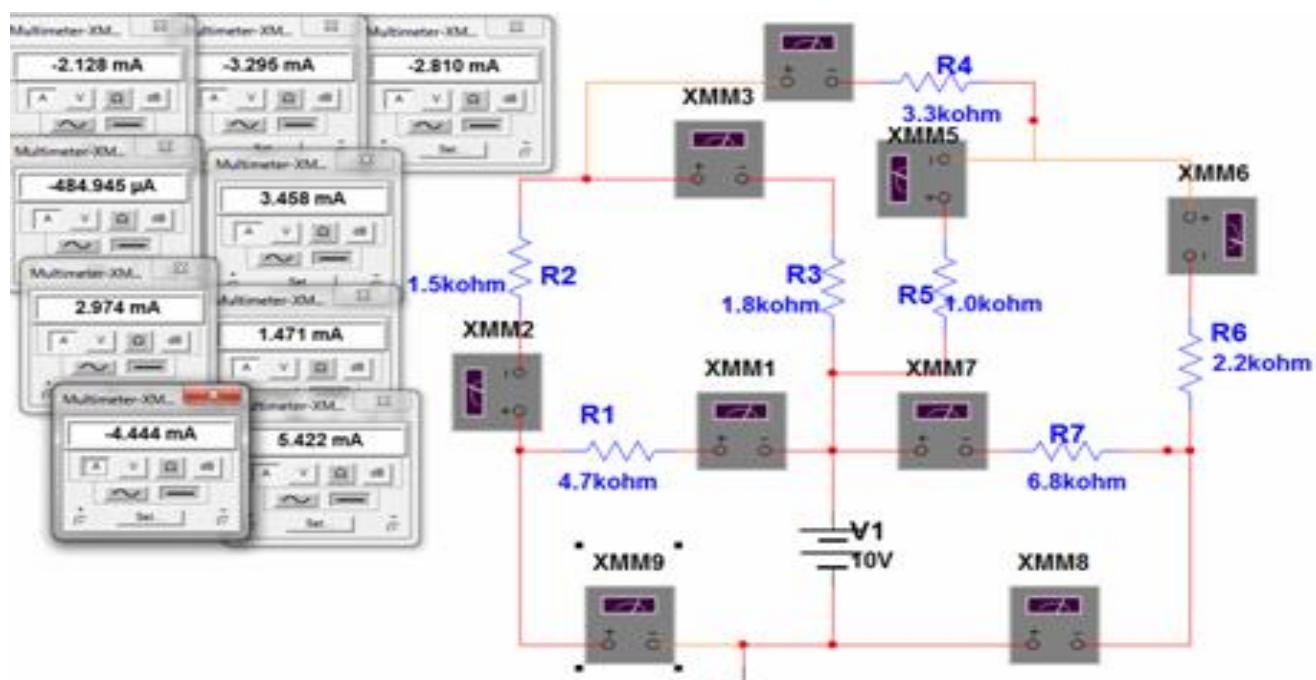



1.Node - Voltage Method:

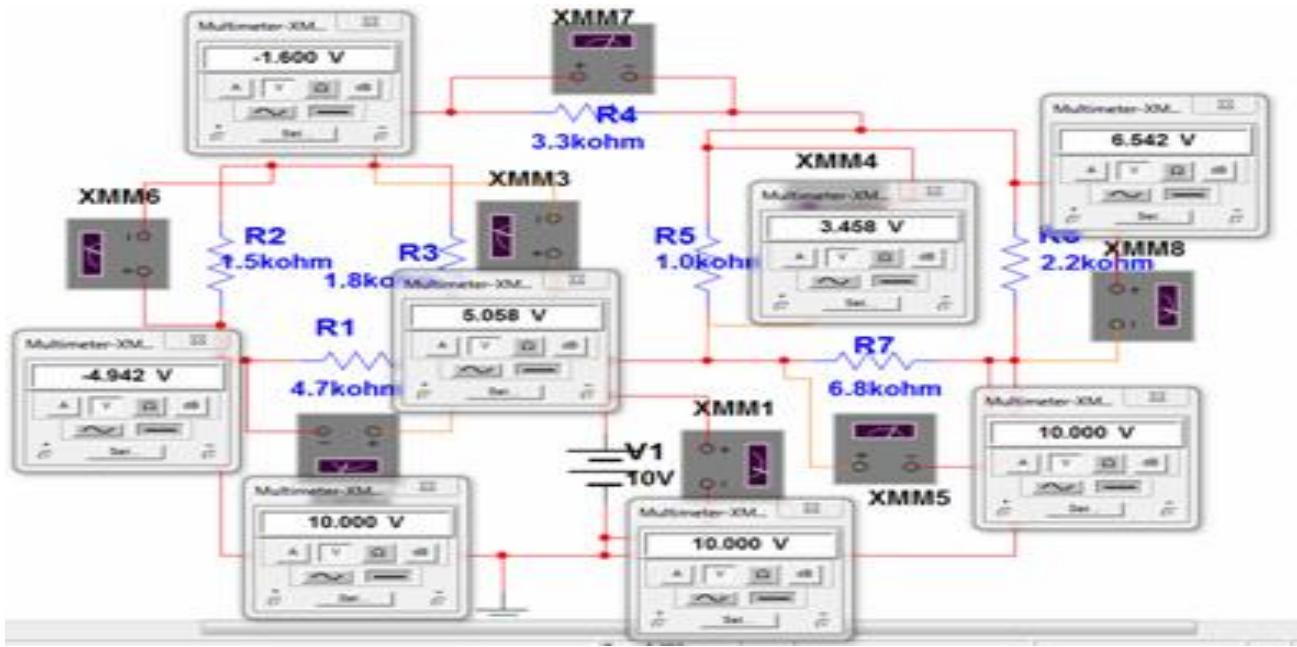


Parameter	Units	Theoretical
VAF	V	10
VAB	V	10
VAC	V	5.058

<i>VAD</i>	V	3.458
<i>VAE</i>	V	10
<i>VBC</i>	V	-4.942
<i>VCD</i>	V	-1.6
<i>VDE</i>	V	6.542
<i>I1</i>	mA	-2.128
<i>I2</i>	mA	-3.295
<i>I3</i>	mA	-2.81
<i>I4</i>	mA	-0.484
<i>I5</i>	mA	3.46
<i>I6</i>	mA	2.97
<i>I7</i>	mA	1.47
<i>I8</i>	mA	-4.444
<i>I9</i>	mA	5.422

2.mesh - current method:


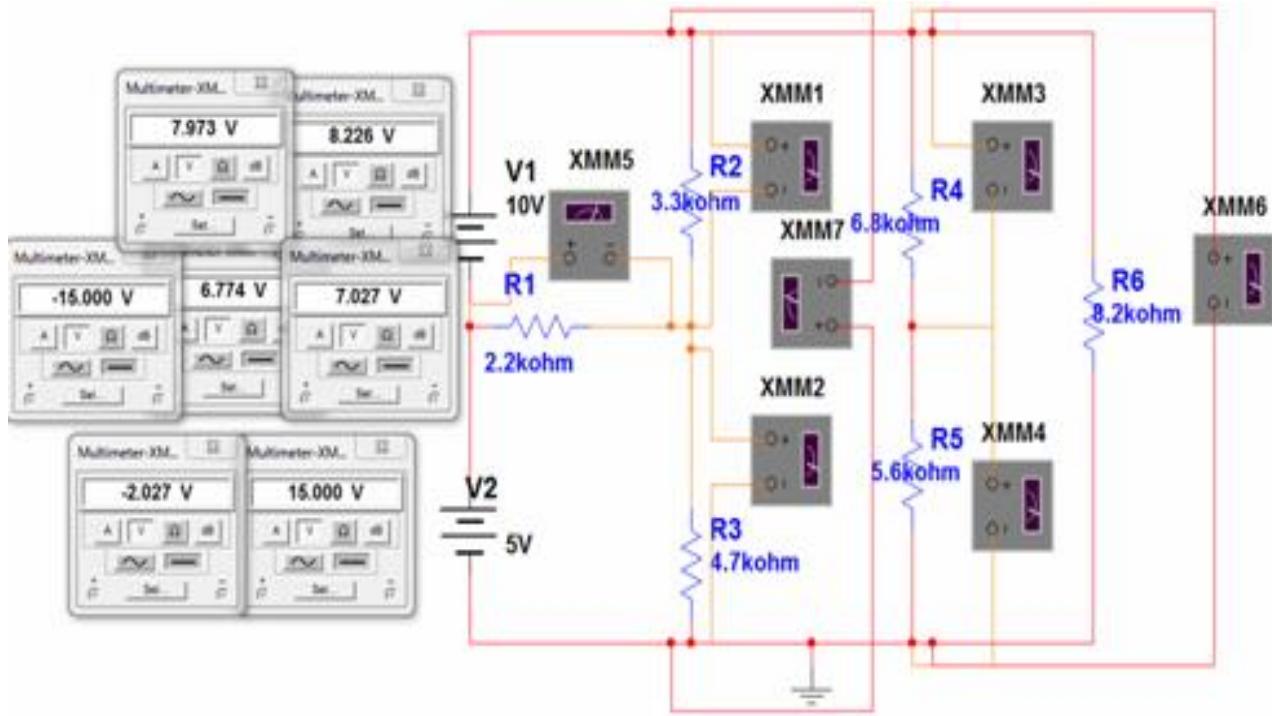


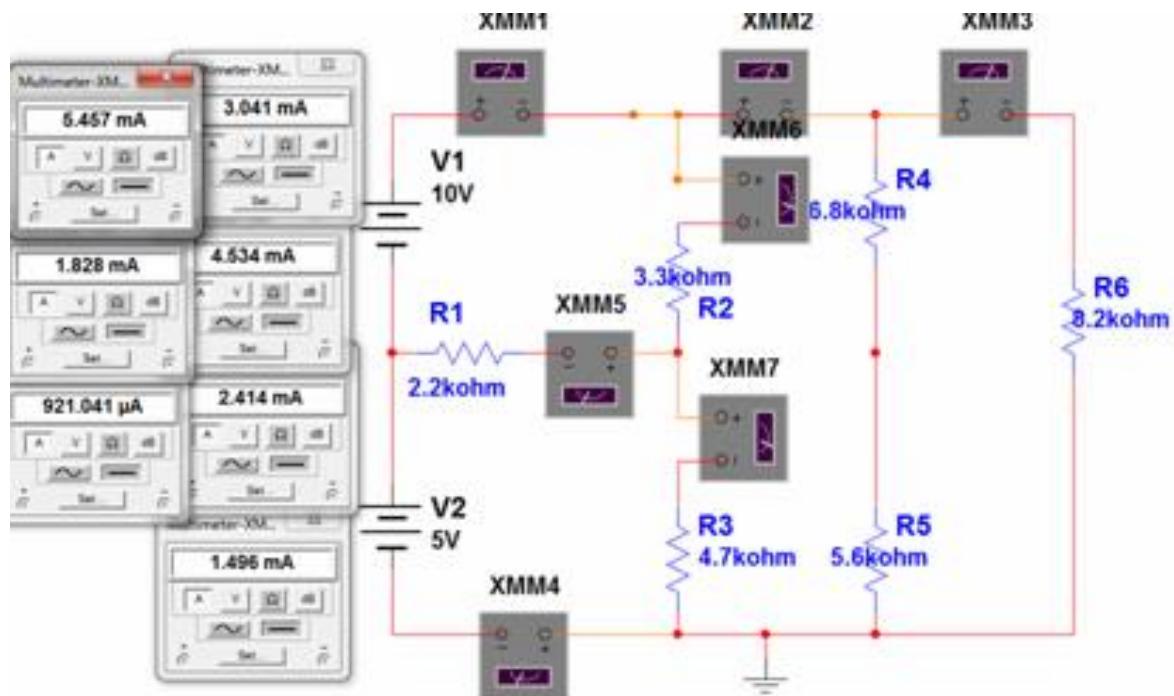

Parameter	Units	Theoretical
VAD	V	7.973
VDF	V	7.027
VBE	V	8.226
VEG	V	6.774
VCD	V	- 2.027
VBG	V	15
VFA	V	- 15
I1	mA	5.452
I2	mA	3.038
I3	mA	1.828
I4	mA	4.530
IDC	mA	0.921
IAD	mA	2.416
IDF	mA	1.495

3. superposition:

Part a:

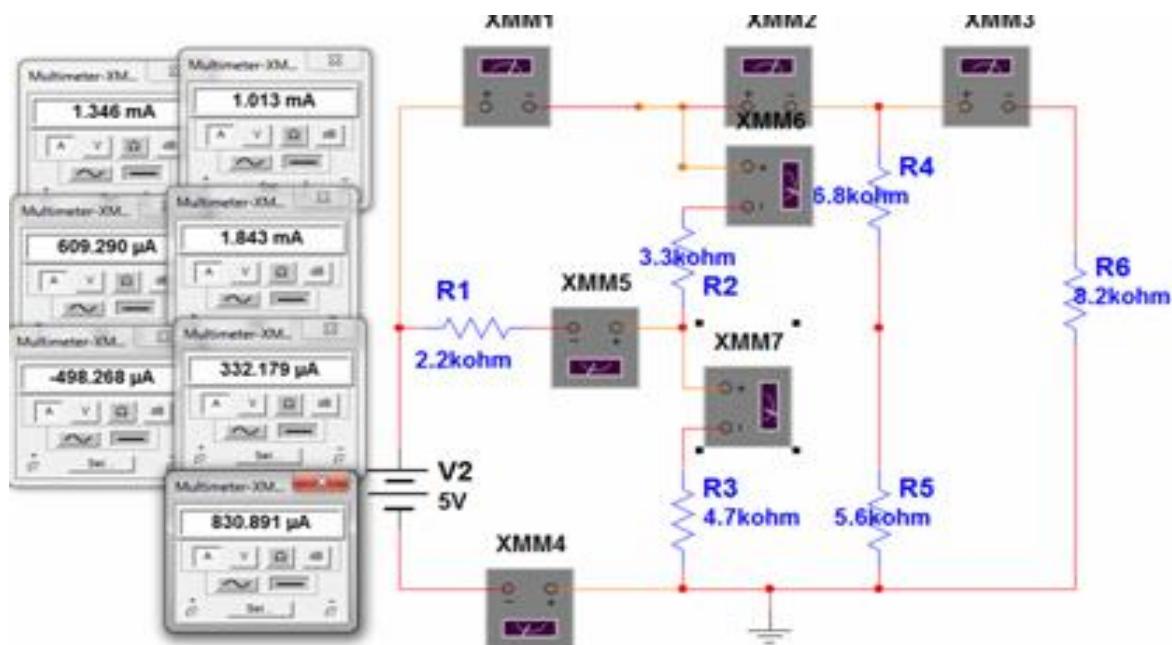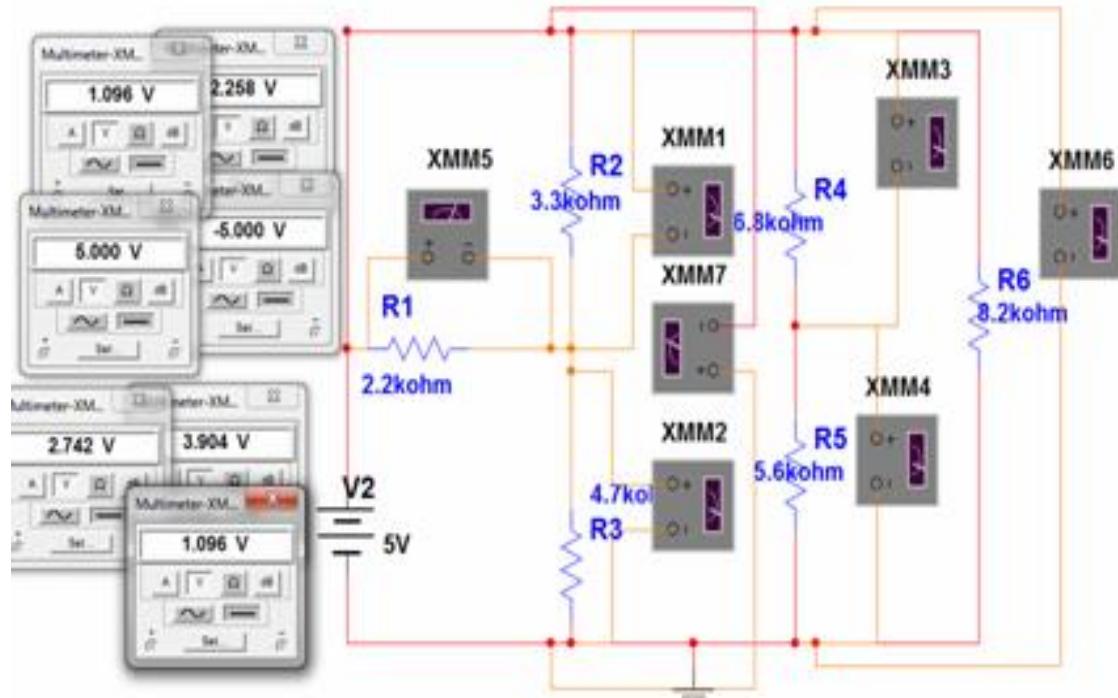



Param	Units	Theoretical
$V'AD$	V	1.096

$V'DF$	V	3.904
$V'BE$	V	2.742
$V'EG$	V	2.258
$V'CD$	V	1.096
$V'BG$	V	5
$V'FA$	V	- 5
$I'1$	mA	1.346
$I'2$	mA	1.013
$I'3$	mA	0.609
$I'4$	mA	1.843
$I'DC$	mA	- 0.498
$I'AD$	mA	0.332
$I'DF$	mA	0.831

3.Superposition:

Part 2:

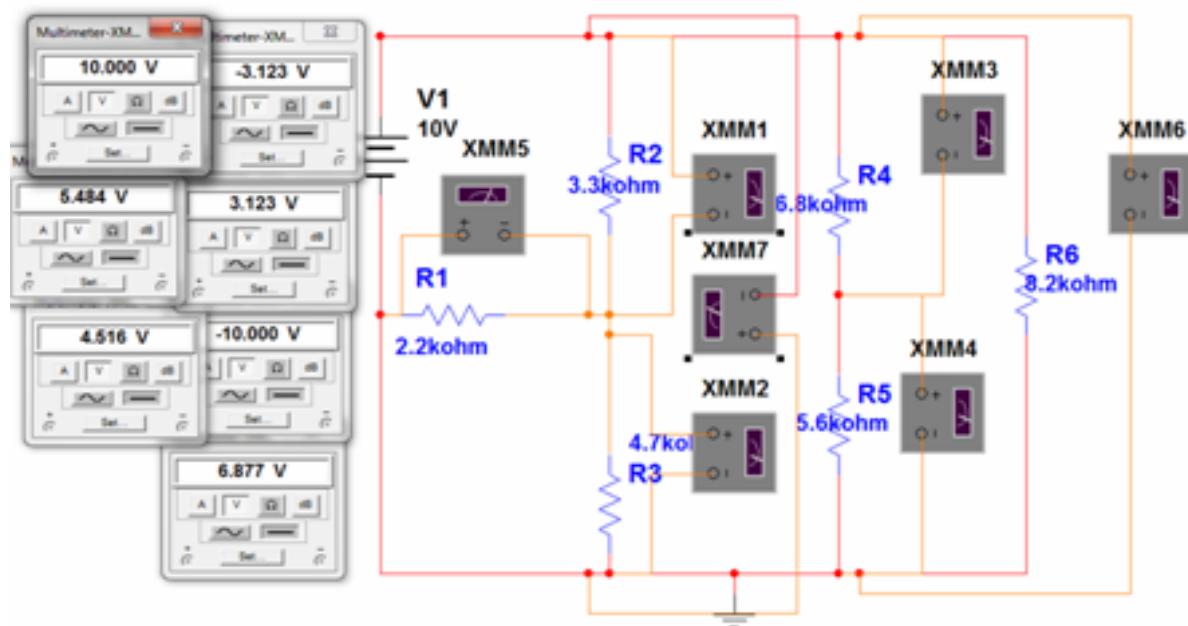

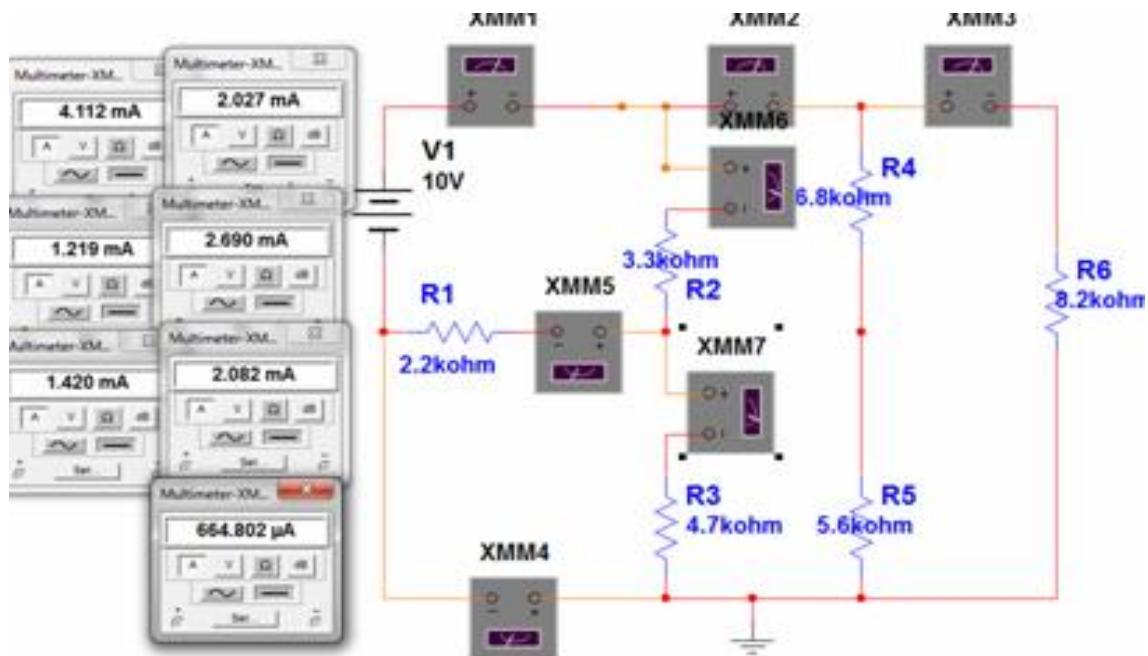

Parameter	Units	Theoretical
$V''AD$	V	6.877
$V''DF$	V	3.123
$V''BE$	V	5.484
$V''EG$	V	4.516
$V''CD$	V	- 3.123
$V''BG$	V	10
$V''FA$	V	- 10
$I''1$	mA	4.112
$I''2$	mA	2.027
$I''3$	mA	1.219
$I''4$	mA	2.69
$I''DC$	mA	1.42
$I''AD$	mA	2.082
$I''DF$	mA	0.665



The Hashemite University
Faculty Of Engineering
Department of Electrical Engineering
Electrical Circuit Lab
(409300)

Experiment "3" (techniques of circuit analysis (1)
(nodal , mesh, superposition))
Prelab "3"

- *Instructor name :Dr. Ahmade Al -Nemrat
- *Eng. Name: Ala'a
- *Student Name:
- *ID:
- *Date: 27/june/2010
- *Day: sunday