
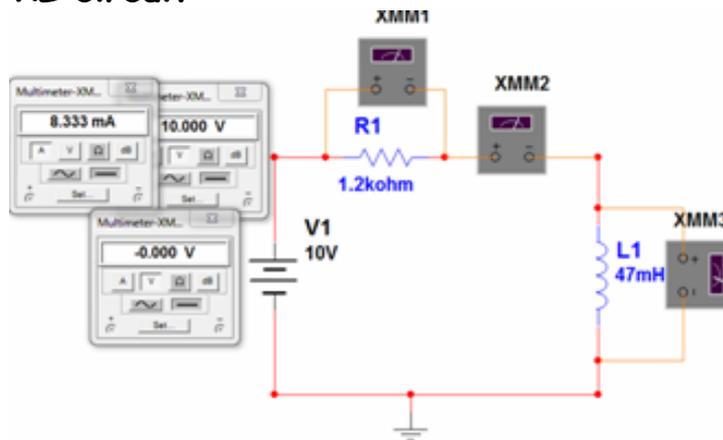


1. a: DC RL circuit:

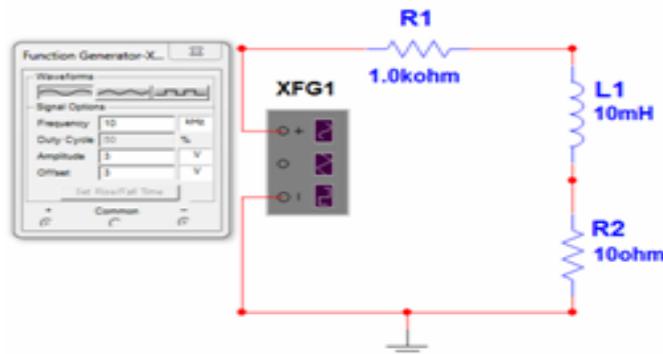


Parameter	R1(k Ω)	L(mH)	Vs(v)	Vr1(v)	VL(v)	IL(mA)
value	1.2	47	10	10	0	8.333

B: transient RL circuit:




Parameter	R1(K Ω)	R2(Ω)	L(mH)	T(η s)
value	1.0	10	10	9.9

2. a: RC circuit:

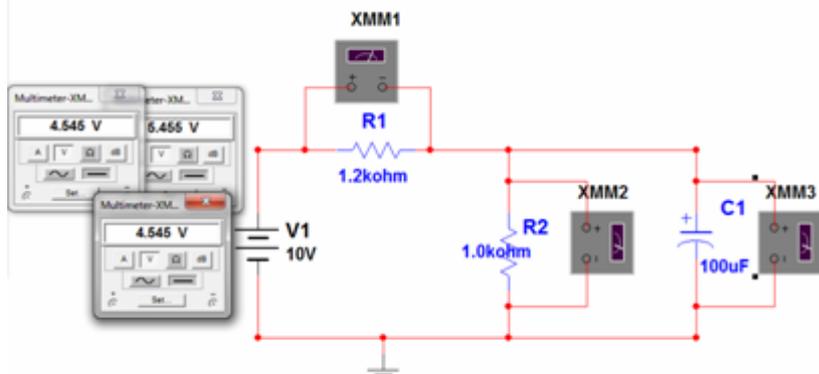


Parameter	R1(K Ω)	R2(K Ω)	C(η F)	Vs(v)	Vr1(v)	Vr2(v)	Vc(v)
value	1.2	1.0	100	10	5.455	4.545	4.545

B: transient RC circuit:

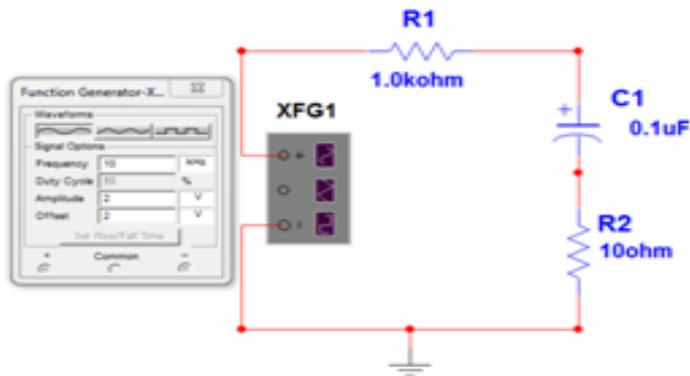

Parameter	R1(K Ω)	R2(Ω)	C(nF)	τ (ns)
value	1.0	10	10	0.101

3. parallel RLC circuit:

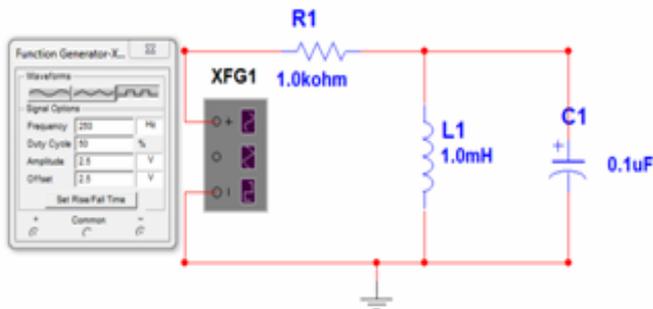

Parameter	R1(K Ω)	L(mH)	C(nf)
value	1.0	1.0	0.1