


Electronics Lab
Lab Session 3: BJT Characteristics and DC Biasing

<i>Students Names</i>	<i>Rami yahia hasan</i>	<i>Sandy Ghassan fathi</i>
<i>ID</i>	<i>1838264</i>	<i>1834471</i>

Part 1: Determining Transistor Parameters and the DC Load Line

1. Connect the circuit as shown in Figure 8 in the lab manual using NPN transistor and fill the following table:

Parameter	Measured
V_C	6.4670v
V_B	4.254v
V_E	3.555v
V_{CEQ}	2.912v
V_{BEQ}	0.698v
I_{BQ}	0.022mA
I_{EQ}	3.555mA
I_{CQ}	3.533mA
β	160.59
α	0.9938

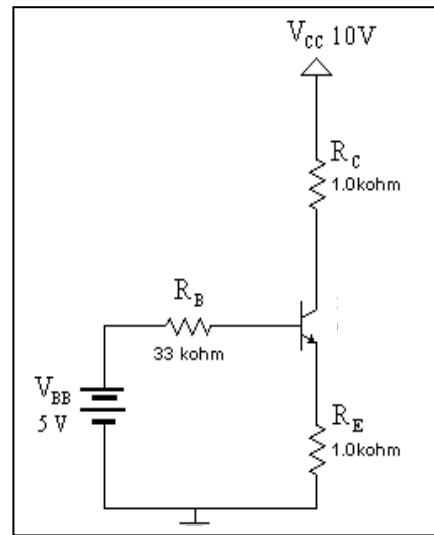


3. Determine the saturation ($I_{C(\text{short})}$) and cutoff ($V_{CE(\text{off})}$) points on the DC load line for this circuit, then plot the DC load line. Locate the Q point based on the measured values of I_{CQ} and V_{CEQ} .



By KVL the DC-load line equ is:

$$I_C = \frac{10 - V_{ce}}{1 + \frac{\beta+1}{\beta}}$$

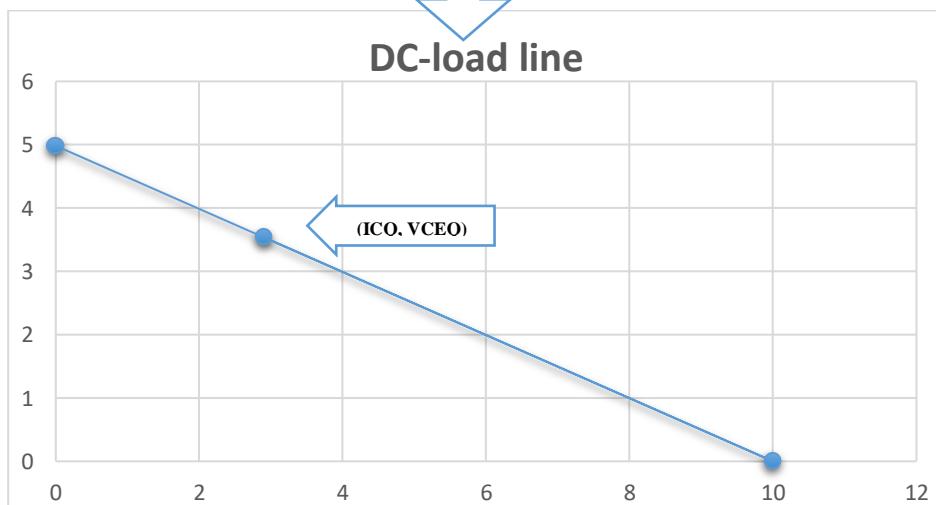so when $I_C = 0$ mA , $V_{ce} = 10$ V
when $V_{ce} = 0$, $V_{ce} = 4.983$ mA




MULTISIM RESULTS FOR PART 1

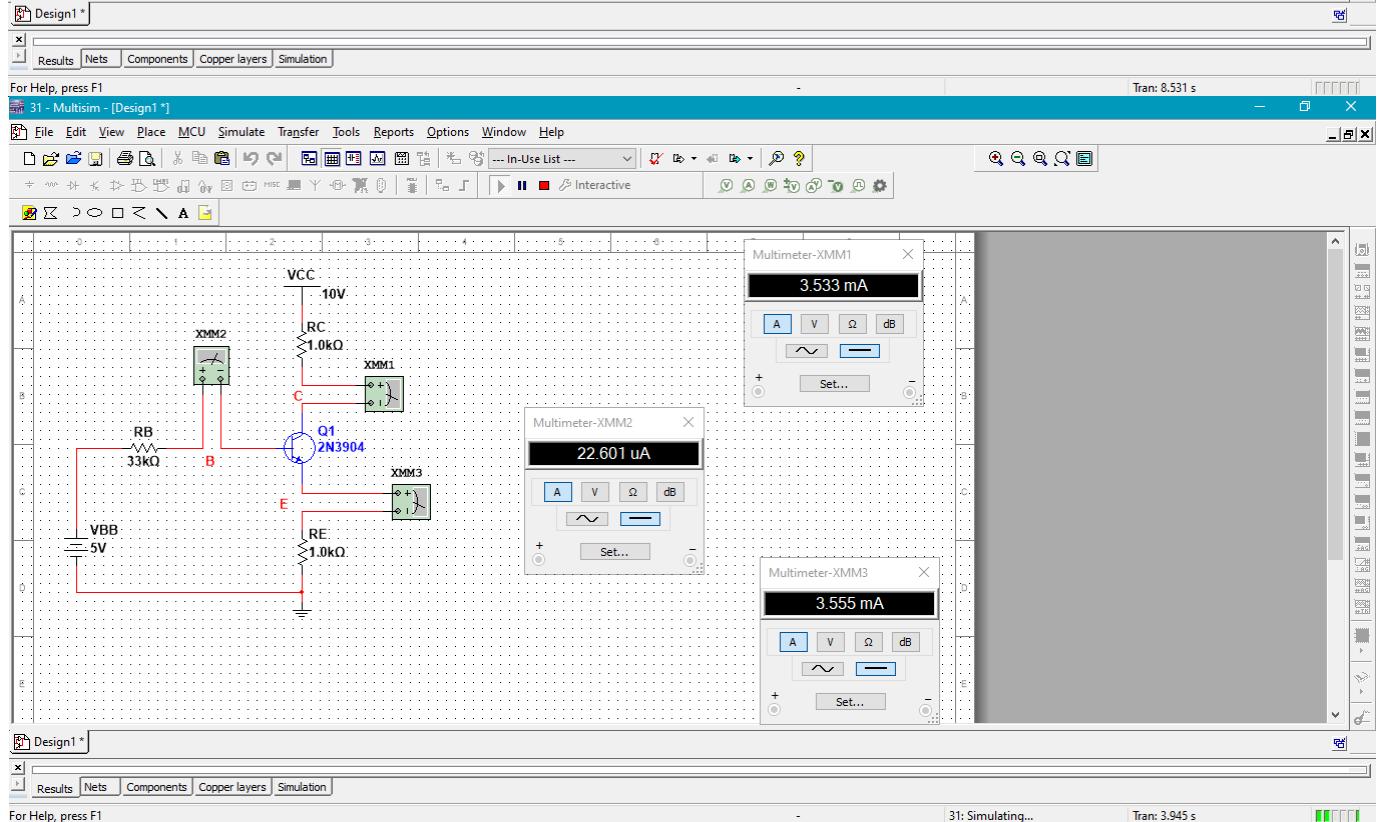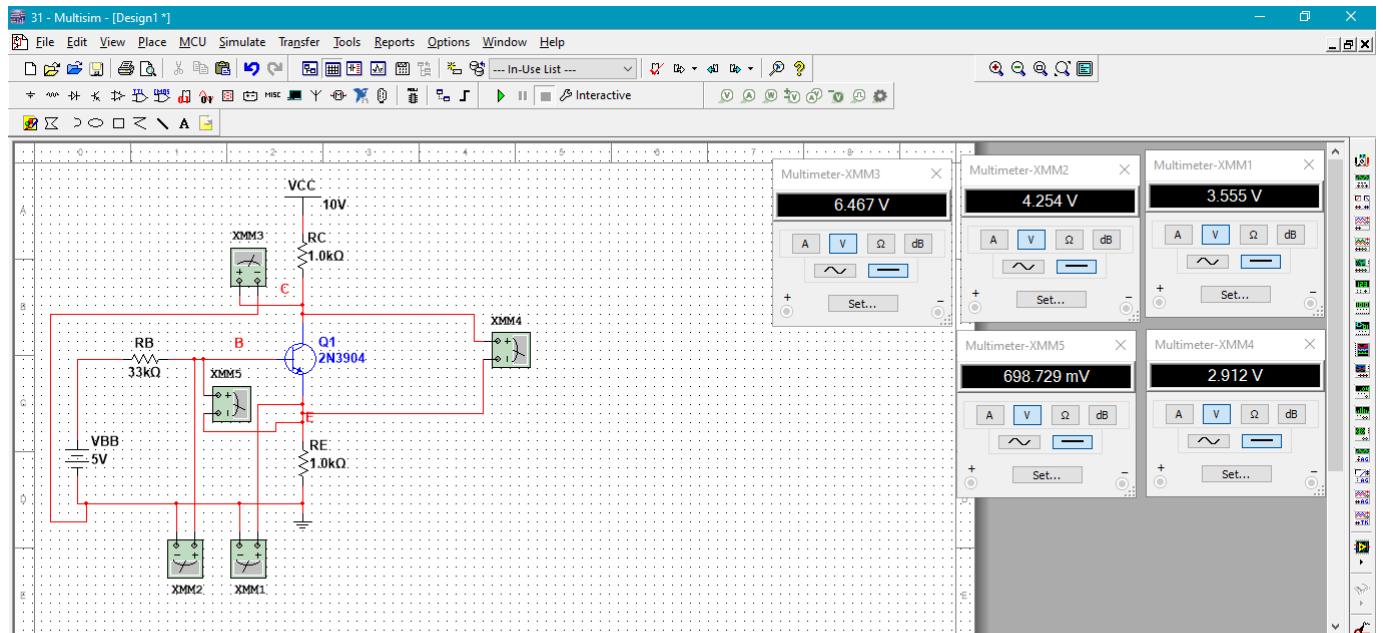

PART2

4. Connect the circuit as shown in Figure 9 in the lab manual using PNP transistor and fill the following table:


Parameter	Measured
V _C	1.752v
V _B	7.527v
V _E	8.24v
V _{ECQ}	6.488v
V _{EBQ}	0.713v
I _{CQ}	1.751mA
I _{BQ}	0.007528mA
I _{EQ}	1.758mA
β	232.59
α	0.9957

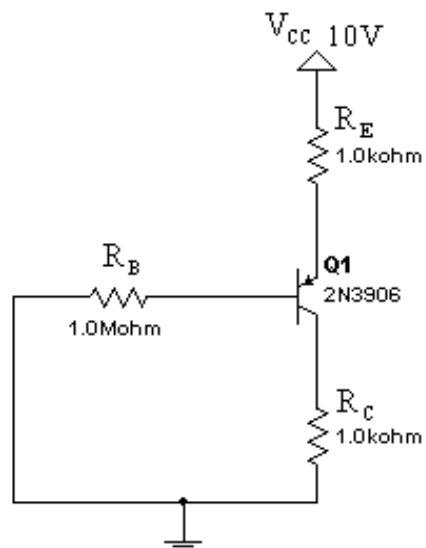


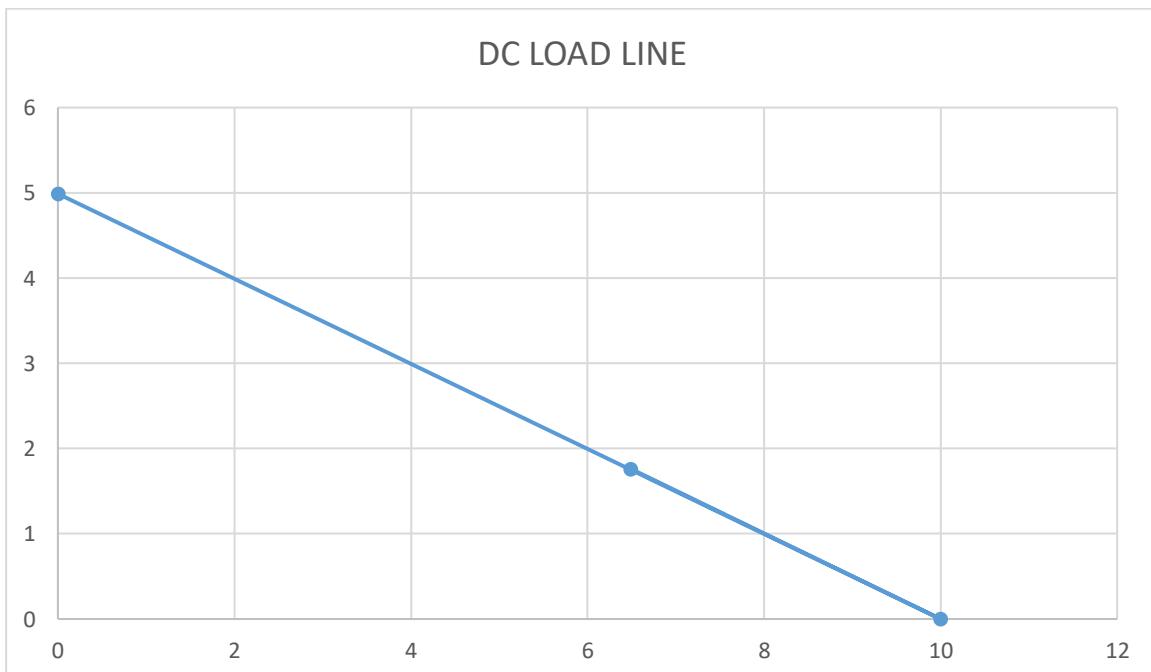
5. Determine the saturation ($I_{C(\text{short})}$) and cutoff ($V_{CE(\text{off})}$) points on the DC load line for this circuit, then plot the DC load line ne. Locate the Q point based on the measured values of I_{CQ} and V_{CEQ} .

$$I_C = \frac{10 - V_{EC}}{1 + \frac{\beta+1}{\beta}}$$

so when $I_C = 0$ mA, $V_{CE} = 10$ V
when $V_{CE} = 0$, $V_I C = 4.989$ mA



MULTISIM RESULTS FOR PART 2

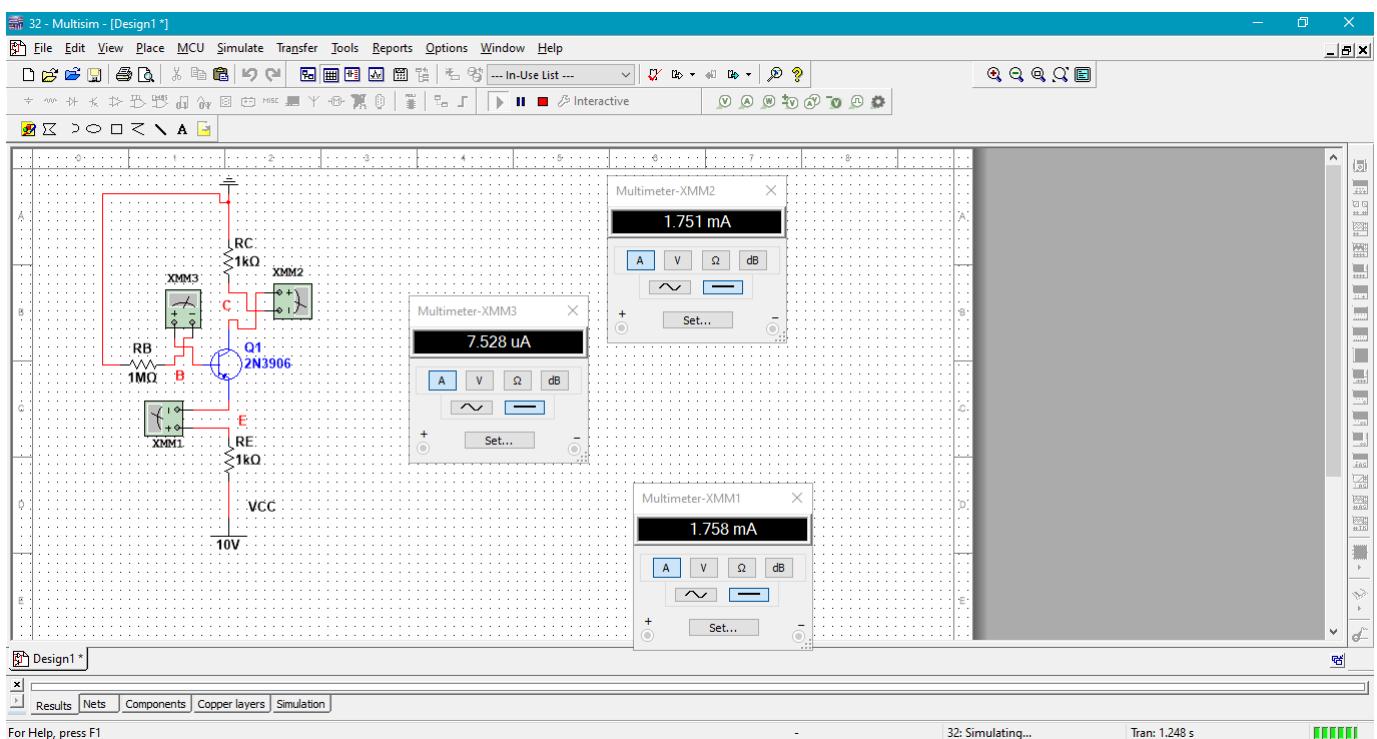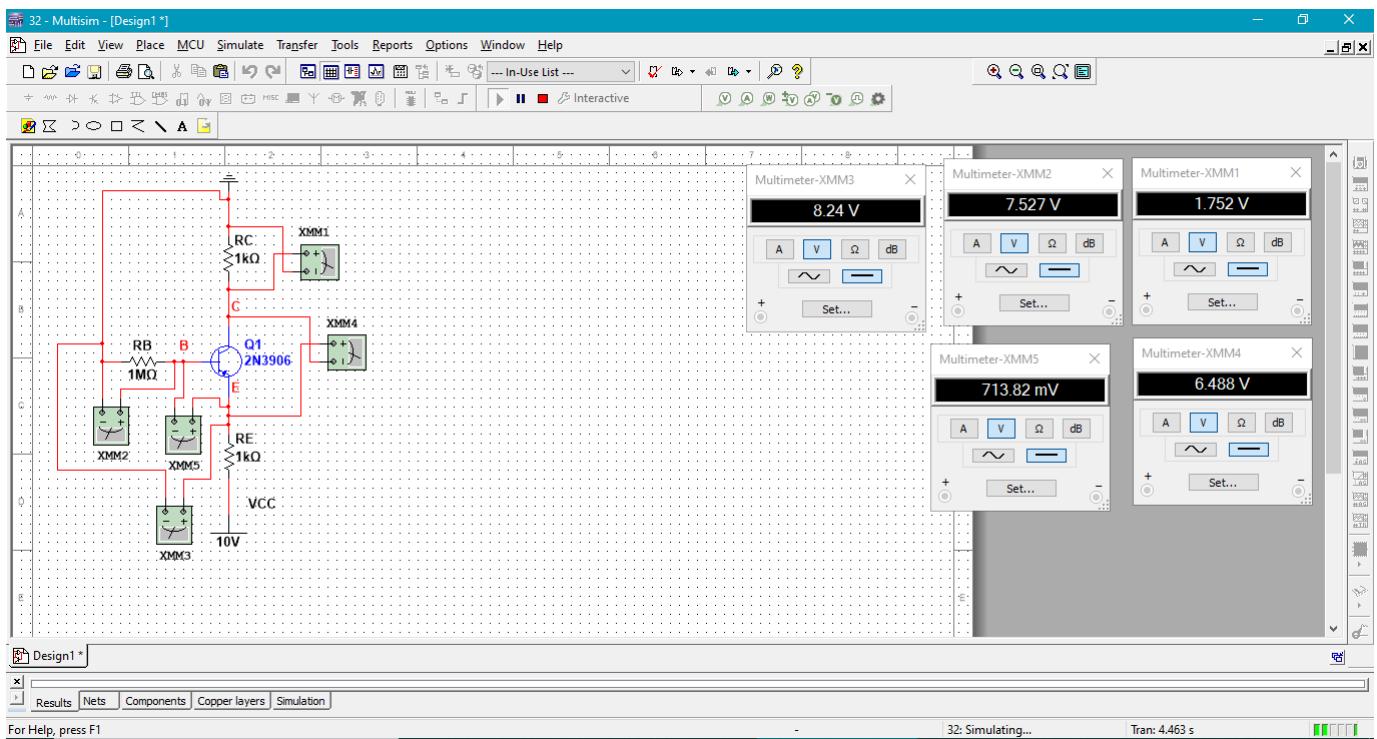

Calculations (PART1 and PART2) calculate All Currents using the Measured Voltages

PART1

$$I_C = \frac{V_C}{R_C} = \frac{10 - 6.46}{1k} = 3.54 \text{ mA}$$

$$I_E = \frac{V_E}{R_E} = \frac{3.555}{1k} = 3.55 \text{ mA}$$

$$I_B = \frac{V_{BB} - V_B}{R_B} = \frac{5 - 4.254}{33K} = 0.0226 \text{ mA}$$

PART2

$$I_C = \frac{V_C}{R_C} = \frac{1.752}{1k} = 1.725 \text{ mA}$$

$$I_E = \frac{V_{CC} - V_E}{R_E} = \frac{10 - 8.24}{1k} = 1.76 \text{ mA}$$

$$I_B = \frac{V_B}{R_B} = \frac{7.527}{1M} = 0.007527 \text{ mA}$$