
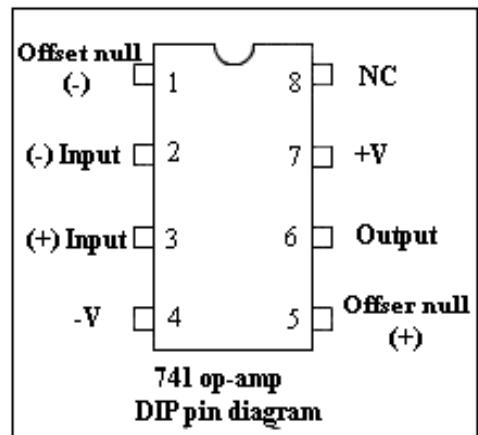


Electronics Lab
Lab Session 7: Operational Amplifier


Students Names	ID#
Rami Yahia ali hassan sande Ghassan Fatehi Qanaeर	1838264 1834471

Part1: Comparator with 741 IC Used as a Level Detector

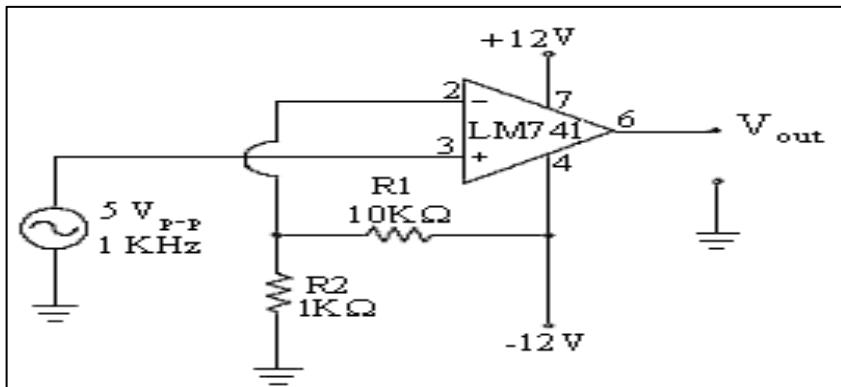1. Construct the circuit shown below, connect a 500 Hz., $5\text{ V}_{\text{p-p}}$ to the input. Sketch the input SIGNAL , Vref and the output signal on the same graph,




$$V_{\text{ref}} = (-12 \cdot R_2) / (R_1 + R_2) = -12 \cdot 1 / (10 + 1) = -1.09$$

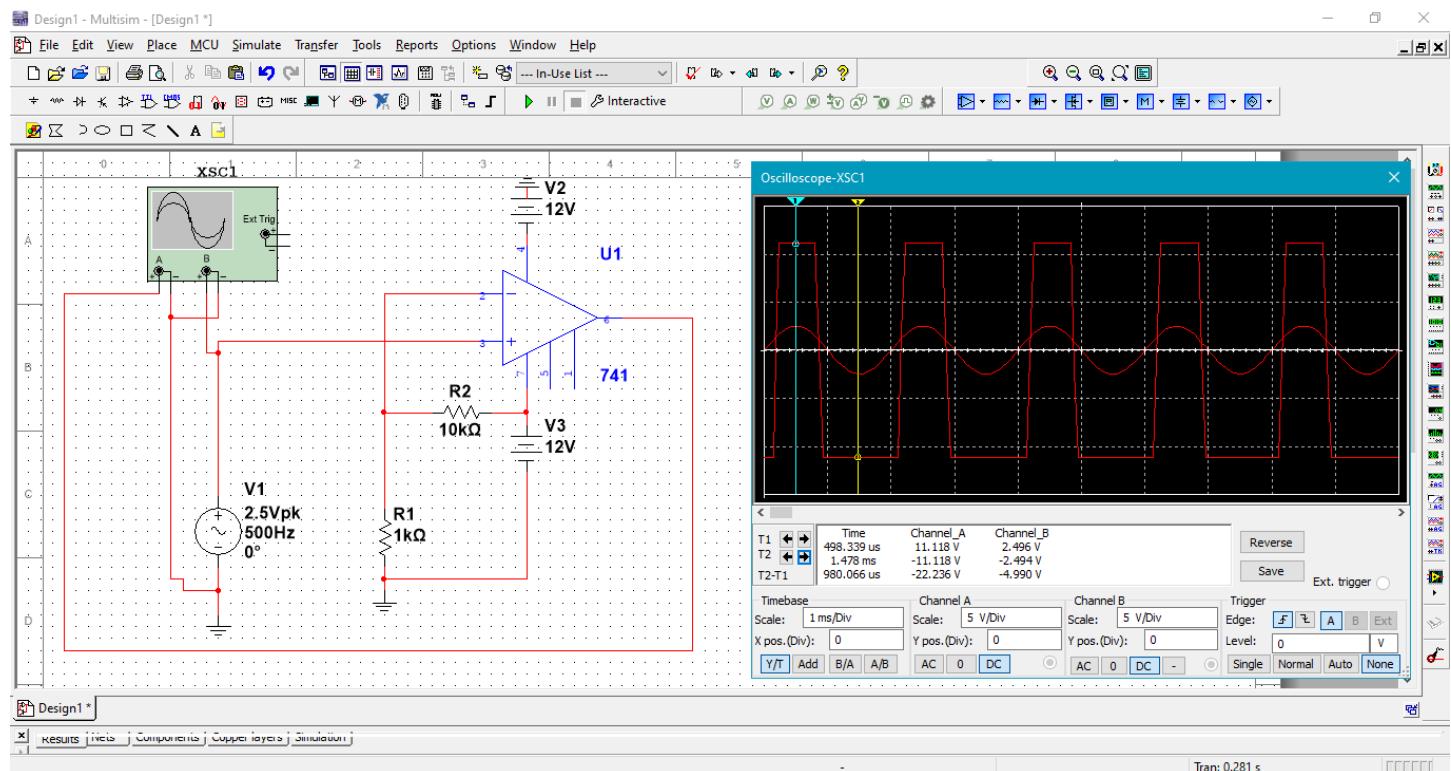


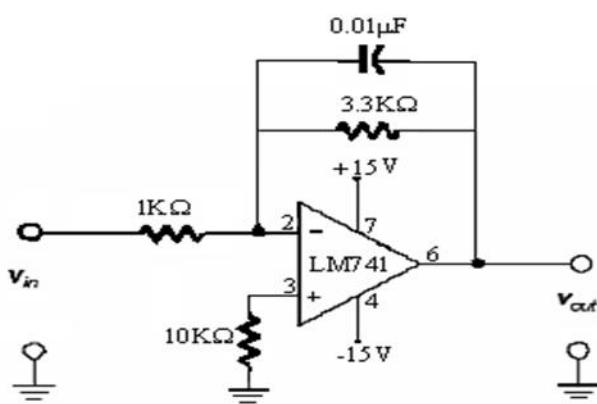Part 4: Integrator



- Construct the circuit shown below, apply a $2 \text{ V}_{\text{p-p}}$ of sine wave.
- Vary the frequency of V_{in} from 200Hz to 50KHz. Calculate the gain. And record the results in the Table 1, and then plot the gain vs. frequency on semi-log graph paper.







Frequency (Hz)	V_{in} (Volt)	V_{out} (Volt)	A_v
50Hz	1V	3.291V	3.291
100Hz	1V	3.289V	3.289
200Hz	1V	3.282V	3.282
400Hz	1V	3.276V	3.276
1K	1V	3.219V	3.219
10K	1V	1.407V	1.407
15K	1V	0.990V	0.99


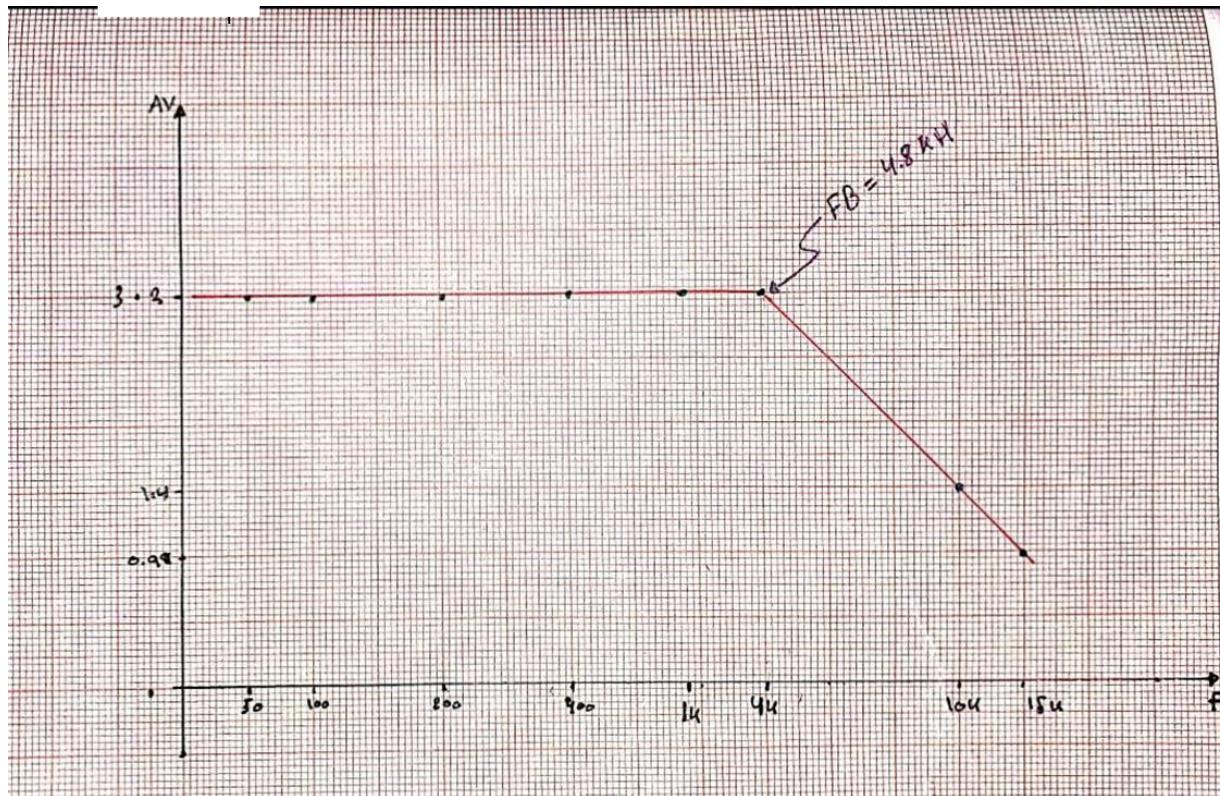


The Break Frequency of the Integrator circuit $FB = 1/2\pi C f R C = 1/(2\pi \cdot 3.3 \cdot 1000 \cdot 10 \cdot 10^{-9}) = 4822.8 \text{ Hz}$

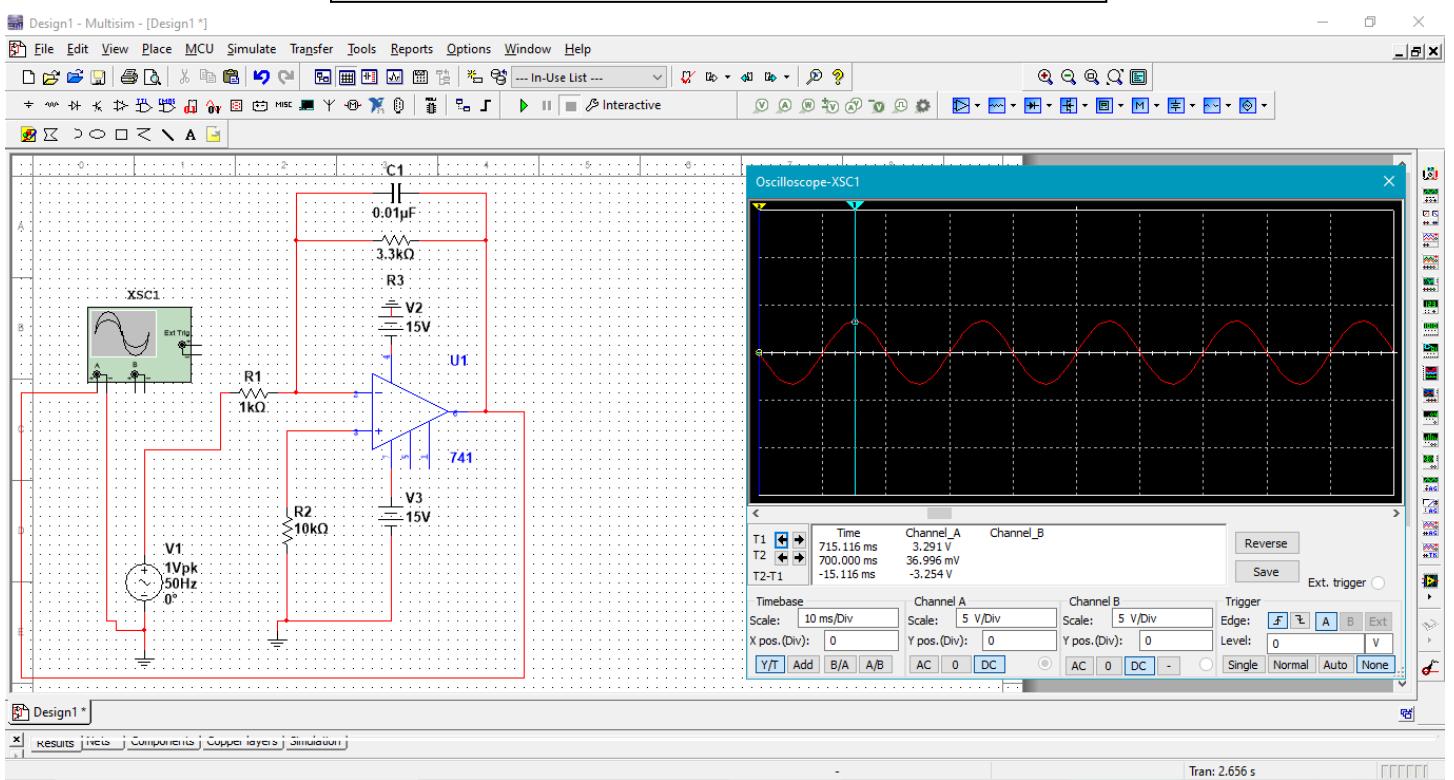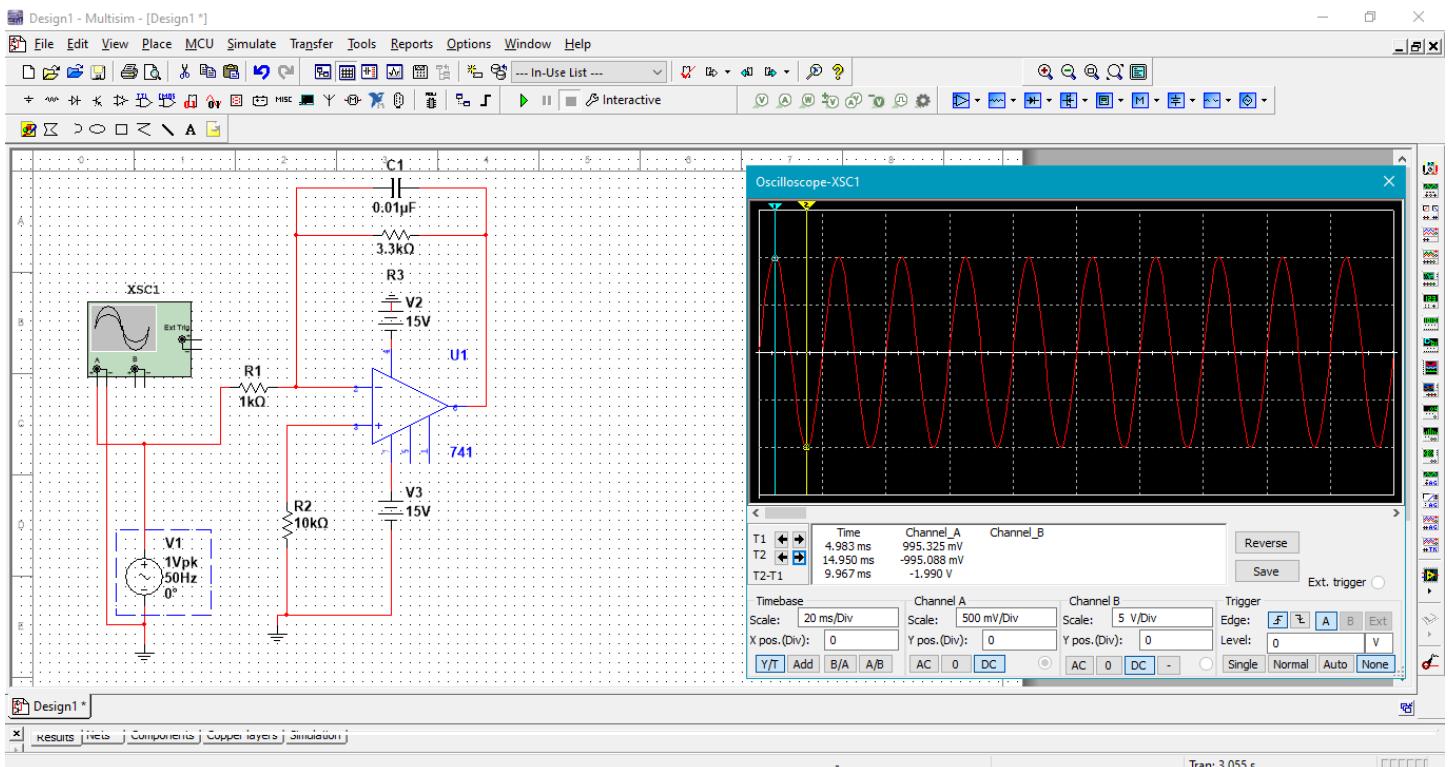

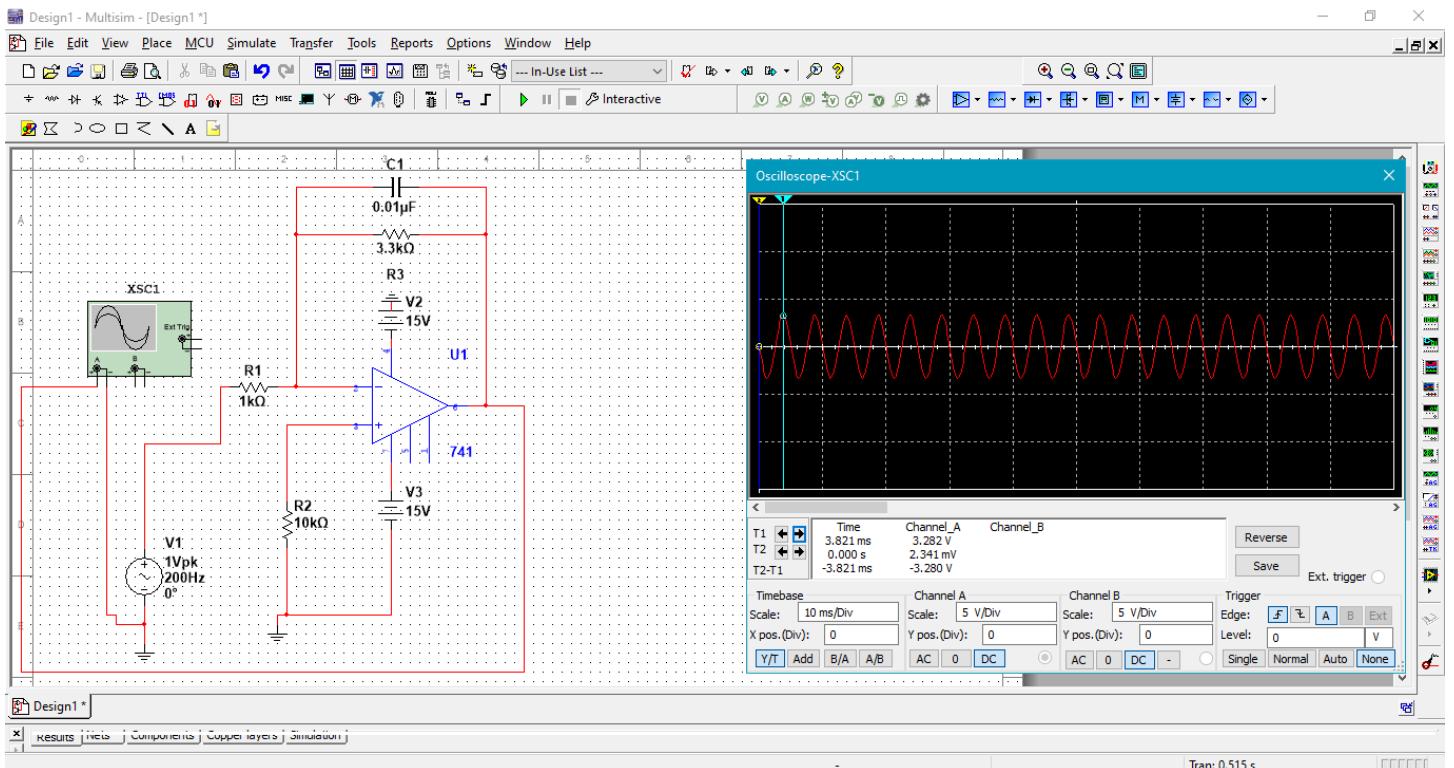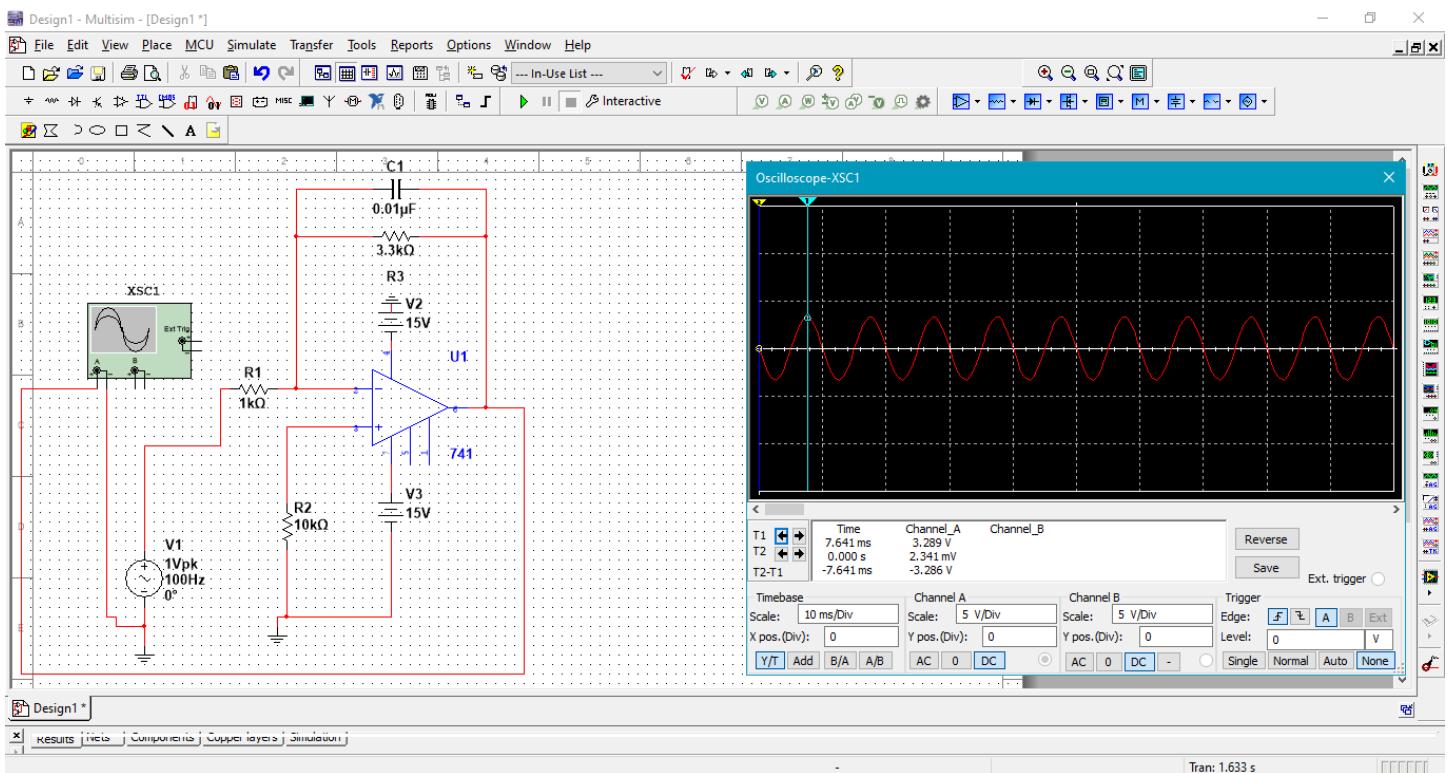

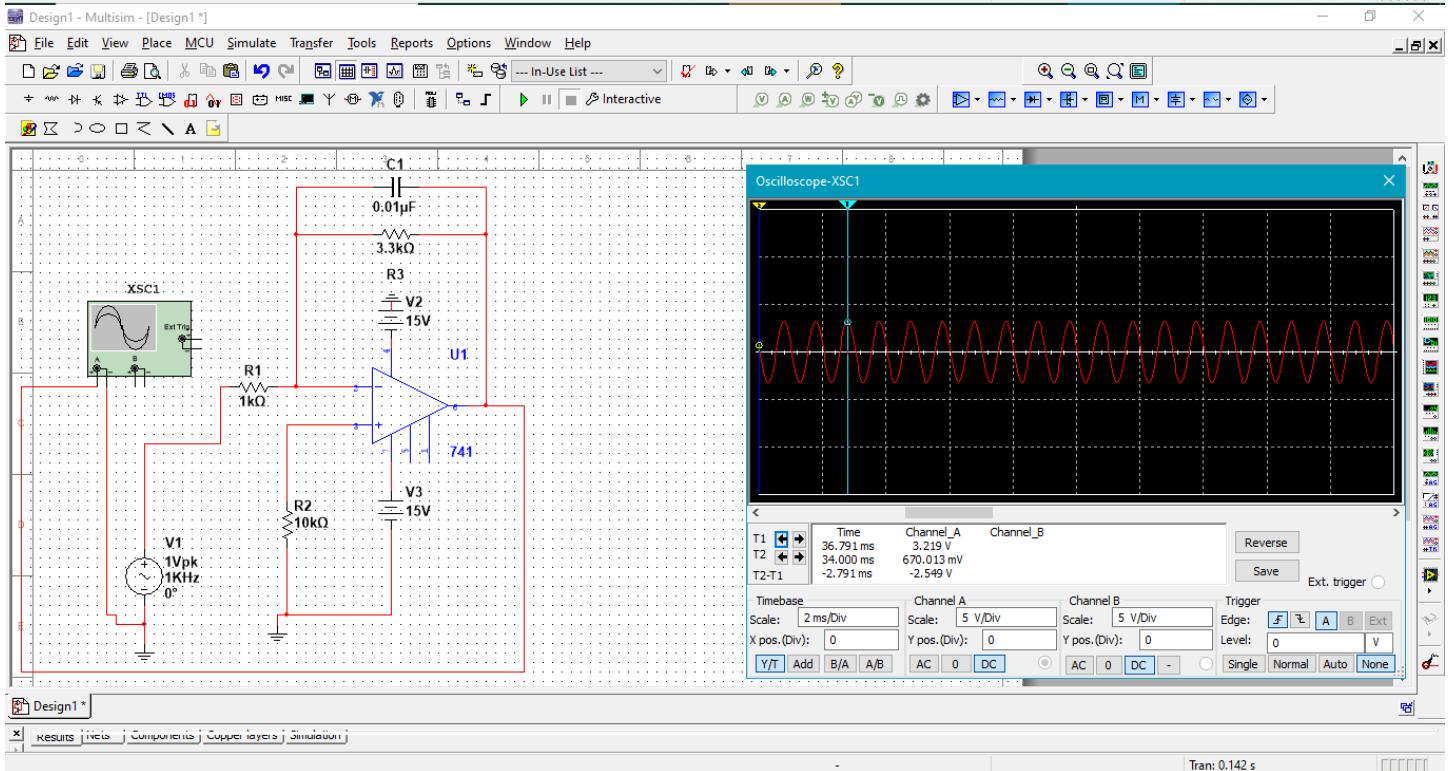
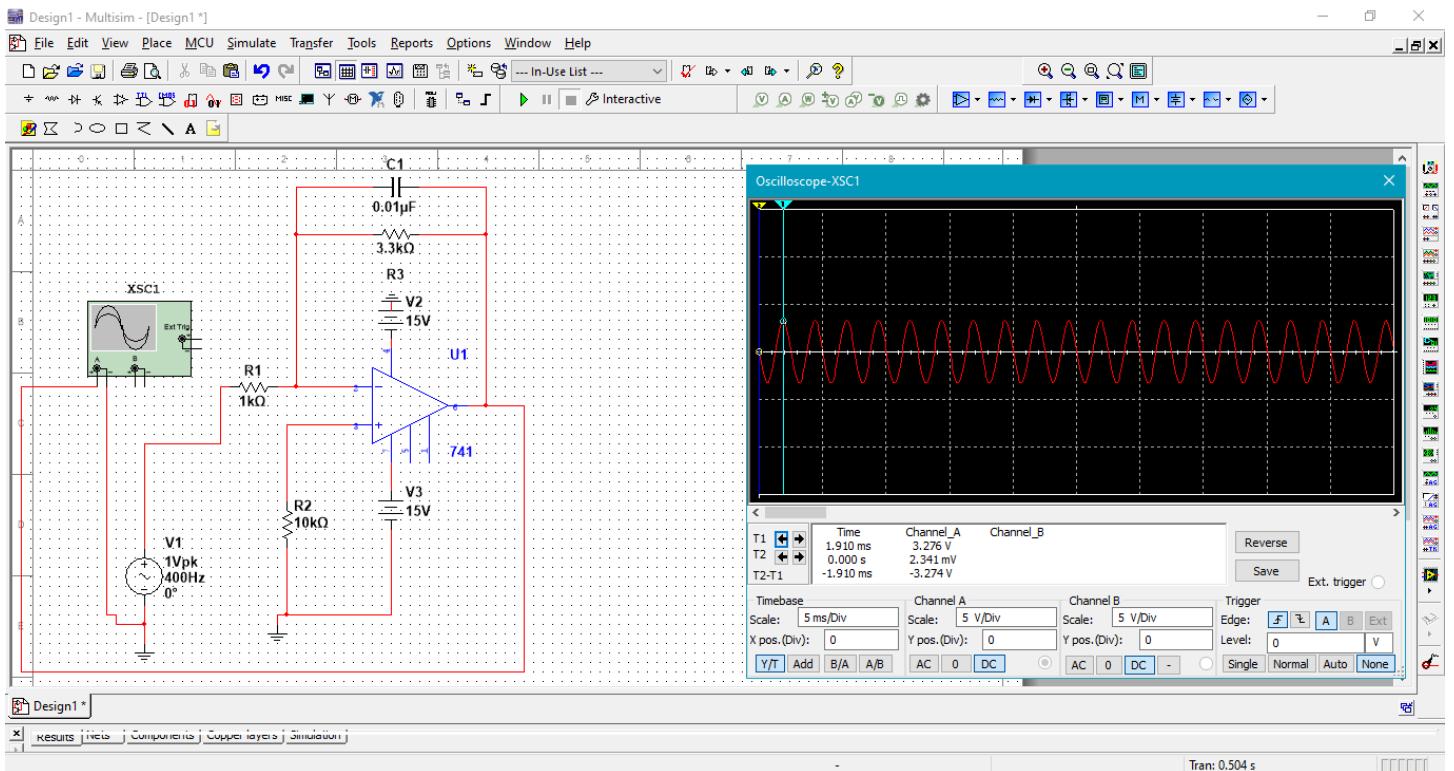


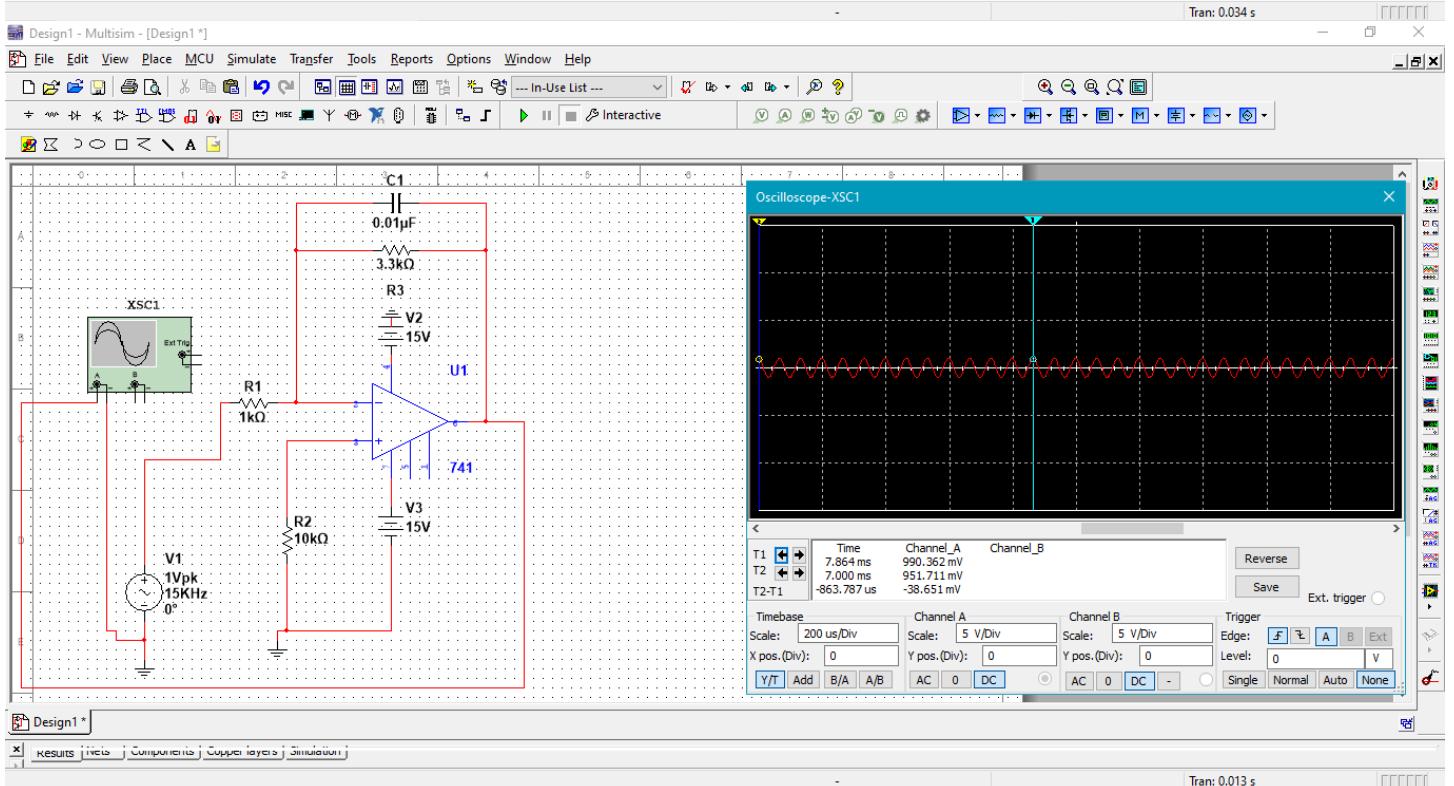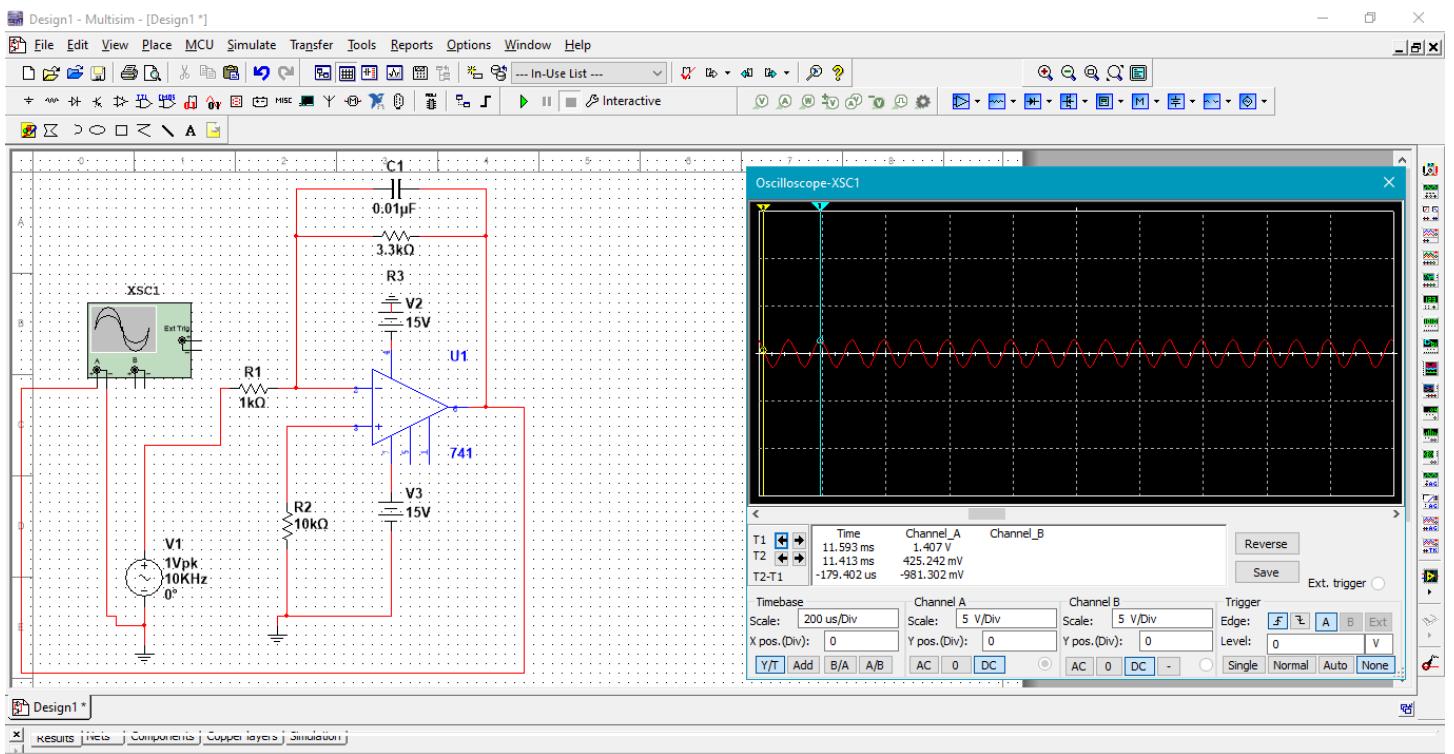

Part5: Differentiator

1. Connect the circuit shown. Apply a $2 \text{ V}_{\text{p-p}}$ sine wave.
2. Vary the frequency of V_{in} as shown in the Table 2 and record the results.
3. Calculate the gain and then plot the gain vs. frequency on semi-log graph paper

Frequency(Hz)	PEAK V_{in} (Volt)	PEAK V_{out} (Volt)	A_v
200Hz	1V	2.671V	2.671
1K	1V	8.123V	8.123
2K	1V	9.333V	9.333
6K	1V	9.094V	9.094
8K	1V	8.569V	8.569

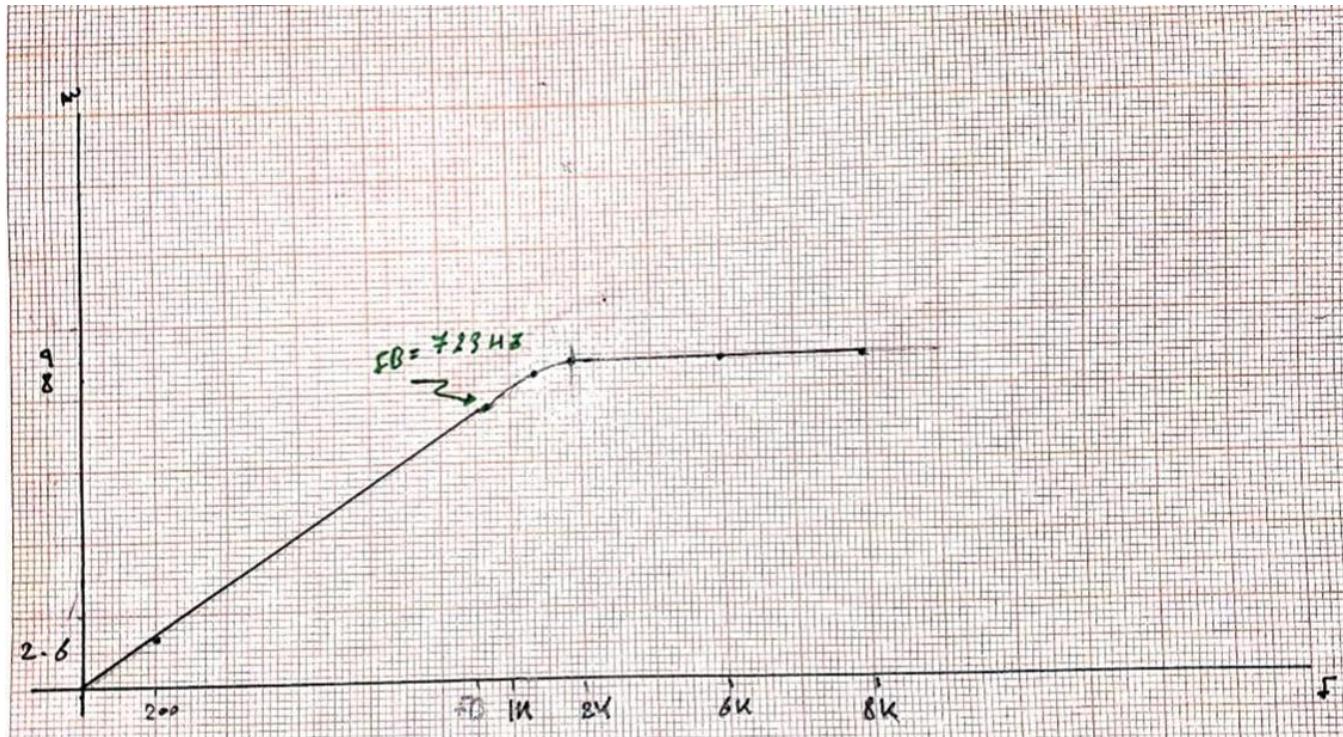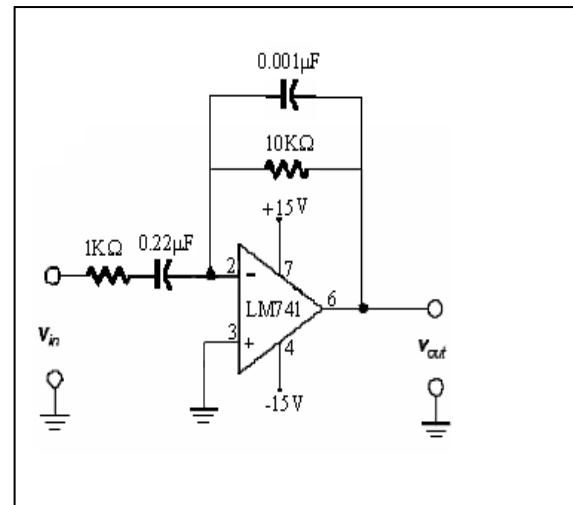

The Break Frequency of the differentiator circuit $FB = 1/(2\pi R_1 C_1)$
 $(2\pi \cdot 1\text{K} \cdot 0.22 \cdot 10^{-6}) = 723.4 \text{ Hz}$

